

College of Sciences Department of Medical Physics





جام<u>عة</u> الم<u>ستقبل</u> AL MUSTAQBAL UNIVERSITY

> كلية العلوم قسم الفيزياء الطبية

**MedicalPhysics** 

المرحله: الأولى الماده: الكهربائية -عملي المختبر:الأول اسم التجربة: " قانون اوم " رقم التجربة: 1

مشرفة المختبر: د . دعاء جعفر

م. زهراء باسم

معيدة المختبر : م. افتخار ثامر

Page | 1





# Ohm's law

# Purpose:

To verify ohm's law (the relation between I and V)

#### **Theory:**

Ohm's law :the ratio of the potential (between the points in a conductor to a current at a given temp. Known as Resistance "R".

# Apparatuses used :

Power supply, Ammeter , constant resistance "R" voltmeter .

# **Procedure:**

• Connect the power supply "E" , the ammeter A the

rheostat and the constant resistance "R" in series . then

connect the voltmeter "V" in parallel with (R) as shown


in fig



**College of Sciences** Department of Medical Physics



الدائرة الكهربائية

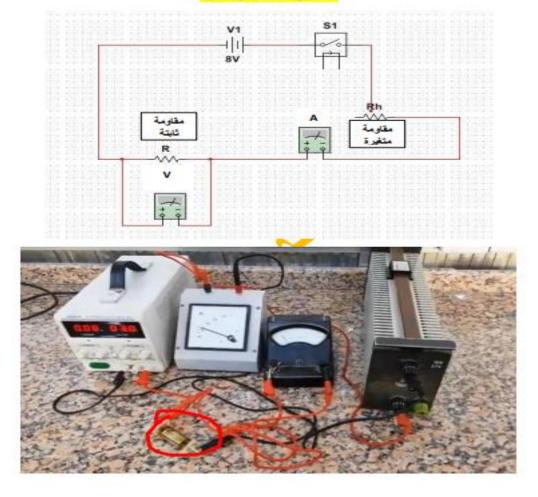



**College of Sciences** Department of Medical Physics



Adjust the rheostat so that the ammeter and voltmeter

are registers a convenient reading on the scale.


• Record both the reading of I of the ammeter and

voltmeter (V)


• Tabulate the results.

V (volt)	l (amp)	<b>R</b> (Ω)	

R(<sub>Ω</sub>)= Slope

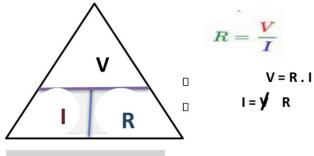


Ohm's law units are<sub>:(Ω)</sub>

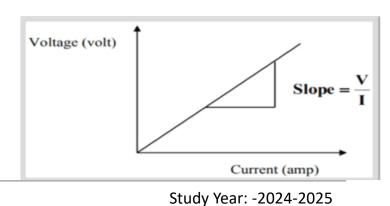



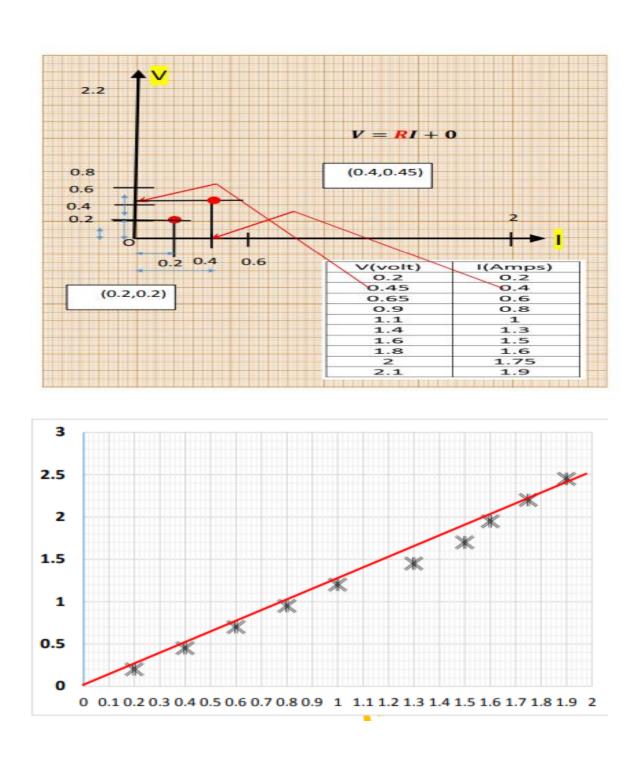College of Sciences Department of Medical Physics







College of Sciences Department of Medical Physics



# **Discussion:**

- Draw the relationship between V & I form table.
- $\bullet$  Is it necessary that the relationship between V & I start with the

original point (0, 0) and why?

 $\bullet$  What does the slopes represent in V & I relationship? Why

should the graphic be a straight line?

- Q- choose the correct answer
- 1- What is the mathematical formula for Ohm's law?
- A. R = V/C
- B. R=V/ I
- C. R= I/ V
- D. R = V/SLOPE
- 2- What is the purpose of Ohm's law?
- A. To verify ohm's law (the relation between I and V)
- B. To verify ohm's law (the relation between R and V)
- C. To verify ohm's law (the relation between R and V)



College of Sciences Department of Medical Physics



- D. To verify ohm's law (the relation between R and T)
- **3-** The slope in Ohm's law is:
- A. V/ R
- B. R/ V
- C. V/ I
- D. I/ V
- 4- the ratio of the potential (between the points in a conductor to
- a current at a given temp. Known as Resistance "R".
- a. Ohm's law :
- b. power law
- c. power momentum law
- d. D- charge law
- 5- Ohm's law units are:
- Α. Ω
- B.V
- C. Ampere
- D. Watt

Page | 7

**College of Sciences** Department of Medical Physics



current	التيار		المناقشة	Discussion
voltage	فولطية		ارسم	draw
Resistance	المقاومة		وضح	Explain
Ω	اوم		الجهد	potential