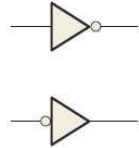


اسم المادة : تقنيات رقمية
اسم التدريسي : م.م. علياء محمد جواد
المرحلة : الثانية
السنة الدراسية : 2023_2024
عنوان المحاضرة: Logic Gates


1

Logic Gates

- The inverter (NOT circuit) performs the operation called *inversion or complementation*.
- The inverter changes one logic level to the opposite level. In terms of bits, it changes a 1 to a 0 and a 0 to a 1.
- Standard logic symbols for the **inverter** are shown below:



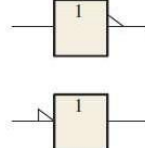(a) Distinctive shape symbols
with negation indicators



(b) Rectangular outline symbols
with polarity indicators

- The “bubble” indicates negation (**inversion or complementation**) when it appears on the input or output of any logic element.

2

Logic Gates

The inverter (NOT circuit)


- Inverter Truth Table

Inverter truth table.

| Input | Output |
|----------|----------|
| LOW (0) | HIGH (1) |
| HIGH (1) | LOW (0) |

- A **truth table** shows the output for each possible input in terms of levels and corresponding bits.

- Inverter Operation

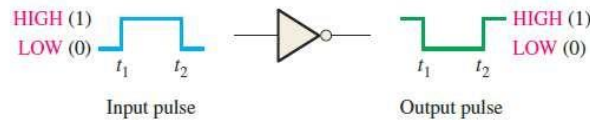

3


Logic Gates

The inverter (NOT circuit)

- Logic Expression for an Inverter

- In **Boolean algebra**, which is the mathematics of logic circuits, a variable is generally designated by one or two letters although there can be more.
- The **complement** of a variable is designated by a bar over the letter.
- The operation of an inverter (NOT circuit) can be expressed as follows: If the input variable is called A and the output variable is called X , then


$$X = \bar{A}$$

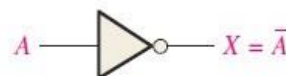

4

The inverter (NOT circuit) An Application

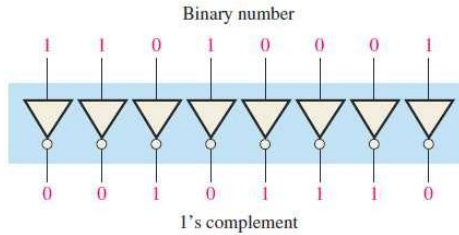- The figure below shows a circuit for producing the 1's complement of an 8-bit binary number.




- The bits of the binary number are applied to the inverter inputs and the 1's complement of the number appears on the outputs.


5

The AND Gate

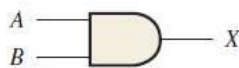- The term *gate* is used to describe a circuit that performs a basic logic operation.
- The **AND gate** is one of the basic gates that can be combined to form any logic function.
- An **AND gate** can have two or more inputs and performs what is known as **logical multiplication**.



(a) Distinctive shape

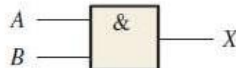

(b) Rectangular outline with the AND (&) qualifying symbol

Truth table for a 2-input AND gate.

| Inputs | | Output |
|--------|---|--------|
| A | B | X |
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

1 = HIGH, 0 = LOW

6

Logic Gates

- The total number of **possible combinations of binary inputs to a gate** is determined by the following formula:

$$N = 2^n$$

where N is the **number of possible input combinations** and n is the **number of input variables**.

Example: Develop the truth table for a 3-input AND gate

Solution:

| Inputs | | | Output |
|--------|---|---|--------|
| A | B | C | X |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |


7

AND Gate

- Logic Expressions for an AND Gate**
- The logical AND function of two variables is represented mathematically either by placing a dot between the two variables, as $A \cdot B$, or by simply writing the adjacent letters without the dot, as AB .
- Boolean multiplication** follows the same basic rules governing binary multiplication, and are as follows:

$$\begin{aligned} 0 \cdot 0 &= 0 \\ 0 \cdot 1 &= 0 \\ 1 \cdot 0 &= 0 \\ 1 \cdot 1 &= 1 \end{aligned}$$

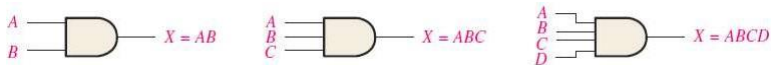Boolean multiplication is the same as the AND function.




Boolean expressions for AND gates with two, three, and four inputs.


8

The OR Gate

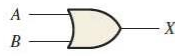- An **OR gate** performs what is known as **logical addition**.
- An **OR gate** can have two or more inputs and one output.



(a) Distinctive shape

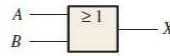

(b) Rectangular outline with the OR (≥ 1) qualifying symbol

OR Gate Truth Table

Truth table for a 2-input OR gate.

| Inputs | | Output |
|--------|---|--------|
| A | B | X |
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

9

OR Gate

- **Logic Expressions for an OR Gate**
- The logical OR function of two variables is represented mathematically by a **+** between the two variables, e.g., $X = A + B$. The plus sign is read as "OR."
- The basic rules for **Boolean addition** are as follows:


$$\begin{aligned} 0 + 0 &= 0 \\ 0 + 1 &= 1 \\ 1 + 0 &= 1 \\ 1 + 1 &= 1 \end{aligned}$$

- **Boolean addition is the same as the OR function.**

10

NAND Gate

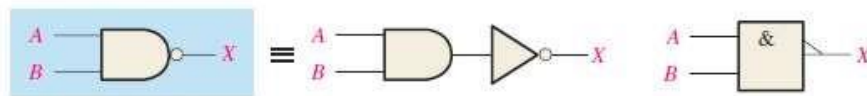- The **NAND gate** is a popular logic element because it can be used as a universal gate such that NAND gates can be used in combination to perform the **AND, OR, and inverter** operations.
- The **NAND gate** is the same as the AND gate except the output is inverted.



(a) Distinctive shape, 2-input NAND gate and its NOT/AND equivalent

(b) Rectangular outline, 2-input NAND gate with polarity indicator

11

NAND Gate

- A **NAND gate** produces a LOW output only when all the inputs are HIGH. When any of the inputs is LOW, the output will be HIGH.
- The table below is for the specific case of a 2-input **NAND gate**

Truth table for a 2-input NAND gate.


| Inputs | | Output |
|--------|---|--------|
| A | B | X |
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

1 = HIGH, 0 = LOW.

12

NAND Gate

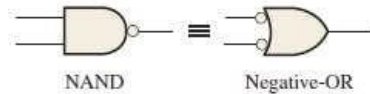- **Negative-OR Equivalent Operation of a NAND Gate**
- For a 2-input NAND gate performing a negative-OR operation, output X is HIGH when either input A or input B is LOW, or when both A and B are LOW.





| A | B | $\overline{AB} = X$ |
|-----|-----|---|
| 0 | 0 | $\overline{0 \cdot 0} = \overline{0} = 1$ |
| 0 | 1 | $\overline{0 \cdot 1} = \overline{0} = 1$ |
| 1 | 0 | $\overline{1 \cdot 0} = \overline{0} = 1$ |
| 1 | 1 | $\overline{1 \cdot 1} = \overline{1} = 0$ |

- **Logic Expressions for a NAND Gate**
- The Boolean expression for the output of a 2-input NAND gate is $X = \overline{AB}$ where a bar over a variable or variables indicates an inversion.

13

The NOR Gate

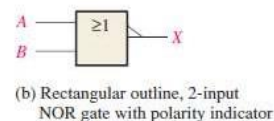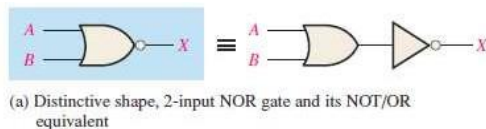- The **NOR gate**, like the NAND gate, is a useful logic element because it can also be used as a universal gate.
- The NOR is the same as the **OR** except the output is inverted.



- **Operation of a NOR Gate**

Truth table for a 2-input NOR gate.


| Inputs | | Output |
|--------|-----|--------|
| A | B | X |
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

1 = HIGH, 0 = LOW.

14

The NOR Gate

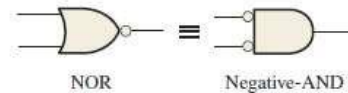- **Negative-AND Equivalent Operation of the NOR Gate**
- For a 2-input NOR gate performing a negative-AND operation, output X is HIGH only when both inputs A and B are LOW.



- **Logic Expressions for a NOR Gate**

The Boolean expression for the output of a 2-input NOR gate can be written as

$$X = \overline{A + B}$$

| A | B | $\overline{A + B} = X$ |
|-----|-----|---------------------------------------|
| 0 | 0 | $\overline{0 + 0} = \overline{0} = 1$ |
| 0 | 1 | $\overline{0 + 1} = \overline{1} = 0$ |
| 1 | 0 | $\overline{1 + 0} = \overline{1} = 0$ |
| 1 | 1 | $\overline{1 + 1} = \overline{1} = 0$ |


15

The Exclusive-OR Gate


- The output of an exclusive-OR gate is HIGH *only* when the two inputs are at opposite logic levels.

Truth table for an exclusive-OR gate.

| Inputs | | Output |
|--------|-----|--------|
| A | B | X |
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

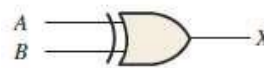

(a) Distinctive shape

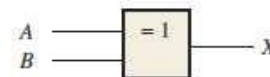

(b) Rectangular outline


16

The Exclusive-NOR Gate


- For an **exclusive-NOR gate**, output X is LOW when input A is LOW and input B is HIGH, or when A is HIGH and B is LOW; X is HIGH when A and B are both HIGH or both LOW.

Truth table for an exclusive-NOR gate.

| Inputs | | Output |
|--------|-----|--------|
| A | B | X |
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

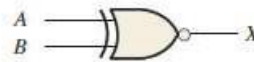

(a) Distinctive shape

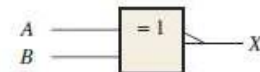

(b) Rectangular outline


17

Timing Diagrams

- a **timing diagram** is basically a graph that accurately displays the relationship of two or more waveforms with respect to each other on a time basis.

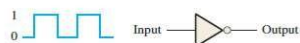- Example:**


- A waveform is applied to an inverter in the figure below.



- Determine the output waveform corresponding to the input and show the timing diagram.

- Solution:**

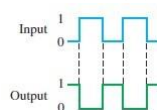- The output waveform is exactly opposite to the input (inverted).



18



Boolean Algebra and Logic Simplification

- Boolean algebra is the mathematics of digital logic.
- A **variable** is a symbol (usually an italic uppercase letter or word) used to represent an action, a condition, or data. In Boolean algebra, any single variable can have only a 1 or a 0 value.
- The **complement** is the inverse of a variable and it is indicated by a bar over the variable (overbar). For example, the complement of the variable A is \bar{A} . If $A = 1$, then $\bar{A} = 0$. If $A = 0$, then $\bar{A} = 1$.
- The **complement** of the variable A is read as “not A ” or “ A bar.” Sometimes a prime symbol rather than an overbar is used to denote the complement of a variable; for example, A' indicates a complement of A .
- A **literal** is a variable or the complement of a variable.

19

Boolean Addition

- The **Boolean addition** is equivalent to the **OR** operation.
- In Boolean algebra, a **sum term** is a sum of literals.
- Some examples of sum terms are $A + B$, $A + \bar{B}$, $A + B + \bar{C}$, and $\bar{A} + B + C + D$.
- A **sum term** is equal to 1 when one or more of the literals in the term are 1. A **sum term** is equal to 0 only if each of the literals is 0.
- **Example:** Determine the values of A , B , C , and D that make the sum term $A + \bar{B} + C + \bar{D}$ equal to 0.
- **Solution:**
- For the sum term to be 0, each of the literals in the term must be 0. Therefore, $A = 0$, $B = 1$ so that $\bar{B} = 0$, $C = 0$, and $D = 1$ so that $\bar{D} = 0$.
- $A + \bar{B} + C + \bar{D} = 0 + 1 + 0 + 1 = 0 + 0 + 0 + 0 = 0$

20


Boolean Multiplication

- **Boolean multiplication** is equivalent to the **AND** operation.
- In Boolean algebra, a **product term** is the product of literals.
- Some examples of product terms are $A\bar{B}$, AB , ABC , and $A\bar{B}C\bar{D}$.
- A **product term** is equal to **1** only if **each** of the **literals** in the term is **1**. A **product term** is equal to **0** when **one or more** of the literals are **0**.
- **Example:** Determine the values of A , B , C , and D that make the product term $ABCD$ equal to 1.
- **Solution:**
 - For the product term to be 1, each of the literals in the term must be 1. Therefore, $A = 1$, $B = 0$ so that $\bar{B} = 1$, $C = 1$, and $D = 0$ so that $\bar{D} = 1$.
 - $ABCD = 1 \cdot 0 \cdot 1 \cdot 0 = 1 \cdot 1 \cdot 1 \cdot 1 = 1$

21

Laws and Rules of Boolean Algebra

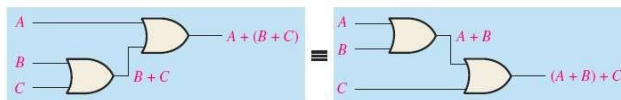- The **commutative law of addition** for two variables is written as:
 $A+B = B+A$
- The **commutative law of multiplication** for two variables is:
 $AB = BA$
- The **associative law of addition** is written as follows for three variables:
 $A+(B+C) = (A+B)+C$



The **associative law of multiplication** is written as follows for three variables:

$$A(BC) = (AB)C$$


22

Laws and Rules of Boolean Algebra

- **Distributive Law**

- The distributive law is written for three variables as follows:

$$A(B+C)=AB+AC$$

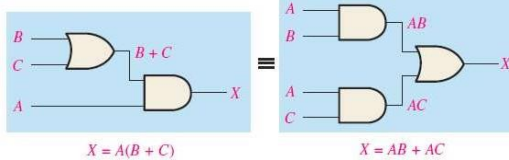

Basic rules of Boolean algebra

- | | |
|----------------------|-------------------------------|
| 1. $A + 0 = A$ | 7. $A \cdot A = A$ |
| 2. $A + 1 = 1$ | 8. $A \cdot \bar{A} = 0$ |
| 3. $A \cdot 0 = 0$ | 9. $\bar{\bar{A}} = A$ |
| 4. $A \cdot 1 = A$ | 10. $A + AB = A$ |
| 5. $A + A = A$ | 11. $A + \bar{A}B = A + B$ |
| 6. $A + \bar{A} = 1$ | 12. $(A + B)(A + C) = A + BC$ |

A , B , or C can represent a single variable or a combination of variables.

23

Rules of Boolean Algebra

- **Rule 1:** $A + 0 = A$. A variable ORed with 0 is always equal to the variable.
- **Rule 2:** $A + 1 = 1$. A variable ORed with 1 is always equal to 1.
- **Rule 3:** $A \cdot 0 = 0$. A variable ANDed with 0 is always equal to 0.
- **Rule 4:** $A \cdot 1 = A$. A variable ANDed with 1 is always equal to the variable.
- **Rule 5:** $A + A = A$. A variable ORed with itself is always equal to the variable.
- **Rule 6:** $A + \bar{A} = 1$. A variable ORed with its complement is always equal to 1.
- **Rule 7:** $A \cdot A = A$. A variable ANDed with itself is always equal to the variable.
- **Rule 8:** $A \cdot \bar{A} = 0$. A variable ANDed with its complement is always equal to 0.
- **Rule 9:** $\bar{\bar{A}} = A$. The double complement of a variable is always equal to the variable.


24

Rules of Boolean Algebra

- **Rule 10:** $A + AB = A$. This rule can be proved by applying the distributive law, rule 2, and rule 4 as follows:

$$\begin{aligned}
 A + AB &= A \cdot 1 + AB = A(1 + B) && \text{Factoring (distributive law)} \\
 &= A \cdot 1 && \text{Rule 2: } (1 + B) = 1 \\
 &= A && \text{Rule 4: } A \cdot 1 = A
 \end{aligned}$$

| A | B | AB | A + AB |
|---|---|----|--------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 |

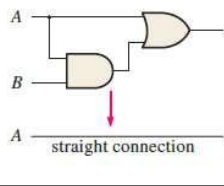

↑ equal ↑


25

Rules of Boolean Algebra

- **Rule 11:** $A + \overline{A}B = A + B$. This rule can be proved as follows:

$$\begin{aligned}
 A + \overline{A}B &= (A + AB) + \overline{A}B && \text{Rule 10: } A = A + AB \\
 &= (AA + AB) + \overline{A}B && \text{Rule 7: } A = AA \\
 &= AA + AB + \overline{A}A + \overline{A}B && \text{Rule 8: adding } \overline{A}A = 0 \\
 &= (A + \overline{A})(A + B) && \text{Factoring} \\
 &= 1 \cdot (A + B) && \text{Rule 6: } A + \overline{A} = 1 \\
 &= A + B && \text{Rule 4: drop the 1}
 \end{aligned}$$

| A | B | $\overline{A}B$ | $A + \overline{A}B$ | $A + B$ |
|---|---|-----------------|---------------------|---------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 |

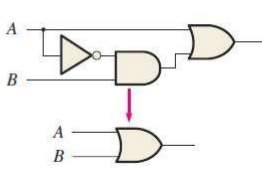

↑ equal ↑


26

Rules of Boolean Algebra

- **Rule 12:** $(A + B)(A + C) = A + BC$. This rule can be proved as follows:

$$\begin{aligned}
 (A + B)(A + C) &= AA + AC + AB + BC && \text{Distributive law} \\
 &= A + AC + AB + BC && \text{Rule 7: } AA = A \\
 &= A(1 + C) + AB + BC && \text{Factoring (distributive law)} \\
 &= A \cdot 1 + AB + BC && \text{Rule 2: } 1 + C = 1 \\
 &= A(1 + B) + BC && \text{Factoring (distributive law)} \\
 &= A \cdot 1 + BC && \text{Rule 2: } 1 + B = 1 \\
 &= A + BC && \text{Rule 4: } A \cdot 1 = A
 \end{aligned}$$

| A | B | C | A + B | A + C | (A + B)(A + C) | BC | A + BC |
|---|---|---|-------|-------|----------------|----|--------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

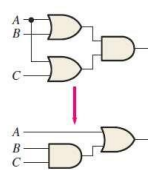

27

DeMorgan's Theorems

- **DeMorgan's first theorem** is stated as follows:
- **The complement of a product of variables is equal to the sum of the complements of the variables.**

The formula for expressing this theorem for two variables is

$$\overline{XY} = \overline{X} + \overline{Y}$$

DeMorgan's second theorem is stated as follows:

- **The complement of a sum of variables is equal to the product of the complements of the variables.**

The formula for expressing this theorem for two variables is

$$\overline{X + Y} = \overline{X} \overline{Y}$$

28



Applying DeMorgan's Theorems

- The following procedure illustrates the application of DeMorgan's theorems and Boolean algebra to the specific expression

$$\overline{\overline{A + BC} + D(E + F)}$$

Step 1: Identify the terms to which you can apply DeMorgan's theorems, and think of each term as a single variable. Let $A + BC = X$ and $D(E + F) = Y$.

Step 2: Since $\overline{X + Y} = \overline{X}\overline{Y}$,

$$\overline{(A + BC) + (D(E + F))} = \overline{(A + BC)}\overline{(D(E + F))}$$

Step 3: Use rule 9 ($\overline{\overline{A}} = A$) to cancel the double bars over the left term (this is not part of DeMorgan's theorem).

$$(A + BC)\overline{(D(E + F))} = (A + BC)\overline{(D(E + F))}$$

Step 4: Apply DeMorgan's theorem to the second term.

$$(A + BC)\overline{(D(E + F))} = (A + BC)(\overline{D} + \overline{(E + F)})$$

Step 5: Use rule 9 ($\overline{\overline{A}} = A$) to cancel the double bars over the $E + F$ part of the term.

$$(A + BC)(\overline{D} + \overline{E + F}) = (A + BC)(\overline{D} + \overline{E} + \overline{F})$$

29

Applying DeMorgan's Theorems

- Example:** Apply DeMorgan's theorems to the following expression:

$$\overline{(A + B + C)D}$$

- Solution:**

Let $A + B + C = X$ and $D = Y$. The expression $\overline{(A + B + C)D}$ is of the form $\overline{XY} = \overline{X} + \overline{Y}$ and can be rewritten as

$$\overline{(A + B + C)D} = \overline{A + B + C} + \overline{D}$$

Next, apply DeMorgan's theorem to the term $\overline{A + B + C}$.

$$\overline{A + B + C} + \overline{D} = \overline{A} \overline{B} \overline{C} + \overline{D}$$

30



Applying DeMorgan's Theorems

- Example: Apply DeMorgan's theorems to the following expression:

$$\overline{ABC + DEF}$$

Solution

Let $ABC = X$ and $DEF = Y$. The expression $\overline{ABC + DEF}$ is of the form $\overline{X + Y} = \overline{XY}$ and can be rewritten as

$$\overline{ABC + DEF} = (\overline{ABC})(\overline{DEF})$$

Next, apply DeMorgan's theorem to each of the terms \overline{ABC} and \overline{DEF} .

$$(\overline{ABC})(\overline{DEF}) = (\overline{A} + \overline{B} + \overline{C})(\overline{D} + \overline{E} + \overline{F})$$

31

Applying DeMorgan's Theorems

- Example: Apply DeMorgan's theorems to the following expression:

$$\overline{\overline{AB} + \overline{CD} + EF}$$

- Solution:

Let $\overline{AB} = X$, $\overline{CD} = Y$, and $EF = Z$. The expression $\overline{\overline{AB} + \overline{CD} + EF}$ is of the form $\overline{X + Y + Z} = \overline{XYZ}$ and can be rewritten as

$$\overline{\overline{AB} + \overline{CD} + EF} = (\overline{\overline{AB}})(\overline{\overline{CD}})(\overline{EF})$$

Next, apply DeMorgan's theorem to each of the terms $\overline{\overline{AB}}$, $\overline{\overline{CD}}$, and \overline{EF} .

$$(\overline{\overline{AB}})(\overline{\overline{CD}})(\overline{EF}) = (\overline{A} + \overline{B})(\overline{C} + \overline{D})(\overline{E} + \overline{F})$$

32



Applying DeMorgan's Theorems

- Example: Apply DeMorgan's theorems to each of the following expressions:

(a) $\overline{\overline{A + B} + \overline{C}}$

(b) $\overline{\overline{A + B} + CD}$

(c) $\overline{(A + B)\overline{CD} + E + \overline{F}}$

- Solution

(a) $\overline{\overline{A + B} + \overline{C}} = \overline{\overline{A + B}}\overline{\overline{C}} = (A + B)C$

(b) $\overline{\overline{A + B} + CD} = \overline{\overline{A + B}}\overline{CD} = (\overline{\overline{A}}\overline{\overline{B}})(\overline{C} + \overline{D}) = \overline{A}\overline{B}(\overline{C} + \overline{D})$

(c) $\overline{(A + B)\overline{CD} + E + \overline{F}} = \overline{(A + B)\overline{CD}}\overline{E + \overline{F}} = \overline{\overline{A + B}}\overline{\overline{CD}}(\overline{E + \overline{F}}) = (\overline{\overline{A}}\overline{\overline{B}} + C + D)\overline{E + \overline{F}}$

33

Applying DeMorgan's Theorem

- Example:

- The Boolean expression for an exclusive-OR gate is $\overline{A}B + A\overline{B}$. With this as a starting point, use DeMorgan's theorems and any other rules or laws that are applicable to develop an expression for the exclusive-NOR gate.

- Solution:

Start by complementing the exclusive-OR expression and then applying DeMorgan's theorems as follows:

$$\overline{\overline{A}B + A\overline{B}} = \overline{\overline{A}B}\overline{A\overline{B}} = (\overline{\overline{A}}\overline{\overline{B}})(\overline{A} + \overline{\overline{B}}) = (\overline{A} + B)(A + \overline{B})$$

Next, apply the distributive law and rule 8 ($A \cdot \overline{A} = 0$).

$$(\overline{A} + B)(A + \overline{B}) = \overline{A}A + \overline{A}\overline{B} + AB + B\overline{B} = \overline{A}\overline{B} + AB$$

The final expression for the XNOR is $\overline{A}\overline{B} + AB$. Note that this expression equals 1 any time both variables are 0s or both variables are 1s.

34

