

1 Equivalent Circuit of a Single-Phase Transformer

The analysis of a transformer can be carried out by using an equivalent circuit which can be derived by considering the following: -

- The primary and secondary windings have finite resistances considered as lumped parameters.
- The leakage fluxes are modelled as leakage reactance in the equivalent circuit.
- The core-loss component of current is modelled using a shunt resistance.
- The magnetization of the core is modelled using a magnetizing reactance as a shunt branch.

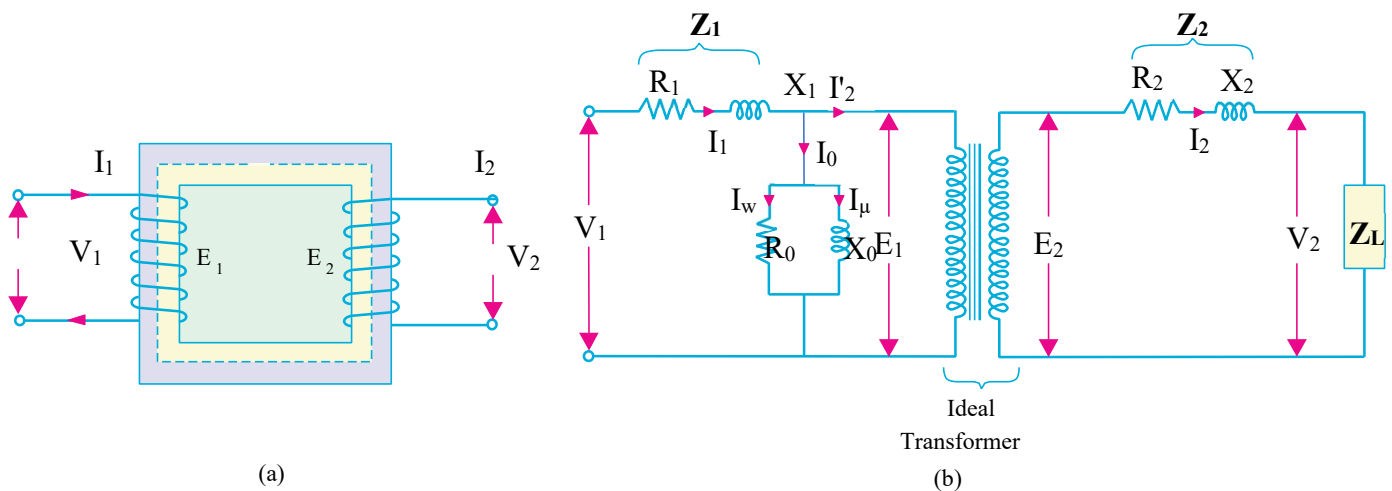


Fig.1 Diagram of equivalent circuit for the transformer with load

The transformer shown diagrammatically in Fig.1 (a) can be resolved into an equivalent circuit in which the resistance and leakage reactance of the transformer are



imagined to be external to the winding whose only function then is to transform the voltage.

Generally, there are two modes of operations in the transformers which are:

- 1- [No-load operation](#).
- 2- [On load operation](#).

The voltages, currents and elements of the circuit can be defined as in Table 1.

SYMBOL	DEFINITION
R_1, R_2	Primary and secondary resistances
X_1, X_2	primary and secondary leakage reactance
R_0	Exciting resistance
X_0	Exciting reactance
I_1	Primary side current
I_0	No-load/Excitation current component of primary current
I_w (or I_{c1})	Core-loss component of no-load current
I_μ (or I_{m1})	Magnetizing component of no-load current
I'_2	Load component of primary current
I_2	Secondary side current (load current)
V_1	Applied primary side voltage
V_2	Secondary side terminal voltage
E_1	Primary side induced emf
E_2	Secondary side induced emf

Table 1 Quantities of equivalent circuit.

1.1 Transformer at No-load

A transformer is said to be on no-load when its secondary winding is kept open and no-load is connected across it. As such, no current flows through the secondary i.e., $I_2 = 0$. Hence, the secondary winding is not causing any effect on the magnetic flux set-up in the core or on the current drawn by the primary. But the losses cannot



be ignored. At no-load, a transformer draws a small current I_0 (usually 2 to 10% of the rated value). This current has to supply the iron losses (hysteresis and eddy current losses) in the core and a very small amount of copper loss in the primary (the primary copper losses are so small as compared to core losses that they are generally neglected moreover secondary copper losses are zero as I_2 is zero).

Therefore, current I_0 lags behind the voltage vector V_1 by an angle ϕ_0 (called hysteresis angle of advance) which is less than 90° , as shown in Fig. 2. The angle of lag depends upon the losses in the transformer.

The basic equations in this mode can viewed as follows: -

Working component,	$I_w = I_0 \cos \phi_0$
Magnetizing component,	$I_\mu = I_0 \sin \phi_0$
No-load current,	$I_0 = \sqrt{I_\mu^2 + I_w^2}$ $I_0 = I_w + jI_\mu$
Primary p.f. at no-load,	$\cos \phi_0 = \frac{I_w}{I_0}$
No-load power input,	$P_0 = V_1 I_0 \cos \phi_0$
Exciting resistance,	$R_0 = \frac{V_1}{I_w}$
Exciting reactance	$X_0 = \frac{V_1}{I_\mu}$

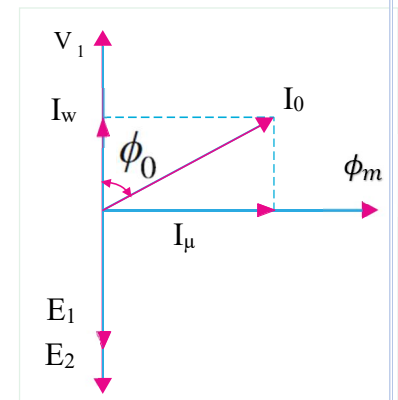


Fig.2 No-load current

Table 2. No-load parameters in transformer.

Examples 1: A 230/110 V single-phase transformer has a core loss of 100 W. If the input under no-load condition is 400 VA, find core loss current, magnetizing current and no-load power factor angle.



Solution

$$\text{No-load current } V_1 I_0 = 400 \text{ VA}, I_0 = \frac{400}{230} = \mathbf{1.739 \text{ A}}$$

$$\text{Core loss current } I_w = \frac{P_i}{V_1} = \frac{100}{230} = \mathbf{0.4348 \text{ A}}$$

$$\text{Magnetizing current } I_\mu = \sqrt{I_0^2 - I_w^2} = \sqrt{(1.739)^2 - (0.4348)^2} = \mathbf{1.684 \text{ A}}$$

$$\text{No-load power factor, } \cos \phi_0 = \frac{I_w}{I_0} = \frac{0.4348}{1.739} = \mathbf{0.25 \text{ lag}}$$

$$\text{No-load power factor angle } \phi_0 = \cos^{-1} 0.25 = \mathbf{75.52^\circ}$$

Example 2: At open circuit, transformer of 10 kVA, 500/250 V, 50 Hz draws a power of 167 watt at 0.745 A, 500 V. Determine the magnetizing current, R_0 current, no-load power factor, hysteresis angle of advance, equivalent resistance and reactance of exciting circuit referred to primary side.

Solution

$$V_1 = 500 \text{ V}, I_0 = 0.745 \text{ A}, P_0 = 167 \text{ W}$$

$$I_w = \frac{P_0}{V_1} = \frac{167}{500} = \mathbf{0.334 \text{ A}}$$

$$I_\mu = \sqrt{I_0^2 - I_w^2} = \sqrt{(0.745)^2 - (0.334)^2} = \mathbf{0.666 \text{ A}}$$

$$\cos \phi_0 = \frac{I_w}{I_0} = \frac{0.334}{0.745} = \mathbf{0.448 \text{ lag}}$$

$$\phi_0 = \cos^{-1} 0.448 = \mathbf{63.36^\circ \text{ lag}}$$

$$R_0 = \frac{V_1}{I_w} = \frac{500}{0.334} = \mathbf{1497 \Omega}$$



$$X_0 = \frac{V_1}{I_\mu} = \frac{500}{0.666} = 750 \, \Omega$$

1.2 Transformer on load

When the secondary is loaded, the secondary current I_2 is set up. The magnitude and phase of I_2 with respect to V_2 is determined by the characteristics of the load. Current I_2 is in phase with V_2 if load is non-inductive, it lags if load is inductive and it leads if load is capacitive. A set of equation can be drawn using basic theory of electric circuit analysis.

Applying KVL in the primary side of equivalent circuit: -

$$V_1 = E_1 + I_1(R_1 + jX_1)$$

Applying KVL in the secondary side of equivalent circuit: -

$$E_2 = V_2 + I_2(R_2 + jX_2)$$

Since $\frac{E_1}{E_2} = \frac{I_2}{I_1'} = a = \frac{1}{k}$ using $E_1 = aE_2$ we get:

$$V_1 = aE_2 + I_1(R_1 + jX_1)$$

Then we can rewrite the equation of V_1 by substituting the equation of E_2 .

$$V_1 = a[V_2 + I_2(R_2 + jX_2)] + I_1(R_1 + jX_1)$$

$$\text{Since } I_2 = aI_1' \Rightarrow V_1 = [aV_2 + I_1'a^2(R_2 + jX_2)] + I_1(R_1 + jX_1)$$

$$\text{Let } R_2' = a^2R_2 \text{ and } X_2' = a^2X_2$$

Where R_2' is called secondary resistance referred to the primary side and X_2' is called secondary leakage reactance referred to the primary side.

Another modification to V_1 applying the same rules above then:

$$V_1 = V_2' + I_2'(R_2' + jX_2') + I_1(R_1 + jX_1)$$

Where

$V_2' = aV_2$ is called secondary voltage referred to the primary side, $I_2' = \frac{I_2}{a}$ is called secondary current referred to the primary side.

In Table 3 shown the quantities of the secondary side with their referred quantities.

Referred to the primary	Referred to the secondary
$E_1 = E_2' = \frac{E_2}{k}$	$E_1' = E_2 = kE_1$
$V_2' = \frac{V_2}{k}$	$V_1' = kV_1$
$I_2' = kI_2$	$I_1' = \frac{I_1}{k}$
$X_2' = \frac{X_2}{k^2}$	$X_1' = k^2X_1$
$R_2' = \frac{R_2}{k^2}$	$R_1' = k^2R_1$

Table 3. Referred quantities.

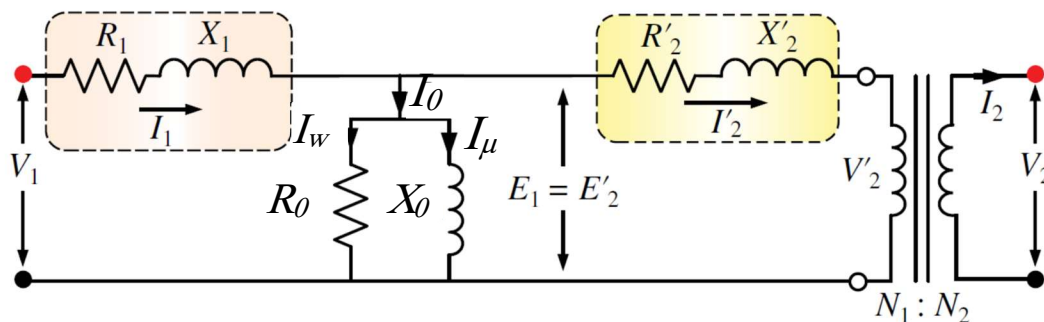


Fig 3. Modified equivalent circuit of a single-phase transformer.

1.3 Exact Equivalent Circuit

The transformer circuit can be moved to the right or left by referring all quantities to the primary or secondary side, respectively. This is almost invariably done. The equivalent circuit moved to primary is shown in Fig. 3.

If we shift all the impedances from one winding to the other, the transformer core is eliminated and we get an equivalent electrical circuit. Various voltages and currents can be readily obtained by solving this electrical circuit.

1.4 Approximate Equivalent Circuit

The equivalent circuit can be simplified by assuming small voltage drop across the primary impedance and $V_1 = E_1$. If the applied voltage and the induced emf are the same then the shunt branch can be moved across the source voltage and the approximate equivalent circuit is drawn as shown in Figure 4.

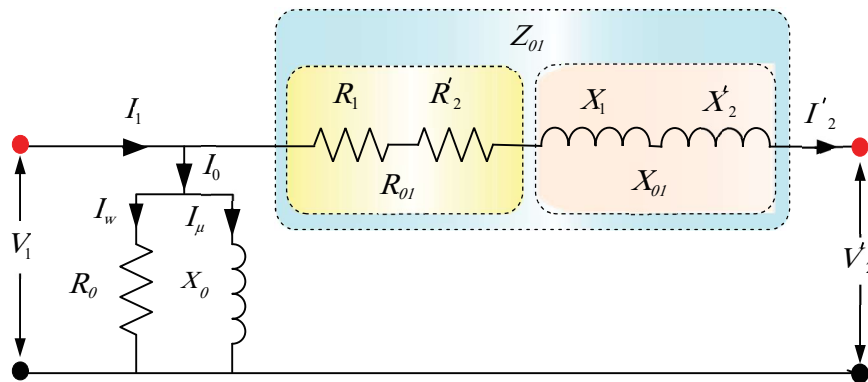


Fig 4. Approximate equivalent circuit

From the equivalent circuit the following relations are obtained

$$R_{01} = R_1 + R_2' \quad , \quad X_{01} = X_1 + X_2'$$

$$Z_{01} = R_{01} + jX_{01}$$



Example 3: A 30 kVA, 2400/120 V, 50-Hz transformer has a high voltage winding resistance of 0.1Ω and a leakage reactance of 0.22Ω . The low voltage winding resistance is 0.035Ω and the leakage reactance is 0.012Ω . Find the equivalent winding resistance, reactance and impedance (only magnitude) referred to:

1- High Voltage Side.

2- Low-Voltage Side.

Solution

$$k = \frac{120}{2400} = 1/20, R_1 = 0.1 \Omega, X_1 = 0.22 \Omega$$

$$R_2 = 0.035 \Omega \text{ and } X_2 = 0.012 \Omega$$

1- For high voltage side

$$R_{01} = R_1 + R'_2 = R_1 + \frac{R_2}{k^2} = 0.1 + \frac{0.035}{\left(\frac{1}{20}\right)^2} = \mathbf{14.1 \Omega}$$

$$X_{01} = X_1 + X'_2 = X_1 + \frac{X_2}{k^2} = 0.22 + \frac{0.012}{\left(\frac{1}{20}\right)^2} = \mathbf{5.02 \Omega}$$

$$Z_{01} = \sqrt{R_{01}^2 + X_{01}^2} = \sqrt{14.1^2 + 5.02^2} = \mathbf{15 \Omega}$$

2- For low voltage side

$$R_{02} = R_2 + R'_1 = R_2 + k^2 R_1 = 0.035 + \left(\frac{1}{20}\right)^2 \times 0.1 = \mathbf{0.03525 \Omega}$$

$$X_{02} = X_2 + X'_1 = X_2 + k^2 X_1 = 0.012 + \left(\frac{1}{20}\right)^2 \times 0.22 = \mathbf{0.0125 \Omega}$$

$$Z_{02} = \sqrt{R_{02}^2 + X_{02}^2} = \sqrt{0.0325^2 + 0.0125^2} = \mathbf{0.0374 \Omega}$$



Example 4: The parameters of a 2300/230 V, 50-Hz transformer are given below:

$$R_1 = 0.286 \, \Omega, \quad R'_2 = 0.319 \, \Omega, \quad R_0 = 250 \, \Omega$$

$$X_1 = 0.73 \, \Omega, \quad X'_2 = 0.73 \, \Omega, \quad X_0 = 1250 \, \Omega$$

The secondary load impedance $Z_L = 0.387 + j 0.29 \, \Omega$. Using the exact equivalent circuit Calculate the following.

- 1- Primary power factor.
- 2- Power input.
- 3- Power output.
- 4- Cu loss.
- 5- Efficiency.

Solution

$$k = 230/2300 = 0.1, \quad Z_L = 0.387 + j 0.29 \, \Omega$$

$$Z'_L = Z_L / k^2 = 100 (0.387 + j 0.29) = 38.7 + j 29 = 48.4 \angle 36.8^\circ \, \Omega$$

$$Z'_2 + Z'_L = (38.7 + 0.319) + j(29 + 0.73) = 39.02 + j29.73 = 49 \angle 37.3^\circ \, \Omega$$

$$1/Z_m = 1/R_0 + 1/jX_0 \Rightarrow Z_m = 240 + j48 = 245 \angle 11.3^\circ \, \Omega$$

$$Z_m // (Z'_2 + Z'_L) = 245 \angle 11.3^\circ // 49 \angle 37.3^\circ = 41.4 \angle 33^\circ \, \Omega$$

$$Z_{t1} = Z_1 + (Z_m // (Z'_2 + Z'_L)) = (0.286 + j 0.73) + 41.4 \angle 33^\circ = 42 \angle 33.7^\circ \, \Omega$$

$$I_1 = V_1 / Z_{t1} = 2300 \angle 0^\circ / 42 \angle 33.7^\circ = 54.8 \angle -33.7^\circ \, A$$

$$Z_m + Z'_2 + Z'_L = 245 \angle 11.3^\circ + 49 \angle 37.3^\circ = 290 \angle 15.6^\circ \, \Omega$$

$$I'_2 = I_1 \times \left(\frac{Z_m}{Z'_2 + Z'_L + Z_m} \right) = 54.8 \angle -33.7^\circ \times 0.845 \angle -4.3^\circ = 46.2 \angle -38^\circ \, A$$

$$I_0 = I_1 \times \left(\frac{Z'_2 + Z'_L}{Z'_2 + Z'_L + Z_m} \right) = 54.8 \angle -33.7^\circ \times \frac{49 \angle 37.3^\circ}{290 \angle 15.6^\circ} = 9.26 \angle -12^\circ \, A$$

- 1- Primary power factor = $\cos(33.7) = 0.832 \, \text{lag}$



2- Power input = $V_1 I_1 \cos \phi_1 = 2300 \times 54.8 \times 0.832 = \mathbf{105 \text{ kW}}$

3- Power output = $I_2'^2 R_L' = 46.2^2 \times 38.7 = \mathbf{82.7 \text{ kW}}$

4- Primary Cu loss = $54.8^2 \times 0.286 = \mathbf{860 \text{ W}}$

Secondary Cu loss = $46.2^2 \times 0.319 = \mathbf{680 \text{ W}}$


Core Cu loss = $9.26^2 \times 240 = \mathbf{20.6 \text{ kW}}$

5- Efficiency = $\frac{82.7}{105} \times 100 = \mathbf{78.8 \%}$

Example 5: The equivalent circuit parameters of a single-phase 240/2400, 50 Hz, transformer are $R_0 = 600 \Omega$, $X_0 = 300 \Omega$, $R_{01} = 0.25 \Omega$, $X_{01} = 0.75 \Omega$. The transformer is supplying a load of $400 + j 200 \Omega$. Keeping the primary voltage of 240V, calculate the

- 1- The secondary terminal voltage
- 2- Current in the primary winding
- 3- Power factor of the primary side
- 4- Power output
- 5- Power Input

Solution

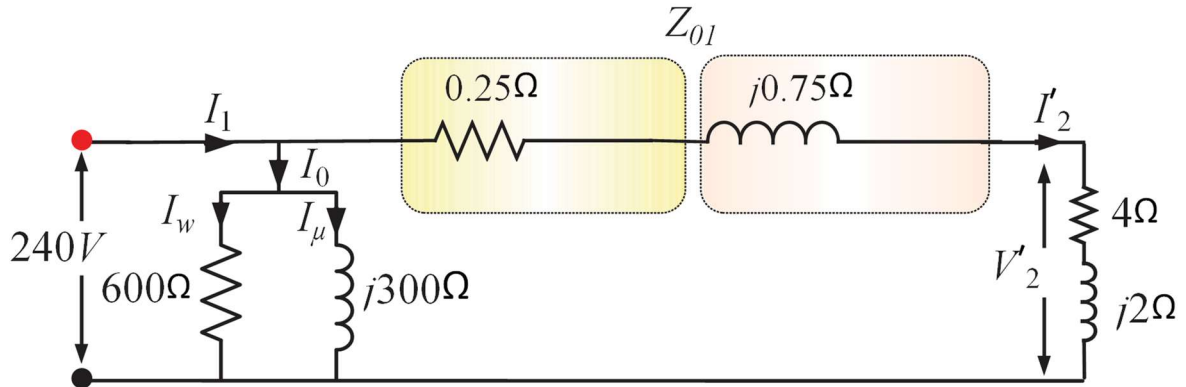

Since the equivalent circuit is referred to the low voltage (primary side), the load impedance is also transformed to the low voltage side.

$$k = 2400/240 = 10$$

$$Z'_L = Z_L / k^2 = (400 + j200) (0.1)^2 = 4 + j2 \Omega$$

$$Z'_L + Z_{01} = 0.25 + j0.75 + 4 + j2 = 4.25 + j2.75 = 5.062 \angle 32.9^\circ \Omega$$

$$I'_2 = V_1 / (Z'_L + Z_{01}) = \frac{240 \angle 0^\circ}{5.062 \angle 32.9^\circ} = 47.412 \angle -32.9^\circ = 39.8 - j25.753 \text{ A}$$

1- Secondary terminal voltage (without phase)

$$V'_2 = I'_2 Z_L = 5.062 \times \sqrt{4^2 + 2^2} = 212.03 \text{ V}$$

2- Primary current:

$$\text{The core loss component of current } I_w = \frac{V_1}{R_0} = \frac{240}{600} = 0.4 \text{ A}$$

$$\text{The magnetizing component of current } I_\mu = \frac{V_1}{X_0} = \frac{240}{300} = 0.8 \text{ A}$$

$$\text{The no-load current } I_0 = I_w + jI_\mu = 0.4 - j0.8 \text{ A}$$

The primary current



$$I_1 = I_0 + I'_2 = 39.8 - j25.753 + 0.4 - j0.8 = 40.2 - j26.553 = \mathbf{48.178 \angle -}$$

33.44 A

3- Power factor of the primary current $\text{pf} = \cos(33.44) = \mathbf{0.834 \text{ lagging}}$

4- Power output $= I_2'^2 R'_L = 47.412^2 \times 4 = \mathbf{8.99 \text{ kW}}$

5- Power Input $= V_1 I_1 \cos \phi_1 = 240 \times 48.178 \times \cos(33.44) = \mathbf{9.65 \text{ kW}}$