



جامعة المستقبل  
AL MUSTAQBAL UNIVERSITY

كلية العلوم  
قسم علوم الامن السيبراني  
Cyber Security Department

**Subject: Shift Registers and Their Types in Stream Ciphers**

**Class: 2nd**

**Lecturer: Asst.Lect Mustafa Ameer Awadh**

**Lecture: (4)**



## Introduction to Shift Registers

Shift registers are fundamental components in digital electronics, playing a crucial role in data storage, manipulation, and transfer. As a type of sequential logic circuit, they are designed to store multiple bits of data and facilitate the movement of this data in a controlled manner. Shift registers can shift data either to the left or to the right, making them versatile tools for various applications, including data serialization, parallel-to-serial conversion, and digital signal processing.

- **Definition:** A shift register is a sequential logic circuit that is used to store and shift data. It's composed of a series of flip-flops connected in a chain, where each flip-flop holds a single bit.
- **Basic Structure:** Typically consists of flip-flops connected in series, with outputs connected to the inputs of the next flip-flop.
- **Data Shifting:** Data moves from one flip-flop to the next on each clock cycle, which is why it's called a "shift" register.


## Types of Shift Registers

- **Serial-in Serial-out (SISO):** Data enters one bit at a time and shifts out one bit at a time. Commonly used for data transmission. (fig.1 shows the SISO operation)
- **Serial-in Parallel-out (SIPO):** Data is input serially, and after shifting through the register, it's available at all output pins simultaneously. Useful for converting serial data to parallel format.



- Parallel-in Serial-out (PISO): Data is loaded into the register simultaneously (in parallel) and then shifted out serially. Useful for converting parallel data to serial.
- Parallel-in Parallel-out (PIPO): Data is loaded and output in parallel. Often used for temporary data storage.


These are used in digital systems for data storage, data transfer, and in cryptographic systems.

 

**Fig.1** shows the SISO operation.

### Initial State:

Assume all the flip-flops (Q1, Q2, and Q3) initially hold 0. **Clock Cycle 1** The data bit at the In input (e.g., 1) is transferred to Q1. Q1 now holds 1, and Q2 and Q3 still hold 0. **Clock Cycle 2** The value of Q1 (now 1) shifts to Q2, and a new bit at the In input enters Q1. If In is 0, then Q1 = 0, Q2 = 1, and Q3 = 0. **Clock Cycle 3** The value of Q2 (now 1) shifts to Q3, and Q1 and Q2 receive new bits from the input and from Q1, respectively.

 

**Fig.2** Shows SIPO operation.

**1. D Flip-Flops (Flip Flop 1, Flip Flop 2, Flip Flop 3, Flip Flop 4):**

- Each block labeled D is a D flip-flop, used to store one bit.
- Each flip-flop has a D input (data), a Q output, a clock input (Clock), and a clear input (Clear).
- When a clock pulse is applied, the bit on the D input is transferred to the Q output.

**2. Serial Input:**

- The Serial Input is where data enters the shift register one bit at a time.
- With each clock pulse, this data bit shifts through the flip-flops.

**3. Clock:**

- The clock signal (Clock) is connected to each flip-flop, ensuring synchronized data transfer with each clock pulse.
- This clock pulse moves data from one flip-flop to the next.



#### **4. Clear:**

- The Clear input resets all flip-flops.
- When activated, it sets the output Q of each flip-flop to 0, effectively clearing the register.

#### **5. Parallel Output:**

- The outputs (Q) of each flip-flop are used as parallel outputs.
- After the data has been shifted through all the flip-flops, it can be read simultaneously from each Q output.

### **3. Shift Registers in Cryptography**

- Importance in Cryptography: Shift registers are key components in digital cryptography, especially for generating pseudorandom sequences in stream ciphers.
- Role in Stream Ciphers: Stream ciphers use shift registers to produce a key stream, which is then XORed with plaintext bits to create cipher-text. This process requires high-quality pseudo-randomness.


### **4. Types of Shift Registers in Stream Ciphers**

Shift registers used in stream ciphers are specifically designed to maximize randomness and security. Here are the two main types:



## 4.1 Linear Feedback Shift Register (LFSR)

- Definition: An LFSR is a type of shift register where the input bit is a linear function (XOR) of its previous states.
- Structure: Contains a sequence of bits that "shift" positions on each clock cycle. Selected bits are XORed to produce the new bit that enters the shift register.
- Feedback Mechanism: Feedback taps are carefully selected to maximize the period (the number of unique states before repeating) and randomness.
- Example in Stream Ciphers:
  - LFSRs are commonly used in stream ciphers due to their simplicity and efficiency in generating pseudorandom sequences.
  - Example: The A5/1 cipher used in GSM mobile communications uses three LFSRs of different lengths.
- Advantages: Simple, fast, and hardware friendly.
- Disadvantages: Linear feedback makes it vulnerable to attacks like the Berlekamp-Massey algorithm, which can determine the structure of an LFSR and break the cipher if enough output bits are known.

 

**Fig.3** Linear Feedback Shift Register (LFSR)

### Basic Concepts

1. **State:** The current configuration of bits in the register.
2. **Feedback Polynomial:** A polynomial that defines which bits are used to calculate the input. For example, for a 4-bit LFSR, a polynomial like  $x^4 + x^3 + 1$  indicates that the 1st and 2nd bits are used for feedback.
3. **Initial State:** The starting state of the LFSR.



## Example Calculation

Let's take a 4-bit LFSR with the feedback polynomial  $x^4 + x^3 + 1$  and an initial state of 1011.

**1.Initial State:** 1011 (This is the binary representation)

**2.Feedback Calculation:**

The bits used for feedback are the 4th and 3rd bits.

Feedback bit = 1 (4th bit) XOR 0 (3rd bit) = 1.

**3.Shift the Register:**

Shift right: The new state becomes 1101.

The new feedback bit is inserted at the leftmost position.

**4.Repeat:**

**Next State Calculation:**

Current state: 1101

Feedback: 1 (4th) XOR 1 (3rd) = 0.

Shift: New state = 0110.






**Next State:** 0110

Feedback:  $0 \text{ (4th)} \text{ XOR } 1 \text{ (3rd)} = 1$ .

Shift: New state = 1011.

## 4.2 Nonlinear Feedback Shift Register (NLFSR)

- Definition: Similar to LFSRs, but the feedback function is nonlinear, making them harder to analyze and predict.
- Structure: Uses non-linear functions (e.g., AND, OR, XOR combinations) in feedback to create complex sequences.
- Usage in Stream Ciphers:
  - NLFSRs are used in some modern stream ciphers to improve security over LFSRs.
  - They can generate more complex and unpredictable key streams, making them resilient to traditional cryptanalysis methods.
- Example in Stream Ciphers: Grain and Trivium are two lightweight stream ciphers that use NLFSRs as part of their key stream generation mechanism.
- Advantages: More secure than LFSRs against linear attacks.
- Disadvantages: More complex and computationally demanding, which can affect performance.

 

**Fig.4** Nonlinear Feedback Shift Register (NLFSR)

### Basic Concept of NLFSR

1. **Registers:** An NLFSR is composed of a series of registers (or bits). Each bit in the register can be either 0 or 1.
2. **Feedback Function:** A non-linear function determines how the feedback bit is calculated. This function often involves operations like XOR, AND, OR, and NOT.
3. **Feedback Process:** In each cycle, the NLFSR shifts the bits to the right, and the feedback bit, calculated using the non-linear function, is placed in the leftmost bit.

### Example NLFSR Calculation

Consider a simple NLFSR with a 4-bit register. Let's define:

- **Initial State:** 1010
- **Non-linear Feedback Function:**  $f(x_1, x_2, x_3, x_4) = x_1 \oplus (x_2 \wedge x_4)$



Here:

- $\oplus$  : *XOR*
- $\wedge$  : *AND*

In each cycle:

1. Calculate the new leftmost bit using the feedback function.
2. Shift all bits to the right.
3. Insert the new bit into the leftmost position.

### Step-by-Step Calculation

#### Cycle 1

- **Current State:** 1010
- **Feedback Bit Calculation:**  $f(x_1, x_2, x_3, x_4) = 1 \oplus (0 \wedge 0) = 1 \oplus 0 = 1$
- **New State:** 1101

#### Cycle 2

- **Current State:** 1101
- **Feedback Bit Calculation:**  $f(x_1, x_2, x_3, x_4) = 1 \oplus (1 \wedge 1) = 1 \oplus 1 = 0$
- **New State:** 0110



### Cycle 3

- **Current State:** 0110
- **Feedback Bit Calculation:**  $f(x_1, x_2, x_3, x_4) = 0 \oplus (1 \wedge 0) = 0 \oplus 0 = 0$
- **New State:** 0011

### Cycle 4

- **Current State:** 0011
- **Feedback Bit Calculation:**  $f(x_1, x_2, x_3, x_4) = 0 \oplus (0 \wedge 1) = 0 \oplus 0 = 0$
- **New State:** 0001

And so on. The NLFSR will continue to generate a sequence based on this feedback function.

## 5. Combining LFSRs and NLFSRs in Stream Ciphers

- **Hybrid Stream Ciphers:** Some stream ciphers use a combination of LFSRs and NLFSRs to balance performance and security. The LFSR provides speed and simplicity, while the NLFSR adds nonlinearity and complexity.



- **Examples:**
  - **Trivium:** A lightweight stream cipher used in IoT devices, combines multiple LFSRs and NLFSRs to create a highly secure but efficient keystream generator.
  - **Grain:** Another lightweight cipher that integrates LFSRs and NLFSRs for secure encryption in resource-constrained environments.

## **6. Applications of Shift Registers in Stream Ciphers**

- **Mobile Communication:** Ciphers like A5/1 and A5/2 for GSM mobile networks use LFSRs to generate keystreams.
- **Wireless Protocols:** Many wireless protocols, including Bluetooth and Wi-Fi, rely on stream ciphers with LFSRs and NLFSRs to secure data transmission.
- **IoT Devices:** Lightweight stream ciphers that use shift registers (like Grain and Trivium) are popular in IoT due to their minimal computational requirements.

## **7. Security Concerns and Attack Techniques**

- **Correlation Attacks:** Attackers exploit statistical weaknesses in LFSRs to correlate the keystream with certain states of the shift register.



- Berlekamp-Massey Algorithm: This algorithm can reconstruct the structure of an LFSR if enough keystream bits are available, making it easy to predict future output.
- Countermeasures:
  - Use NLFSRs to increase complexity.
  - Combine multiple LFSRs and NLFSRs with different feedback mechanisms.
  - Regularly reseed the shift registers to prevent long-term correlations.

## 8. Advantages and Disadvantages of Using Shift Registers in Stream Ciphers

- Advantages:
  - Efficient in hardware, allowing for high-speed cryptographic applications.
  - Simple to implement and analyze, especially in the case of LFSRs.
- Disadvantages:
  - LFSRs are vulnerable to various cryptographic attacks due to their linearity.
  - NLFSRs, though more secure, are complex to design and may consume more power.