



Electric Circuit Analysis
Practical

Assist. Lec
Zahraa Hazim

ASSIST LEACTURE
SALWAN SAUD HATIF

EXP NO. 1

EX NO 1: R L Series Circuit

This experiment is to study the shape of current and voltage and the phase different between them in R L series connection and study this value



2- theory

The ideal coil make delay between current and voltage in phase of $\pi/2$ and the resistance make the current and voltage in the same phase .

In the circuit that connection non ideal coil (i.e have resistance) the delay of current w.r.t voltage will be in phase phase, which value depend on capacitor of xe for the capacitor and its resistance, and with calculated of this shape which is equal to:

$$\tan\phi = \frac{V_L}{V_R}$$

$$\phi = \tan^{-1} \frac{L}{R}$$

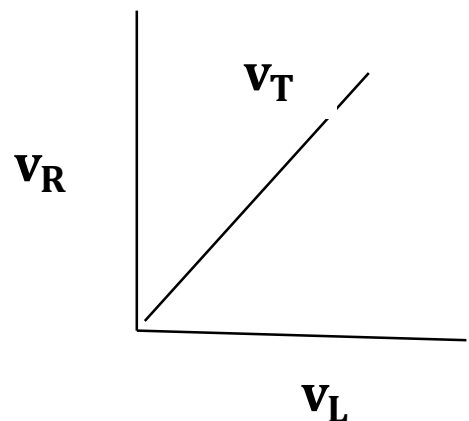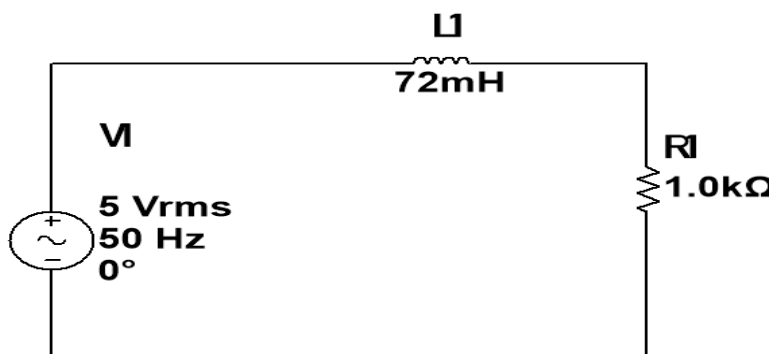

$$X_L = 2 \pi F L$$

Procedure

- 1- Connection the circuit in the figure 2
- 2- Set the value of input voltage as 5 v p.p
- 3- Measure the voltage across resistance and inductor with the varying the frequency as shown in table below
- 4- Find the value X_L

F(HZ)	X_L	V_L	Z	V_R	ϕ

4 – DISCUSSION

- 1- Draw the relation between f and v for the V_R and V_L By using semi-log paper
- 2- Draw the relation between