

Tutorial

Q1: Determine whether each diode in Figure 1 is forward-biased or reverse-biased

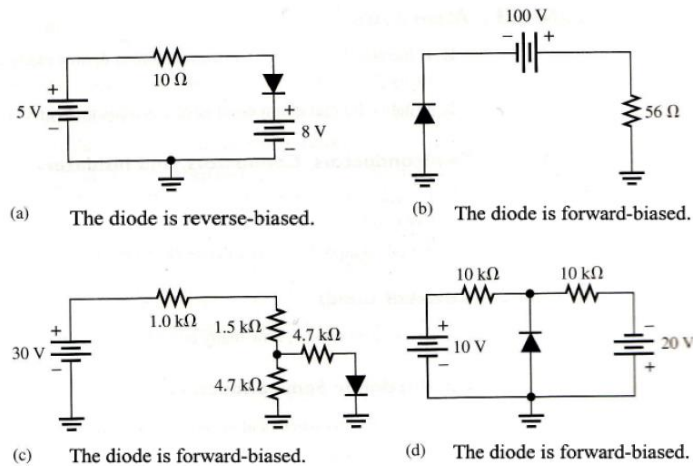


Figure 1

Q2: Draw the output voltage waveform for the circuit in Figure 2 and include the voltage values. Calculate the peak forward current through the diode.

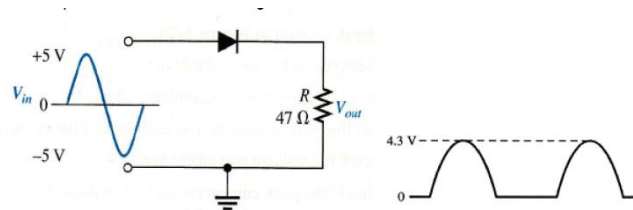


Figure 2

$$I_F = \frac{V_{(p)in} - 0.7 \text{ V}}{R} = \frac{5 \text{ V} - 0.7 \text{ V}}{47 \Omega} = \frac{4.3 \text{ V}}{47 \Omega} = 91.5 \text{ mA}$$

Q3: Determine the peak and average power delivered to R_L in Figure 3.

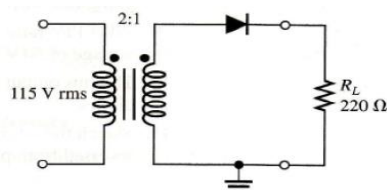


Figure 3

$$\begin{aligned} V_{sec} &= nV_{pri} = (0.5)115 \text{ V} = 57.5 \text{ V rms} \\ V_{p(sec)} &= 1.414(57.5 \text{ V}) = 81.3 \text{ V} \\ V_{avg(sec)} &= \frac{V_{p(sec)}}{\pi} = \frac{81.3 \text{ V}}{\pi} = 25.9 \text{ V} \\ P_{L(p)} &= \frac{(V_{p(sec)} - 0.7 \text{ V})^2}{R_L} = \frac{(80.6 \text{ V})^2}{220 \Omega} = 29.5 \text{ W} \\ P_{L(avg)} &= \frac{(V_{avg(sec)})^2}{R_L} = \frac{(25.9 \text{ V})^2}{220 \Omega} = 3.05 \text{ W} \end{aligned}$$

Q4: Consider the circuit in Figure 4.

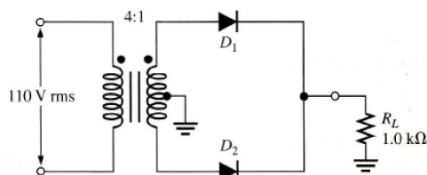


Figure 4

- What type of circuit is this? Center-tapped full-wave rectifier
- What is the total peak secondary voltage? $V_{p(sec)} = (0.25)(1.414)110 \text{ V} = 38.9 \text{ V}$
- Find the peak voltage across each half of the secondary.

$$\frac{V_{p(sec)}}{2} = \frac{38.9 \text{ V}}{2} = 19.4 \text{ V}$$
- Sketch the voltage waveform across R_L .
 $V_{RL} = 19.4 \text{ V} - 0.7 \text{ V} = 18.7 \text{ V}$



Q5: Sketch the output voltage of the bridge rectifier in Figure 5.

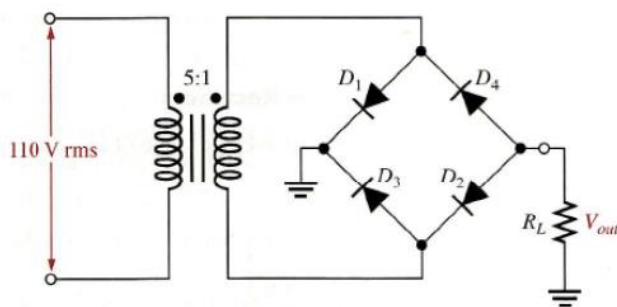


Figure 5



Q6: Determine the output voltage waveform for each circuit in Figure 6.


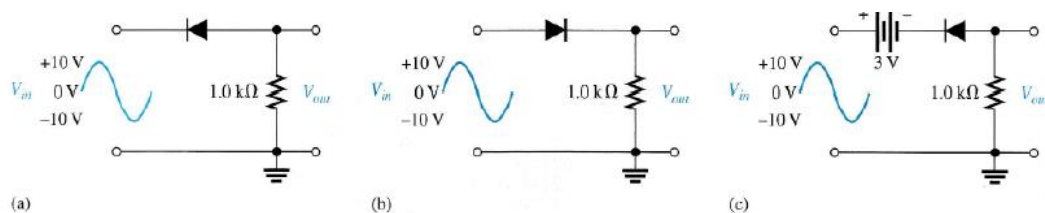


Figure 6

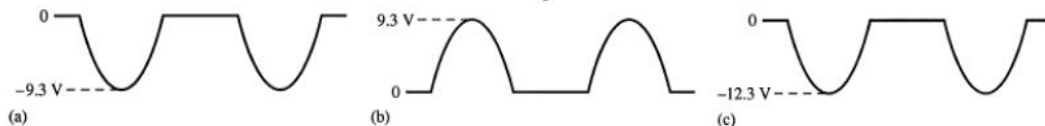


Q7: A full-wave rectifier produces an 80 V peak rectified voltage from a 60 Hz ac source. If a 10 μ F filter capacitor is used, determine the ripple factor for a load resistance of 100 k Ω .

$$V_{r(pp)} = \frac{V_{p(in)}}{fR_L C} = \frac{80 \text{ V}}{(120 \text{ Hz})(100 \text{ k}\Omega)(10 \mu\text{F})} = 0.67 \text{ V}$$


$$V_{DC} = \left(1 - \frac{1}{2fR_L C}\right) V_{p(in)} = \left(1 - \frac{1}{(240 \text{ Hz})(100 \text{ k}\Omega)(10 \mu\text{F})}\right) 80 \text{ V} = 79.67 \text{ V}$$

$$r = \frac{V_{r(pp)}}{V_{DC}} = \frac{0.67 \text{ V}}{79.67 \text{ V}} = 8.41 \times 10^{-3}$$

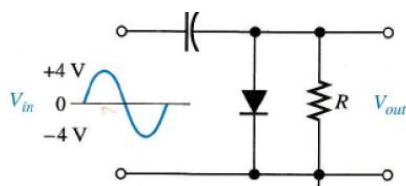Q8: Describe the output waveform of each circuit in Figure 8, Assume the RC time constant is much greater than the period of the input.



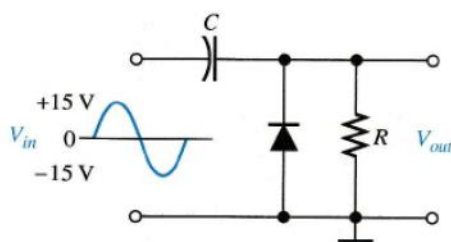A sine wave with a positive peak at 0.7 V, a negative peak at -7.3 V, and a dc value of -3.3 V.



A sine wave with a positive peak at 29.3 V, a negative peak at -0.7 V, and a dc value of +14.3 V.