

## Experiment No.4

### Full-Wave Bridge Rectifier

#### 1. Objectives:

- Construct the full-wave bridge rectifier circuit.
- Measure/plot the input and output waveform.
- Find the peak and average values of the output signal
- Define the turns ratio  $n$  of the transformer.

#### 2. Components and equipment

- A standard transformer
- A two-channel Oscilloscope.
- Multimeter
- Breadboard, four semiconductor Diodes, and a  $1\text{K}\Omega$  Resistor.

#### 3. Theory

The circuit of a full wave bridge rectifier uses four diodes  $D_1$ ,  $D_2$ ,  $D_3$  and  $D_4$  connected as shown in Fig. 1. During the positive half cycle of secondary voltage, the diodes  $D_1$  and  $D_2$  are forward-biased, and  $D_3$  and  $D_4$  are reverse-biased. Therefore, the diodes  $D_1$  and  $D_2$  conduct, and current flow through load resistor  $R_L$ .

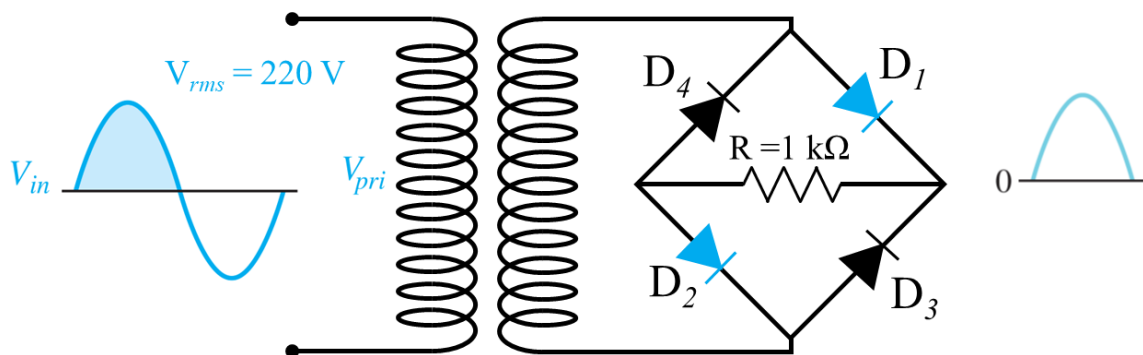


Figure 1: During positive half-cycles,  $D_1$  and  $D_2$  are forward-biased, and  $D_3$  and  $D_4$  are reverse-biased

During the negative half cycle, the diodes  $D_3$  and  $D_4$  are forward-biased, and  $D_1$  and  $D_2$  are reverse-biased. Therefore, the diodes  $D_3$  and  $D_4$  conduct and current flows through the load resistor  $R_L$  in the same direction, as shown in Fig. 2.

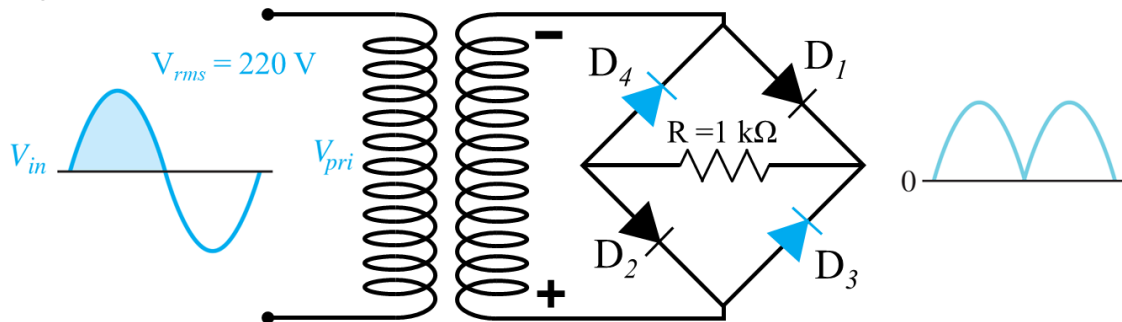


Figure 2: During negative half-cycles,  $D_3$  and  $D_4$  are forward-biased, and  $D_1$  and  $D_2$  are reverse-biased.

During both half cycles, there is a continuous current flow through the load resistor  $R_L$ , which will get a unidirectional current, as shown in Fig. 3.

The difference between center-tapped full-wave and bridge rectifiers is that a center-tapped full-wave rectifier requires two diodes only to rectify the full wave allowing unidirectional current to pass the load during the entire  $2\pi$  of the input signal, as shown in Fig. 3.

However, it requires a center-tapped transformer. In contrast, a full-wave bridge rectifier requires four diodes and a standard (two terminal) transformer, allowing unidirectional current to pass the load as well.

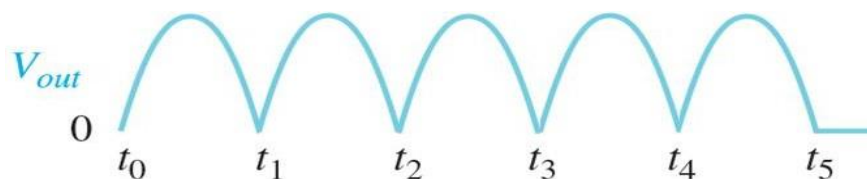


Figure 3: Fig. Output of a full-wave bridge rectifier

### Average Value of the Output Voltage

The average value of a full wave rectified output voltage is the value you would measure on a DC voltmeter. It can be calculated with the following equation, where  $V_{p(out)}$  is the peak value of the full wave rectified output voltage:



$$V_{AVG} = \frac{2V_{p(out)}}{\pi}$$

#### 4. Experiment procedure

1. Connect the circuit as shown in Fig. 1 using a standard transformer, four diodes, a  $1k\Omega$  resistor ( $R_L$ )
2. Connect the primary winding to the 220 V and a frequency of 50 Hz.
3. Display the input and output signal on the oscilloscope.
4. Measure the  $V_{p,p}$ ,  $V_{max}$ ,  $V_{rms}$ ,  $V_{AVG}$ , and input signal frequency.
5. Measure the  $V_{p,p}$ ,  $V_{max}$ ,  $V_{rms}$ ,  $V_{AVG}$ , and output signal frequency.
6. Draw the input and output signal
7. Find the turns ratio ( $n$ ) of the transformer
8. Tabulate your measurement results in a table as shown.

Input Signal (FWR) across sec. winding	Output Signal ( $R_L$ )
$V_{rms} =$	$V_{rms} =$
$V_{p(out)} =$	$V_p =$
$V_{p(sec)} =$	$V_{p,p} =$
$V_{AVG} =$ (Exp.)	$V_{AVG} =$ (Exp.)
$V_{AVG} =$ (Theo.)	$V_{AVG} =$ (Theo.)
$f =$	$f =$
Draw the input signal	Draw the output signal
Find the turns ratio ( $n$ ) of the transformer.	

#### 5. Discussion

1. What would be the PIV of each diode in the above circuit?
2. On a graphic paper, draw the input and output signals on one chart (on top of each other), indicating the voltages ( $V_p$ ,  $V_{rms}$ , and  $V_{AVG}$ ).



3. Calculate the period of the input and output signals.