

## Bias Stabilization

### Basic Definitions:

The stability of system is a measure of sensitivity of a circuit to variations in its parameters. In any amplifier employing a transistor the **collector current**  $I_C$  is sensitive to each of the following parameters:

- ◀  $I_{CO}$  (reverse saturation current): doubles in value for every  $10^\circ\text{C}$  increase in temperature.
- ◀  $|V_{BE}|$  (base-to-emitter voltage): decrease about 7.5 mV per  $1^\circ\text{C}$  increase in temperature.
- ◀  $\beta$  (forward current gain): increase with increase in temperature.

Any or all of these factors can cause the bias point to drift from the design point of operation.

### Stability Factors, $S(I_{CO})$ , $S(V_{BE})$ , and $S(\beta)$ :

A stability factor,  $S$ , is defined for each of the parameters affecting bias stability as listed below:

$$S(I_{CO}) = \frac{\Delta I_C}{\Delta I_{CO}} = \frac{\partial I_C}{\partial I_{CO}} \bigg|_{V_{BE}, \beta = \text{const.}} \quad [10.1a]$$

$$S(V_{BE}) = \frac{\Delta I_C}{\Delta V_{BE}} = \frac{\partial I_C}{\partial V_{BE}} \bigg|_{I_{CO}, \beta = \text{const.}} \quad [10.1b]$$

$$S(\beta) = \frac{\Delta I_C}{\Delta \beta} = \frac{\partial I_C}{\partial \beta} \bigg|_{I_{CO}, V_{BE} = \text{const.}} \quad [10.1c]$$

Generally, networks that are quite stable and relatively insensitive to temperature variations have low stability factors. In some ways it would seem more appropriate to consider the quantities defined by Eqs. [10.1a - 10.1c] to be sensitivity factors because: the higher the stability factor, the more sensitive the network to variations in that parameter.

The total effect on the collector current can be determined using the following equation:

$$\Delta I_C = S(I_{CO})\Delta I_{CO} + S(V_{BE})\Delta V_{BE} + S(\beta)\Delta \beta \quad [10.2]$$

## Derivation of Stability Factors for Standard Bias Circuits:

For the **voltage-divider bias circuit**, the exact analysis (using Thevenin theorem) for the input (base-emitter) loop will result in:

$$\begin{aligned}
 & E_{Th} - I_B R_{Th} - V_{BE} - I_E R_E = 0, \\
 \text{and } & I_E = I_C + I_B \Rightarrow \\
 & I_C R_E + I_B (R_E + R_{Th}) + V_{BE} = E_{Th}, \\
 \text{and } & I_C = \beta I_B + (\beta + 1) I_{CO}, \\
 \text{or } & I_B = \frac{I_C}{\beta} - \frac{\beta + 1}{\beta} I_{CO} \Rightarrow
 \end{aligned}$$

$$\boxed{I_C \left[ \frac{(\beta + 1) R_E + R_{Th}}{\beta} \right] - I_{CO} \left[ \frac{(\beta + 1)(R_E + R_{Th})}{\beta} \right] + V_{BE} = E_{Th}} \quad [10.3]$$

The partial derivation of the Eq. [10.3] with respect to  $I_{CO}$  will result:

$$\begin{aligned}
 & \frac{\partial I_C}{\partial I_{CO}} \cdot \frac{(\beta + 1) R_E + R_{Th}}{\beta} - \frac{(\beta + 1)(R_E + R_{Th})}{\beta} = 0 \\
 & \boxed{S(I_{CO}) = \frac{(\beta + 1)(R_E + R_{Th})}{(\beta + 1) R_E + R_{Th}}} \quad [10.4a]
 \end{aligned}$$

Also, the partial derivation of the Eq. [10.3] with respect to  $V_{BE}$  will result:

$$\begin{aligned}
 & \frac{\partial I_C}{\partial V_{BE}} \cdot \frac{(\beta + 1) R_E + R_{Th}}{\beta} + 1 = 0 \\
 & \boxed{S(V_{BE}) = \frac{-\beta}{(\beta + 1) R_E + R_{Th}}} \quad [10.4b]
 \end{aligned}$$

The mathematical development of the last stability factor  $S(\beta)$  is more complex than encountered for  $S(I_{CO})$  and  $S(V_{BE})$ . Thus,  $S(\beta)$  is suggested by the following equation:

$$\boxed{S(\beta) = \frac{(I_{C_1} / \beta_1)(R_E + R_{Th})}{(\beta_2 + 1) R_E + R_{Th}}} \quad [10.4c]$$

For the **emitter-stabilized bias circuit**, the stability factors are the same as these obtained above for the voltage-divider bias circuit except that  $R_{Th}$  will be replaced by  $R_B$ . These are:

$$S(I_{CO}) = \frac{(\beta + 1)(R_E + R_B)}{(\beta + 1)R_E + R_B} \quad [10.5a]$$

$$S(V_{BE}) = \frac{-\beta}{(\beta + 1)R_E + R_B} \quad [10.5b]$$

$$S(\beta) = \frac{(I_{C_1} / \beta_1)(R_E + R_B)}{(\beta_2 + 1)R_E + R_B} \quad [10.5c]$$

For the **fixed-bias circuit**, if we plug in  $R_E = 0$  the following equation will result:

$$S(I_{CO}) = \beta + 1 \quad [10.6a]$$

$$S(V_{BE}) = -\frac{\beta}{R_B} \quad [10.6b]$$

$$S(\beta) = \frac{I_{C_1}}{\beta_1} \quad [10.6c]$$

Finally, for the case of the **voltage-feedback bias circuit**, the following equation will result:

$$S(I_{CO}) = \frac{(\beta + 1)(R_C + R_E + R_B)}{(\beta + 1)(R_C + R_E) + R_B} \quad [10.7a]$$

$$S(V_{BE}) = \frac{-\beta}{(\beta + 1)(R_C + R_E) + R_B} \quad [10.7b]$$

$$S(\beta) = \frac{(I_{C_1} / \beta_1)(R_C + R_E + R_B)}{(\beta_2 + 1)(R_C + R_E) + R_B} \quad [10.7c]$$

### Example 10-1:

1. Design a voltage-divider bias circuit using a  $V_{CC}$  supply of +18 V, and an npn silicon transistor with  $\beta$  of 80. Choose  $R_C = 5R_E$ , and set  $I_C$  at 1 mA and the stability factor  $S(I_{CO})$  at 3.8.
2. For the circuit designed in part (1), determine the change in  $I_C$  if a change in operating conditions results in  $I_{CO}$  increasing from 0.2 to 10  $\mu\text{A}$ ,  $V_{BE}$  drops from 0.7 to 0.5 V, and  $\beta$  increases 25%.
3. Calculate the change in  $I_C$  from 25° to 75°C for the same circuit designed in part (1), if  $I_{CO} = 0.2 \mu\text{A}$  and  $V_{BE} = 0.7 \text{ V}$ .

### Solution:

Part 1:

$$V_{CE} = V_{CC} / 2 = 18 / 2 = 9 \text{ V}.$$

$$V_{CE} = V_{CC} - I_C (R_C + R_E), \quad R_C = 5R_E \Rightarrow$$

$$9 = 18 - (1\text{m})(5R_E + R_E) \Rightarrow R_E = 1.5\text{k}\Omega.$$

$$R_C = 5(1.5\text{k}) = 7.5\text{k}\Omega.$$

$$I_E \cong I_C = 1\text{mA}, \quad V_E = I_E R_E = (1\text{m})(1.5\text{k}) = 1.5\text{V}.$$

$$V_B = V_E + V_{BE} = 1.5 + 0.7 = 2.2\text{V}.$$

$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2} \Rightarrow \boxed{\frac{R_2}{R_1 + R_2} = \frac{V_B}{V_{CC}} = \frac{2.2}{18}}$$

$$S(I_{CO}) = \frac{(\beta + 1)(R_E + R_{Th})}{(\beta + 1)R_E + R_{Th}} \Rightarrow$$

$$3.8 = \frac{(81)(1.5\text{k} + R_{Th})}{(81)(1.5\text{k}) + R_{Th}} \Rightarrow R_{Th} = 4.4\text{k}\Omega.$$

$$R_{Th} = \frac{R_1 R_2}{R_1 + R_2} \Rightarrow \boxed{\frac{R_2}{R_1 + R_2} = \frac{R_{Th}}{R_1} = \frac{4.4\text{k}}{R_1}}$$

From Eqs. [10.8a] and [10.8b]:

$$\frac{4.4\text{k}}{R_1} = \frac{2.2}{18} \Rightarrow R_1 = 36\text{k}\Omega.$$

From Eq. [10.8a]:

$$\frac{R_2}{36\text{k} + R_2} = \frac{2.2}{18} \Rightarrow R_2 = 5\text{k}\Omega.$$

Fig. 10-1 shows the final circuit.

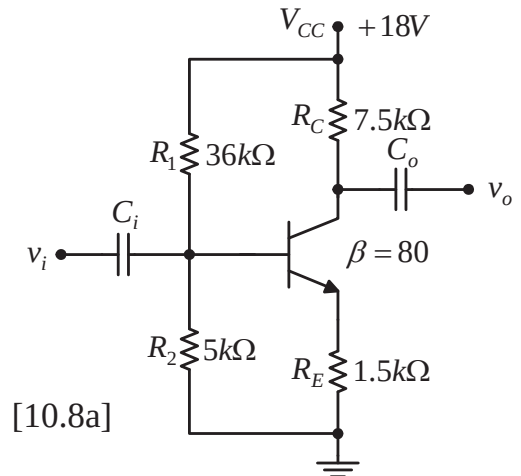


Fig. 10-1

[10.8a]

[10.8b]

Part 2:

$$S(I_{CO}) = 3.8,$$

$$\Delta I_{CO} = 10\mu - 0.2\mu = 9.8\mu A.$$

$$S(V_{BE}) = \frac{-\beta}{(\beta + 1)R_E + R_{Th}} = \frac{-80}{(81)(1.5k) + 4.4k} = -0.635mS,$$

$$\Delta V_{BE} = 0.5 - 0.7 = -0.2V.$$

$$\beta_2 = \beta_1(1 + 25/100) = 1.25\beta_1 = 1.25(80) = 100,$$

$$S(\beta) = \frac{(I_{C_1} / \beta_1)(R_E + R_{Th})}{(\beta_2 + 1)R_E + R_{Th}} = \frac{(1m/80)(1.5k + 4.4k)}{(101)(1.5k) + 4.4k} = 0.473\mu A,$$

$$\Delta\beta = 100 - 80 = 20.$$

$$\begin{aligned}\Delta I_C &= S(I_{CO})\Delta I_{CO} + S(V_{BE})\Delta V_{BE} + S(\beta)\Delta\beta \\ &= (3.8)(9.8\mu) + (-0.635m)(-0.2) + (0.473\mu)(20) = 0.174mA.\end{aligned}$$

Part 3:

Since  $I_{CO}$ , doubles in value for every  $10^\circ C$  increase in temperature.

$$\text{Thus } N = \frac{\Delta T}{10} = \frac{75 - 25}{10} = 5, \quad I_{CO}(75^\circ C) = 2^N \cdot I_{CO}(25^\circ C) = (2^5)(0.2\mu) = 6.4\mu A.$$

$$\Delta I_{CO} = 6.4\mu - 0.2\mu = 6.2\mu A.$$

Since  $V_{BE}$ , decreases about 7.5 mV per  $1^\circ C$  increase in temperature.

$$\text{Thus } \Delta T = 75 - 25 = 50^\circ C, \quad V_{BE}(25^\circ C) = 0.7V \Rightarrow$$

$$V_{BE}(75^\circ C) = 0.7 - 50(7.5m) = 0.325V.$$

$$\begin{aligned}\Delta I_C &= S(I_{CO})\Delta I_{CO} + S(V_{BE})\Delta V_{BE} \\ &= (3.8)(6.2\mu) + (-0.635m)(-0.375) = 0.262mA.\end{aligned}$$

## Exercises:

1. Derive a mathematical expression to determine the stability factor  $S(V_{CC}) = \Delta I_C / \Delta V_{CC}$  for the emitter-stabilized bias circuit.
2. Discuss and compare (by equations) between the relative levels of stability for the following biasing circuits:
  - i. the fixed-bias circuit,
  - ii. the emitter-stabilized bias circuit,
  - iii. the voltage-divider bias circuit, and
  - iv. the voltage-feedback circuit.