



Lecture 4:

Nodal Analysis

The nodal analysis is a general procedure for analyzing circuits using node voltages as the circuit variables. This methodology reduces the number of equations that must solve it together.

Steps to Determine Node Voltages :

1. Select a node as the reference node (it's voltage equal zero). Assign voltages V_1, V_2, \dots, V_{n-1} to the remaining $n-1$ nodes. The voltages are referenced with respect to the reference node.
2. Apply KCL to each of the $n-1$ non reference nodes. Use Ohm's law to express the branch currents in terms of node voltages.
3. Solve the resulting equations together to obtain the unknown node voltages.

Example 1: Using nodal analysis, determine the current in (3Ω) of the circuit shown in **Figure (1)**.

Solution:

At node (1) :

$$\frac{V_1 - (2 + 4)}{3 + 2} + \frac{V_1}{2} + \frac{V_1 - 4}{2} = 0$$

$$\frac{V_1}{5} - \frac{6}{5} + \frac{V_1}{2} + \frac{V_1}{2} - \frac{4}{2} = 0$$

$$\left\{ \frac{V_1}{5} - \frac{6}{5} + 2\left(\frac{V_1}{2}\right) - 2 = 0 \right\} \times 5$$

$$V_1 - 6 + 5V_1 - 10 = 0$$

$$6V_1 - 16 = 0 \rightarrow V_1 = \frac{16}{6}$$

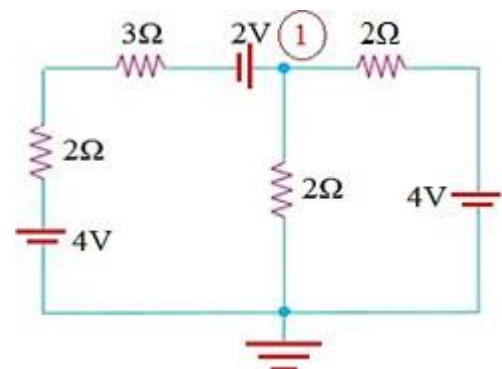


Fig.(1)



$$\therefore V_1 = 2.667 \text{ V}$$

So the current through (3Ω)

$$I_{3\Omega} = \frac{V_1 - 2 - 4}{3 + 2} = \frac{2.67 - 2 - 4}{5}$$

$$I_{3\Omega} = -0.666 \text{ A}$$

Example 2: Determine the current in (7Ω) & (1Ω) resistors using nodal analysis of the circuit shown in **Figure (2)**.

Solution:

Redraw the circuit and indicate the nodes and reference node as shown in **Figure (3)**.

At node (1) :

$$\left(\frac{V_1 - V_2}{3}\right) + \left(\frac{V_1 - V_3}{4}\right) = -8 - 3$$

$$\left(\frac{V_1 - V_2}{3}\right) + \left(\frac{V_1 - V_3}{4}\right) + 8 + 3 = 0$$

$$0.583V_1 - 0.333V_2 - 0.25V_3 = -11 \dots(1)$$

At node (2) :

$$\frac{V_2 - V_1}{3} + \frac{V_2}{1} + \frac{V_2 - V_3}{7} - 3 = 0$$

$$-0.333V_1 + 1.4762V_2 - 0.1429V_3 = 3 \dots(2)$$

At node (3) :

$$\frac{V_3}{5} + \frac{V_3 - V_2}{7} + \frac{V_3 - V_1}{4} - 25 = 0$$


$$-0.25V_1 - 0.1429V_2 + 0.5929V_3 = 25 \dots(3)$$

Solving Equ (1), (2) & (3) we get,

$$V_1 = 5.41 \text{ V},$$

$$V_2 = 7.736 \text{ V},$$

$$V_3 = 46.3109 \text{ V}$$

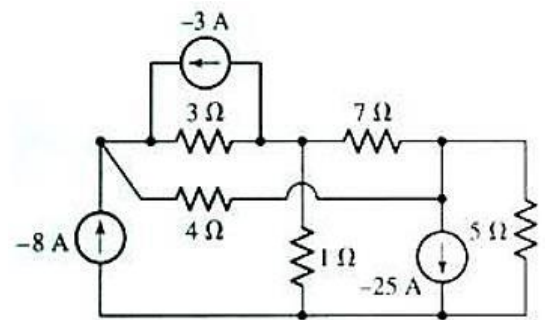

Fig(2)

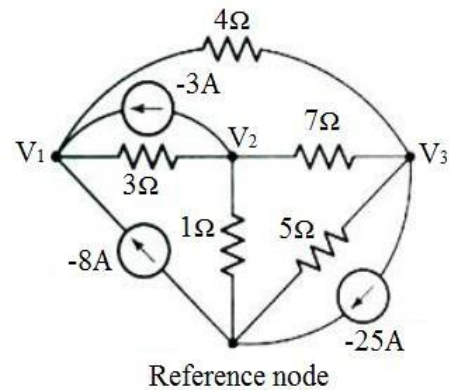


Fig.(3)



Now, Current in (7Ω) is,

$$I_{7\Omega} = \frac{V_3 - V_2}{7} = \frac{46.32 - 7.736}{7} = 5.512A$$

Current in (1Ω) is,

$$I_{1\Omega} = \frac{V_2 - V_0}{1} = \frac{V_2 - 0}{1}$$

$$I_{1\Omega} = \frac{7.736}{1} = 7.736A$$

Example 3: Determine the power supplied by the dependent source of the **Figure (3)** using nodal analysis.

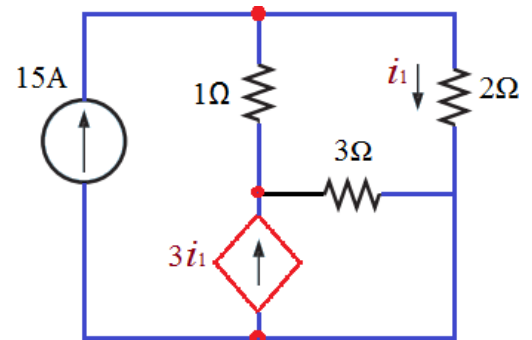


Fig.(3)

Solution:

Redraw the circuit and indicate the nodes and reference node as shown in **Figure (4)**.

At node (1) :

$$\frac{V_1 - V_2}{1} + \frac{V_1}{2} = 15$$

$$\frac{V_1 - V_2}{1} + \frac{V_1}{2} - 15 = 0$$

$$\therefore 1.5 V_1 - V_2 = 15 \quad \dots(1)$$

At node (2) :

$$\left\{ \frac{V_2 - V_1}{1} + \frac{V_2}{3} = 3i_1 \right\} \times 3$$

$$3V_2 - 3V_1 + V_2 - 9i_1 = 0$$

$$-3V_1 + 4V_2 - 9i_1 = 0$$

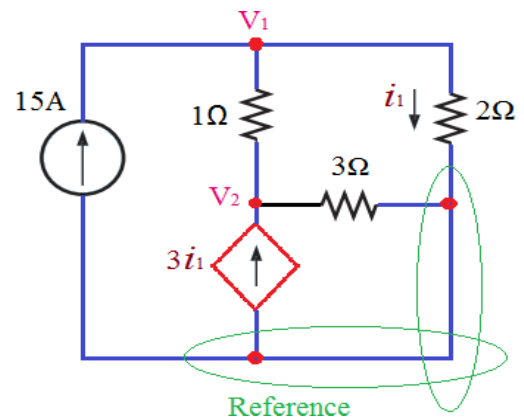


Fig.(4)



Since, $i_1 = \frac{V_1}{2}$

$$-3V_1 + 4V_2 - 9\left(\frac{V_1}{2}\right) = 0$$

$$\therefore -7.5V_1 + 4V_2 = 0 \quad \dots(2)$$

Solve Equ.s (1) & (2) we get,

$$V_1 = -40 \text{ V} \text{ \& } V_2 = -75 \text{ V}$$

$$i_1 = \frac{V_1}{2} = \frac{-40}{2} = -20 \text{ A}$$

Now the power supplied by the dependent source is,

$$P = I \times V$$

$$\rightarrow P = (3i_1) v_2 = (3 \times (-20)) \times (-75)$$

$$P = 4500 \text{ W} = 4.5 \text{ kW}$$

H.W.:- Find V_1 , V_2 and V_3 in the circuit of **Figure (5)** using nodal analysis.

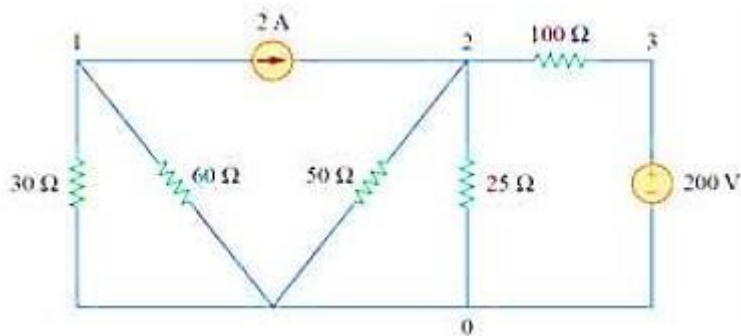


Fig.(5)