

# THREE PHASE SYSTEM

Lec . Zahraa Hazim

Balanced three-phase circuits

## Part I/ Three-Phase Circuits (polyphase)



Figure 1. Single-phase system with two-wire type

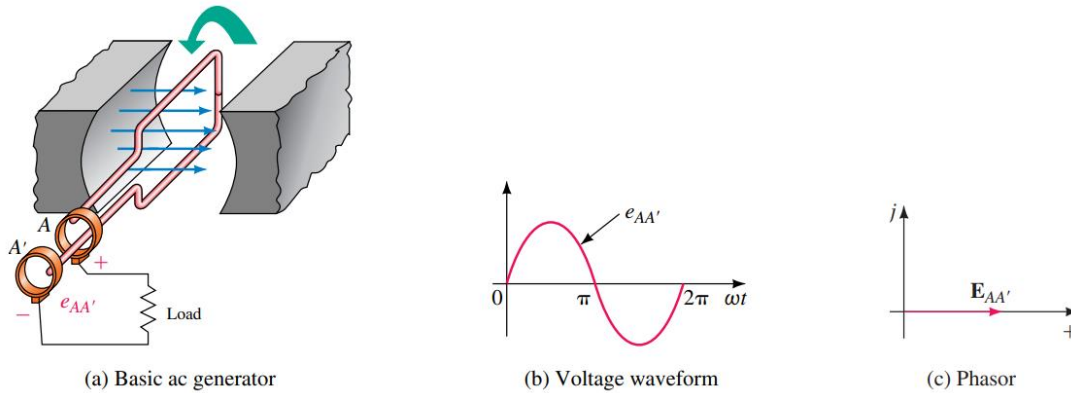


Figure 2. A basic single-phase generator

A Polyphase system is a system in which the AC sources operate at the same frequency but different phases.

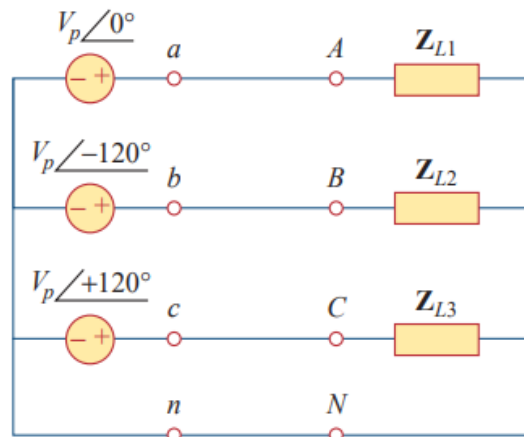


Figure 3. Three-phase four-wire system

### Balanced Three-Phase Voltages

Balanced phase voltages are equal in magnitude and are out of phase with each other by  $120^\circ$ .

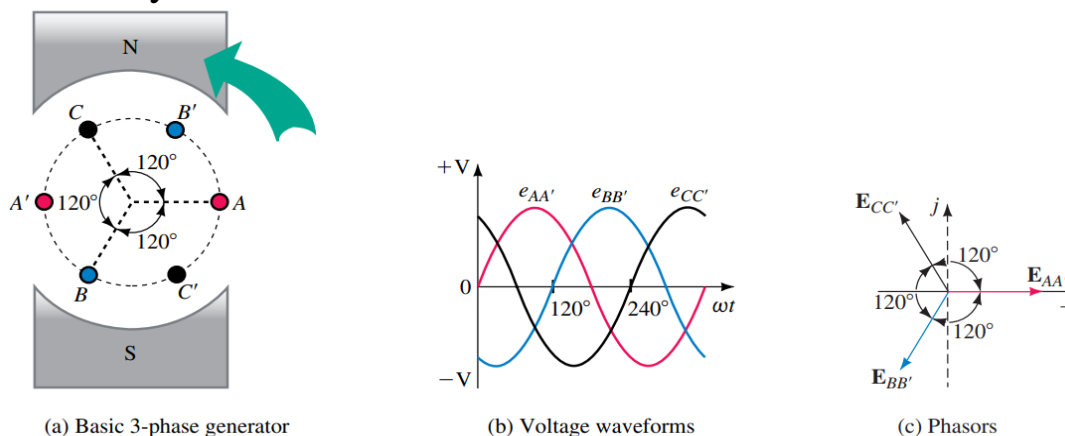


Figure 4. Three sets of coils are used to produce three balanced voltages.

- There are two phase sequences, abc and acb
- abc is similar to bca and to cab.
- The phase sequence is the time order in which the voltages pass through their respective maximum values.
- The default sequence is the abc unless otherwise stated.

### Three-phase voltage sources connections

The connection could be a star (Y) or delta( $\Delta$ ), but the star is more relevant one

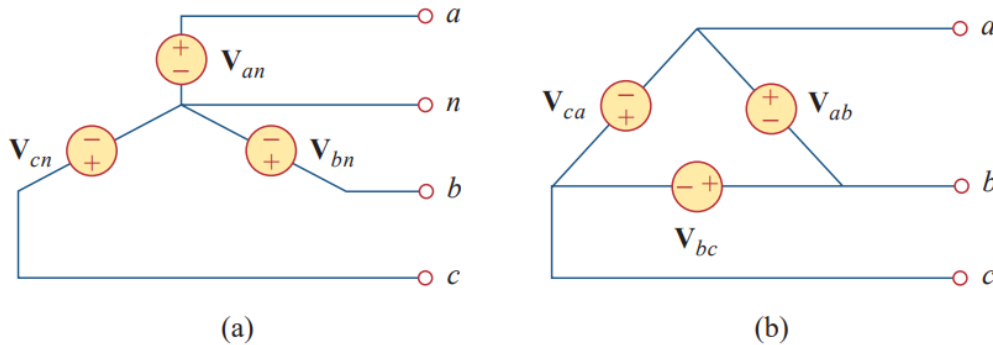


Figure 5 Three-phase voltage sources: (a) Y-connected source, (b)  $\Delta$ -connected source

### The phasor diagram and phase sequences

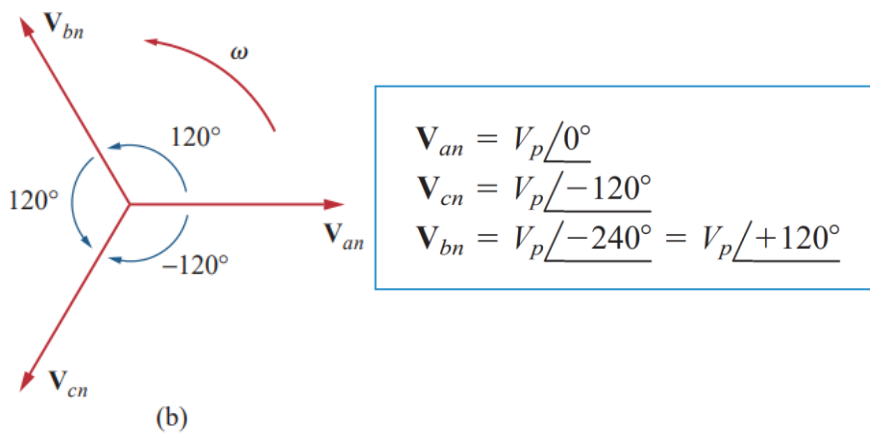
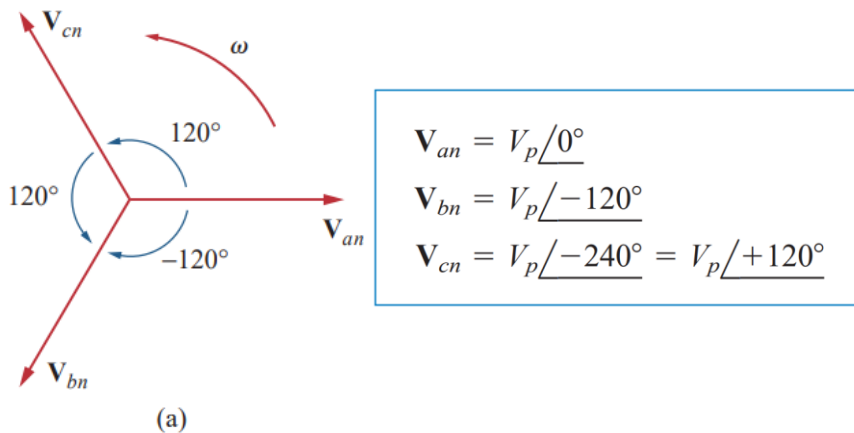


Figure 6. Phase sequences for Y-connected source  
(a) abc or positive sequence,  
(b) acb or negative sequence

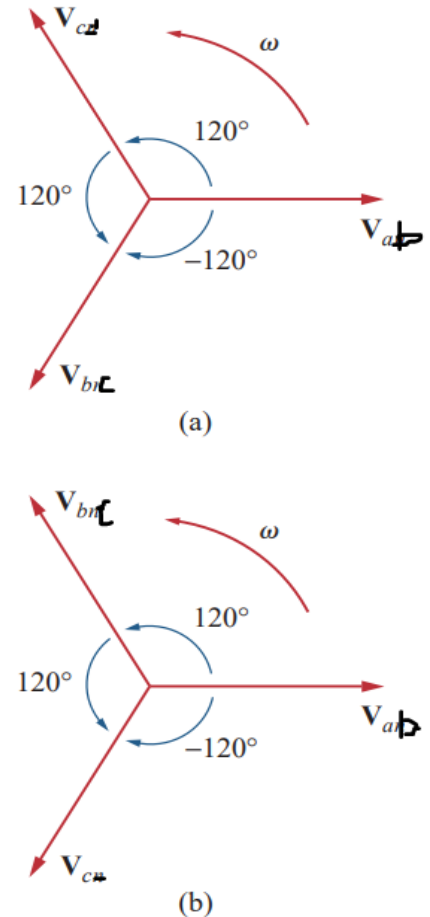


Figure 7. Phase sequences for  $\Delta$ -connected source  
(a) abc or positive sequence,  
(b) acb or negative sequence

For only balanced three phase systems

$$\mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} = 0$$

$$|\mathbf{V}_{an}| = |\mathbf{V}_{bn}| = |\mathbf{V}_{cn}|$$

$$\begin{aligned}\mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} &= V_p \angle 0^\circ + V_p \angle -120^\circ + V_p \angle +120^\circ \\ &= V_p(1.0 - 0.5 - j0.866 - 0.5 + j0.866) \\ &= 0\end{aligned}$$

### Example 1

- If  $\mathbf{E}_{AA'} = 277 \text{ V} \angle 0^\circ$ , what are  $\mathbf{E}_{BB'}$  and  $\mathbf{E}_{CC'}$ ?
- If  $\mathbf{E}_{BB'} = 347 \text{ V} \angle -120^\circ$ , what are  $\mathbf{E}_{AA'}$  and  $\mathbf{E}_{CC'}$ ?
- If  $\mathbf{E}_{CC'} = 120 \text{ V} \angle 150^\circ$ , what are  $\mathbf{E}_{AA'}$  and  $\mathbf{E}_{BB'}$ ?

Sketch the phasors for each set.

Answers

- $\mathbf{E}_{BB'} = 277 \text{ V} \angle -120^\circ$ ;  $\mathbf{E}_{CC'} = 277 \text{ V} \angle 120^\circ$
- $\mathbf{E}_{AA'} = 347 \text{ V} \angle 0^\circ$ ;  $\mathbf{E}_{CC'} = 347 \text{ V} \angle 120^\circ$
- $\mathbf{E}_{AA'} = 120 \text{ V} \angle 30^\circ$ ;  $\mathbf{E}_{BB'} = 120 \text{ V} \angle -90^\circ$

### Three-phase load

Three-phase load can be either wye-connected or delta-connected

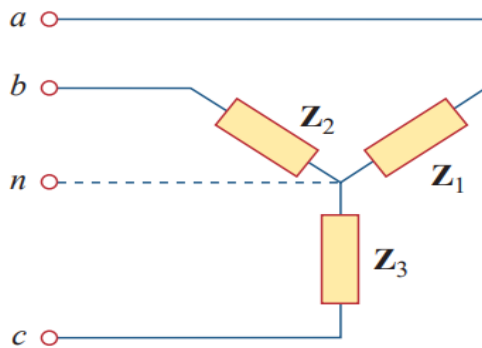


Figure 8. a Y-connected load.

For a balanced wye-connected load,

$$\mathbf{Z}_1 = \mathbf{Z}_2 = \mathbf{Z}_3 = \mathbf{Z}_Y$$

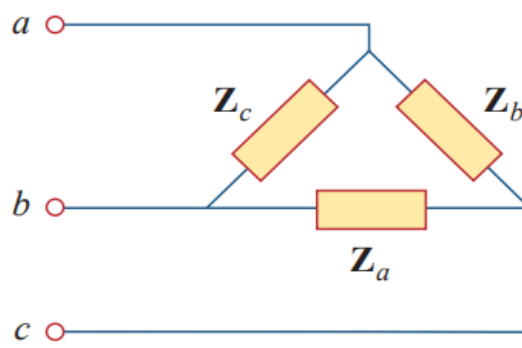


Figure 9 a  $\Delta$ -connected load.

For a balanced delta-connected load,

$$\mathbf{Z}_a = \mathbf{Z}_b = \mathbf{Z}_c = \mathbf{Z}_\Delta$$

#### Y-to- $\Delta$ Transformation

$$\mathbf{Z}_A = \frac{\mathbf{Z}_1 \mathbf{Z}_2 + \mathbf{Z}_1 \mathbf{Z}_3 + \mathbf{Z}_2 \mathbf{Z}_3}{\mathbf{Z}_3}$$

$$\mathbf{Z}_B = \frac{\mathbf{Z}_1 \mathbf{Z}_2 + \mathbf{Z}_1 \mathbf{Z}_3 + \mathbf{Z}_2 \mathbf{Z}_3}{\mathbf{Z}_2}$$

$$\mathbf{Z}_C = \frac{\mathbf{Z}_1 \mathbf{Z}_2 + \mathbf{Z}_1 \mathbf{Z}_3 + \mathbf{Z}_2 \mathbf{Z}_3}{\mathbf{Z}_1}$$

#### $\Delta$ -to-Y Transformation

$$\mathbf{Z}_1 = \frac{\mathbf{Z}_A \mathbf{Z}_B}{\mathbf{Z}_A + \mathbf{Z}_B + \mathbf{Z}_C}$$

$$\mathbf{Z}_2 = \frac{\mathbf{Z}_A \mathbf{Z}_C}{\mathbf{Z}_A + \mathbf{Z}_B + \mathbf{Z}_C}$$

$$\mathbf{Z}_3 = \frac{\mathbf{Z}_B \mathbf{Z}_C}{\mathbf{Z}_A + \mathbf{Z}_B + \mathbf{Z}_C}$$

For a balanced load only  $\mathbf{Z}_\Delta = 3\mathbf{Z}_Y$

### Example 2

Determine the phase sequence of the set of voltages

$$v_{an} = 200 \cos(\omega t + 10^\circ)$$

$$v_{bn} = 200 \cos(\omega t - 230^\circ), \quad v_{cn} = 200 \cos(\omega t - 110^\circ)$$

#### Solution:

The voltages can be expressed in phasor form as

$$\mathbf{V}_{an} = 200 \angle 10^\circ \text{ V}, \quad \mathbf{V}_{bn} = 200 \angle -230^\circ \text{ V}, \quad \mathbf{V}_{cn} = 200 \angle -110^\circ \text{ V}$$

We notice that  $\mathbf{V}_{an}$  leads  $\mathbf{V}_{cn}$  by  $120^\circ$  and  $\mathbf{V}_{cn}$  in turn leads  $\mathbf{V}_{bn}$  by  $120^\circ$ . Hence, we have an *acb* sequence.

---

There are four possible of connections:

Source	Load
Y	Y
Y	$\Delta$
$\Delta$	Y
$\Delta$	$\Delta$

### Balanced Y-Y Connection

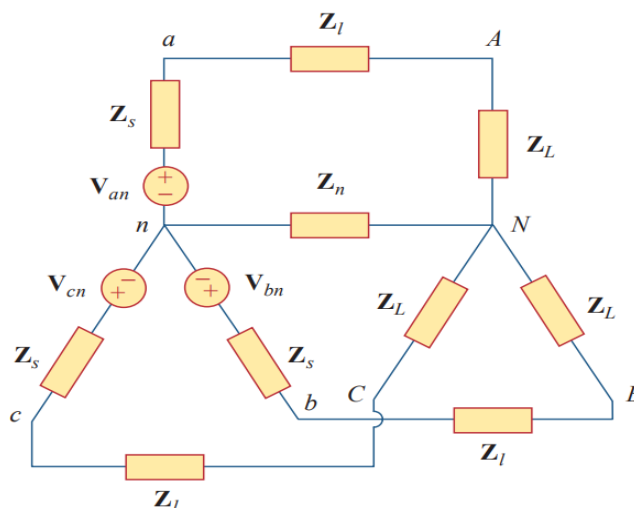


Figure 10. A balanced Y-Y system, showing the source, line, and load impedances

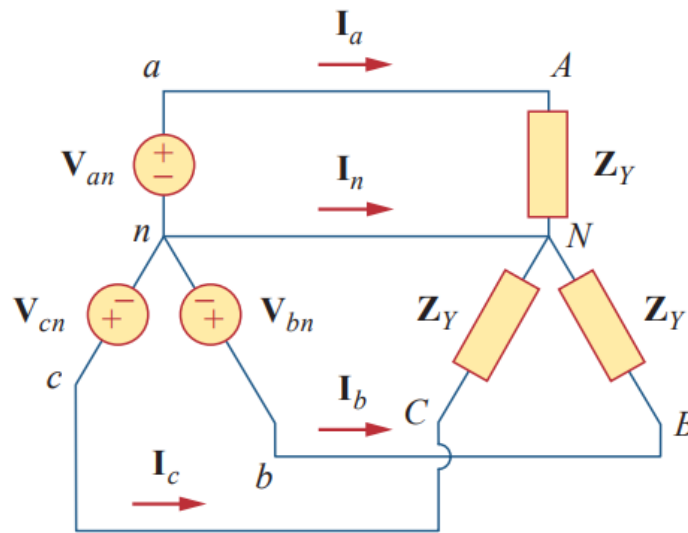


Figure 13. Balanced Y-Y connection.

$$\mathbf{Z}_Y = \mathbf{Z}_s + \mathbf{Z}_\ell + \mathbf{Z}_L$$

For abc (positive sequence)

$$\begin{aligned}\mathbf{V}_{an} &= V_p \angle 0^\circ \\ \mathbf{V}_{bn} &= V_p \angle -120^\circ, \quad \mathbf{V}_{cn} = V_p \angle +120^\circ\end{aligned}$$

The line-to-line voltages or simply line voltages are related to the phase voltages. For example,

$$\begin{aligned}\mathbf{V}_{ab} &= \mathbf{V}_{an} - \mathbf{V}_{bn} = V_p \angle 0^\circ - V_p \angle -120^\circ \\ &= V_p \left( 1 + \frac{1}{2} + j\frac{\sqrt{3}}{2} \right) = \sqrt{3}V_p \angle 30^\circ\end{aligned}$$

$$\mathbf{V}_{bc} = \mathbf{V}_{bn} - \mathbf{V}_{cn} = \sqrt{3}V_p \angle -90^\circ$$

$$\mathbf{V}_{ca} = \mathbf{V}_{cn} - \mathbf{V}_{an} = \sqrt{3}V_p \angle -210^\circ$$

$$V_L = \sqrt{3}V_p$$

$$V_p = |\mathbf{V}_{an}| = |\mathbf{V}_{bn}| = |\mathbf{V}_{cn}|$$

$$V_L = |\mathbf{V}_{ab}| = |\mathbf{V}_{bc}| = |\mathbf{V}_{ca}|$$

$$Z_A = Z_B = Z_C = Z_Y$$

$$I_N = I_A + I_B + I_C = 0$$

$$V_{AN} = |V| \angle \phi_{AN}$$

$$V_{BN} = |V| \angle (\phi_{AN} - 120^\circ)$$

$$V_{CN} = |V| \angle (\phi_{AN} - 240^\circ)$$

$$V_{AB} = V_{AN} - V_{BN} = |V_{AN}| \sqrt{3} \angle (\phi_{AN} + 30^\circ)$$

$$V_{BC} = V_{BN} - V_{CN} = |V_{AN}| \sqrt{3} \angle (\phi_{AN} - 120^\circ + 30^\circ)$$

$$V_{CA} = V_{CN} - V_{AN} = |V_{AN}| \sqrt{3} \angle (\phi_{AN} - 240^\circ + 30^\circ)$$

The line voltages sum up to zero as do the phase voltages.

$\mathbf{V}_{an} + \mathbf{V}_{bn} + \mathbf{V}_{cn} = 0$  (for balanced load only)

and

$\mathbf{V}_{ab} + \mathbf{V}_{bc} + \mathbf{V}_{ca} = 0$  (for balanced load only)

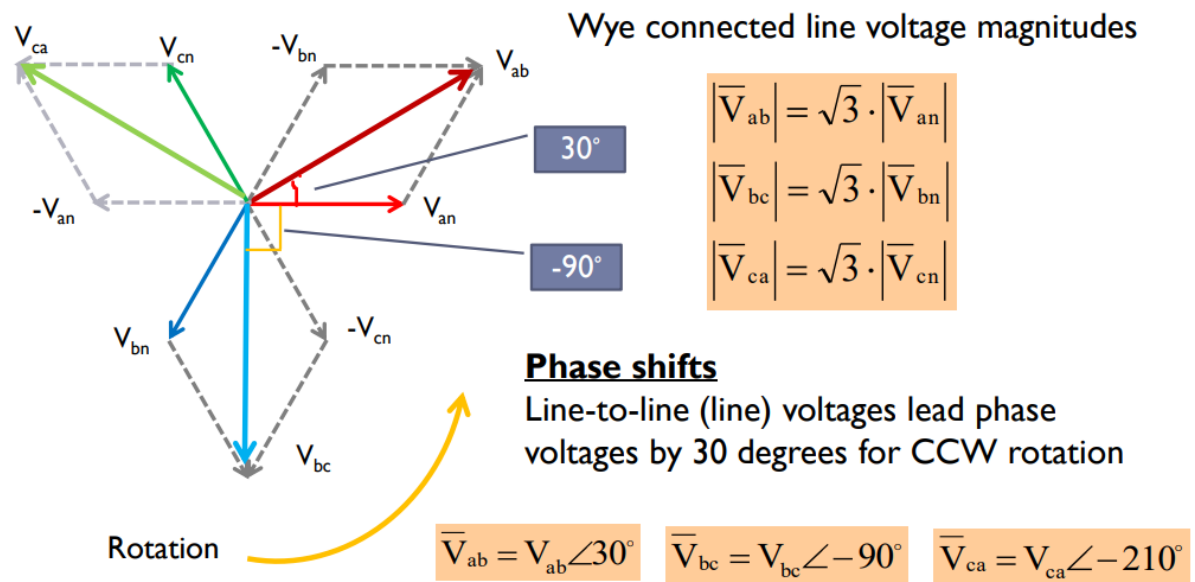


Figure 11. The relation between line and phase voltages

**The line currents are equal to phase currents in Y- connection and their sum is equal to zero in a balanced system.**

$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_Y}, \quad \mathbf{I}_b = \frac{\mathbf{V}_{bn}}{\mathbf{Z}_Y} = \frac{\mathbf{V}_{an} \angle -120^\circ}{\mathbf{Z}_Y} = \mathbf{I}_a \angle -120^\circ$$

$$\mathbf{I}_c = \frac{\mathbf{V}_{cn}}{\mathbf{Z}_Y} = \frac{\mathbf{V}_{an} \angle -240^\circ}{\mathbf{Z}_Y} = \mathbf{I}_a \angle -240^\circ$$

$$\mathbf{I}_a + \mathbf{I}_b + \mathbf{I}_c = 0$$

$$\mathbf{I}_n = -(\mathbf{I}_a + \mathbf{I}_b + \mathbf{I}_c) = 0$$

$$\mathbf{V}_{nN} = \mathbf{Z}_n \mathbf{I}_n = 0$$

## The Single-Phase Equivalent

An alternative way of analyzing a balanced Y-Y system is to do so on a “per phase”

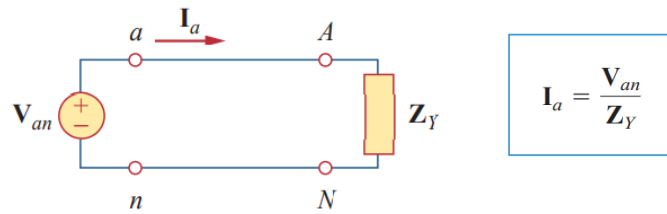


Figure 12. A single-phase equivalent circuit.

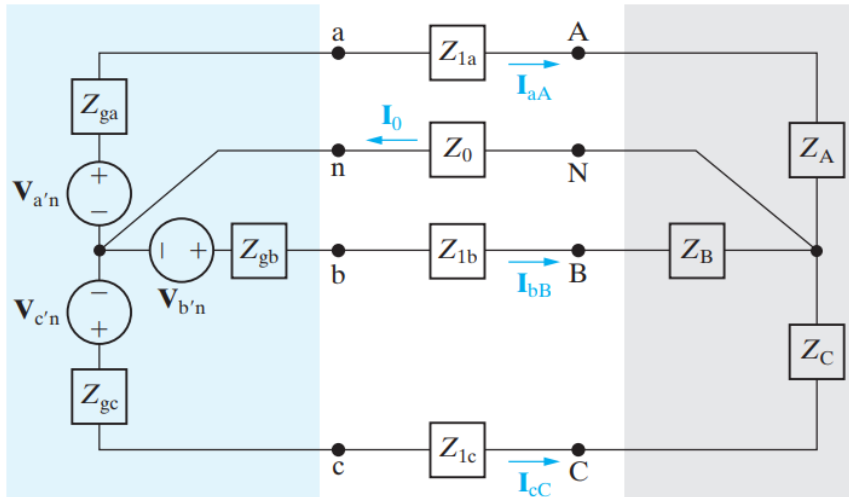


Figure 13. A three-phase Y-Y system.

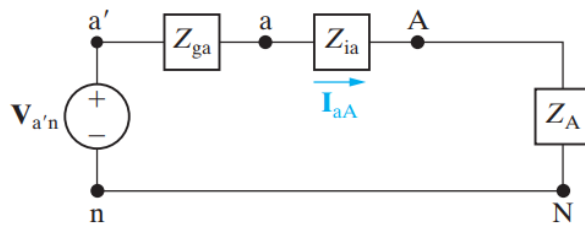


Figure 14 A single-phase equivalent circuit



### Example 3

Calculate the line currents in the three-wire Y-Y system of Fig.15

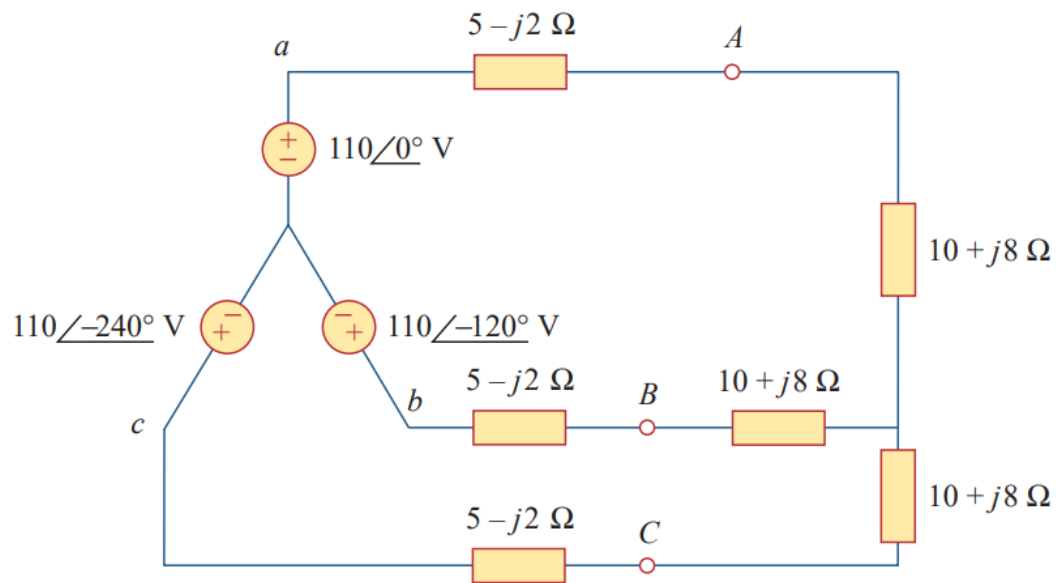


Figure 15. Three-wire Y-Y system

**solution:**

$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_Y}$$

where  $\mathbf{Z}_Y = (5 - j2) + (10 + j8) = 15 + j6 = 16.155\angle 21.8^\circ$ . Hence,

$$\mathbf{I}_a = \frac{110\angle 0^\circ}{16.155\angle 21.8^\circ} = 6.81\angle -21.8^\circ \text{ A}$$

$$\mathbf{I}_b = \mathbf{I}_a\angle -120^\circ = 6.81\angle -141.8^\circ \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_a\angle -240^\circ = 6.81\angle -261.8^\circ \text{ A} = 6.81\angle 98.2^\circ \text{ A}$$

**Sketch the phasor currents**



### Example 4

For Fig. 16,  $E_{AN} = 120 \text{ V} \angle 0^\circ$ .

- Solve for the line currents.
- Solve for the phase voltages at the load.
- Solve for the line voltages at the load

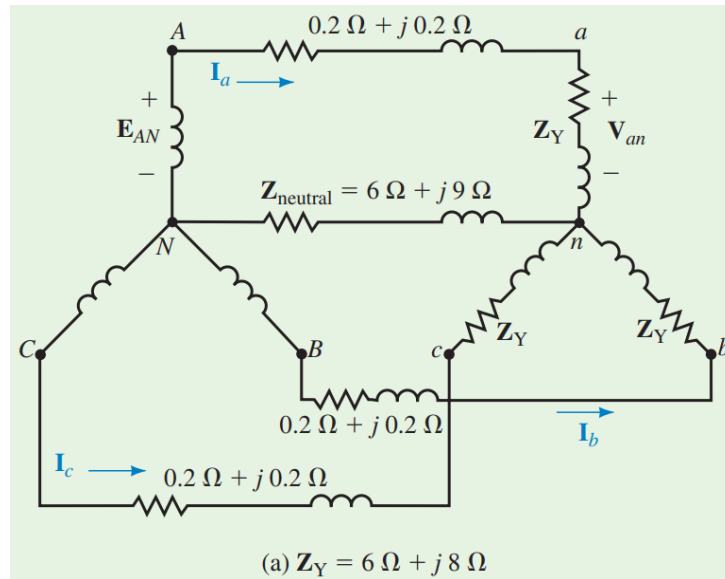


Figure 16 Y-Y connection.

### Solution:

- Reduce the circuit to its single-phase equivalent as shown in Fig. 21

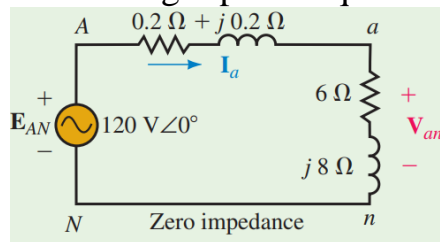


Figure 21 Single-phase equivalent.

Since the neutral conductor carries no current, its impedance has no effect on the solution

$$I_a = \frac{E_{AN}}{Z_T} = \frac{120 \angle 0^\circ}{(0.2 + j0.2) + (6 + j8)} = 11.67 \text{ A} \angle -52.91^\circ$$

Therefore,

$$I_b = 11.67 \text{ A} \angle -172.91^\circ \quad \text{and} \quad I_c = 11.67 \text{ A} \angle 67.09^\circ$$

$$\text{b. } V_{an} = I_a \times Z_{an} = (11.67 \angle -52.91^\circ)(6 + j8) = 116.7 \text{ V} \angle 0.223^\circ$$

Thus,

$$V_{bn} = 116.7 \text{ V} \angle -119.777^\circ \quad \text{and} \quad V_{cn} = 116.7 \text{ V} \angle 120.223^\circ$$

$$\text{c. } V_{ab} = \sqrt{3} V_{an} \angle 30^\circ = \sqrt{3} \times 116.7 \angle (0.223^\circ + 30^\circ) = 202.2 \text{ V} \angle 30.223^\circ$$

Thus,

$$V_{bc} = 202.2 \text{ V} \angle -89.777^\circ \quad \text{and} \quad V_{ca} = 202.2 \text{ V} \angle 150.223^\circ$$

## Star- Delta Connection

Consider the Y-  $\Delta$  connection in Fig. 17

$$V_{an} = V_p \angle 0^\circ$$

$$V_{bn} = V_p \angle -120^\circ, \quad V_{cn} = V_p \angle +120^\circ$$

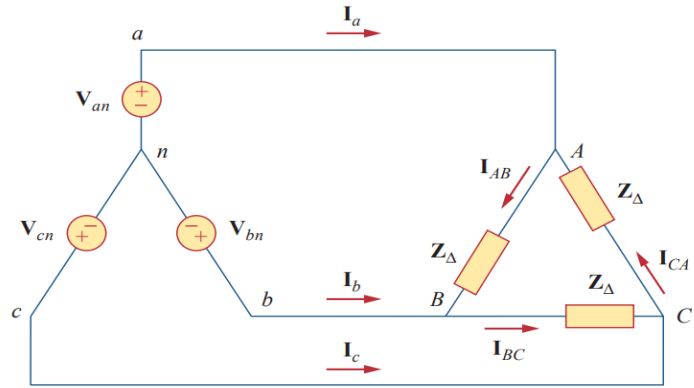


Figure 17 Y- $\Delta$  connection

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}}, \quad I_{BC} = \frac{V_{BC}}{Z_{\Delta}}, \quad I_{CA} = \frac{V_{CA}}{Z_{\Delta}}$$

Or

$$V_{ab} = \sqrt{3}V_p \angle 30^\circ = V_{AB}, \quad V_{bc} = \sqrt{3}V_p \angle -90^\circ = V_{BC}$$

$$V_{ca} = \sqrt{3}V_p \angle +150^\circ = V_{CA}$$

$$-V_{an} + Z_{\Delta}I_{AB} + V_{bn} = 0$$

$$I_{AB} = \frac{V_{an} - V_{bn}}{Z_{\Delta}} = \frac{V_{ab}}{Z_{\Delta}} = \frac{V_{AB}}{Z_{\Delta}}$$

$$I_a = I_{AB} - I_{CA}, \quad I_b = I_{BC} - I_{AB}, \quad I_c = I_{CA} - I_{BC}$$

Since  $I_{CA} = I_{AB} \angle -240^\circ$ ,

$$I_a = I_{AB} - I_{CA} = I_{AB}(1 - 1 \angle -240^\circ)$$

$$= I_{AB}(1 + 0.5 - j0.866) = I_{AB}\sqrt{3} \angle -30^\circ$$

$$I_L = \sqrt{3}I_p$$

$$I_L = |I_a| = |I_b| = |I_c|$$

$$I_p = |I_{AB}| = |I_{BC}| = |I_{CA}|$$

The set of line currents lags the set of phase currents by  $30^\circ$ .

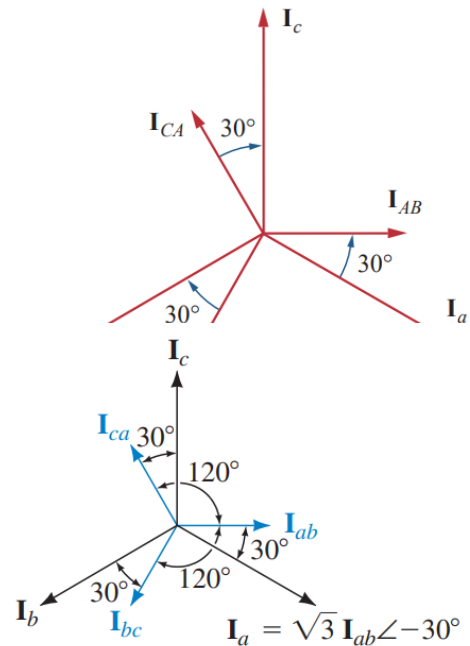


Figure 23 phasor diagram of the line and phase currents in a  $\Delta$  connected load

$$\mathbf{I}_{aA} = \mathbf{I}_{AB} - \mathbf{I}_{CA}$$

$$= I_\phi \angle 0^\circ - I_\phi \angle 120^\circ$$

$$= \sqrt{3}I_\phi \angle -30^\circ,$$

$$\mathbf{I}_{bB} = \mathbf{I}_{BC} - \mathbf{I}_{AB}$$


$$= I_\phi \angle -120^\circ - I_\phi \angle 0^\circ$$

$$= \sqrt{3}I_\phi \angle -150^\circ,$$

$$\mathbf{I}_{cC} = \mathbf{I}_{CA} - \mathbf{I}_{BC}$$

$$= I_\phi \angle 120^\circ - I_\phi \angle -120^\circ$$

$$= \sqrt{3}I_\phi \angle 90^\circ.$$

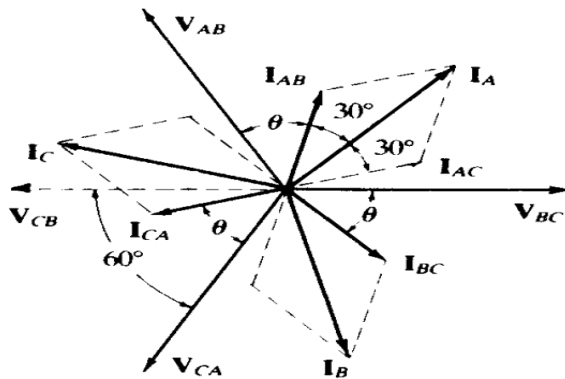

$$Z_{AB} = Z_{BC} = Z_{CA} = Z_\Delta$$

$$I_{AB} = |I_\phi| \angle \phi_{AB}$$

$$I_{BC} = |I_\phi| \angle (\phi_{AB} - 120^\circ)$$

$$I_{CA} = |I_\phi| \angle (\phi_{AB} - 240^\circ)$$

$$I_A = I_{AB} - I_{CA} = |I_\phi| \sqrt{3} \angle (\phi_{AB} - 30^\circ)$$

$$I_B = I_{BC} - I_{AB} = |I_\phi| \sqrt{3} \angle (\phi_{AB} - 120^\circ - 30^\circ)$$

$$I_C = I_{CA} - I_{BC} = |I_\phi| \sqrt{3} \angle (\phi_{AB} - 240^\circ - 30^\circ)$$

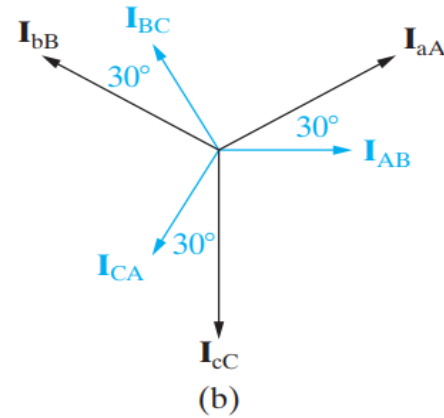
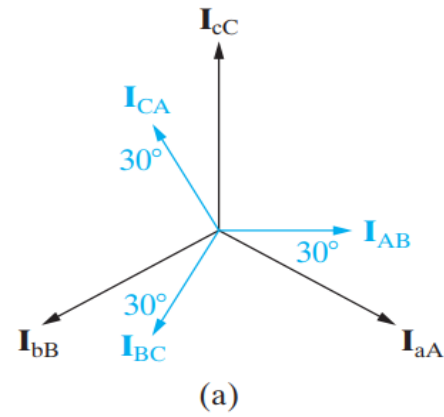


Figure 24 Phasor diagrams of the line and phase currents in a  $\Delta$  connected load.

(a) The positive sequence.

(b) The negative sequence

### Example 6

A balanced *abc*-sequence Y-connected source with  $V_{an} = 100\angle 10^\circ$  V is connected to a  $\Delta$ -connected balanced load  $(8 + j4) \Omega$  per phase. Calculate the phase and line currents.

#### Solution:

This can be solved in two ways.

■ **METHOD 1** The load impedance is

$$Z_{\Delta} = 8 + j4 = 8.944\angle 26.57^\circ \Omega$$

If the phase voltage  $V_{an} = 100\angle 10^\circ$ , then the line voltage is

$$V_{ab} = V_{an}\sqrt{3}\angle 30^\circ = 100\sqrt{3}\angle 10^\circ + 30^\circ = V_{AB}$$

or

$$V_{AB} = 173.2\angle 40^\circ \text{ V}$$

The phase currents are

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{173.2\angle 40^\circ}{8.944\angle 26.57^\circ} = 19.36\angle 13.43^\circ \text{ A}$$

$$I_{BC} = I_{AB}\angle -120^\circ = 19.36\angle -106.57^\circ \text{ A}$$

$$I_{CA} = I_{AB}\angle +120^\circ = 19.36\angle 133.43^\circ \text{ A}$$

The line currents are

$$\begin{aligned} I_a &= I_{AB}\sqrt{3}\angle -30^\circ = \sqrt{3}(19.36)\angle 13.43^\circ - 30^\circ \\ &= 33.53\angle -16.57^\circ \text{ A} \end{aligned}$$

$$I_b = I_a\angle -120^\circ = 33.53\angle -136.57^\circ \text{ A}$$

$$I_c = I_a\angle +120^\circ = 33.53\angle 103.43^\circ \text{ A}$$

■ **METHOD 2** Alternatively, using single-phase analysis,

$$I_a = \frac{V_{an}}{Z_{\Delta}/3} = \frac{100\angle 10^\circ}{2.981\angle 26.57^\circ} = 33.54\angle -16.57^\circ \text{ A}$$

as above. Other line currents are obtained using the *abc* phase sequence.

---

### Example 7

Suppose  $V_{ab}=240\text{ V}\angle 15^\circ$  for the circuit of Fig. 25

- Determine the phase currents.
- Determine the line currents.
- Sketch the phasor diagram.

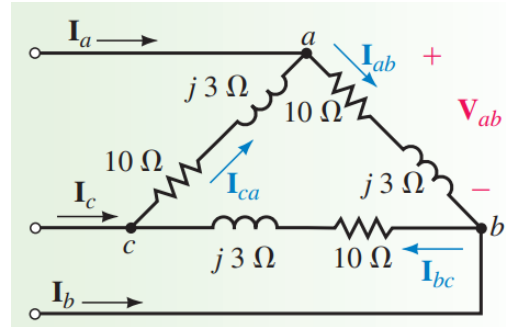


Figure 25 balanced delta load

#### Solution:

a. 
$$I_{ab} = \frac{V_{ab}}{Z_{ab}} = \frac{240\angle 15^\circ}{10 + j3} = 23.0\text{ A}\angle -1.70^\circ$$

Thus,


$$I_{bc} = 23.0\text{ A}\angle -121.7^\circ \text{ and } I_{ca} = 23.0\text{ A}\angle 118.3^\circ$$

b. 
$$I_a = \sqrt{3}I_{ab}\angle -30^\circ = 39.8\text{ A}\angle -31.7^\circ$$

Thus,

$$I_b = 39.8\text{ A}\angle -151.7^\circ \text{ and } I_c = 39.8\text{ A}\angle 88.3^\circ$$

- c. Phasors are shown in Figure 24–15.

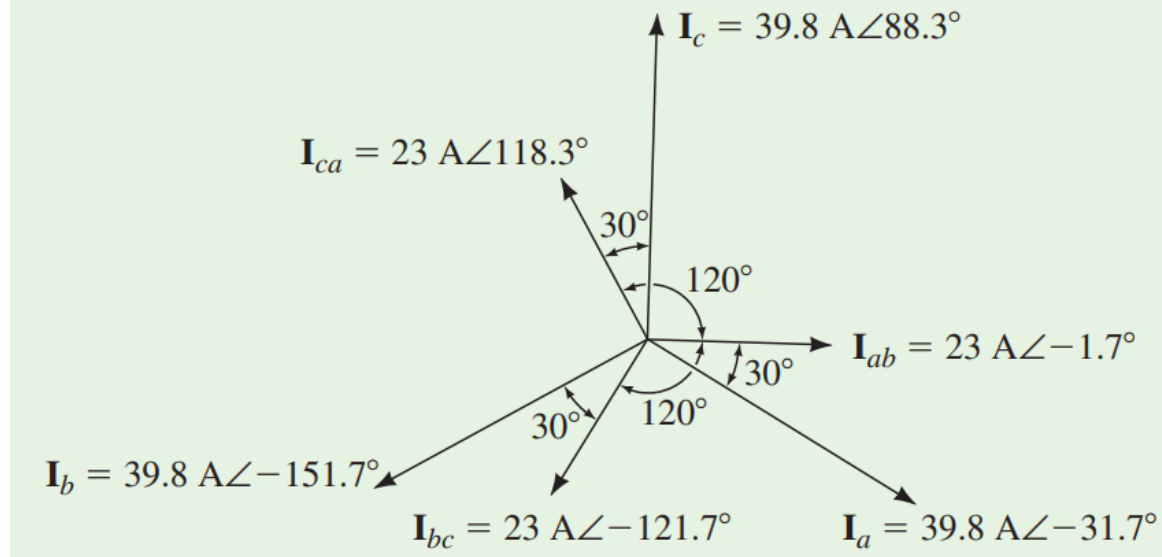

### Example 8

For the circuit of Fig. 26,  $E_{AB} = 208 \text{ V} \angle 30^\circ$ .

- Determine the phase currents.
- Determine the line currents.

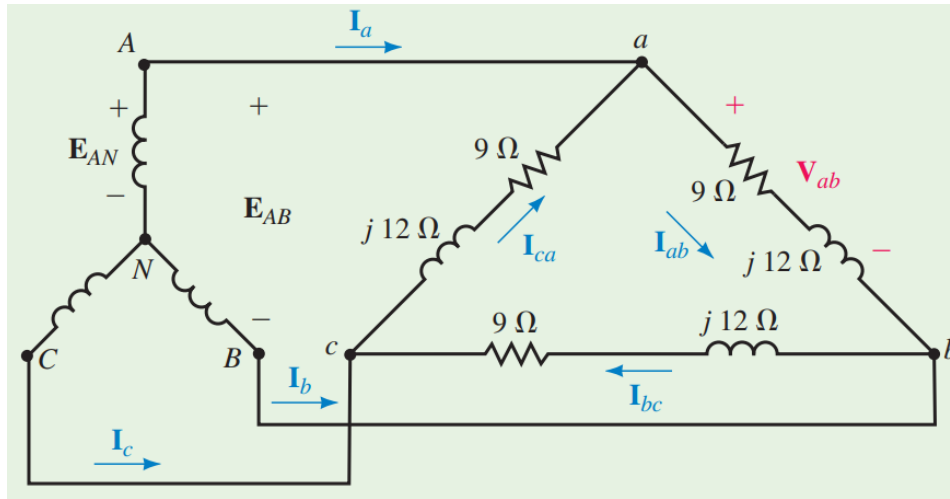


Figure 26 A Y-Δ connection

#### Solution:

- Since this circuit has no line impedance, the load connects directly to the source and  $V_{ab} = E_{AB} = 208 \text{ V} \angle 30^\circ$ . Current  $I_{ab}$  can be found as

$$I_{ab} = \frac{V_{ab}}{Z_{ab}} = \frac{208 \angle 30^\circ}{9 + j12} = \frac{208 \angle 30^\circ}{15 \angle 53.13^\circ} = 13.9 \text{ A} \angle -23.13^\circ$$

Thus,

$$I_{bc} = 13.9 \text{ A} \angle -143.13^\circ \quad \text{and} \quad I_{ca} = 13.9 \text{ A} \angle 96.87^\circ$$

- $I_a = \sqrt{3} I_{ab} \angle -30^\circ = \sqrt{3} (13.9) \angle (-30^\circ - 23.13^\circ) = 24 \text{ A} \angle -53.13^\circ$

Thus,

$$I_b = 24 \text{ A} \angle -173.13^\circ \quad \text{and} \quad I_c = 24 \text{ A} \angle 66.87^\circ$$

### Example 9

For the circuit of Fig. 27, the magnitude of the line voltage at the generator is 207.8 volts. Solve for the line voltage  $V_{ab}$  at the load.

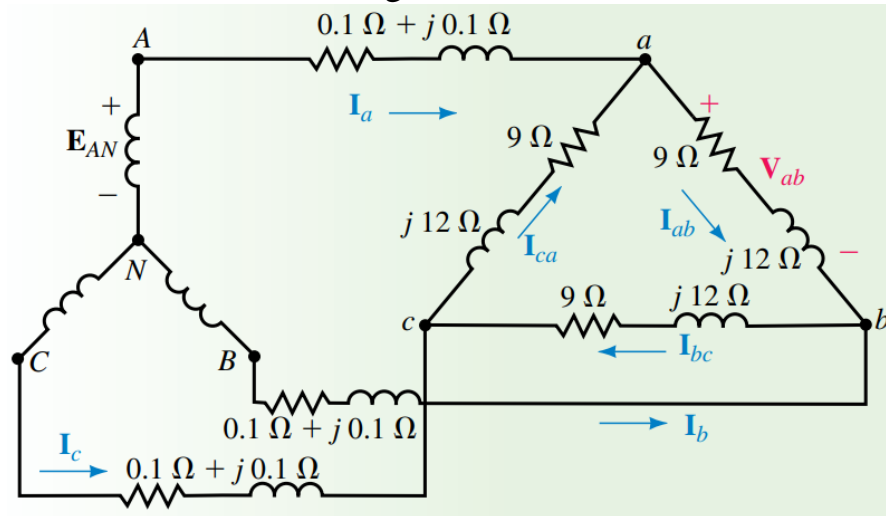


Figure 27 A Y-  $\Delta$  circuit with line impedances.

### Solution:

Since points A-a and B-b are not directly joined,  $V_{ab} \neq E_{AB}$ . Use the single-phase equivalent as in Fig. 28.

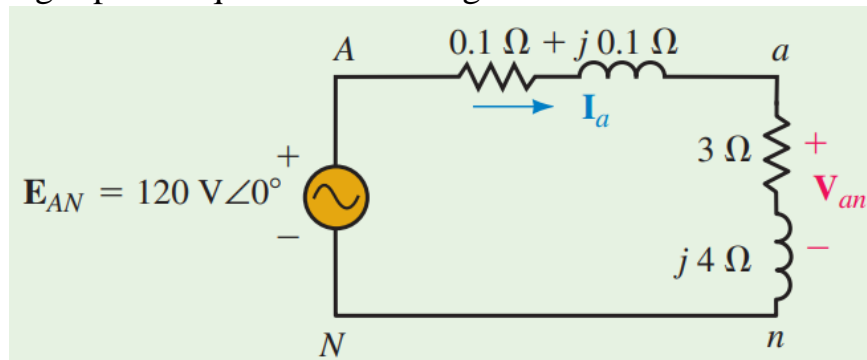


Figure 28 Single-phase equivalent

Phase voltage at the source is  $207.8/\sqrt{3} = 120 \text{ V}$ . Choose  $E_{AN}$  as reference:  $E_{AN} = 120 \text{ V} \angle 0^\circ$ .

$$Z_Y = Z_{\Delta}/3 = (9 + j12)/3 = 3 \Omega + j4 \Omega.$$

Now use the voltage divider rule to find  $V_{an}$ :

$$V_{an} = \left( \frac{3 + j4}{3.1 + j4.1} \right) \times 120 \angle 0^\circ = 116.7 \text{ V} \angle 0.223^\circ$$

Thus,

$$V_{ab} = \sqrt{3} V_{an} \angle 30^\circ = \sqrt{3} (116.7 \text{ V}) \angle 30.223^\circ = 202.2 \text{ V} \angle 30.223^\circ$$



## Balanced Delta-Wye Connection

A balanced -Y system consists of a balanced  $\Delta$  -connected source feeding a balanced Y-connected load. Consider the circuit in Fig. 31

$$\begin{aligned} V_{ab} &= V_p \angle 0^\circ, & V_{bc} &= V_p \angle -120^\circ \\ V_{ca} &= V_p \angle +120^\circ \end{aligned}$$

To obtain the line currents, apply KVL to loop aANBba in Fig. 31, writing

$$-V_{ab} + Z_Y I_a - Z_Y I_b = 0$$

or

$$Z_Y (I_a - I_b) = V_{ab} = V_p \angle 0^\circ$$

Thus,

$$I_a - I_b = \frac{V_p \angle 0^\circ}{Z_Y}$$

But  $I_b$  lags  $I_a$  by  $\angle 120^\circ$  since we assumed the abc sequence; that is,  $I_b = I_a \angle -120^\circ$ . Then,

$$\begin{aligned} I_a - I_b &= I_a (1 - 1 \angle -120^\circ) \\ &= I_a \left( 1 + \frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = I_a \sqrt{3} \angle 30^\circ \end{aligned}$$

$$I_a = \frac{V_p / \sqrt{3} \angle -30^\circ}{Z_Y}$$

$$I_b = I_a \angle -120^\circ, I_c = I_a \angle +120^\circ$$

Another way to obtain the line currents is to replace the delta-connected source with its equivalent wye-connected source, as shown in Fig. 32

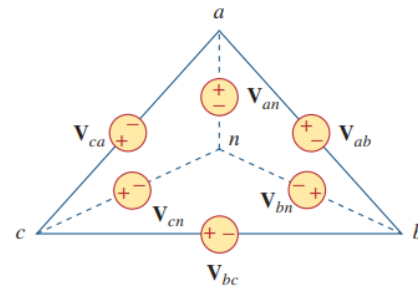


Figure 32 Transforming a  $\Delta$  -connected source to an equivalent Y-connected source

Thus, the equivalent wye-connected source has the phase voltages

$$V_{an} = \frac{V_p}{\sqrt{3}} \angle -30^\circ$$

$$V_{bn} = \frac{V_p}{\sqrt{3}} \angle -150^\circ, \quad V_{cn} = \frac{V_p}{\sqrt{3}} \angle +90^\circ$$

Therefore, we can use the equivalent single-phase circuit shown in Fig. 33

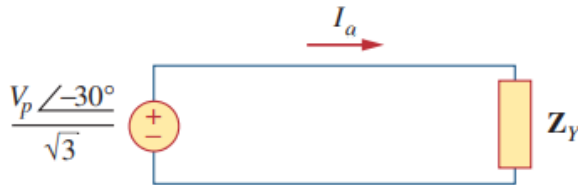


Figure 33 The single-phase equivalent circuit.

$$I_a = \frac{V_p / \sqrt{3} \angle -30^\circ}{Z_Y}$$

$$V_{AN} = I_a Z_Y = \frac{V_p}{\sqrt{3}} \angle -30^\circ$$

$$V_{BN} = V_{AN} \angle -120^\circ, \quad V_{CN} = V_{AN} \angle +120^\circ$$

### Example 11

---

A balanced Y-connected load with a phase impedance of  $40 + j25 \, \Omega$  is supplied by a balanced, positive sequence  $\Delta$ -connected source with a line voltage of 210 V. Calculate the phase currents. Use  $\mathbf{V}_{ab}$  as a reference.

**Solution:**

The load impedance is

$$\mathbf{Z}_Y = 40 + j25 = 47.17 \angle 32^\circ \, \Omega$$

and the source voltage is

$$\mathbf{V}_{ab} = 210 \angle 0^\circ \, \text{V}$$

When the  $\Delta$ -connected source is transformed to a Y-connected source,

$$\mathbf{V}_{an} = \frac{\mathbf{V}_{ab}}{\sqrt{3}} \angle -30^\circ = 121.2 \angle -30^\circ \, \text{V}$$

The line currents are

$$\mathbf{I}_a = \frac{\mathbf{V}_{an}}{\mathbf{Z}_Y} = \frac{121.2 \angle -30^\circ}{47.12 \angle 32^\circ} = 2.57 \angle -62^\circ \, \text{A}$$

$$\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ = 2.57 \angle -178^\circ \, \text{A}$$

$$\mathbf{I}_c = \mathbf{I}_a \angle 120^\circ = 2.57 \angle 58^\circ \, \text{A}$$

which are the same as the phase currents.

---

## Balanced Delta-Delta Connection

Consider the  $\Delta$ - $\Delta$  connection in the circuit shown in Fig. 34

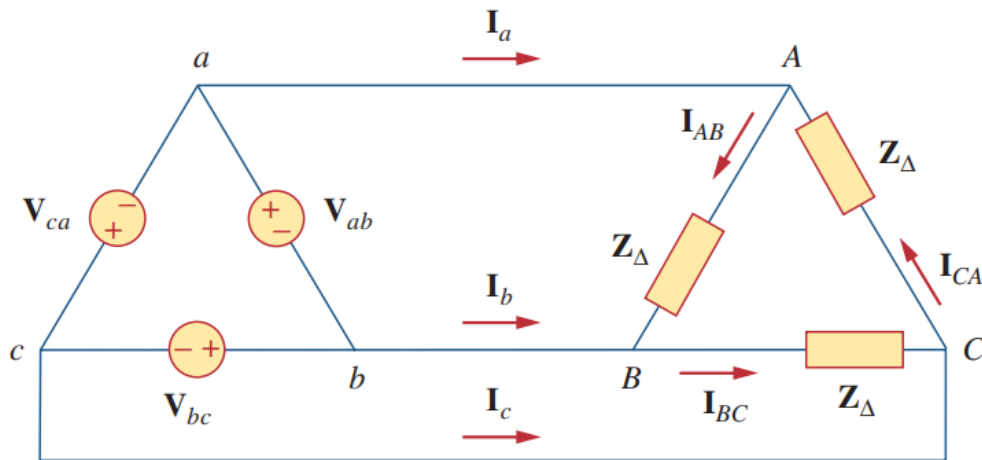


Figure 34 A balanced  $\Delta$ - $\Delta$  connection.

For abc sequence:

$$\begin{aligned} \mathbf{V}_{ab} &= V_p \angle 0^\circ \\ \mathbf{V}_{bc} &= V_p \angle -120^\circ, \quad \mathbf{V}_{ca} = V_p \angle +120^\circ \end{aligned}$$

The line voltages are the same as the phase voltages.

Assuming there is no line impedances,

$$\mathbf{V}_{ab} = \mathbf{V}_{AB}, \quad \mathbf{V}_{bc} = \mathbf{V}_{BC}, \quad \mathbf{V}_{ca} = \mathbf{V}_{CA}$$

The phase currents are


$$\begin{aligned} \mathbf{I}_{AB} &= \frac{\mathbf{V}_{AB}}{Z_\Delta} = \frac{\mathbf{V}_{ab}}{Z_\Delta}, \quad \mathbf{I}_{BC} = \frac{\mathbf{V}_{BC}}{Z_\Delta} = \frac{\mathbf{V}_{bc}}{Z_\Delta} \\ \mathbf{I}_{CA} &= \frac{\mathbf{V}_{CA}}{Z_\Delta} = \frac{\mathbf{V}_{ca}}{Z_\Delta} \end{aligned}$$

The line currents are

$$\mathbf{I}_a = \mathbf{I}_{AB} - \mathbf{I}_{CA}, \quad \mathbf{I}_b = \mathbf{I}_{BC} - \mathbf{I}_{AB}, \quad \mathbf{I}_c = \mathbf{I}_{CA} - \mathbf{I}_{BC}$$

Each line current lags the corresponding phase current by  $30^\circ$  and the magnitude of

$$I_L = \sqrt{3} I_p$$

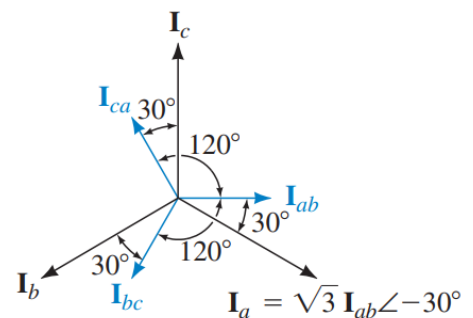

An alternative way of analyzing the circuit is to convert both the source and the load to their Y equivalents

**Example 12**

---

A balanced  $\Delta$ -connected load having an impedance  $20 - j15 \Omega$  is connected to a  $\Delta$ -connected, positive-sequence generator having  $V_{ab} = 330 \angle 0^\circ \text{ V}$ . Calculate the phase currents of the load and the line currents.

**Solution:**

The load impedance per phase is

$$\mathbf{Z}_{\Delta} = 20 - j15 = 25 \angle -36.87^\circ \Omega$$

Since  $V_{AB} = V_{ab}$ , the phase currents are

$$\mathbf{I}_{AB} = \frac{\mathbf{V}_{AB}}{\mathbf{Z}_{\Delta}} = \frac{330 \angle 0^\circ}{25 \angle -36.87^\circ} = 13.2 \angle 36.87^\circ \text{ A}$$

$$\mathbf{I}_{BC} = \mathbf{I}_{AB} \angle -120^\circ = 13.2 \angle -83.13^\circ \text{ A}$$

$$\mathbf{I}_{CA} = \mathbf{I}_{AB} \angle +120^\circ = 13.2 \angle 156.87^\circ \text{ A}$$

For a delta load, the line current always lags the corresponding phase current by  $30^\circ$  and has a magnitude  $\sqrt{3}$  times that of the phase current. Hence, the line currents are

$$\begin{aligned} \mathbf{I}_a &= \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ = (13.2 \angle 36.87^\circ)(\sqrt{3} \angle -30^\circ) \\ &= 22.86 \angle 6.87^\circ \text{ A} \end{aligned}$$

$$\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ = 22.86 \angle -113.13^\circ \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ = 22.86 \angle 126.87^\circ \text{ A}$$

---

# Summary of phase and line voltages/currents for balanced three-phase systems.<sup>1</sup>

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ <p>Same as line currents</p>	$\mathbf{V}_{ab} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{V}_{an} / \mathbf{Z}_Y$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
Y- $\Delta$	$\mathbf{V}_{an} = V_p \angle 0^\circ$ $\mathbf{V}_{bn} = V_p \angle -120^\circ$ $\mathbf{V}_{cn} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{AB} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{BC} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{CA} / \mathbf{Z}_\Delta$	$\mathbf{V}_{ab} = \mathbf{V}_{AB} = \sqrt{3}V_p \angle 30^\circ$ $\mathbf{V}_{bc} = \mathbf{V}_{BC} = \mathbf{V}_{ab} \angle -120^\circ$ $\mathbf{V}_{ca} = \mathbf{V}_{CA} = \mathbf{V}_{ab} \angle +120^\circ$ $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
$\Delta$ - $\Delta$	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ $\mathbf{I}_{AB} = \mathbf{V}_{ab} / \mathbf{Z}_\Delta$ $\mathbf{I}_{BC} = \mathbf{V}_{bc} / \mathbf{Z}_\Delta$ $\mathbf{I}_{CA} = \mathbf{V}_{ca} / \mathbf{Z}_\Delta$	<p>Same as phase voltages</p> $\mathbf{I}_a = \mathbf{I}_{AB} \sqrt{3} \angle -30^\circ$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$
$\Delta$ -Y	$\mathbf{V}_{ab} = V_p \angle 0^\circ$ $\mathbf{V}_{bc} = V_p \angle -120^\circ$ $\mathbf{V}_{ca} = V_p \angle +120^\circ$ <p>Same as line currents</p>	<p>Same as phase voltages</p> $\mathbf{I}_a = \frac{V_p \angle -30^\circ}{\sqrt{3}\mathbf{Z}_Y}$ $\mathbf{I}_b = \mathbf{I}_a \angle -120^\circ$ $\mathbf{I}_c = \mathbf{I}_a \angle +120^\circ$

<sup>1</sup> Positive or abc sequence is assumed