



COLLEGE OF ENGINEERING AND TECHNOLOGIES
ALMUSTAQBAL UNIVERSITY

Electronics

CTE 207

Lecture 17

- Voltage Feedback Bias -
(2023 - 2024)


Dr. Zaidoon AL-Shammari

Lecturer / Researcher


zaidoon.waleed@mustaqbal-college.edu.iq

- An improved level of stability can also be obtained by introducing a feedback path from collector to base as shown in Figure below.
- Although the Q-point is not totally independent of beta (even under approximate conditions), the sensitivity to changes in beta or temperature variations is normally less than encountered for the fixed-bias or emitter-biased configurations.
- The analysis will again be performed by first analyzing the base – emitter loop with the results applied to the collector – emitter loop.

Voltage Feedback Bias

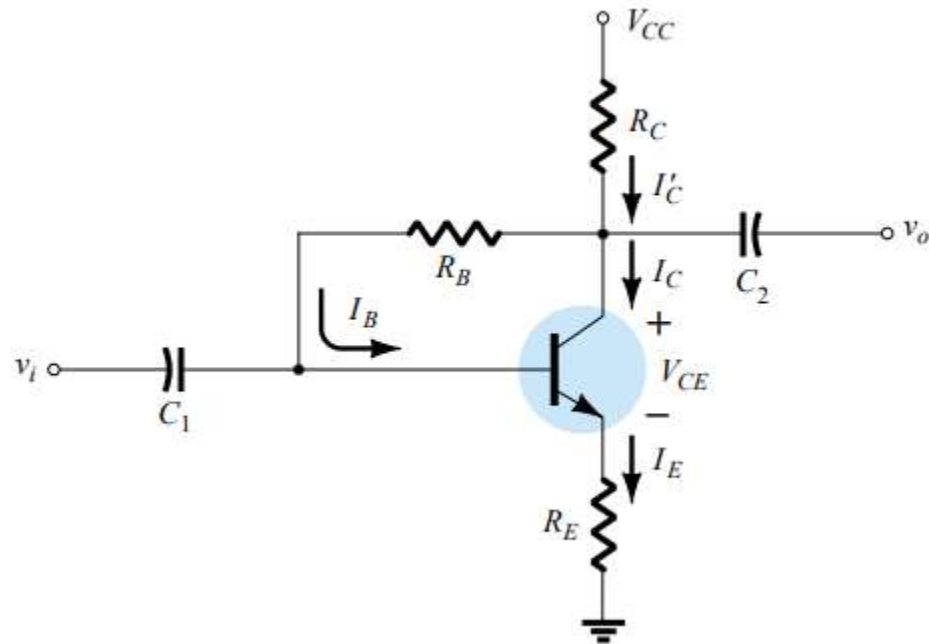

DC bias circuit with voltage feedback

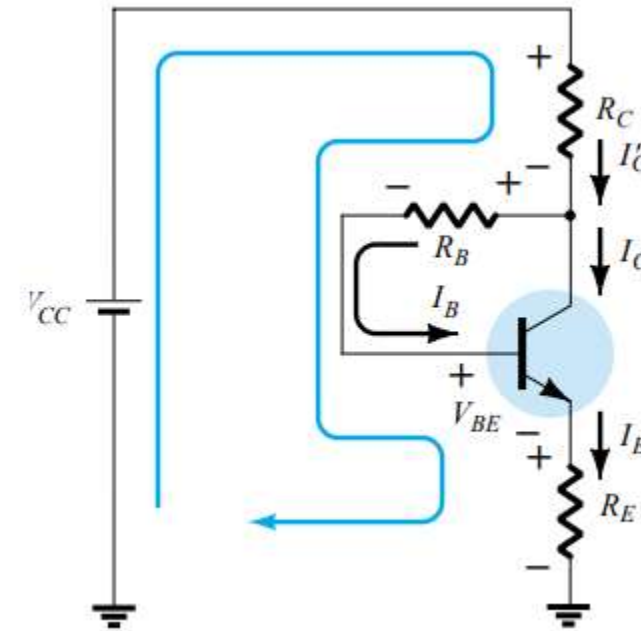

Base – emitter loop for the network

- The Figure above shows the base–emitter loop for the voltage feedback configuration.
- Writing Kirchhoff’s voltage law around the indicated loop in the clockwise direction will result in

$$V_{CC} - I_C R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

Base – Emitter Loop

$$V_{CC} - I'_C R_C - I_B R_B - V_{BE} - I_E R_E = 0$$

Substituting $I'_C \cong I_C = \beta I_B$ and $I_E \cong I_C$

$$V_{CC} - \beta I_B R_C - I_B R_B - V_{BE} - \beta I_B R_E = 0$$

$$V_{CC} - \beta I_B (R_C + R_E) - I_B R_B - V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{\beta(R_C + R_E) + R_B}$$

Collector – Emitter Loop

- The collector–emitter loop for the network of Figure below is provided.
- Applying Kirchhoff's voltage law around the indicated loop in the clockwise direction will result in


$$I_E R_E + V_{CE} + I'_C R_C - V_{CC} = 0$$

Since $I'_C \cong I_C$ and $I_E \cong I_C$, we have

$$I_C (R_C + R_E) + V_{CE} - V_{CC} = 0$$

and


$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

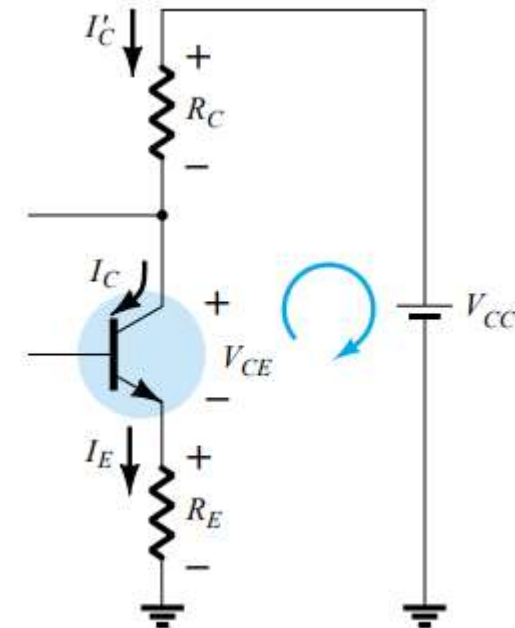

Collector – emitter loop

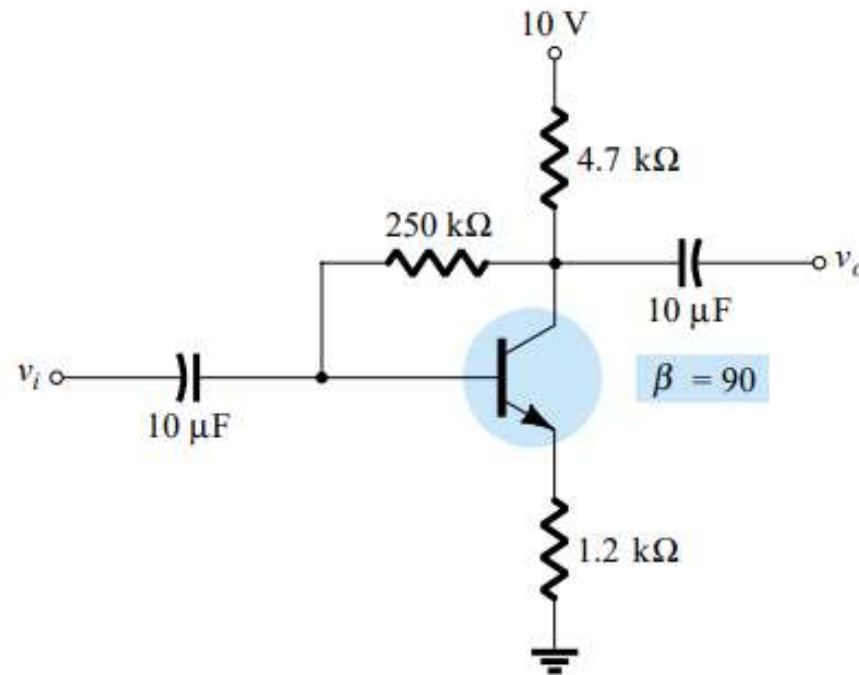Example 1

Determine the quiescent levels of I_C and V_{CE} for the network of the Figure below.



Network for Example 1

Solution

$$\begin{aligned}I_B &= \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)} \\&= \frac{10 \text{ V} - 0.7 \text{ V}}{250 \text{ k}\Omega + (90)(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega)} \\&= \frac{9.3 \text{ V}}{250 \text{ k}\Omega + 531 \text{ k}\Omega} = \frac{9.3 \text{ V}}{781 \text{ k}\Omega} \\&= 11.91 \mu\text{A}\end{aligned}$$

$$\begin{aligned}I_{C_Q} &= \beta I_B = (90)(11.91 \mu\text{A}) \\&= \mathbf{1.07 \text{ mA}}\end{aligned}$$

$$\begin{aligned}V_{CE_Q} &= V_{CC} - I_C(R_C + R_E) \\&= 10 \text{ V} - (1.07 \text{ mA})(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega) \\&= 10 \text{ V} - 6.31 \text{ V} \\&= \mathbf{3.69 \text{ V}}\end{aligned}$$

Example 2

Repeat Example 1 by using a beta of 135 (50% more than Example 1).

Sol:

$$\begin{aligned} I_B &= \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)} = \\ &= \frac{10 \text{ V} - 0.7 \text{ V}}{250 \text{ k}\Omega + (135)(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega)} \\ &= \frac{9.3 \text{ V}}{250 \text{ k}\Omega + 796.5 \text{ k}\Omega} = \frac{9.3 \text{ V}}{1046.5 \text{ k}\Omega} \\ &= 8.89 \mu\text{A} \end{aligned}$$


and
$$I_{C_Q} = \beta I_B$$
$$= (135)(8.89 \mu\text{A})$$
$$= \mathbf{1.2 \text{ mA}}$$

and
$$V_{CE_Q} = V_{CC} - I_C(R_C + R_E)$$
$$= 10 \text{ V} - (1.2 \text{ mA})(4.7 \text{ k}\Omega + 1.2 \text{ k}\Omega)$$
$$= 10 \text{ V} - 7.08 \text{ V}$$
$$= \mathbf{2.92 \text{ V}}$$

- Even though the level of beta increased 50%, the level of ICQ only increased 12.1% while the level of VCEQ decreased about 20.9%.
- If the network were a fixed-bias design, a 50% increase in β would have resulted in a 50% increase in ICQ and a dramatic change in the location of the Q - poin.

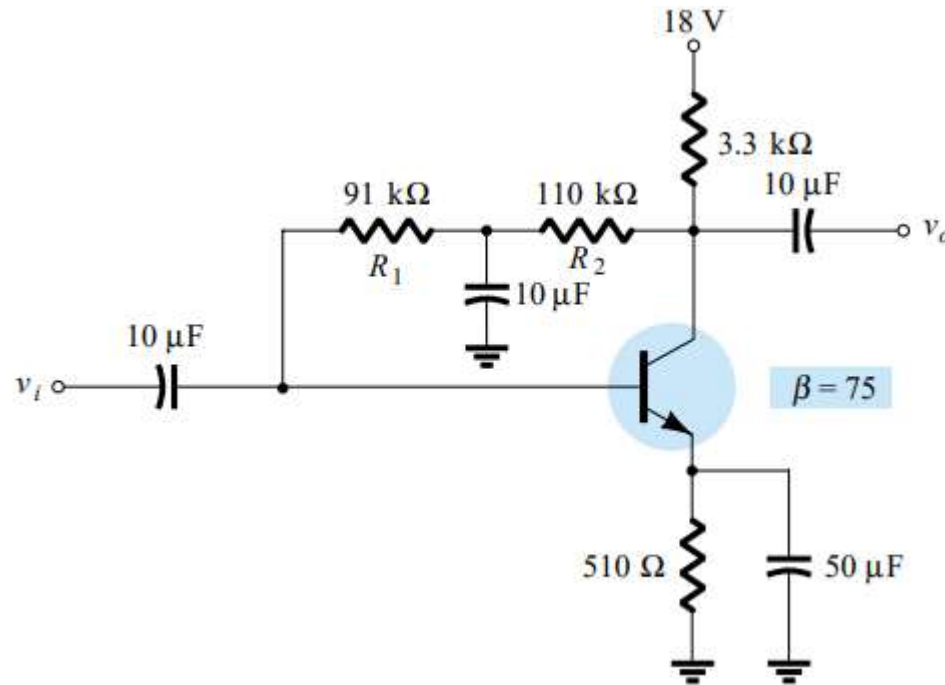Example 3

Determine the DC level of I_B and V_C for the network of the Figure below.



Network for Example 3

In this case, the base resistance for the DC analysis is composed of two resistors with a capacitor connected from their junction to ground.

For the dc mode, the capacitor assumes the open-circuit equivalence and $R_B = R_1 + R_2$.

Solving for I_B gives

$$\begin{aligned} I_B &= \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)} \\ &= \frac{18 \text{ V} - 0.7 \text{ V}}{(91 \text{ k}\Omega + 110 \text{ k}\Omega) + (75)(3.3 \text{ k}\Omega + 0.51 \text{ k}\Omega)} \\ &= \frac{17.3 \text{ V}}{201 \text{ k}\Omega + 285.75 \text{ k}\Omega} = \frac{17.3 \text{ V}}{486.75 \text{ k}\Omega} \\ &= \mathbf{35.5 \mu A} \end{aligned}$$

$$\begin{aligned}I_C &= \beta I_B \\ &= (75)(35.5 \mu\text{A}) \\ &= 2.66 \text{ mA}\end{aligned}$$

$$\begin{aligned}V_C &= V_{CC} - I_C' R_C \cong V_{CC} - I_C R_C \\ &= 18 \text{ V} - (2.66 \text{ mA})(3.3 \text{ k}\Omega) \\ &= 18 \text{ V} - 8.78 \text{ V} \\ &= \mathbf{9.22 \text{ V}}\end{aligned}$$

