



Ministry of Higher Education and Scientific Research
Almustaqbal University, College of Engineering
And Engineering Technologies
Computer Technology Engineering Department

Six week :

Parallel Ac Circuits (R L C)

Course Name : Fundamentals of Electricity

Stage : One

Academic Year : 2024


Assist. Prof. Zahraa Hazim Al-Fatlawi

PARALLEL AC CIRCUITS

15.7 ADMITTANCE AND SUSCEPTANCE

In ac circuits, we define **admittance (Y)** as being equal to $1/Z$. The unit of measure for admittance as defined by the SI system is **siemens**, which has the symbol **S**.

$$Y_T = Y_1 + Y_2 + Y_3 + \cdots + Y_N$$

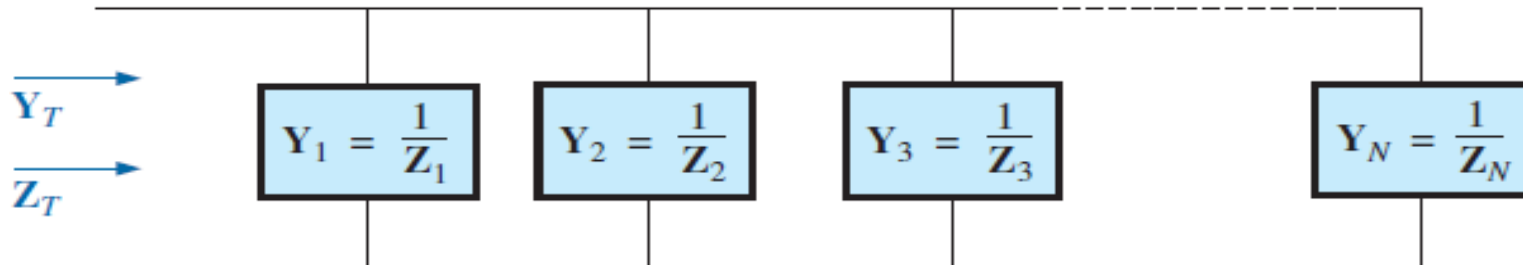

since $Z = 1/Y$,

$$\frac{1}{Z_T} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \cdots + \frac{1}{Z_N}$$

and

$$Z_T = \frac{1}{\frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \cdots + \frac{1}{Z_N}}$$

Conductance is the reciprocal of resistance,

The reciprocal of reactance (1/X) is called **susceptance** and is a measure of how

susceptible an element is to the passage of current through it. Susceptance is also measured in **Siemens** and is represented by the capital letter **B**.

For the capacitor,

$$Y_C = \frac{1}{Z_C} = \frac{1}{X_C \angle -90^\circ} = \frac{1}{X_C} \angle 90^\circ$$

Defining $B_C = \frac{1}{X_C}$ (siemens, S)

we have $Y_C = B_C \angle 90^\circ$

$$Y_R = \frac{1}{Z_R} = \frac{1}{R \angle 0^\circ} = G \angle 0^\circ$$


For the inductor,

$$Y_L = \frac{1}{Z_L} = \frac{1}{X_L \angle 90^\circ} = \frac{1}{X_L} \angle -90^\circ$$

Defining $B_L = \frac{1}{X_L}$ (siemens, S)

we have $Y_L = B_L \angle -90^\circ$

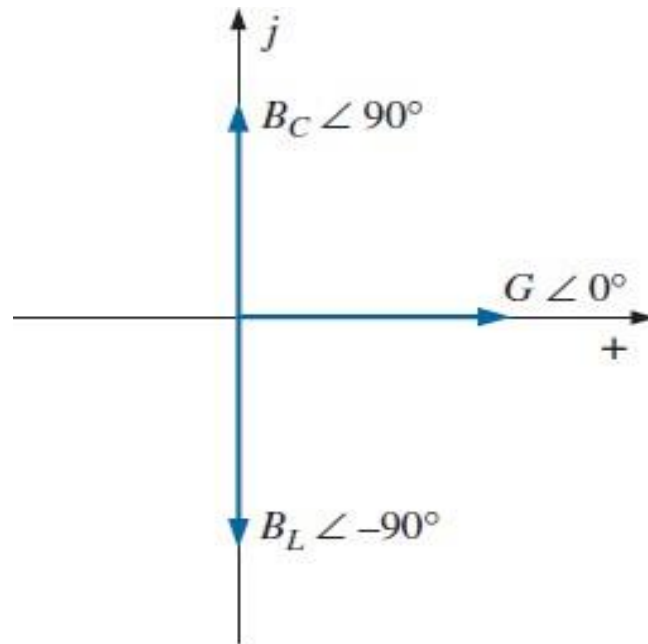
For any configuration (series, parallel, series-parallel, and so on), the angle associated with the total admittance is the angle by which the source current leads the applied voltage. For inductive networks, θ_T is negative, whereas for capacitive networks, θ_T is positive.



Admittance diagram.

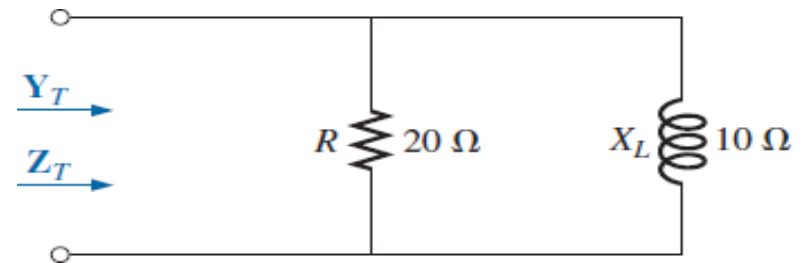EXAMPLE 15.13 For the network in Fig. :

- Calculate the input impedance.
- Draw the impedance diagram.
- Find the admittance of each parallel branch.
- Determine the input admittance and draw the admittance diagram.




$$\begin{aligned} \text{a. } Z_T &= \frac{Z_R Z_L}{Z_R + Z_L} = \frac{(20 \Omega \angle 0^\circ)(10 \Omega \angle 90^\circ)}{20 \Omega + j 10 \Omega} \\ &= \frac{200 \Omega \angle 90^\circ}{22.361 \angle 26.57^\circ} = \mathbf{8.93 \Omega \angle 63.43^\circ} \\ &= \mathbf{4.00 \Omega + j 7.95 \Omega} = R_T + j X_{L_T} \end{aligned}$$

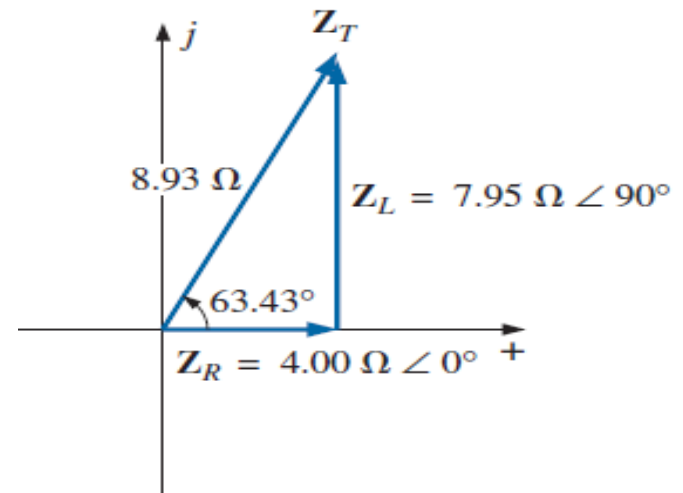b. The impedance diagram appears in Fig.


$$\begin{aligned} \text{c. } Y_R &= G \angle 0^\circ = \frac{1}{R} \angle 0^\circ = \frac{1}{20 \Omega} \angle 0^\circ = \mathbf{0.05 \text{ S} \angle 0^\circ} \\ &= \mathbf{0.05 \text{ S} + j 0} \end{aligned}$$

$$\begin{aligned} Y_L &= B_L \angle -90^\circ = \frac{1}{X_L} \angle -90^\circ = \frac{1}{10 \Omega} \angle -90^\circ \\ &= \mathbf{0.1 \text{ S} \angle -90^\circ} = \mathbf{0 - j 0.1 \text{ S}} \end{aligned}$$



$$\begin{aligned} \text{d. } \mathbf{Y}_T &= \mathbf{Y}_R + \mathbf{Y}_L = (0.05 \text{ S} + j 0) + (0 - j 0.1 \text{ S}) \\ &= \mathbf{0.05 \text{ S} - j 0.1 \text{ S} = G - jB_L} \end{aligned}$$

The admittance diagram appears in Fig.


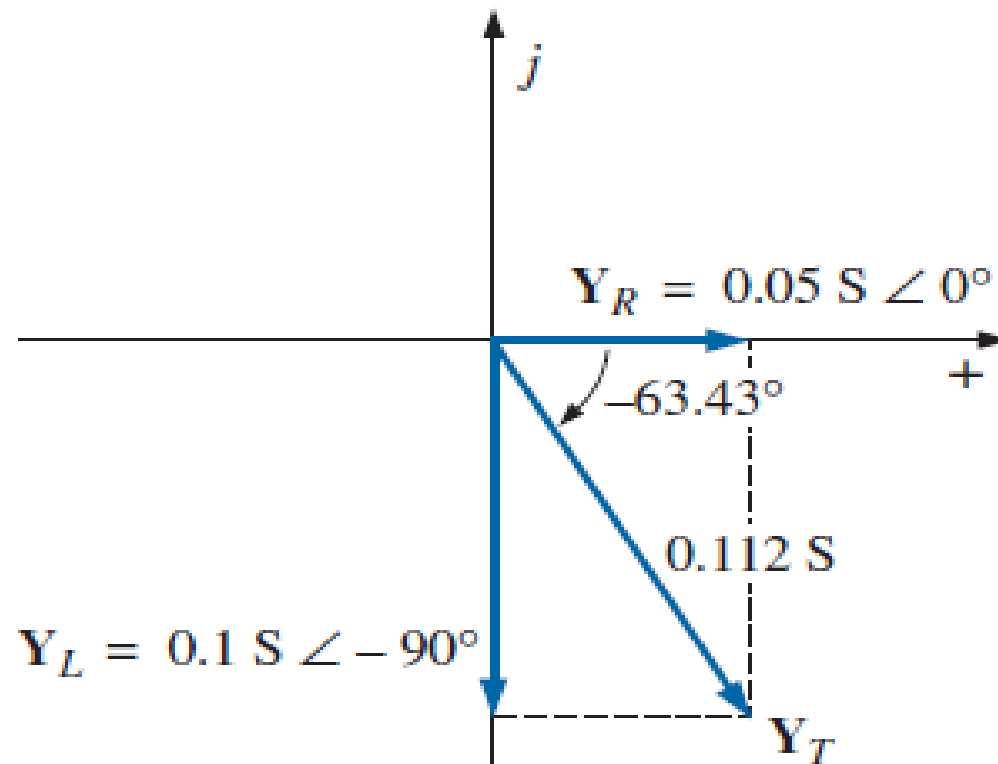


15.9 CURRENT DIVIDER RULE

The basic format for the **current divider** rule in ac circuits is exactly the same as that for dc circuits; that is, for two parallel branches with impedances **Z₁** and **Z₂** as shown in Fig.

$$I_1 = \frac{Z_2 I_T}{Z_1 + Z_2} \quad \text{or} \quad I_2 = \frac{Z_1 I_T}{Z_1 + Z_2}$$

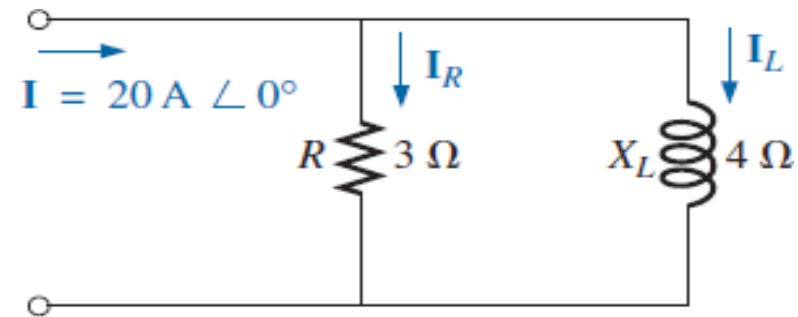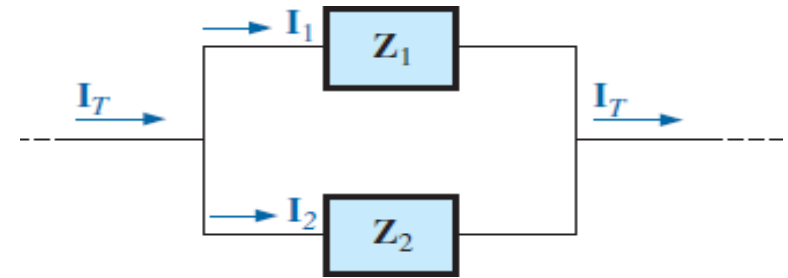EXAMPLE 15.16 Using the current divider rule, find the current through each impedance in Fig.




Draw the Current Phasor Diagram

$$I_R = \frac{Z_L I_T}{Z_R + Z_L} = \frac{(4 \Omega \angle 90^\circ)(20 \text{ A} \angle 0^\circ)}{3 \Omega \angle 0^\circ + 4 \Omega \angle 90^\circ} = \frac{80 \text{ A} \angle 90^\circ}{5 \angle 53.13^\circ} = 16 \text{ A} \angle 36.87^\circ$$

$$I_L = \frac{Z_R I_T}{Z_R + Z_L} = \frac{(3 \Omega \angle 0^\circ)(20 \text{ A} \angle 0^\circ)}{5 \Omega \angle 53.13^\circ} = \frac{60 \text{ A} \angle 0^\circ}{5 \angle 53.13^\circ} = 12 \text{ A} \angle -53.13^\circ$$

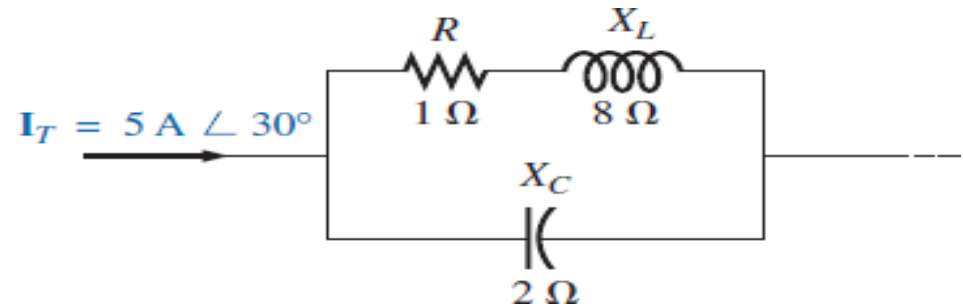
EXAMPLE 15.17 Using the current divider rule, find the current through each parallel branch in Fig.




$$\begin{aligned} \mathbf{I}_{R-L} &= \frac{\mathbf{Z}_C \mathbf{I}_T}{\mathbf{Z}_C + \mathbf{Z}_{R-L}} = \frac{(2 \Omega \angle -90^\circ)(5 \text{ A} \angle 30^\circ)}{-j 2 \Omega + 1 \Omega + j 8 \Omega} = \frac{10 \text{ A} \angle -60^\circ}{1 + j 6} \\ &= \frac{10 \text{ A} \angle -60^\circ}{6.083 \angle 80.54^\circ} \equiv \mathbf{1.64 \text{ A} \angle -140.54^\circ} \end{aligned}$$

$$\begin{aligned} \mathbf{I}_C &= \frac{\mathbf{Z}_{R-L} \mathbf{I}_T}{\mathbf{Z}_{R-L} + \mathbf{Z}_C} = \frac{(1 \Omega + j 8 \Omega)(5 \text{ A} \angle 30^\circ)}{6.08 \Omega \angle 80.54^\circ} \\ &= \frac{(8.06 \angle 82.87^\circ)(5 \text{ A} \angle 30^\circ)}{6.08 \angle 80.54^\circ} = \frac{40.30 \text{ A} \angle 112.87^\circ}{6.083 \angle 80.54^\circ} \\ &= \mathbf{6.63 \text{ A} \angle 32.33^\circ} \end{aligned}$$

15.12 EQUIVALENT CIRCUITS

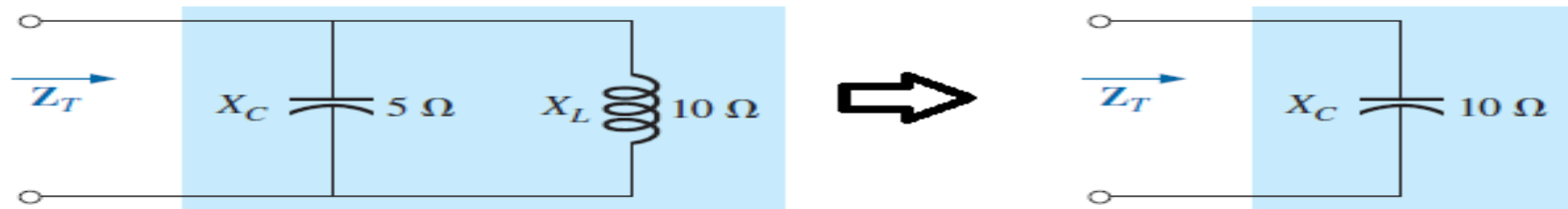
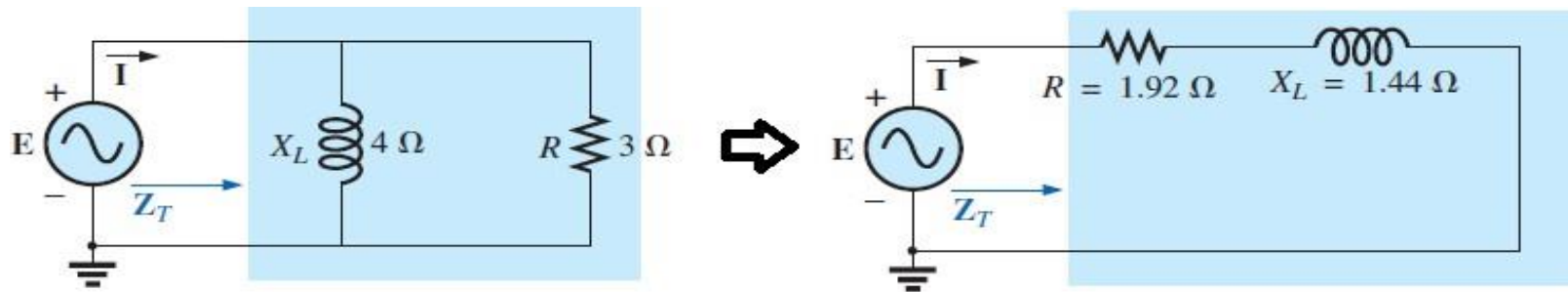
$$\begin{aligned} Z_T &= \frac{Z_C Z_L}{Z_C + Z_L} = \frac{(5\ \Omega \angle -90^\circ)(10\ \Omega \angle 90^\circ)}{5\ \Omega \angle -90^\circ + 10\ \Omega \angle 90^\circ} = \frac{50 \angle 0^\circ}{5 \angle 90^\circ} \\ &= 10\ \Omega \angle -90^\circ \end{aligned}$$




$$\begin{aligned} Z_T &= \frac{Z_L Z_R}{Z_L + Z_R} = \frac{(4\ \Omega \angle 90^\circ)(3\ \Omega \angle 0^\circ)}{4\ \Omega \angle 90^\circ + 3\ \Omega \angle 0^\circ} \\ &= \frac{12 \angle 90^\circ}{5 \angle 53.13^\circ} = 2.40\ \Omega \angle 36.87^\circ = 1.92\ \Omega + j 1.44\ \Omega \end{aligned}$$

$$\mathbf{Y}_p = \frac{1}{R_p} + \frac{1}{\pm jX_p} = \frac{1}{R_p} \mp j \frac{1}{X_p}$$

and
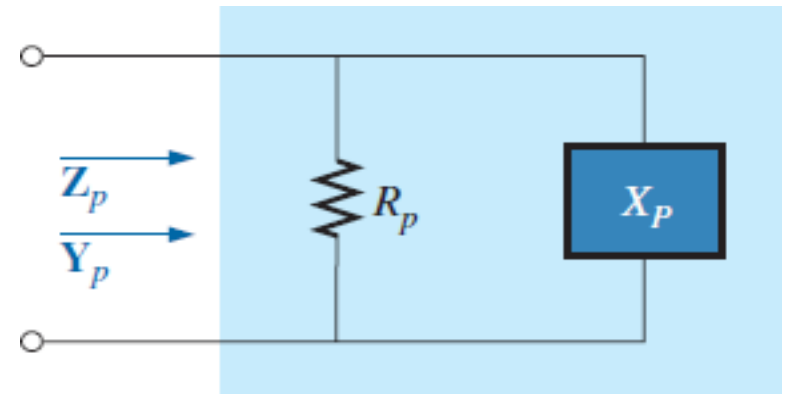
$$\begin{aligned} \mathbf{Z}_p &= \frac{1}{\mathbf{Y}_p} = \frac{1}{(1/R_p) \mp j(1/X_p)} \\ &= \frac{1/R_p}{(1/R_p)^2 + (1/X_p)^2} \pm j \frac{1/X_p}{(1/R_p)^2 + (1/X_p)^2} \end{aligned}$$



Multiplying the numerator and denominator of each term by $R_p^2 X_p^2$:


results in

$$\begin{aligned} \mathbf{Z}_p &= \frac{R_p X_p^2}{X_p^2 + R_p^2} \pm j \frac{R_p^2 X_p}{X_p^2 + R_p^2} \\ &= R_s \pm j X_s \end{aligned}$$

and

$$R_s = \frac{R_p X_p^2}{X_p^2 + R_p^2}$$
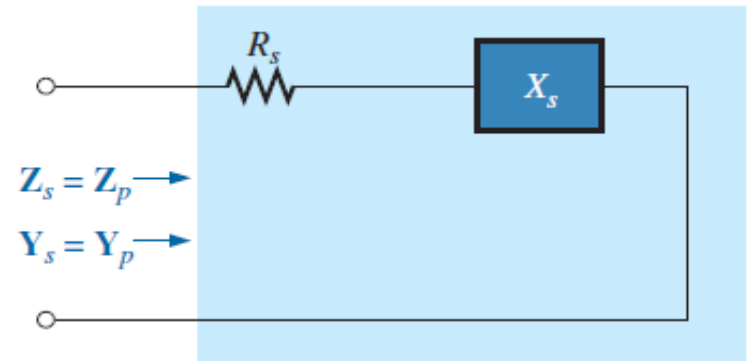
$$X_s = \frac{R_p^2 X_p}{X_p^2 + R_p^2}$$




$$Z_s = R_s \pm jX_s$$

$$\begin{aligned} Y_s &= \frac{1}{Z_s} = \frac{1}{R_s \pm jX_s} = \frac{R_s}{R_s^2 + X_s^2} \mp j \frac{X_s}{R_s^2 + X_s^2} \\ &= G_p \mp jB_p = \frac{1}{R_p} \mp j \frac{1}{X_p} \end{aligned}$$


or

$$R_p = \frac{R_s^2 + X_s^2}{R_s} \quad X_p = \frac{R_s^2 + X_s^2}{X_s}$$

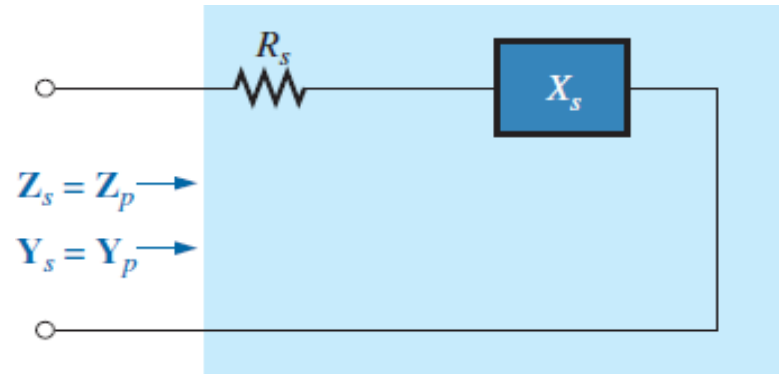

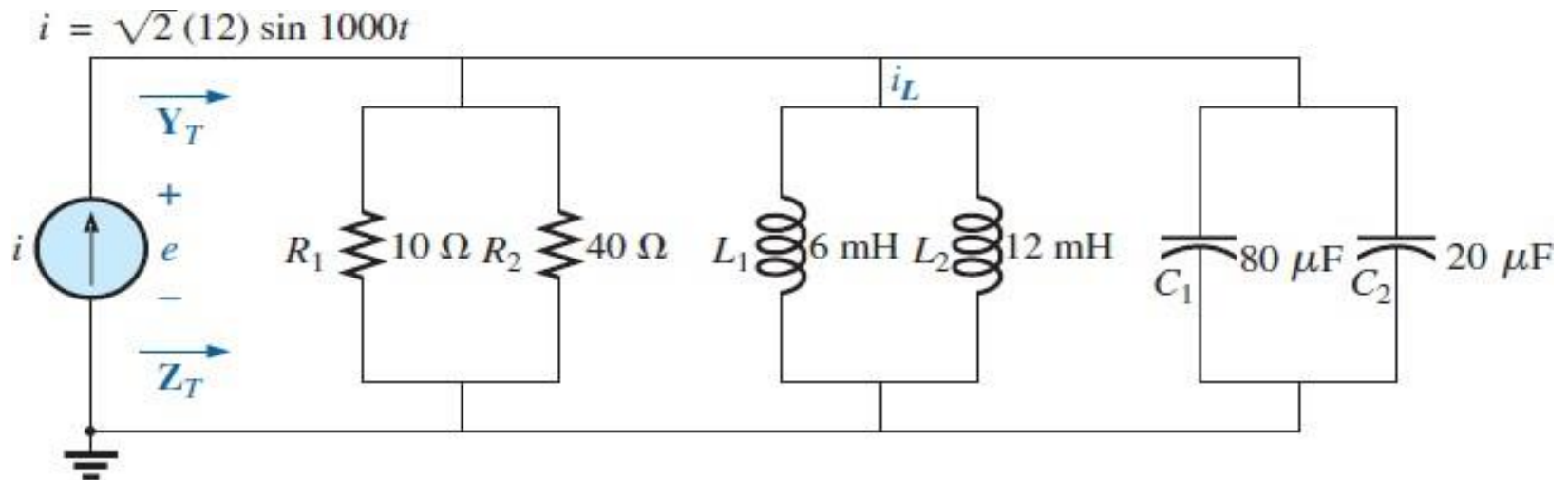EXAMPLE 15.19 For the network in Fig. :

- Determine $\mathbf{Y_T}$ and $\mathbf{Z_T}$.
- Sketch the admittance diagram.
- Find \mathbf{E} and $\mathbf{I_L}$.
- Compute the power factor of the network and the power delivered to the network.
- Determine the equivalent series circuit.
- Using the equivalent circuit developed in part (e), calculate \mathbf{E} , and compare it with the result of part (c).
- Determine the power delivered to the network, and compare it with the solution of part (d).
- Determine the equivalent parallel network from the equivalent series circuit, and calculate the total admittance $\mathbf{Y_T}$. Compare the result with the solution of part (a).



a. Combining common elements and finding the reactance of the inductor and capacitor, we obtain


$$R_T = 10 \, \Omega \parallel 40 \, \Omega = 8 \, \Omega$$

$$L_T = 6 \, \text{mH} \parallel 12 \, \text{mH} = 4 \, \text{mH}$$

$$C_T = 80 \, \mu\text{F} + 20 \, \mu\text{F} = 100 \, \mu\text{F}$$

$$X_L = \omega L = (1000 \, \text{rad/s})(4 \, \text{mH}) = 4 \, \Omega$$
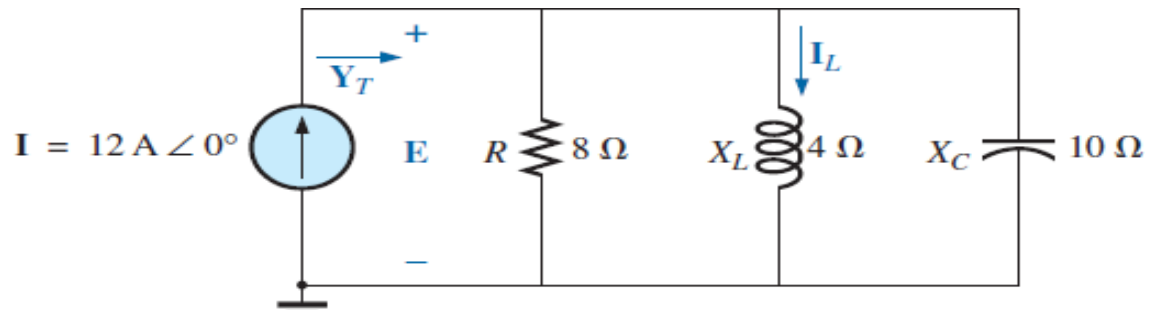
$$X_C = \frac{1}{\omega C} = \frac{1}{(1000 \, \text{rad/s})(100 \, \mu\text{F})} = 10 \, \Omega$$



$$\mathbf{Y}_T = \mathbf{Y}_R + \mathbf{Y}_L + \mathbf{Y}_C$$

$$= G \angle 0^\circ + B_L \angle -90^\circ + B_C \angle +90^\circ$$

$$= \frac{1}{8 \, \Omega} \angle 0^\circ + \frac{1}{4 \, \Omega} \angle -90^\circ + \frac{1}{10 \, \Omega} \angle +90^\circ$$


$$= 0.125 \, \text{S} \angle 0^\circ + 0.25 \, \text{S} \angle -90^\circ + 0.1 \, \text{S} \angle +90^\circ$$

$$= 0.125 \, \text{S} - j 0.25 \, \text{S} + j 0.1 \, \text{S}$$

$$= 0.125 \, \text{S} - j 0.15 \, \text{S} = \mathbf{0.195 \, \text{S} \angle -50.194^\circ}$$

$$\mathbf{Z}_T = \frac{1}{\mathbf{Y}_T} = \frac{1}{0.195 \, \text{S}} \angle -50.194^\circ = \mathbf{5.13 \, \Omega \angle 50.19^\circ}$$

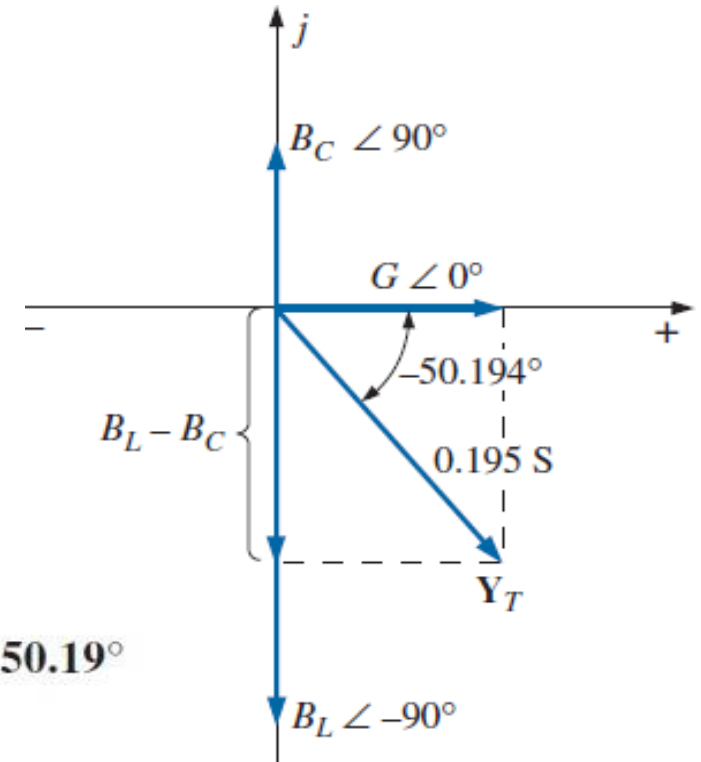b- Admittance diagram for the parallel R-L-C network



$$\text{c. } \mathbf{E} = \mathbf{I} \mathbf{Z}_T = \frac{\mathbf{I}}{\mathbf{Y}_T} = \frac{12 \text{ A } \angle 0^\circ}{0.195 \text{ S } \angle -50.194^\circ} = \mathbf{61.54 \text{ V } \angle 50.19^\circ}$$

$$\mathbf{I}_L = \frac{\mathbf{V}_L}{\mathbf{Z}_L} = \frac{\mathbf{E}}{\mathbf{Z}_L} = \frac{61.538 \text{ V } \angle 50.194^\circ}{4 \Omega \angle 90^\circ} = \mathbf{15.39 \text{ A } \angle -39.81^\circ}$$

$$\text{d. } F_p = \cos \theta = \frac{G}{Y_T} = \frac{0.125 \text{ S}}{0.195 \text{ S}} = \mathbf{0.641 \text{ lagging (E leads I)}}$$

$$P = EI \cos \theta = (61.538 \text{ V})(12 \text{ A}) \cos 50.194^\circ \\ = \mathbf{472.75 \text{ W}}$$


e.
$$\mathbf{Z}_T = \frac{1}{\mathbf{Y}_T} = \frac{1}{0.195 \text{ S } \angle -50.194^\circ} = 5.128 \Omega \angle +50.194^\circ$$

$$= 3.28 \Omega + j 3.94 \Omega$$

$$= R + j X_L$$

$$X_L = 3.94 \Omega = \omega L$$
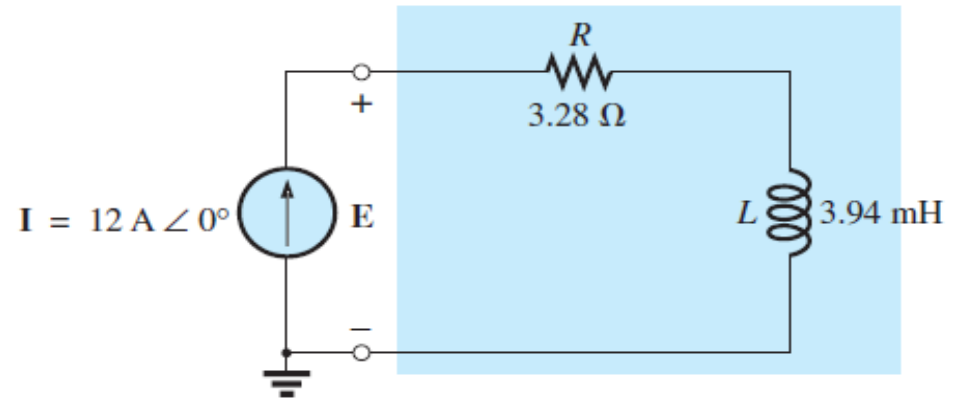
$$L = \frac{3.94 \Omega}{\omega} = \frac{3.94 \Omega}{1000 \text{ rad/s}} = \mathbf{3.94 \text{ mH}}$$



f.
$$\mathbf{E} = \mathbf{I}\mathbf{Z}_T = (12 \text{ A } \angle 0^\circ)(5.128 \Omega \angle 50.194^\circ)$$


$$= \mathbf{61.54 \text{ V } \angle 50.194^\circ} \text{ (as above)}$$

g.
$$P = I^2 R = (12 \text{ A})^2 (3.28 \Omega) = \mathbf{472.32 \text{ W}} \quad \text{(as above)}$$

h.
$$R_p = \frac{R_s^2 + X_s^2}{R_s} = \frac{(3.28 \Omega)^2 + (3.94 \Omega)^2}{3.28 \Omega} = \mathbf{8 \Omega}$$

$$X_p = \frac{R_s^2 + X_s^2}{X_s} = \frac{(3.28 \Omega)^2 + (3.94 \Omega)^2}{3.94 \Omega} = \mathbf{6.67 \Omega}$$

The parallel equivalent circuit

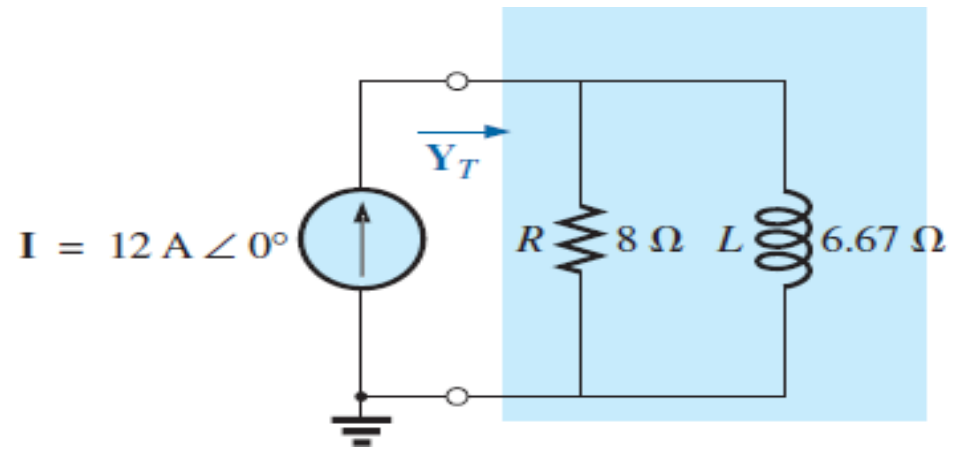

$$\begin{aligned} Y_T &= G \angle 0^\circ + B_L \angle -90^\circ = \frac{1}{8 \Omega} \angle 0^\circ + \frac{1}{6.675 \Omega} \angle -90^\circ \\ &= 0.125 \text{ S} \angle 0^\circ + 0.15 \text{ S} \angle -90^\circ \\ &= 0.125 \text{ S} - j 0.15 \text{ S} = \mathbf{0.195 \text{ S} \angle -50.194^\circ} \quad (\text{as above}) \end{aligned}$$

PROBLEMS

SECTION 15.2 Impedance and the Phasor Diagram: 1, 2

SECTION 15.3 Series Configuration: 4, 5, 6, 7, 9, 10

SECTION 15.4 Voltage Divider Rule: 15, 17, 20

SECTION 15.7 Admittance and Susceptance: 25, 26

SECTION 15.9 Current Divider Rule: 34

SECTION 15.12 Equivalent Circuits: 40, 42, 44

Thank you very much

