

*Lab 5*

*First Stage*

*Intelligent Medical Systems Department*



# *Logic Design*

**Lab 5: The Exclusive-NOR Gate**

**By**


*Asst. Lect. Ali Saleem Haleem*


## 1. The Exclusive-NOR Gate

The Exclusive-NOR gate is equivalent to X-OR gate followed by NOT gate. Standard symbols for an Exclusive-NOR (X-NOR) gate and Boolean expression for the output of a 2-input X-NOR gate can be written as:


$$Q = \bar{A}\bar{B} + AB = \overline{A \oplus B}$$

### 2-input X-NOR Gate

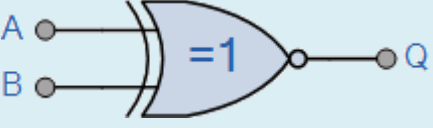Symbol	Truth Table		
 <p>2-input X-NOR Gate</p>	B	A	Q
	0	0	1
	0	1	0
	1	0	0
	1	1	1
Boolean Expression $Q = \overline{A \oplus B}$	Read if A AND B the SAME gives Q		

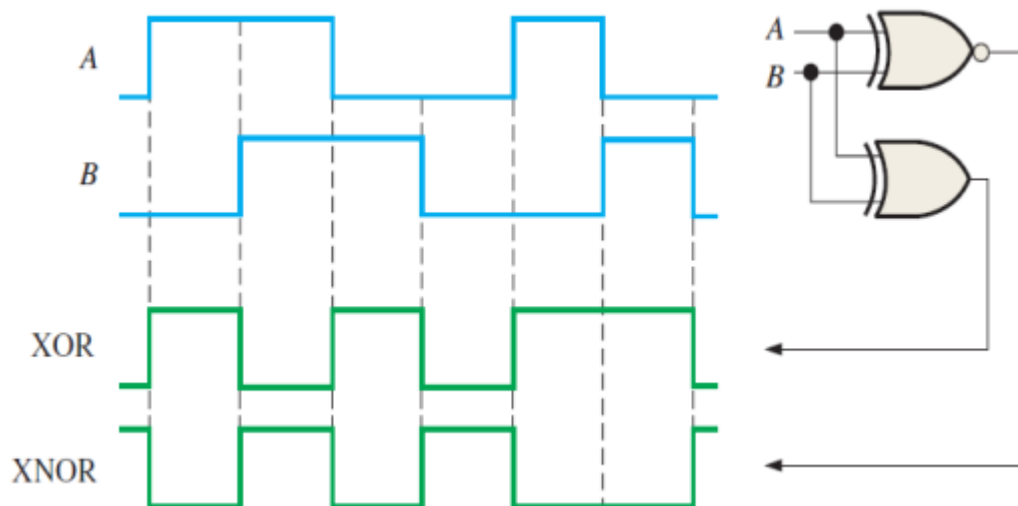

### 3-input XNOR Gate


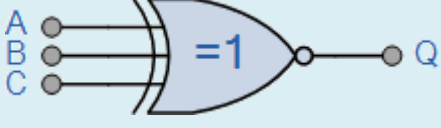
Symbol	Truth Table			
 <p>3-input XNOR Gate</p>	C	B	A	Q
	0	0	0	1
	0	0	1	0
	0	1	0	0
	0	1	1	1
	1	0	0	0
	1	0	1	1
	1	1	0	1

	1	1	1	0
Boolean Expression $Q = \overline{A \oplus B \oplus C}$	Read as “any <b>EVEN</b> number of Inputs” gives Q			

Giving the Boolean expression of:  $Q = \overline{ABC} + A\overline{B}\overline{C} + A\overline{B}C + \overline{A}BC$

## 2. Implementation

### 2-input XNOR Gate

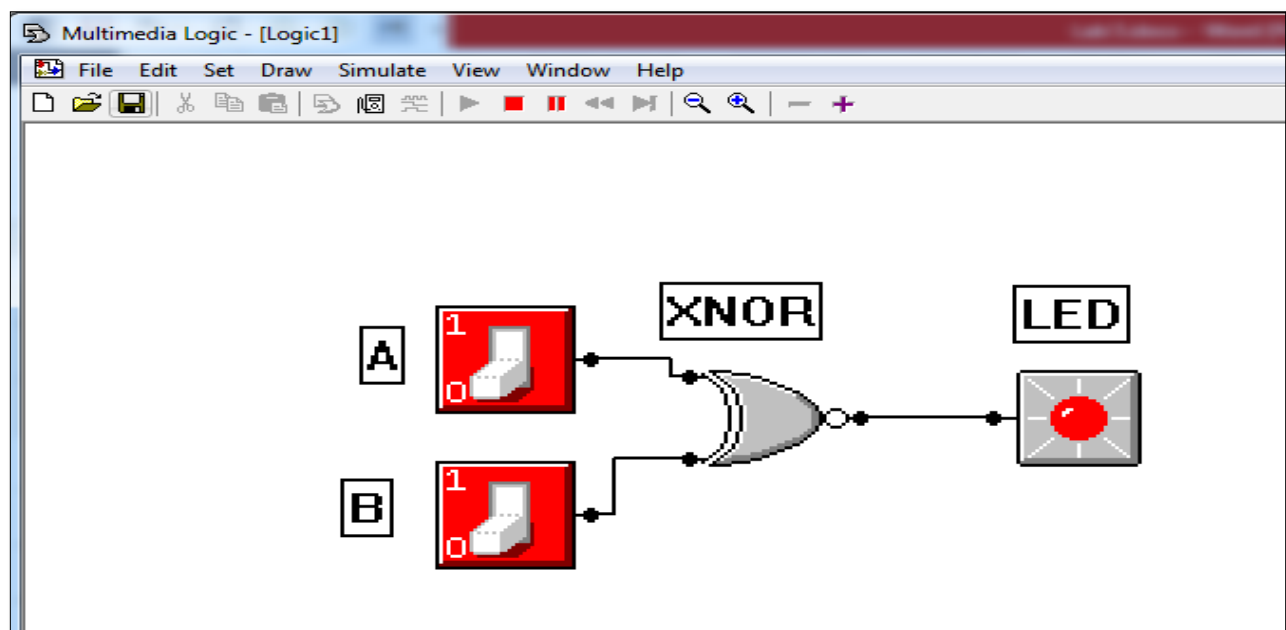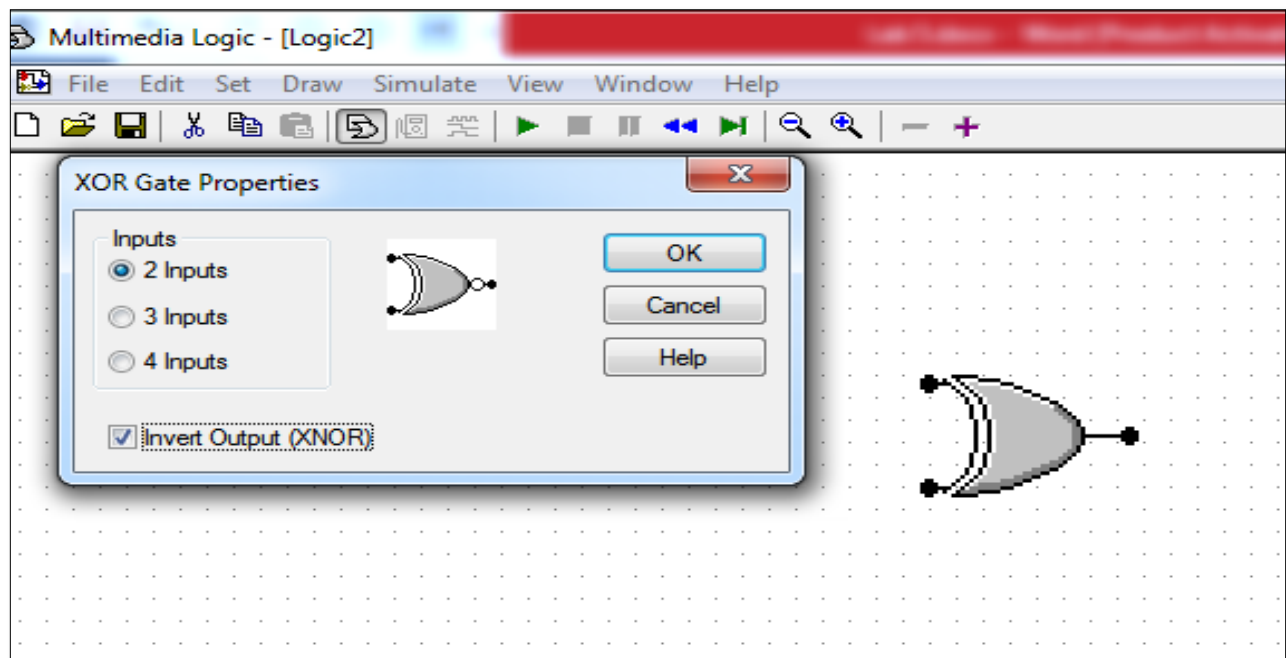


Truth Table

Switches		LED
0	0	Lit / 1
0	1	Dark / 0
1	0	Dark / 0
1	1	Lit / 1

**XNOR** is short for **Exclusive Nor**. This gate combines a [Xor Gate](#) with its output connected through an [Inverter Gate](#) in one device. The output of this gate is a "0" only if **one** of its inputs is a "1"

### Negative Triple of 3-input XNOR Gate

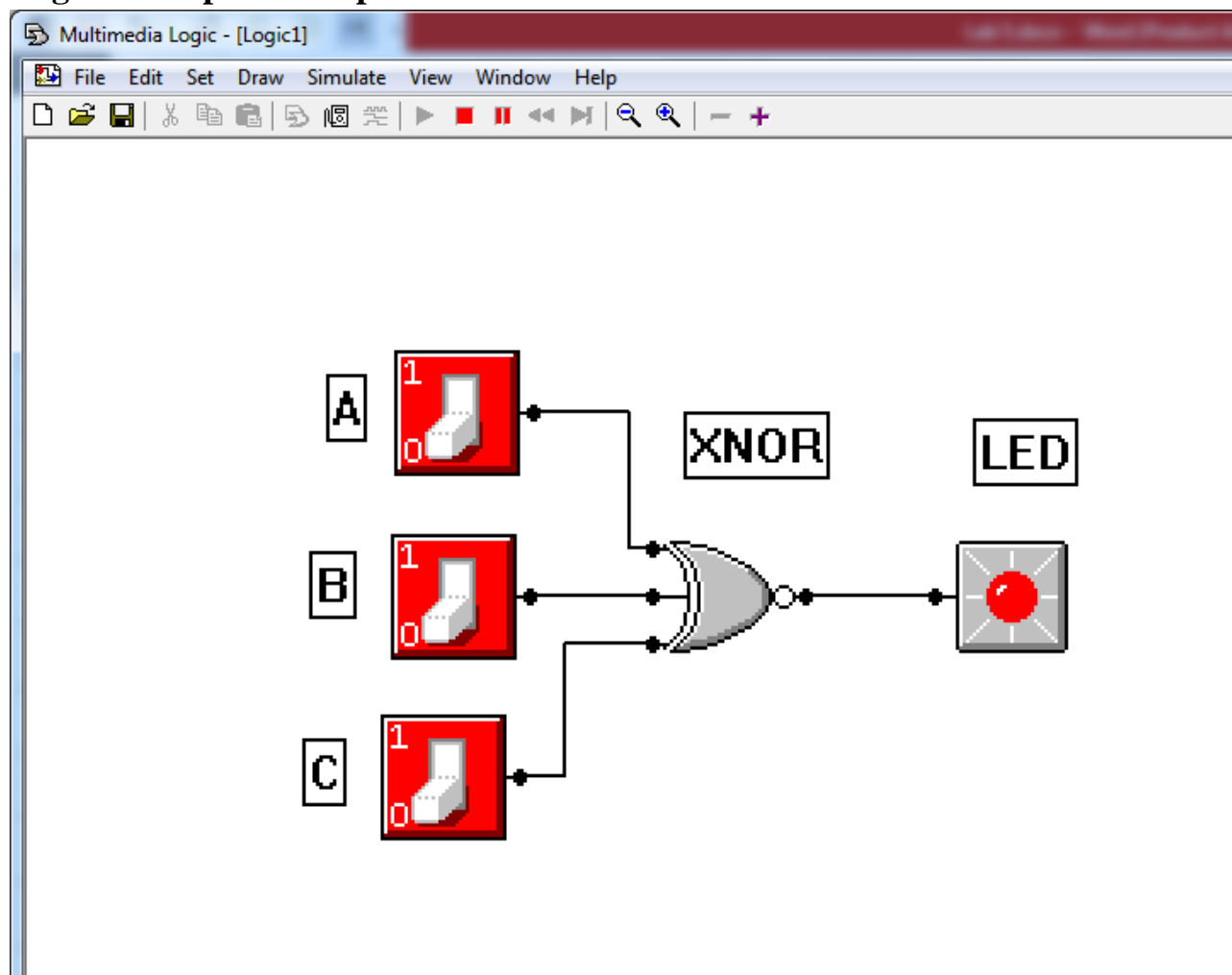

**Truth Table**

Switches			LED
0	0	0	Lit / 1
0	0	1	Dark / 0
0	1	0	Dark / 0
0	1	1	Lit / 1
1	0	0	Dark / 0
1	0	1	Lit / 1
1	1	0	Lit / 1
1	1	1	Dark / 0

**XNOR** is short for **Exclusive Nor**. This gate will output a "0" if only **one** or **all** of its inputs are a "1"