



Module Title: Fundamental of Electrical Engineering (DC)

Module Code:	UOMU024011
---------------------	-------------------

Chapter 2

Week (5, 6) Review Questions with answer

Solve problems on Delta star and star delta connection



2.6 Wye-Delta Transformations

Situations often arise in circuit analysis when the resistors are neither in parallel nor in series, For example , the circuit shown in figure (15-2):-

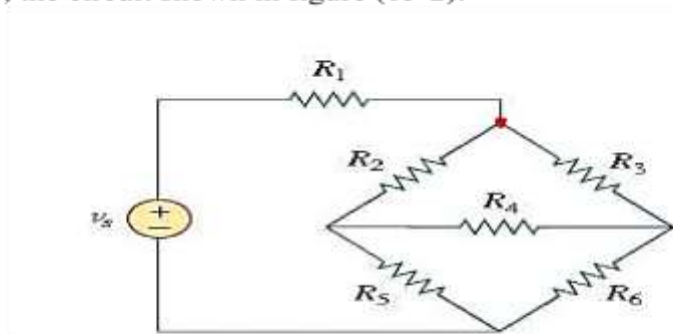


Figure 15-2: The bridge network

In this circuit R_1 , R_2 , R_3 , R_4 , R_5 , and R_6 are neither in series nor in parallel

❖ the wye (Y) or tee (T) or star network shown in Figure (16- 2)

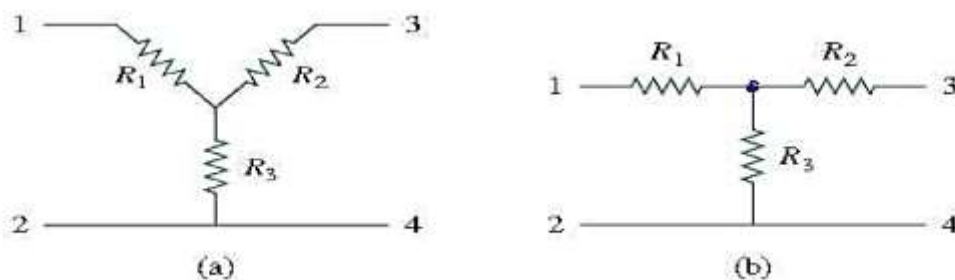


Figure 16-2 : (a) wye (Y), (b) tee (T)



2.6.1 Delta to Wye Conversion

In this case transfer the (Δ) to (Y) connection, let consider the the circuit shown in the figure (18-2) that is help us to understand the transfer process

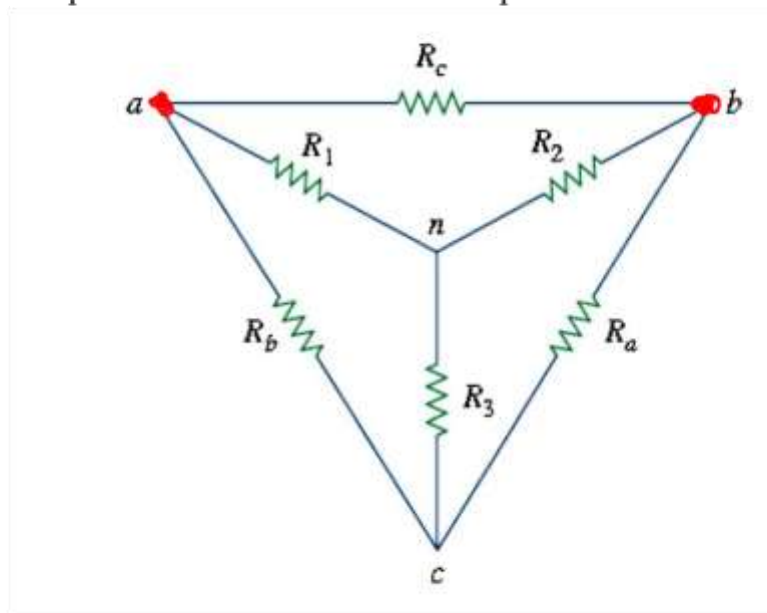


figure (18-2) : Delta to Wye Conversion



$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

2.6.2 Wye to Delta Conversion

In this case transfer the(Y) to (Δ) connection , let consider the same circuit shown in the figure (18-2) that is help us to understand laws of the transformation



$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$




If the all value of the resistances are balanced thus,

$$R_1=R_2=R_3=R_Y \quad R_A=R_B=R_C=R_{\Delta}$$

Under these conditions, conversion formulas become


$$R_Y = \frac{R_{\Delta}}{3} \quad \text{or} \quad R_{\Delta} = 3R_Y$$

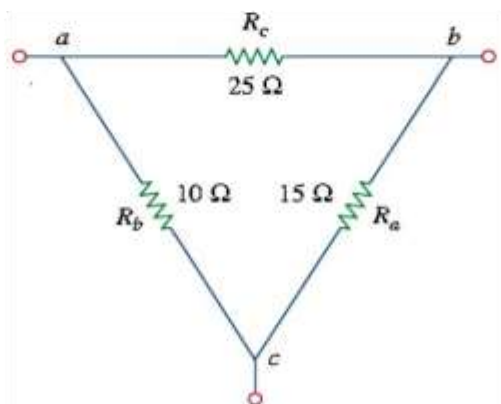Example : Convert the Δ network in Figure shown below to an equivalent Y network






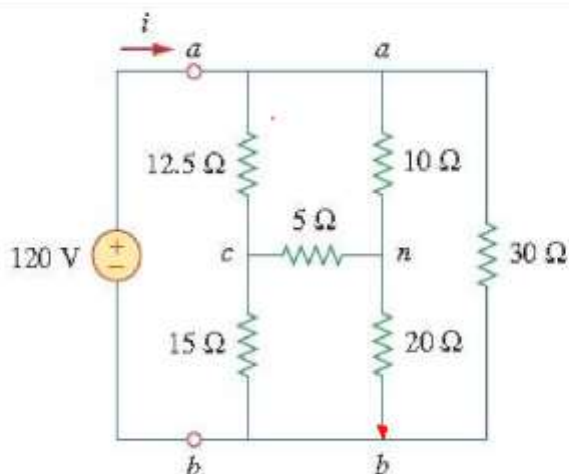Example: - Obtain the equivalent resistance R_{ab} for the circuit in Figure shown below and use it to find current i .





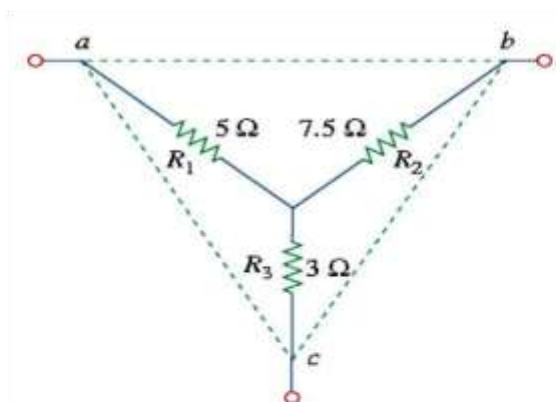Solution :- start to draw the Y- connection as shown below , and apply the (Δ to Y) laws



$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} = \frac{10 \times 25}{15 + 10 + 25} = \frac{250}{50} = 5 \Omega$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c} = \frac{25 \times 15}{50} = 7.5 \Omega$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} = \frac{15 \times 10}{50} = 3 \Omega$$

The equivalent Y network is shown in Figure that shown above

Solution :- In this circuit, there are two Y networks and three Δ networks. Transforming just one of these will simplify the circuit. If we convert the Y network comprising the 5Ω, 10Ω and 20Ω resistors, we may select

$$R_1 = 10 \Omega, \quad R_2 = 20 \Omega, \quad R_3 = 5 \Omega$$



Star delta connection: Formula with example




$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{10 \times 20 + 20 \times 5 + 5 \times 10}{10}$$

$$= \frac{350}{10} = 35 \Omega$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{350}{20} = 17.5 \Omega$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{350}{5} = 70 \Omega$$

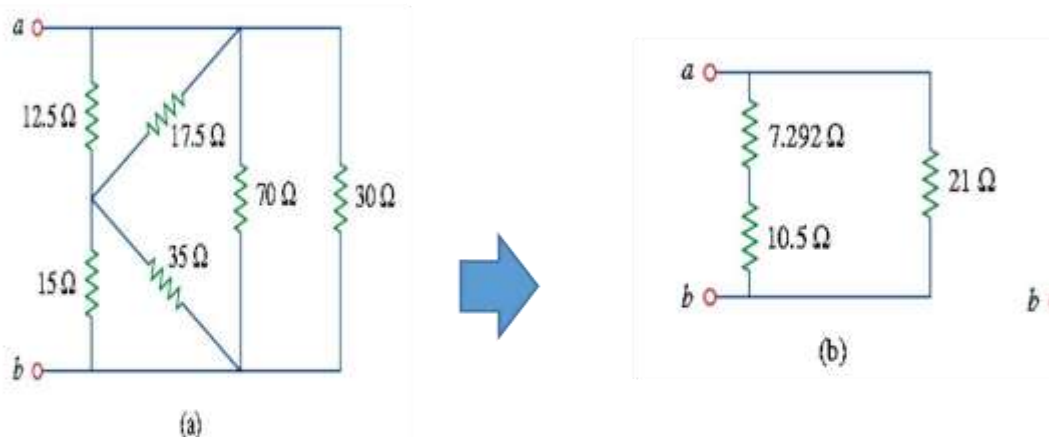Thus the result of transfer (Y to Δ) will be as shown in figure (a) and simplify it to be as shown in figure (b)



The process of the simplify is

$$70 \parallel 30 = \frac{70 \times 30}{70 + 30} = 21 \Omega$$

$$12.5 \parallel 17.5 = \frac{12.5 \times 17.5}{12.5 + 17.5} = 7.292 \Omega$$

$$15 \parallel 35 = \frac{15 \times 35}{15 + 35} = 10.5 \Omega$$

Hence, we find

$$R_{ab} = (7.292 + 10.5) \parallel 21 = \frac{17.792 \times 21}{17.792 + 21} = 9.632 \Omega$$


Then

$$i = \frac{v_s}{R_{ab}} = \frac{120}{9.632} = 12.458 \text{ A}$$




Home work:

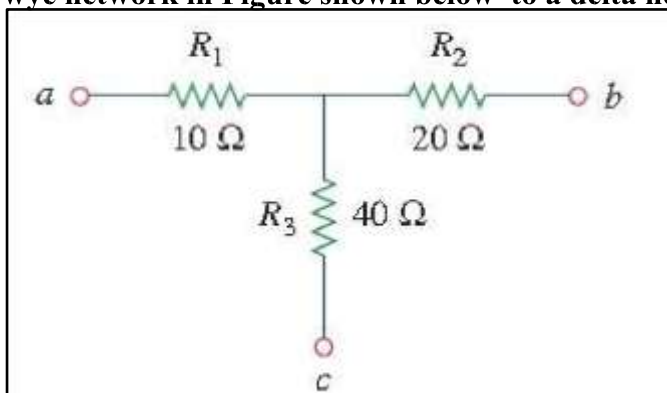❖ Transform the wye network in Figure shown below to a delta network



Answer: $R_a = 140 \Omega$, $R_b = 70 \Omega$, $R_c = 35 \Omega$

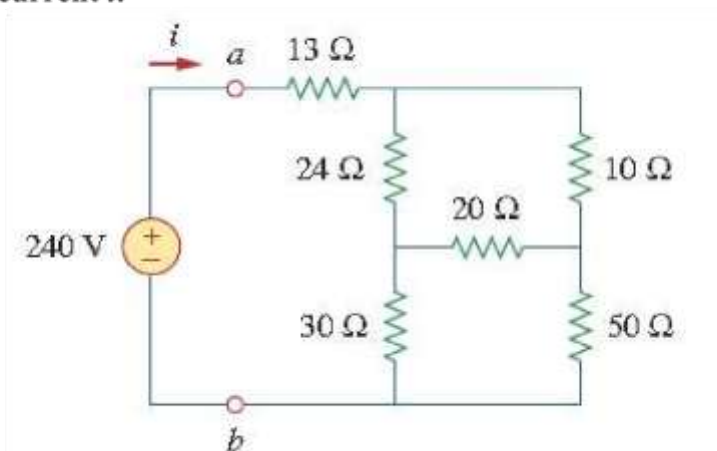❖ Obtain the equivalent resistance R_{ab} for the circuit in Figure shown below and use it to find current i .



Answer : 40Ω , 6 A .