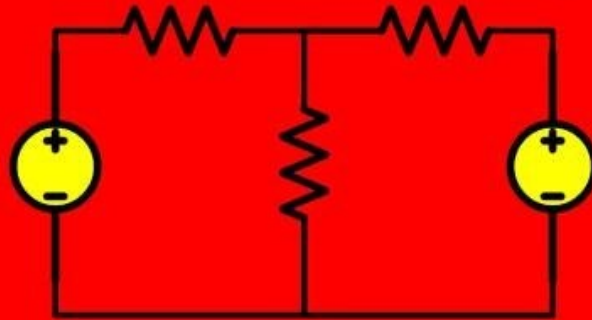




Mesh Current Analysis



Formula and Example



The mesh current method is a network analysis technique where mesh (or loop) current directions are assigned arbitrarily, and then Kirchhoff's voltage law (KVL) and Ohm's law are applied systematically to solve for the unknown currents and voltages.

MAXWELL'S LOOP CURRENT METHOD (MESH ANALYSIS)

Statement:-


This method determines branch currents and voltages across the elements of a network.

Method:-

1. Here, instead of taking branch currents (as in Kickoff's law) loop currents are taken which are assumed to flow in the clockwise direction.
2. Branch currents can be found in terms of loop currents
3. Sign conventions for the IR drops and battery emfs are the same as for Kickoff's law.
4. This method is easy if all the sources are given as voltage sluices. If theie is a currents source present in a network then convert it into equivalent voltage sluice.

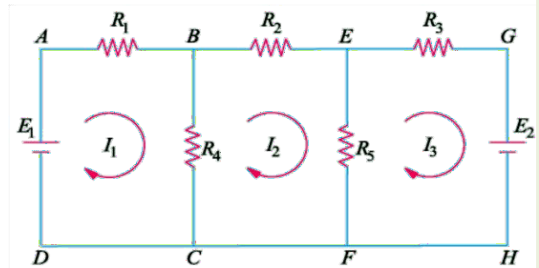Example:-

Consider a network as shown in Fig. below. It contains three meshes. Let I_1 , I_2 and I_3 are the mesh currents of three meshes directed in clockwise



$$\begin{aligned} E_1 - I_1 R_1 - R_4 (I_1 - I_2) &= 0 \quad \text{or} \quad I_1 (R_1 + R_4) - I_2 R_4 - E_1 = 0 && \dots \text{loop 1} \\ \text{Similarly,} \quad -I_2 R_2 - R_5 (I_2 - I_3) - R_4 (I_2 - I_1) &= 0 \\ \text{or} \quad I_2 R_4 - I_2 (R_2 + R_4 + R_5) + I_3 R_5 &= 0 && \dots \text{loop 2} \\ \text{Also} \quad -I_3 R_3 - E_2 - R_5 (I_3 - I_2) &= 0 \quad \text{or} \quad I_2 R_5 - I_3 (R_3 + R_5) - E_2 = 0 && \dots \text{loop 3} \end{aligned}$$

Note: When we consider mesh-1, the current I_1 is greater than I_2 . So, current through R_4 is $I_1 - I_2$. Similarly, when we consider mesh-2, the current I_2 is greater than I_1 and I_3 . So, current through R_4 is $I_2 - I_1$, and the current through R_5 is $I_2 - I_3$.

Mesh Analysis Using Matrix Form

Example

Write the impedance matrix of the network shown in Fig. 2.53 and find the value of current I_3 . (Network Analysis A.M.I.E. Sec. B.W. 1980)

Solution. Different items of the mesh-resistance matrix $[R_m]$ are as under :

$$R_{11} = 1 + 3 + 2 = 6 \, \Omega; \quad R_{22} = 2 + 1 + 4 = 7 \, \Omega; \quad R_{33} = 3 + 2 + 1 = 6 \, \Omega;$$

$$R_{12} = R_{21} = -2 \, \Omega; \quad R_{23} = R_{32} = -1 \, \Omega; \quad R_{13} = R_{31} = -3 \, \Omega;$$

$$E_1 = +5 \, \text{V}; \quad E_2 = 0; \quad E_3 = 0.$$

The mesh equations in the matrix form are

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} E_1 \\ E_2 \\ E_3 \end{bmatrix} \quad \text{or} \quad \begin{bmatrix} 6 & -2 & -3 \\ -2 & 7 & -1 \\ -3 & -1 & 6 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 6 & -2 & -3 \\ -2 & 7 & -1 \\ -3 & -1 & 6 \end{vmatrix} = 6(42 - 1) + 2(-12 - 3) - 3(2 + 21) = 147$$

$$\Delta_3 = \begin{vmatrix} 6 & -2 & 5 \\ -2 & 7 & 0 \\ -3 & -1 & 0 \end{vmatrix} = 6 + 2(5) - 3(-35) = 121$$

$$I_3 = \Delta_3 / \Delta = \frac{121}{147} = 0.823 \, \text{A}$$

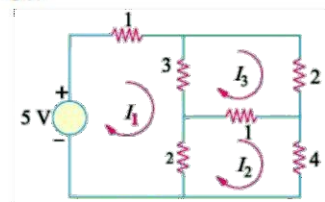


Fig. 2.53

Example

Determine the current supplied by each battery in the circuit shown in Fig. 2.54.

(Electrical Engg. Aligarh Univ.)

Solution. Since there are three meshes, let the three loop currents be shown in Fig. 2.51.

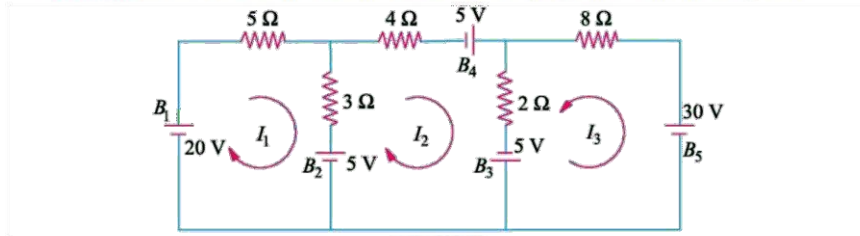


Fig. 2.54

For loop 1 we get

$$20 - 5I_1 - 3(I_1 - I_2) - 5 = 0 \quad \text{or} \quad 8I_1 - 3I_2 = 15 \quad \dots(i)$$

For loop 2 we have

$$-4I_2 + 5 - 2(I_2 - I_3) + 5 + 5 - 3(I_2 - I_1) = 0 \quad \text{or} \quad 3I_1 - 9I_2 + 2I_3 = -15 \quad \dots(ii)$$

Similarly, for loop 3, we get

$$-8I_3 - 30 - 5 - 2(I_3 - I_2) = 0 \quad \text{or} \quad 2I_2 - 10I_3 = 35 \quad \dots(iii)$$

$$\text{Eliminating } I_1 \text{ from (i) and (ii), we get} \quad 63I_2 - 16I_3 = 165 \quad \dots(iv)$$

$$\text{Similarly, for } I_2 \text{ from (iii) and (iv), we have} \quad I_2 = 542/299 \text{ A}$$

$$\text{From (iv),} \quad I_3 = -1875/598 \text{ A}$$

$$\text{Substituting the value of } I_2 \text{ in (i), we get} \quad I_1 = 765/299 \text{ A}$$

Example

Discharge current of $B_1 = 765/299 \text{ A}$

Charging current of $B_2 = I_1 - I_2 = 220/299 \text{ A}$

Discharge current of $B_3 = I_2 + I_3 = 2965/598 \text{ A}$

Discharge current of $B_4 = I_2 = 545/299 \text{ A}$; Discharge current of $B_5 = 1875/598 \text{ A}$

Solution by Using Mesh Resistance Matrix.

The different items of the mesh-resistance matrix $[R_m]$ are as under :

$$R_{11} = 5 + 3 = 8 \Omega; R_{22} = 4 + 2 + 3 = 9 \Omega; R_{33} = 8 + 2 = 10 \Omega$$

$$R_{12} = R_{21} = -3 \Omega; R_{13} = R_{31} = 0; R_{23} = R_{32} = -2 \Omega$$

$$E_1 = \text{algebraic sum of the voltages around mesh (i)} = 20 - 5 = 15 \text{ V}$$

$$E_2 = 5 + 5 + 5 = 15 \text{ V}; E_3 = -30 - 5 = -35 \text{ V}$$

Example

Hence, the mesh equations in the matrix form are

$$\begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} E_1 \\ E_2 \\ E_3 \end{bmatrix} \text{ or } \begin{bmatrix} 8 & -3 & 0 \\ -3 & 9 & -2 \\ 0 & -2 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 15 \\ 15 \\ -35 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 8 & -3 & 0 \\ -3 & 9 & -2 \\ 0 & -2 & 10 \end{vmatrix} = 8(90 - 4) + 3(-30) = 598$$

$$\Delta_1 = \begin{vmatrix} 15 & -3 & 0 \\ 15 & 9 & -2 \\ -35 & -2 & 10 \end{vmatrix} = 15(90 - 4) - 15(-30) - 35(6) = 1530$$

$$\Delta_2 = \begin{vmatrix} 8 & 15 & 0 \\ -3 & 15 & -2 \\ 0 & -35 & 10 \end{vmatrix} = 8(150 - 70) + 3(150 + 0) = 1090$$

$$\Delta_3 = \begin{vmatrix} 8 & -3 & 15 \\ -3 & 9 & 15 \\ 0 & -2 & -35 \end{vmatrix} = 8(-315 + 30) + 3(105 + 30) = -1875$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{1530}{598} = \frac{765}{299} \text{ A}; I_2 = \frac{\Delta_2}{\Delta} = \frac{1090}{598} = \frac{545}{299} \text{ A}; I_3 = \frac{\Delta_3}{\Delta} = \frac{-1875}{598} \text{ A}$$

Home Work

1. Find the ammeter current in Fig. 2.57 by using loop analysis. [1/7 A]
2. Using mesh analysis, determine the voltage across the 10 kΩ resistor at terminals a-b of the circuit shown in Fig. 2.58. [2.65 V]
3. Apply loop current method to find loop currents I_1 , I_2 and I_3 in the circuit of Fig. 2.59. [$I_1 = 3.75 \text{ A}$, $I_2 = 0$, $I_3 = 1.25 \text{ A}$]

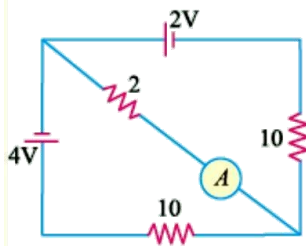


Fig. 2.57

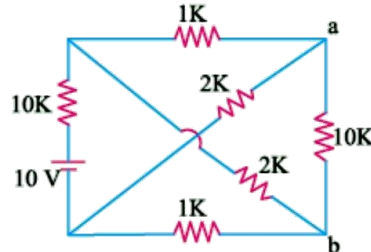


Fig. 2.58

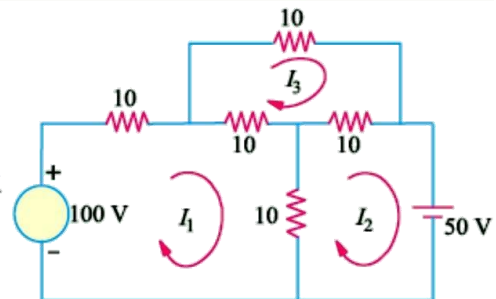


Fig. 2.59

MESH ANALYSIS WITH CURRENT SOURCES


Case 1

- Current source exist only in one mesh
- One mesh variable is reduced

Case 2

- Current source exists between two meshes, a **super-mesh** is obtained.

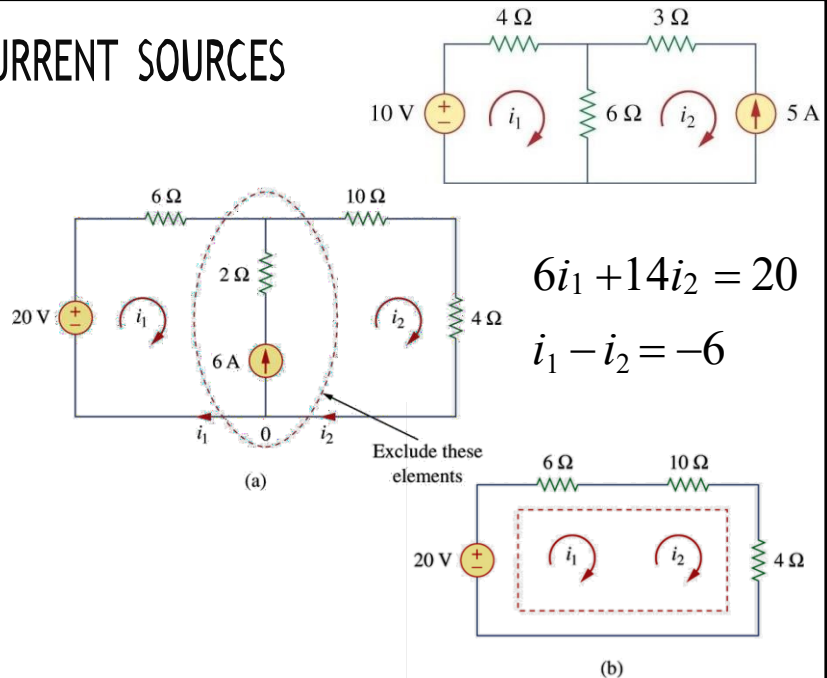a **supermesh** results when two meshes have a (dependent , independent) current source in common.



Example


For the circuit in Fig. 3.24, find i_1 to i_4 using mesh analysis.

$$2i_1 + 4i_3 + 8(i_3 - i_4) + 6i_2 = 0$$

$$i_1 - i_2 = -5$$


$$i_2 - i_3 = 3I_o = -3i_4$$

$$2i_4 + 8(i_4 - i_3) = -10$$

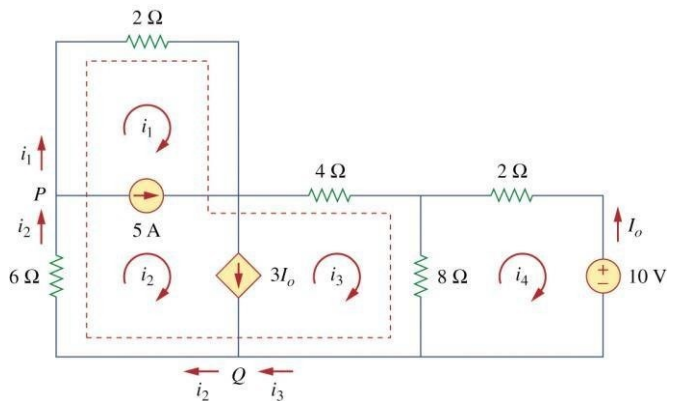

Home Work

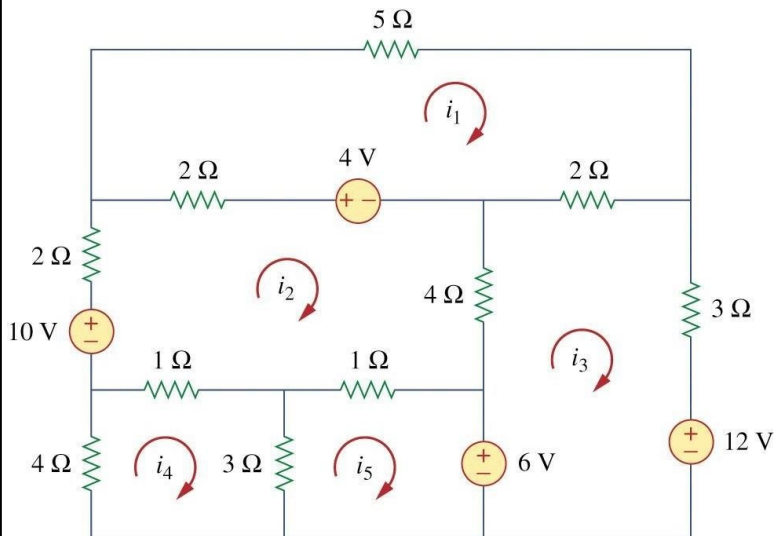
Write the mesh current equations in Figure below.



$$\begin{bmatrix} 9 & -2 & -2 & 0 & 0 \\ -2 & 10 & -4 & -1 & -1 \\ -2 & -4 & 9 & 0 & 0 \\ 0 & -1 & 0 & 8 & -3 \\ 0 & -1 & 0 & -3 & 4 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix} = \begin{bmatrix} 4 \\ 6 \\ -6 \\ 0 \\ -6 \end{bmatrix}$$

Nodal Analysis

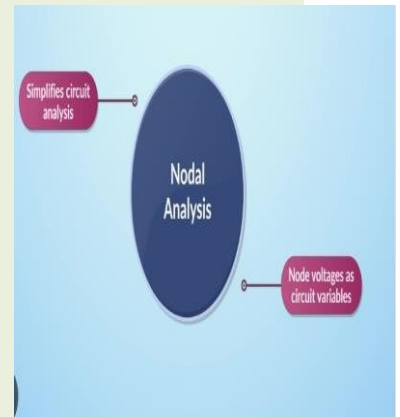Nodal analysis is used for solving any electrical network, and it is defined as the mathematical method for calculating the voltage distribution between the circuit nodes.



This method is also known as the node-voltage method since the node voltages are with respect to the ground. The following are the three laws that define the equation related to the voltage that is measured between each circuit node:

Ohm's law

Kirchhoff's voltage law

Kirchhoff's current law

NODAL ANALYSIS

Steps to **Determine Node Voltages**:

1. Select a node as the **reference node**. Assign voltage $v_1, v_2, \dots, v_{n-1}$ to the remaining $n-1$ nodes. The voltages are referenced with respect to the reference node.
2. Apply **KCL to each of the $n-1$ nonreference nodes**. Use Ohm's law to express the branch currents in terms of node voltages.
3. Solve the resulting simultaneous equations to obtain the unknown node voltages.

Common symbols for indicating a reference node,

- (a) common ground,
- (b) ground,
- (c) chassis.

NODAL ANALYSIS

Typical circuit for nodal analysis

$$I_1 = I_2 + i_1 +$$



I

$$i = \frac{v_{\text{higher}} - v_{\text{lower}}}{R}$$

$$i_1 = \frac{v_1 - 0}{R_1} \quad \text{or} \quad i_1 = G_1 v_1$$

$$i_2 = \frac{v_1 - v_2}{R_2} \quad \text{or} \quad i_2 =$$

$$i_3 = \frac{v_2}{R_3}$$

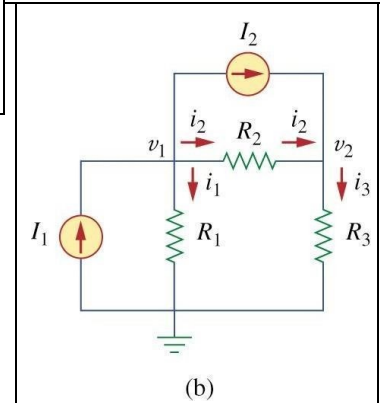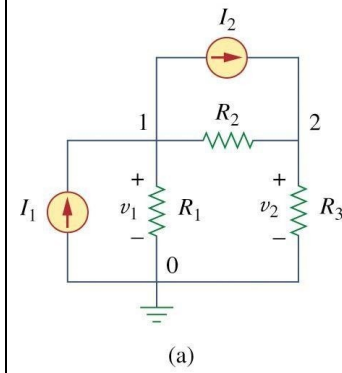

NODAL ANALYSIS


$$\Rightarrow I_1 = I_2 + \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2}$$

$$I_2 + \frac{v_1 - v_2}{R_2} = \frac{v_2}{R_3}$$

$$\Rightarrow I_1 - I_2 = G_1 v_1 + G_2 (v_1 - v_2)$$

$$I_2 = -G_2 (v_1 - v_2) + G_3 v_2$$
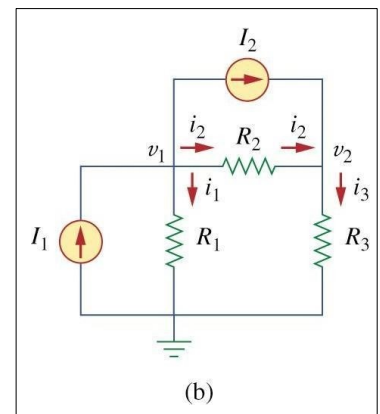
$$\Rightarrow \begin{bmatrix} G_1 + G_2 & -G_2 \\ -G_2 & G_2 + G_3 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} I_1 - I_2 \\ I_2 \end{bmatrix}$$



Example Calculus the node voltage in the circuit shown in Fig. 3.3(a)

At node 1 $i_1 = i_2 + i_3$


$$\Rightarrow 5 = \frac{v_1 - v_2}{4} + \frac{v_1 - 0}{2}$$

At node 2 $i_2 + i_4 = i_1 + i_5$

$$\Rightarrow 5 = \frac{v_2 - v_1}{4} + \frac{v_2 - 0}{6}$$

In matrix form:
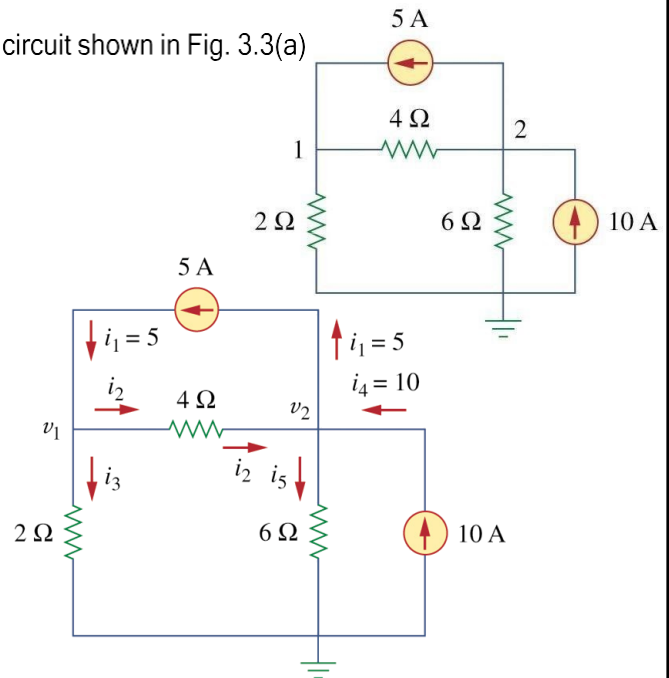
$$\begin{bmatrix} \frac{1}{2} + \frac{1}{4} & -\frac{1}{4} \\ -\frac{1}{4} & \frac{1}{6} + \frac{1}{4} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 5 \end{bmatrix}$$



Example Determine the voltage at the nodes in Fig. 3.5(a)

At node 1. $3 = i_1 + i_x$

$$\Rightarrow 3 = \frac{v_1 - v_2}{2} + i_x$$

At node 2 $i_x = i_2 + i_3$



$$\Rightarrow \frac{v_1 - v_2}{2} = \frac{v_2 - v_3}{8} + \frac{v_2 - 0}{4}$$

At node 3 $i_1 + i_2 = 2i_x$

$$\Rightarrow \frac{v_1 - v_3}{4} + \frac{v_2 - v_3}{8} = \frac{2(v_1 - v_2)}{2}$$

In matrix form:
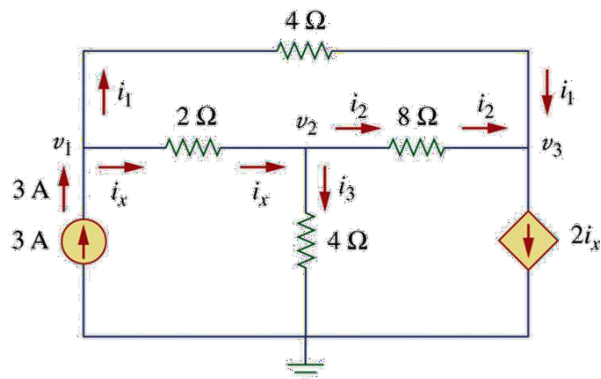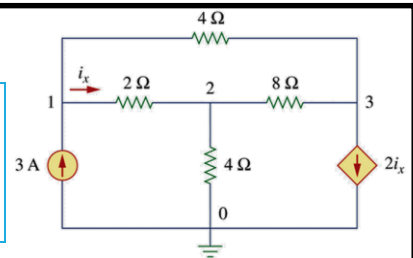
$$\begin{bmatrix} \frac{1}{2} & -\frac{1}{2} & 0 \\ -\frac{1}{2} & \frac{1}{4} + \frac{1}{8} & -\frac{1}{8} \\ \frac{1}{4} & -\frac{1}{8} & \frac{1}{4} + \frac{1}{8} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 3 \\ 0 \\ 0 \end{bmatrix}$$




NODAL ANALYSIS WITH VOLTAGE SOURCES

Case 1: The voltage source is connected **between a nonreference node and the reference node**: The nonreference node voltage is equal to the magnitude of voltage source and the number of unknown nonreference nodes is reduced by one.

Case 2: The voltage source is connected **between two nonreferenced nodes**: a generalized node (**supernode**) is formed.

Fig. 3.7 A circuit with a supernode.

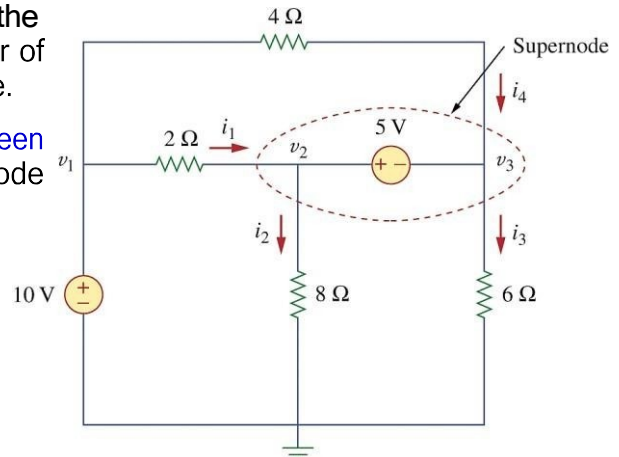

Example For the circuit shown, find the node voltages.


$$2 - 7 - i_{2\Omega} - i_{4\Omega} = 0$$

$$2 - 7 - \frac{v_1}{2} - \frac{v_2}{4} = 0$$

$$\therefore 2v_1 + v_2 = -20 \dots (1)$$

and

$$v_1 - v_2 = -2 \dots (2)$$

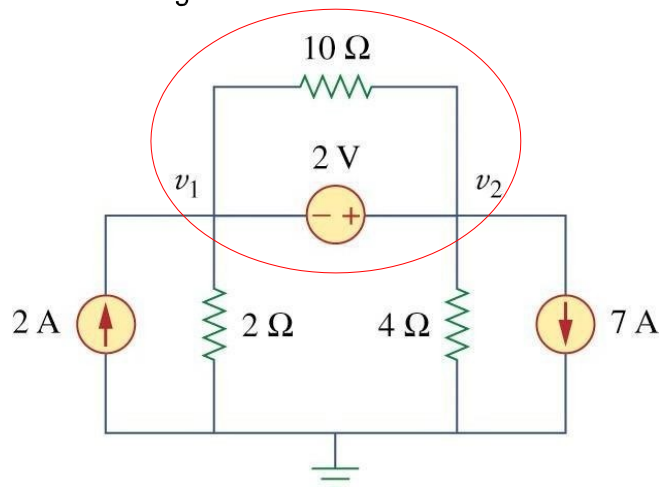

Example Find the node voltages in the circuit of Fig. 3.12.

At supernode 1-2,


$$\frac{v_1}{2} + \frac{v_1 - v_4}{3} + \frac{v_2 - v_3}{6} = 10$$

$$v_1 - v_2 = 20$$

At supernode 3-4,


$$\frac{v_3}{4} + \frac{v_4}{1} + \frac{v_3 - v_2}{6} + \frac{v_4 - v_1}{3} = 0$$

$$v_3 - v_4 = 3v_x = 3(v_1 - v_4)$$

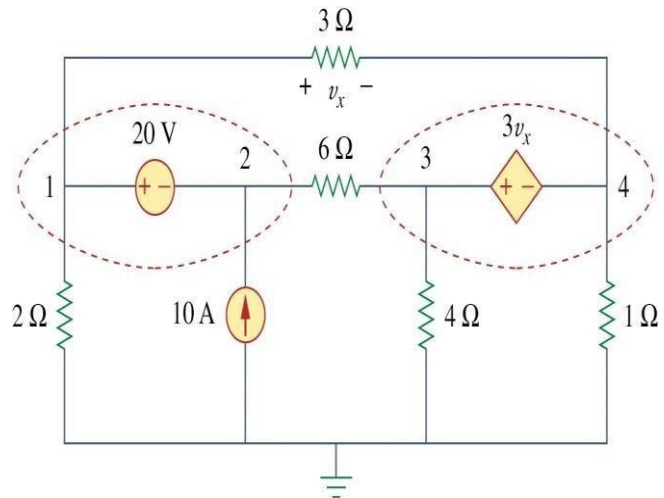

Home Work

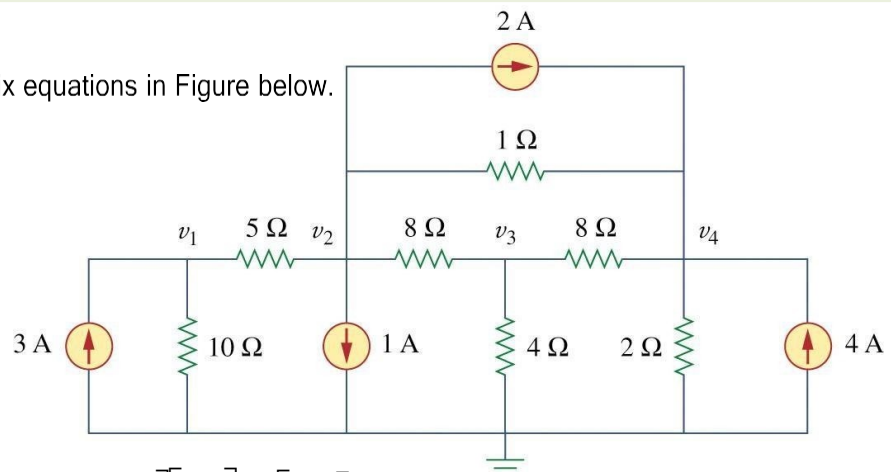Write the node voltage matrix equations in Figure below.



$$\begin{bmatrix} 0.3 & -0.2 & 0 & 0 \\ -0.2 & 1.325 & -0.125 & -1 \\ 0 & -0.125 & 0.5 & -0.125 \\ 0 & -1 & -0.125 & 1.625 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} = \begin{bmatrix} 3 \\ -3 \\ 0 \\ 6 \end{bmatrix}$$


SOURCE CONVERSION

A given **voltage source** with a **series resistance** can be converted into (or replaced by) and equivalent **current source** with a **parallel resistance**.

This current is $I = V/R$





Conversely, a **current source** with a **parallel resistance** can be converted into a **voltage source** with a **series resistance**.

The voltage source of voltage $V = IR$

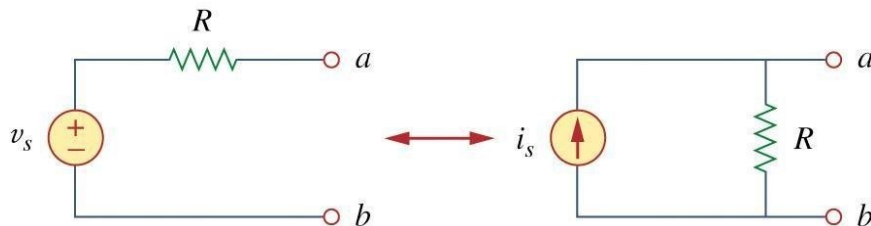

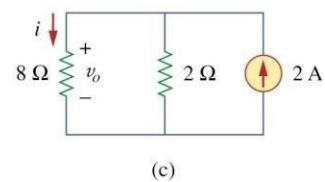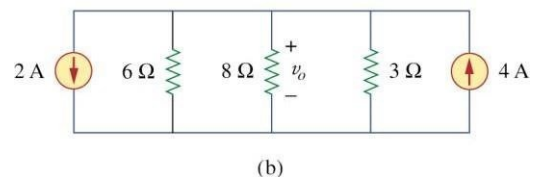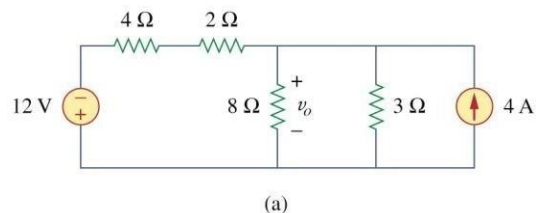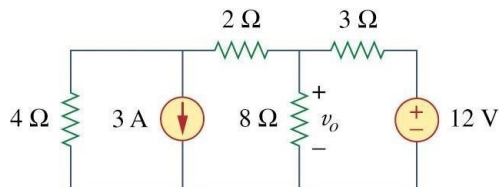Example

Use source transformation to find v_o in the circuit in Figure



we use current division in Figure (c) to get

$$i = \frac{2}{2+8}(2) = 0.4\text{A}$$

and

$$v_o = 8i = 8(0.4) = 3.2\text{V}$$

ExampleFind v_x in Figure below using source transformation

Applying KVL around the loop in Figure (b) gives

$$-3 + 5i + v_x + 18 = 0 \quad \text{or} \quad 15 + 5i + v_x = 0$$

Applying KVL to the loop containing only the 3V voltage source, the 1Ω resistor, and v_x yields

$$-3 + 1i + v_x = 0 \Rightarrow v_x = 3 - i$$

Substituting this into first Equation, we obtain

$$15 + 5i + 3 - i = 0 \quad \text{or} \quad 4i = -18 \Rightarrow i = -4.5\text{A}$$

Alternatively

$$-v_x + 4i + v_x + 18 = 0 \Rightarrow i = -4.5\text{A}$$

thus

$$v_x = 3 - i = 7.5\text{V}$$

