



**COLLEGE OF ENGINEERING AND TECHNOLOGIES**  
**ALMUSTAQBAL UNIVERSITY**

**Electronics Circuits**  
**CTE 204**

**Lecture 2**

**- FET Biasing -**  
**(2024 - 2025)**


Dr. Zaidoon AL-Shammari

Lecturer / Researcher

[zaidoon.waleed@mustaqbal-college.edu.iq](mailto:zaidoon.waleed@mustaqbal-college.edu.iq)

- The p-channel JFET is constructed in exactly the same manner as the n-channel device, but with a reversal of the p and n type materials as shown in Figure below.


# P - Channel Devices

 


*p-Channel JFET.*

- The defined current directions are reversed, as are the actual polarities for the voltages  $V_{GS}$  and  $V_{DS}$ .
- For the p-channel device, the channel will be constricted by increasing positive voltages from gate to source and the double-subscript notation for  $V_{DS}$  will result in negative voltages for  $V_{DS}$  on the characteristics of Figure below.

# P - Channel Devices

 

 *p-Channel JFET characteristics with  $I_{DSS} = 6$  mA and  $V_P = +6$  V.*



*JFET symbols: (a) n-channel; (b) p-channel.*


# Transfer Characteristics

The relationship between  $I_D$  and  $V_{GS}$  is defined by *Shockley's equation*:

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

control variable

constants

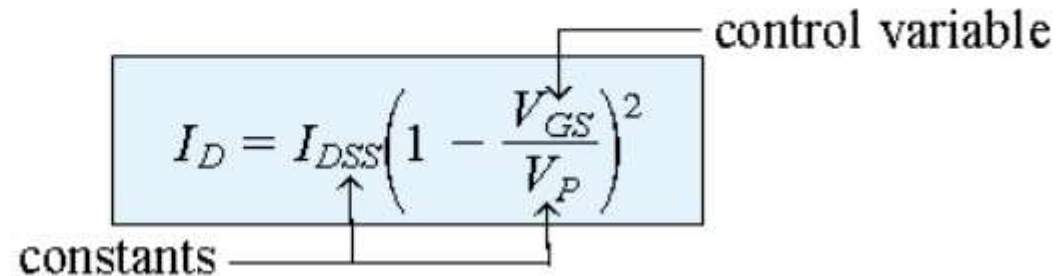

- The squared term of the equation will result in a nonlinear relationship between  $I_D$  and  $V_{GS}$ , producing a curve that grows exponentially with decreasing magnitudes of  $V_{GS}$ .

- The transfer characteristics defined by Shockley's equation are unaffected by the network in which the device is employed.
- By using basic algebra we can obtain an equation for the resulting level of  $V_{GS}$  for a given level of  $I_D$ .

$$V_{GS} = V_P \left( 1 - \sqrt{\frac{I_D}{I_{DSS}}} \right)$$

- In the Figure below two graphs are provided, with the vertical scaling in milliamperes for each graph.
- One is a plot of  $I_D$  versus  $V_{DS}$ , while the other is  $I_D$  versus  $V_{GS}$ .

## IMPORTANT RELATIONSHIPS:

<i>JFET</i>	<i>BJT</i>
$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 \Leftrightarrow$	$I_C = \beta I_B$
$I_D = I_S \Leftrightarrow$	$I_C \cong I_E$
$I_G \cong 0 \text{ A} \Leftrightarrow$	$V_{BE} \cong 0.7 \text{ V}$




In review:

*When  $V_{GS} = 0\text{ V}$ ,  $I_D = I_{DSS}$ , and when  $V_{GS} = V_P$ ,  $I_D = 0\text{ mA}$ .*

The total device dissipation at 25°C (room temperature) is the maximum power the device can dissipate under normal operating conditions and is defined by

$$P_D = V_{DS} I_D$$

# Transfer Characteristics

 

*Obtaining the transfer curve from the drain characteristics.*

- The general relationships that can be applied to the dc analysis of all FET amplifiers are

$$I_G \approx 0 \text{ A} \quad \text{and} \quad I_D = I_S$$

- The simplest of biasing arrangements for the n-channel JFET appears in the Figure below.
- Referred to as the fixed-bias configuration, it is one of the few FET configurations that can be solved just as directly using either a mathematical or graphical approach.

# Fixed - Bias Configuration


$$I_G = 0 \text{ A} \quad \text{and} \quad V_{RG} = I_G R_G = (0 \text{ A}) R_G = 0 \text{ V}$$

Applying Kirchhoff's voltage law in the clockwise direction of the indicated loop of Fig. will result in

$$-V_{GG} - V_{GS} = 0 \quad \text{and} \quad V_{GS} = -V_{GG}$$

The drain-to-source voltage of the output section can be determined by applying Kirchhoff's voltage law as follows:
 
$$+V_{DS} + I_D R_D - V_{DD} = 0 \quad \text{and} \quad V_{DS} = V_{DD} - I_D R_D$$



Network for dc analysis.

# Fixed - Bias Configuration

For the configuration of Fig

$$V_S = 0$$

Using double-subscript notation:

$$V_{DS} = V_D - V_S \text{ or } V_D = V_{DS} + V_S = V_{DS} + 0V \text{ and } V_D = V_{DS}$$

$$\text{In addition, } V_{GS} = V_G - V_S \text{ or } V_G = V_{GS} + V_S = V_{GS} + 0V \text{ and } V_G = V_{GS}$$

# Fixed - Bias Configuration

The drain-to-source voltage of the output section can be determined by applying Kirchhoff's voltage law as follows:

$$+V_{DS} + I_D R_D - V_{DD} = 0$$

and

$$V_{DS} = V_{DD} - I_D R_D$$

Recall that single-subscript voltages refer to the voltage at a point with respect to ground. For the configuration of Fig.

$$V_S = 0 \text{ V}$$

Using double-subscript notation, we have

$$V_{DS} = V_D - V_S$$

or

$$V_D = V_{DS} + V_S = V_{DS} + 0 \text{ V}$$

and

$$V_D = V_{DS}$$

In addition,

$$V_{GS} = V_G - V_S$$

or

$$V_G = V_{GS} + V_S = V_{GS} + 0 \text{ V}$$

and

$$V_G = V_{GS}$$

