



COLLEGE OF ENGINEERING AND TECHNOLOGIES
ALMUSTAQBAL UNIVERSITY

Electronics Circuits
CTE 204

Lecture 1

- Field Effect Transistor (FET) -
(2024 - 2025)


Dr. Zaidoon AL-Shammari

Lecturer / Researcher

zaidoon.waleed@mustaqbal-college.edu.iq

- The field effect transistor (FET) is a three-terminal device used for a variety of applications that match, to a large extent, those of the BJT transistor.
- Although there are important differences between the two types of devices, there are also many similarities that will be pointed out in the sections to follow.

 - The primary difference between the two types of transistors is the fact that the BJT transistor is a current-controlled device as depicted in Figure (a), while the JFET transistor is a voltage-controlled device as shown in Figure (b).




- In other words, the current I_C in Figure (a) is a direct function of the level of I_B .
- For the FET the current I will be a function of the voltage V_{GS} applied to the input circuit as shown in Figure (b).
- In each case the current of the output circuit is being controlled by a parameter of the input circuit in one case a current level and in the other an applied voltage.

- There are n-channel and p-channel field-effect transistors
- Two types of FETs will be introduced:
 - The junction field-effect transistor (JFET) and
 - The metal-oxide-semiconductor field-effect transistor (MOSFET).

- The basic construction of the n-channel JFET is shown in Figure below.
- Note that the major part of the structure is the n-type material that forms the channel between the embedded layers of p-type material.
- The top of the n-type channel is connected through an ohmic contact to a terminal referred to as the drain (D), while the lower end of the same material is connected through an ohmic contact to a terminal referred to as the source (S).

- The two p-type materials are connected together and to the gate (G) terminal.
- In essence, therefore, the drain and source are connected to the ends of the n-type channel and the gate to the two layers of p-type material.
- In the absence of any applied potentials the JFET has two p-n junctions under no-bias conditions.

Junction Field Effect Transistor

 

Junction field-effect transistor (JFET).


- In Figure below, a positive voltage V_{DS} has been applied across the channel and the gate has been connected directly to the source to establish the condition $V_{GS} = 0$ V.
- As the voltage V_{DS} is increased from 0 to a few volts, the current will increase as determined by Ohm's law and the plot of I_D versus V_{DS} will appear.

- If V_{DS} is increased to a level where it appears that the two depletion regions would “touch”, a condition referred to as pinch-off will result.

I_{DSS} is the maximum drain current for a JFET and is defined by the conditions

$$V_{GS} = 0 \text{ V and } V_{DS} > |V_p|.$$

Construction and Characteristics of JFET

 

JFET at $V_{GS} = 0\text{ V}$ and $V_{DS} > 0\text{ V}$.

 


FIG. 6.7

I_D versus V_{DS} for $V_{GS} = 0\text{ V}$.


- The voltage from gate to source, denoted V_{GS} , is the controlling voltage of the JFET, curves of I_D versus V_{DS} for various levels of V_{GS} can be developed for the JFET.
- Note also on the Figure below how the pinch-off voltage continues to drop in a parabolic manner as V_{GS} becomes more and more negative.

- Eventually, V_{GS} when $V_{GS} = V_p$ will be sufficiently negative to establish a saturation level that is essentially 0 mA, and for all practical purposes the device has been “turned off.”
- The level of V_{GS} that results in $I_D = 0$ mA is defined by $V_{GS} = V_p$, with V_p being a negative voltage for n-channel devices and a positive voltage for p-channel JFETs.

Construction and Characteristics of JFET

- The region to the left of the pinch-off locus of this Figure is referred to as the ohmic or voltage-controlled resistance region.
- In this region the JFET can actually be employed as a variable resistor (possibly for an automatic gain control system) whose resistance is controlled by the applied gate-to-source voltage

$$r_d = \frac{r_o}{(1 - V_{GS}/V_P)^2}$$

 

n-Channel JFET characteristics with $I_{DSS} = 8$ mA and $V_P = -4$ V.

