



جامعة المستقبل
AL MUSTAQBAL UNIVERSITY

كلية العلوم
قسم الفيزياء الطبية

MedicalPhysics

المرحلة : الأولى

المادة : الكهربائية – عملي

المختبر: الأول

اسم التجربة: " قنطرة ويتستون "

رقم التجربة : 2

مشرفة المختبر: د. دعاء جعفر

معيدة المختبر : م. افتخار ثامر



Wheatstone Bridge

In the year 1843 AD, the English physicist Charles Wheatstone (1802 – 1875) made an electrical circuit to measure the amount of unknown resistance. This circuit was distinguished by its high accuracy in finding the amount of resistance. It relied on finding the value of the unknown resistance in proportion to the values of known resistors.

The purpose:

It is to find the amount of unknown resistance .


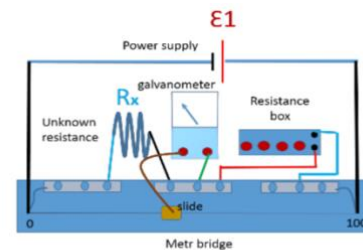


Figure (1)

Used equipments:

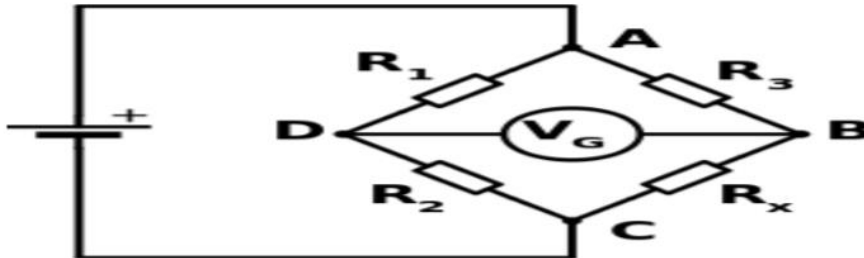Voltage source (battery), known resistance, wire of unknown resistance, meter bridge, galvanometer, wires .



Experiment theory:

When an electrical circuit is connected as in Figure (2) and a current passes through the circuit, the current will be divided into two parts. I_1 passes through resistors R_3 and R_x and I_2 passes through resistors R_1 and R_2 .

If the potential of point B is equal to the potential of point D, which is what we call the state of equilibrium, then the potential difference of two points AB is equal to the potential difference of two points AD and the potential difference of two points CB is equal to the potential difference of two points CD.



$$V_{AB} = V_{AD} \dots\dots\dots (1)$$

$$V_{CB} = V_{CD} \dots\dots\dots (2)$$

Therefore, we can compensate for the resistances and currents, and this is:

$$R_3 I_1 = R_2 I_2 \dots\dots\dots (3)$$

$$R_x I_1 = R_1 I_2 \dots\dots\dots (4)$$

By dividing the two equations, we find that:

$$R_x = R_3 * R_1 / R_2 \dots\dots\dots (5)$$

If R_1 and R_2 are resistors from the same wire, their resistance is equal:

$$R_1 = \rho_1 * L_1 / A_1 \dots\dots\dots (6)$$

$$R_2 = \rho_2 * L_2 / A_2 \dots\dots\dots (7)$$



Since, as we mentioned, they are from the same wire,
they have the same specific resistance p and have the
same cross-sectional area A , by dividing (6) by (7)

Equation becomes as follows

$$R_x = R \cdot L_1/L_2 \dots\dots\dots (8)$$

$$R_1/R_2 = R_3/R_4$$

R	L₁	L₂=L- L₁	R_x=R*L₁/L₂



Some question

Q\FIND ($R_4=?$)($R_1=20, R_2=40, R_3=42$)
(a-892)(b-8kS2)(c-1652)(d-392)

°Q/What is the law total resistance?
(a- $R_x=R \cdot L_2/L_1$)(b- $R_c=R \cdot L_2/L_1$)(c- $R_x=R \cdot L_1/L_2$)(d- $R_x=R \cdot L_1/L$)

Q\FIND ($L_2=?$)($L_1=84$)
(a-9)(b-16)(c-0.1)(d-0.16)