

Logic Gate



College of
Engineering & Technology



Al-Mustaqbal
University

Level 1 , Semester 1
@ Department of prosthetic and orthotic Engineering

Prepared by
Dr. Samir Badrawi
2024-2025

Binary Adders , Compotators , Decoders

The majority of this course material is based on text and presentations of :

Floyd, Digital Fundamentals, 10Th ed., © 2009 Pearson Education, Upper Saddle River, NJ 07458. All Rights Reserved

Some Application of Digital Logic circuits

Digital Electronics - Binary Arithmetic

Binary arithmetic is one of the fundamental concepts in the field of digital electronics. It is basically the **mathematics on binary digits (bits)**.

Rules of Binary Addition

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 0 \text{ with carry } 1$$

$$1 + 1 = 10$$

$$1 + 1 + 1 = 1 \text{ with carry } 1$$

$$1 + 1 + 1 = 11$$

$$(\text{Sum} = 0 \text{ \& Carry} = 1)$$

$$(\text{Sum} = 1 \text{ \& Carry} = 1)$$

Inputs		Outputs	
A	B	C_{out}	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Binary Addition

$$\begin{array}{r} 0111 \\ 00111 \quad 7 \\ 10101 \quad 21 \\ \hline 11100 = 28 \end{array}$$



$$\begin{array}{r} 1111.11 \\ 1101.101 \\ 1101.001 \\ \hline 10101.000 \end{array}$$

Half-Adder

Basic rules of binary addition are performed by a **half adder**, which has two binary inputs (A and B) and two binary outputs (**C**arry out and **S**um).

The inputs and outputs can be summarized on a truth table.

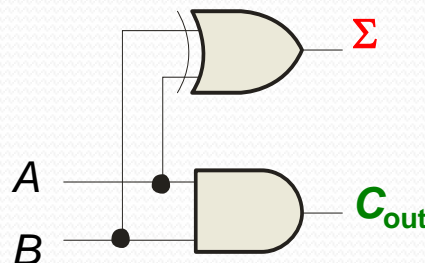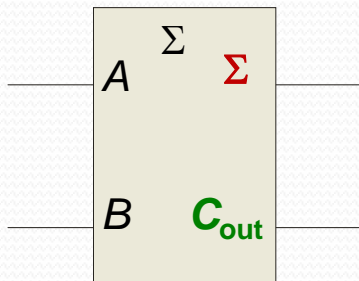The logic symbol and equivalent circuit are:




Inputs		Outputs	
A	B	C _{out}	Σ
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Full-Adder


By contrast, a **full adder** has three binary inputs (A , B , and **Carry in**) and two binary outputs (**Carry out** and **Sum**).

The truth table summarizes the operation.

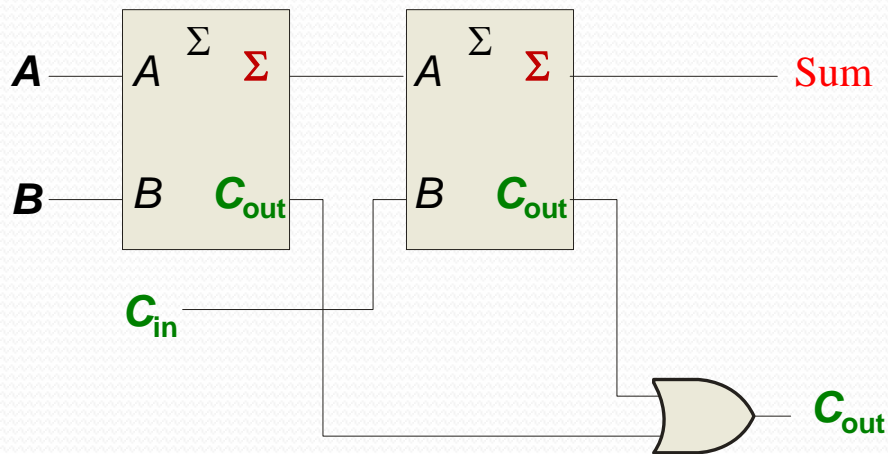A full-adder can be constructed from two half adders as shown:



Inputs			Outputs	
A	B	C_{in}	C_{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

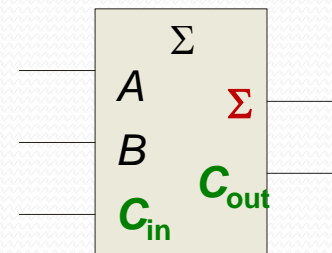

Symbol

Full-Adder

Example


For the given inputs, determine the intermediate and final outputs of the full adder.

Solution

The first half-adder has inputs of 1 and 0; therefore the **Sum = 1** and the **Carry out = 0**.

The second half-adder has inputs of 1 and 1; therefore the Sum = 0 and the Carry out = 1.

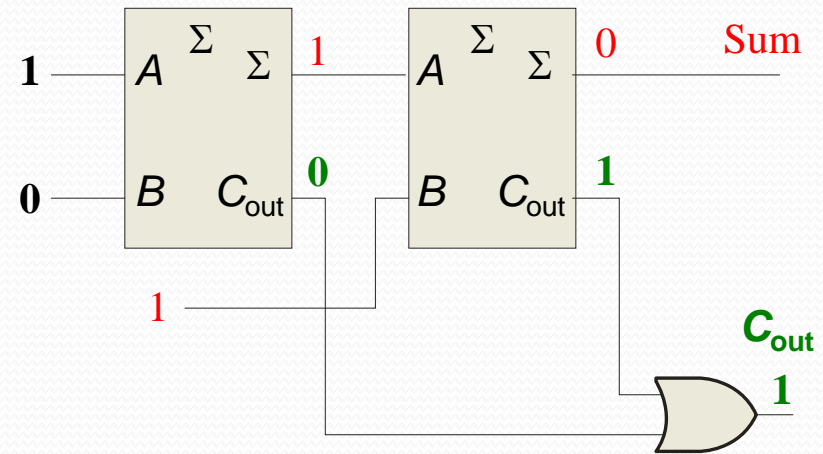The OR gate has inputs of 1 and 0, therefore the final carry out = 1.



Inputs			Outputs	
A	B	C _{in}	C _{out}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Comparators

The function of a comparator is to compare the magnitudes of two binary numbers to determine the relationship between them.

In its simplest form, a comparator circuit determines whether two numbers are equal.

وظيفة جهاز المقارنة هي مقارنة مقادير رقمين ثنائيين (binary) لتحديد العلاقة بينهما. في أبسط صورها، تحدد دائرة المقارنة ما إذا كان الرقمان متساويان أم لا.

In exclusive-NOR gate, the output is a 0 if the two input bits are not equal and a 1 if the input bits are equal.


في بوابة NOR الحصرية (XNOR)، تكون المخرجات (0) إذا كانت البتات المدخلة (two input bits) غير متساوية، و (1) إذا كانت بتات الإدخال متساوية.

Thus, in the simplest form, a comparator can test for equality using **exclusive NOR gates**. (why ?)

ولذلك، في أبسط صورها فإن دائرة جهاز المقارنة للمساواة بين الأرقام الثنائية يمكن أن تكون عبارة عن بوابة NOR الحصرية (XNOR)

Comparators

A Basic Comparator

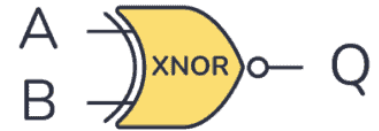

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	1

0
0

1 The input bits are equal.

1
1

1 The input bits are equal.

0
1

0 The input bits are not equal.

1
0


0 The input bits are not equal.

Comparators

In order to compare binary numbers containing two bits each, an additional exclusive-NOR gate is necessary.

من أجل مقارنة الأرقام الثنائية التي تحتوي كل منها على بتتين (يعني $A = A_1A_0$)، فمن الضروري وجود بوابة NOR حصرية إضافية.

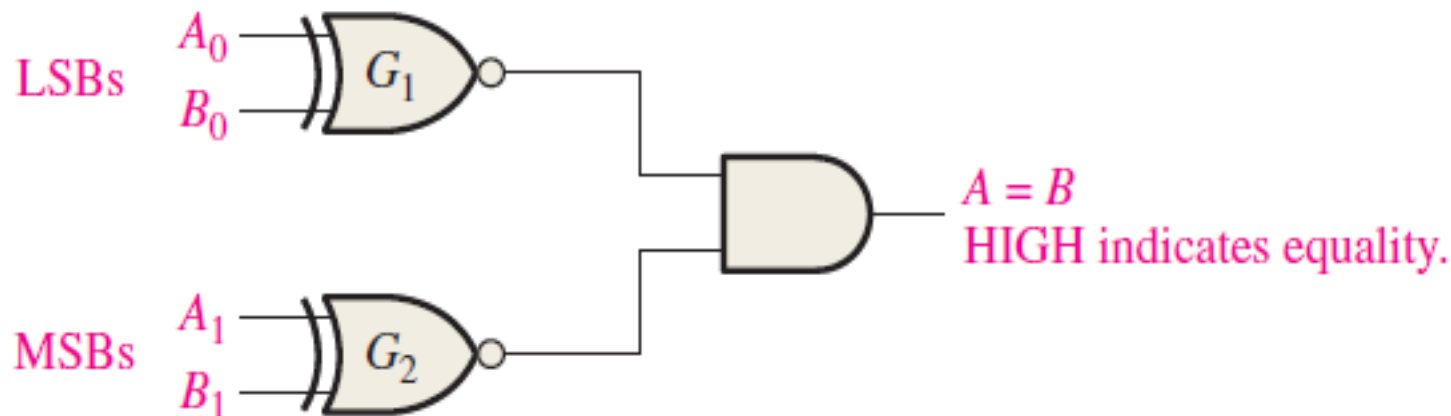The two least significant bits (LSBs) of the two numbers are compared by gate G_1 , and the two most significant bits (MSBs) are compared by gate G_2 .



General format: Binary number $A \rightarrow A_1A_0$
Binary number $B \rightarrow B_1B_0$


مثلاً

$A = 1\ 0$

$B = 1\ 0$

Comparators

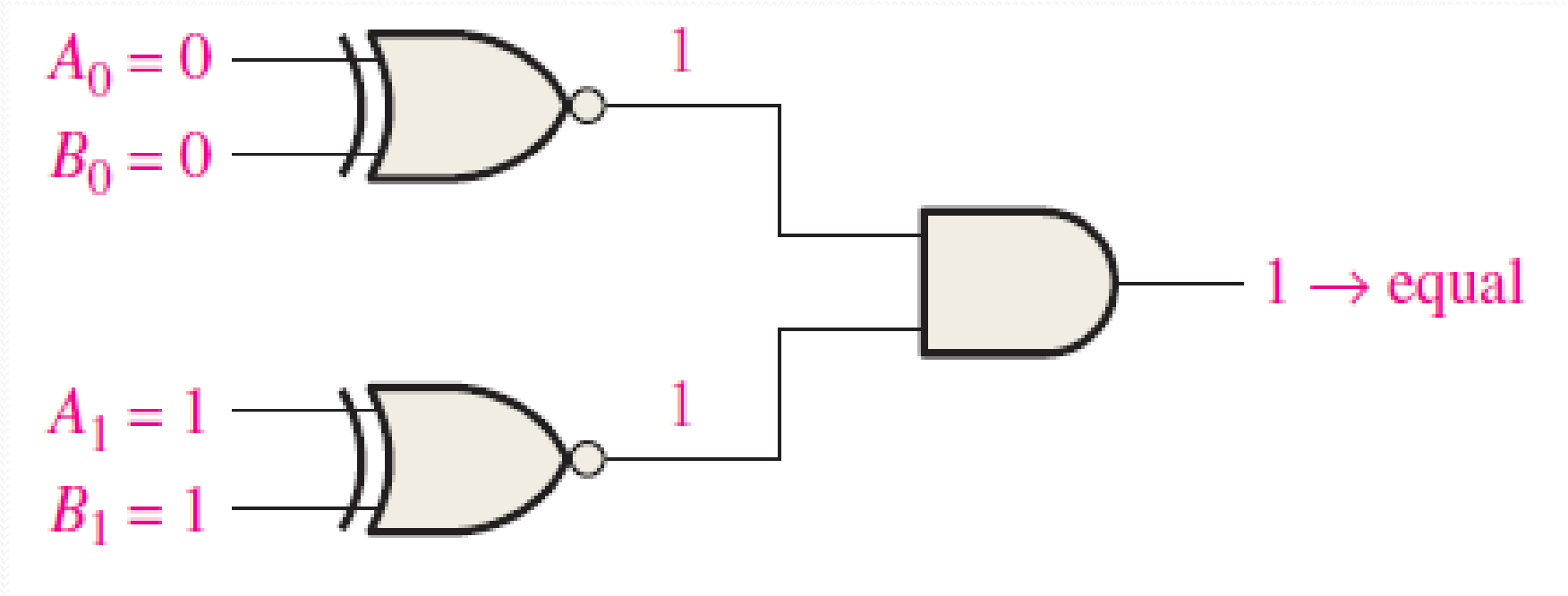
Example 1:- Apply the (10) and (10) binary numbers to the comparator inputs given below, and determine the output by following the logic levels through the circuit.



Solution: The output is 1 for inputs 10 and 10

Comparators

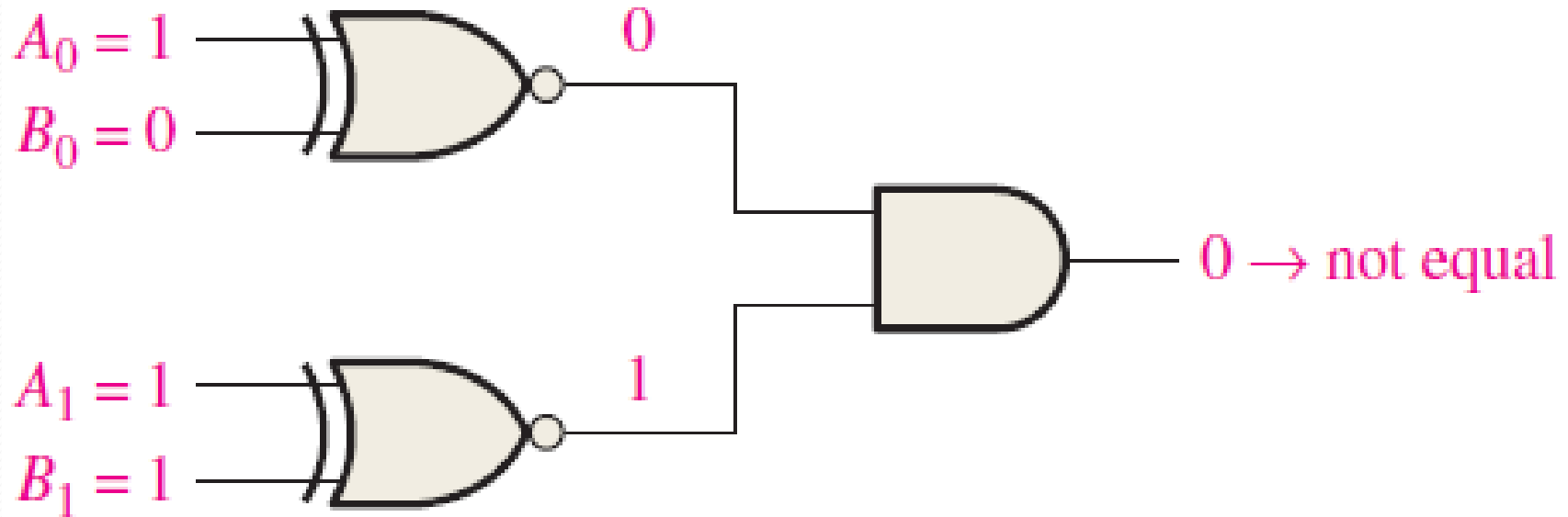Example 2:- Apply the (**10**) and (**11**) binary numbers to the comparator inputs given below, and determine the output by following the logic levels through the circuit.



Solution: The output is **0** for inputs 11 and 10

Comparators


إذا كان لدينا أكثر من (2) بت في الرقم الثنائي .. فلكل بت هناك بوابة (XNOR)

The function of a comparator is to compare the magnitudes of two binary numbers to determine the relationship between them. In the simplest form, a comparator can test for equality using XNOR gates.

Example Solution

How could you test two 4-bit numbers for equality?

AND the outputs of four XNOR gates.

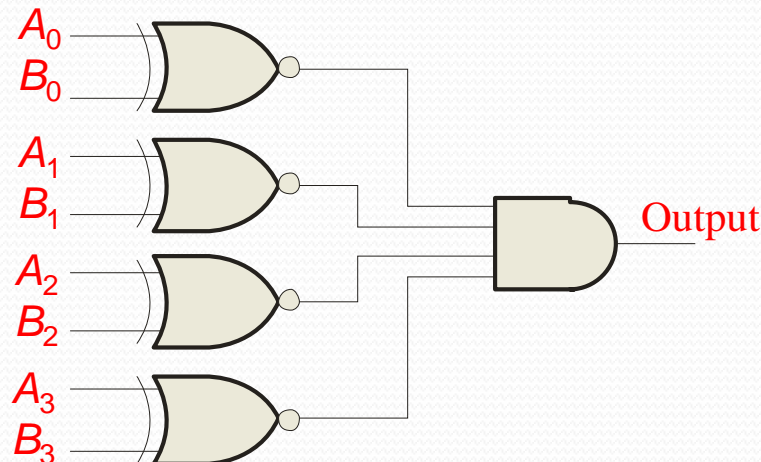

مثال

A = 1 0 1 0

B = 0 1 1 0


Decoders

A **decoder** is a digital circuit that detects the presence of a specified combination of bits (code) on its inputs and indicates the presence of that code by a specified output level.

جهاز فك التشفير عبارة عن دائرة رقمية تكتشف وجود مجموعة محددة من البتات (الكود) على مدخلاتها وتشير إلى وجود هذا الرمز من خلال مخرج محدد..

A simple decoder that detect the presence of the binary code (**A = 0011**) is shown below:-

ملاحظة (Active HIGH)
يعني ال مخرج هو (1)

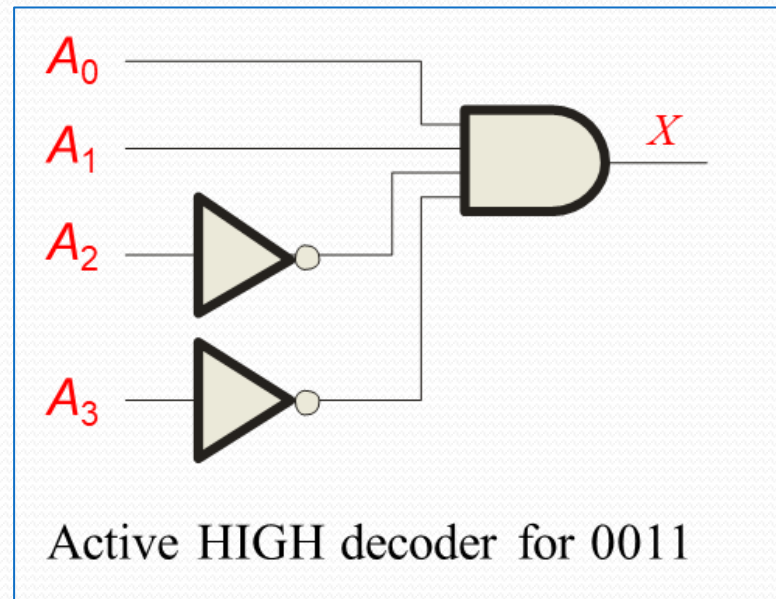

Decoders

Question

Assume the output of the decoder shown is a logic 1. What are the inputs to the decoder?

