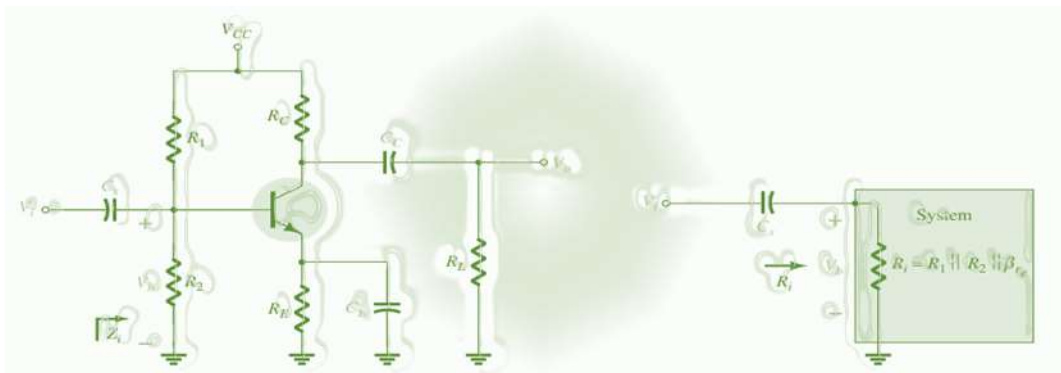




Electronic Circuit

Lecture 3 (4th & 5th Week)

BJT & FET Frequency Response





1.1. Introduction to BJT Amplifiers

The frequency response of a Bipolar Junction Transistor (BJT) describes how its performance changes with varying signal frequency. The response varies across low, and high frequencies.

- ✚ **Low Frequencies:** The performance is affected by coupling and bypass capacitors, leading to a drop in response at very low frequencies.
- ✚ **High Frequencies:** The effects of parasitic capacitances (such as base-collector capacitance C_{bc} and base-emitter capacitance C_{be} become significant, reducing gain and altering circuit response.

1.2 Low Frequency Response BJT Amplifier with R_L

The analysis of this section will employ the loaded R_L voltage-divider BJT bias configuration introduced earlier lecture. For the network of Fig. 1, the capacitors C_s , C_c , and C_E will determine the low-frequency response. We will now examine the impact of each independently in the order listed.

C_s Because is normally connected between the applied source and the active device, the general form of the RC configuration is established by the network of Fig. 2, matching that with $R_i = R_1 \parallel R_2 \parallel \beta r_e$.

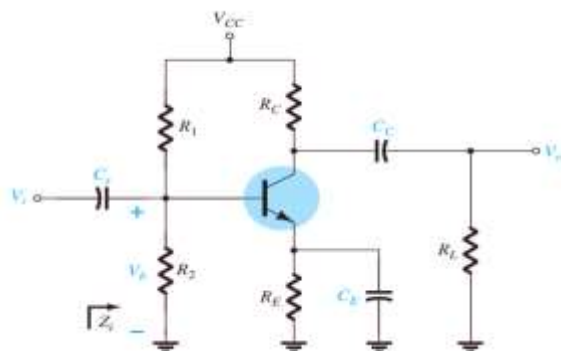


Fig.1. Loaded BJT amplifier with capacitors that affect the low- frequency response.

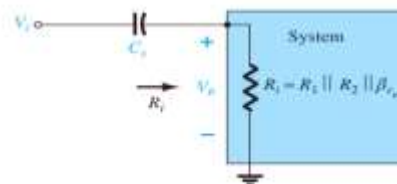


Fig.2. Determining the effect of C_s on the low- frequency response.



Applying the voltage-divider rule:

$$\mathbf{V}_b = \frac{R_i \mathbf{V}_i}{R_i - jX_{C_s}}$$

The cutoff frequency defined by C_s can be determined by manipulating the above equation into a standard form or simply. For future RC networks, will simply be applied.

$$\frac{\mathbf{V}_b}{\mathbf{V}_i} = \frac{R_i}{R_i - jX_{C_s}} = \frac{1}{1 - j \frac{X_{C_s}}{R_i}}$$

The factor

$$\frac{X_{C_s}}{R_i} = \left(\frac{1}{2\pi f C_s} \right) \left(\frac{1}{R_i} \right) = \frac{1}{2\pi f R_i C_s}$$

Defining

$$f_{L_s} = \frac{1}{2\pi R_i C_s}$$

we have

$$\mathbf{A}_v = \frac{\mathbf{V}_b}{\mathbf{V}_i} = \frac{1}{1 - j(f_{L_s}/f)}$$

For the network of Fig.1, when we analyze the effects of C_s we must make the as Sumption that C_E and C_c are performing their designed function or the analysis becomes too unwieldy, that is, that the magnitudes of the reactance of C_E and C_c permit employing a short-circuit equivalent in comparison to the magnitude of the other series impedances.



C_c Because the coupling capacitor is normally connected between the output of the active device and the applied load, the RC configuration that determines the low-cutoff frequency due to C_c appears in Fig.3. The total series resistance is now $R_o + R_L$, and the cutoff frequency due to C_c is determined by:

$$f_{Lc} = \frac{1}{2\pi(R_o + R_L)C_c}$$

Ignoring the effects of C_s and C_E , we find that the output voltage V_o . For the network of Fig.3, the ac equivalent network for the output section with $V_i = 0$ V appears in Fig.3 The resulting value for R_o in Eq. below is then simply:

$$R_o = R_C \parallel r_o$$

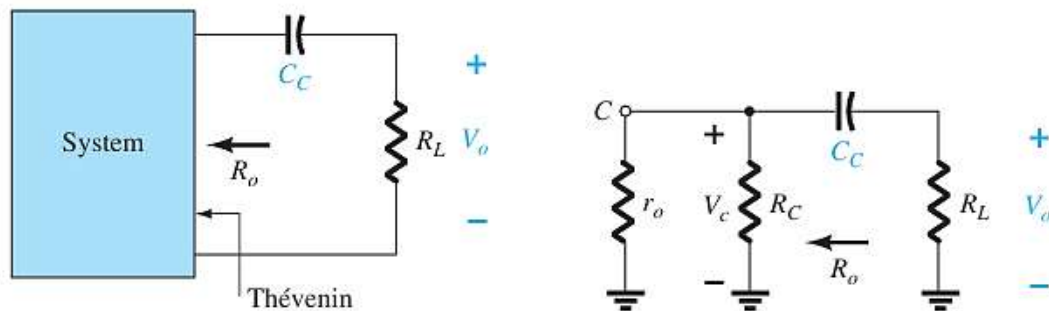


Fig.3. Determining the effect of C_c on the low-frequency response. Localized ac equivalent for C_c with $V_i = 0$ V.

C_E To determine f_{LE} , the network “seen” by C_E must be determined as shown in Fig.3. Once the level of R_e is established, the cutoff frequency due to C_E can be determined using the following equation:

$$f_{LE} = \frac{1}{2\pi R_e C_E}$$



For the network, the ac equivalent as “seen” by C_E appears in Fig.4. The value of R_e is therefore determined by:

$$R_e = R_E \parallel \left(\frac{R_1 \parallel R_2}{\beta} + r_e \right)$$

The effect of C_E on the gain is best described in a quantitative manner by recalling that the gain for the configuration of Fig.4. is given by

$$A_v = \frac{-R_C}{r_e + R_E}$$

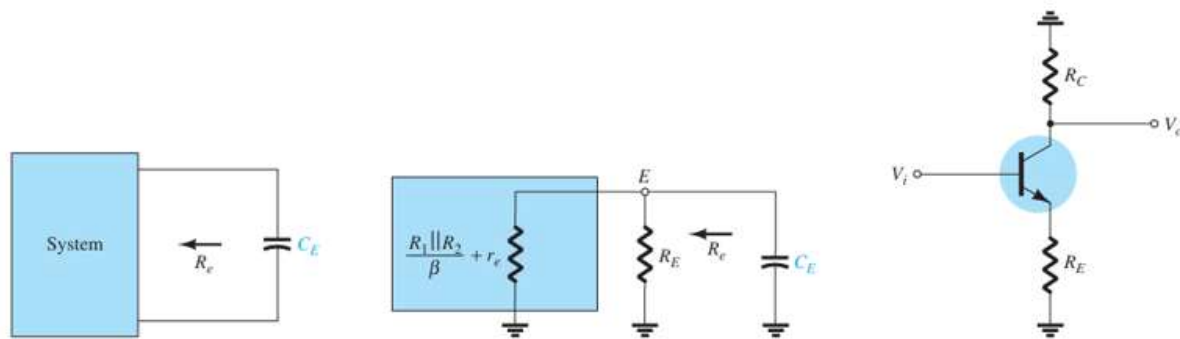


Fig.4. (a)Determining the effect of C_E on the low-frequency response. (b) Localized ac equivalent of C_E . (c) Network employed to describe the effect of C_E on the amplifier gain.

The maximum gain is obviously available where R_E is 0. At low frequencies, with the bypass capacitor C_E in its “open-circuit” equivalent state, all of R_E appears in the gain equation above, resulting in the minimum gain. As the frequency increases, the reactance of the capacitor C_E will decrease, reducing the parallel impedance of R_E and C_E until the resistor R_E is effectively “shorted out” by C_E . The result is a maximum or midband gain determined by $A_v = -R_C/r_e$. At f_{LE} the gain will be 3 dB below the midband value determined with R_E “shorted out.”




Example1: Determine the cutoff frequencies for the network of Fig.1. using the following parameters:

$C_s = 10 \text{ mF}$, $C_E = 20 \text{ mF}$, $C_C = 1 \text{ mF}$

$R_1 = 40 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$, $R_E = 2 \text{ k}\Omega$,

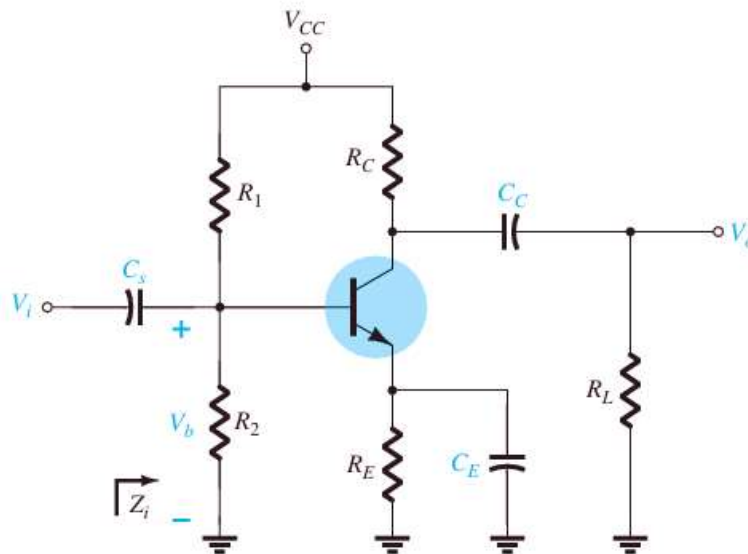$R_C = 4 \text{ k}\Omega$, $R_L = 2.2 \text{ k}\Omega$, $\beta = 100$, $r_e = \infty \Omega$, $V_{CC} = 20 \text{ V}$



Sol:

To determine r_e for dc conditions, we first apply the test equation:

$$\beta R_E = (100)(2 \text{ k}\Omega) = 200 \text{ k}\Omega \gg 10R_2 = 100 \text{ k}\Omega$$

Since satisfied the dc base voltage is determined by

$$V_B \cong \frac{R_2 V_{CC}}{R_2 + R_1} = \frac{10 \text{ k}\Omega (20 \text{ V})}{10 \text{ k}\Omega + 40 \text{ k}\Omega} = \frac{200 \text{ V}}{50} = 4 \text{ V}$$

with

$$I_E = \frac{V_E}{R_E} = \frac{4 \text{ V} - 0.7 \text{ V}}{2 \text{ k}\Omega} = \frac{3.3 \text{ V}}{2 \text{ k}\Omega} = 1.65 \text{ mA}$$

so that

$$r_e = \frac{26 \text{ mV}}{1.65 \text{ mA}} \cong \mathbf{15.76 \Omega}$$

and

$$\beta r_e = 100(15.76 \Omega) = 1576 \Omega = \mathbf{1.576 \text{ k}\Omega}$$



Midband Gain $A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel R_L}{r_e} = -\frac{(4 \text{ k}\Omega) \parallel (2.2 \text{ k}\Omega)}{15.76 \Omega} \cong -90$

C_s $R_i = R_1 \parallel R_2 \parallel \beta r_e = 40 \text{ k}\Omega \parallel 10 \text{ k}\Omega \parallel 1.576 \text{ k}\Omega \cong 1.32 \text{ k}\Omega$

$$f_{L_s} = \frac{1}{2\pi R_i C_s} = \frac{1}{(6.28)(1.32 \text{ k}\Omega)(10 \mu\text{F})}$$

$$f_{L_s} \cong \mathbf{12.06 \text{ Hz}}$$

C_c $f_{L_c} = \frac{1}{2\pi(R_o + R_L)C_C} \quad \text{with} \quad R_o = R_C \parallel r_o \cong R_C$

$$= \frac{1}{(6.28)(4 \text{ k}\Omega + 2.2 \text{ k}\Omega)(1 \mu\text{F})}$$

$$\cong \mathbf{25.68 \text{ Hz}}$$

C_E $R_e = R_E \parallel \left(\frac{R_1 \parallel R_2}{\beta} + r_e \right)$

$$= 2 \text{ k}\Omega \parallel \left(\frac{40 \text{ k}\Omega \parallel 10 \text{ k}\Omega}{100} + 15.76 \Omega \right)$$

$$= 2 \text{ k}\Omega \parallel \left(\frac{8 \text{ k}\Omega}{100} + 15.76 \Omega \right)$$

$$= 2 \text{ k}\Omega \parallel (80 \Omega + 15.76 \Omega)$$

$$= 2 \text{ k}\Omega \parallel 95.76 \Omega$$

$$= 91.38 \Omega$$

$$f_{L_E} = \frac{1}{2\pi R_e C_E} = \frac{1}{(6.28)(91.38 \Omega)(20 \mu\text{F})} = \frac{10^6}{11,477.73} \cong \mathbf{87.13 \text{ Hz}}$$

Since $f_{L_E} \gg f_{L_C}$ or f_{L_s} the bypass capacitor C_E is determining the lower cutoff frequency of the amplifier.



1.3 Impact of R_s on the BJT Low Frequency response

In this section we will investigate the impact of the source resistance on the various cutoff frequencies. In Fig. 5 a signal source and associated resistance have been added to the configuration of Fig.1. The gain will now be between the output voltage V_o and the signal source V_s .

As The equivalent circuit at the input is now as shown in Fig.5, with R_i continuing to be equal to $R_1 \parallel R_2 \parallel \beta r_e$.

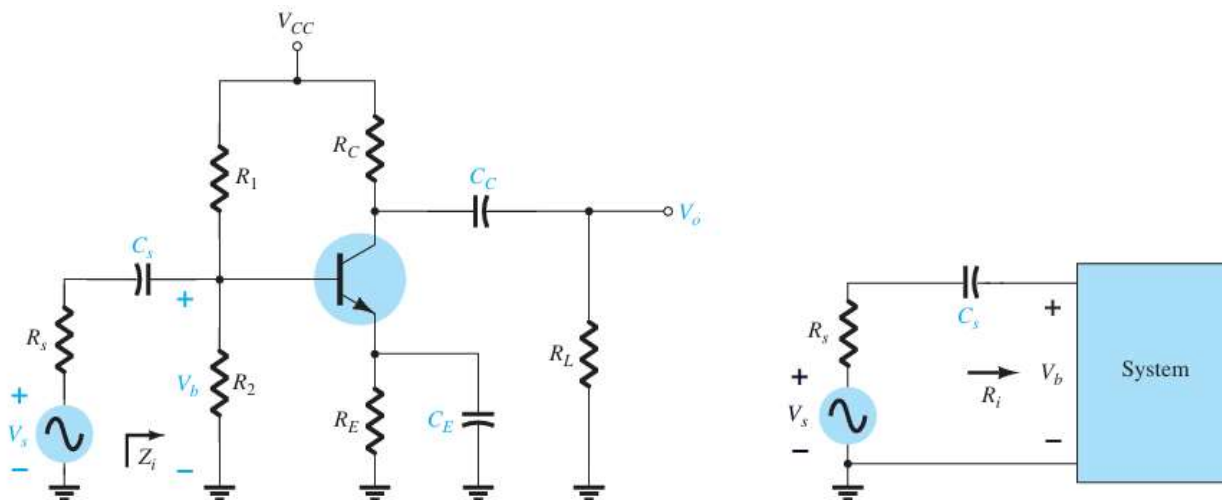


Fig.5. Determining the effect of R_s on the low-frequency response of a BJT amplifier. Determining the effect of C_s on the low frequency response.

Using the results of the last section it would appear we could simply find the total sum of the series resistors. Doing so would result in the following equation for the cutoff frequency:

$$f_{L_s} = \frac{1}{2\pi(R_i + R_s)C_s}$$



However, it would be best to validate our assumption by first applying the voltage-divider rule in the following manner:

$$\mathbf{V_b = \frac{R_i V_s}{R_s + R_i - jX_{C_s}}}$$

The cutoff frequency defined by C_s can be determined by manipulating the above equation into a standard form, as demonstrated below.

$$\begin{aligned} \frac{V_b}{V_s} &= \frac{R_i}{R_s + R_i - jX_{C_s}} = \frac{1}{1 + \frac{R_s}{R_i} - j\frac{X_{C_s}}{R_i}} \\ &= \frac{1}{\left(1 + \frac{R_s}{R_i}\right) \left[1 - j\frac{X_{C_s}}{R_i} \left(\frac{1}{1 + \frac{R_s}{R_i}}\right)\right]} = \frac{1}{\left(1 + \frac{R_s}{R_i}\right) \left(1 - j\frac{X_{C_s}}{R_i + R_s}\right)} \end{aligned}$$

The factor

$$\frac{X_{C_s}}{R_i + R_s} = \left(\frac{1}{2\pi f C_s}\right) \left(\frac{1}{R_i + R_s}\right) = \frac{1}{2\pi f (R_i + R_s) C_s}$$

Defining

$$f_{L_s} = \frac{1}{2\pi (R_i + R_s) C_s}$$

we have

$$\frac{V_b}{V_s} = \frac{1}{\left(\frac{1}{1 + \frac{R_s}{R_i}}\right) \left(1 - \frac{1}{1 - jf_{L_s}/f}\right)}$$

and finally

$$\mathbf{A_v = \frac{V_b}{V_s} = \left[\frac{R_i}{R_i + R_s}\right] \left[\frac{1}{1 - j(f_{L_s}/f)}\right]}$$

For the midband frequencies, the input network will appear as shown:

$$\mathbf{A_{v_{mid}} = \frac{V_b}{V_s} = \frac{R_i}{R_i + R_s}}$$



$$\frac{A_v}{A_{v_{mid}}} = \frac{1}{1 - j(f_{L_s}/f)}$$

Noting the similarities with Eq. above the cutoff frequency is defined by f_{L_s} above and:

$$f_{L_s} = \frac{1}{2\pi(R_s + R_i)C_s}$$

Cc Reviewing the analysis for the coupling capacitor Cc, we find that the derivation of the equation for the cutoff frequency remains the same. That is,

$$f_{L_c} = \frac{1}{2\pi(R_o + R_L)C_C}$$

CE Again, following the analysis for the same capacitor, we find that Rs will affect the resistance level substituted into the cutoff equation so that

$$f_{L_E} = \frac{1}{2\pi R_e C_E}$$



Example 2: Repeat the analysis of Example 1 but with a source resistance R_s of $1\text{ k}\Omega$. The gain of interest will now be V_o/V_s rather than V_o/V_i . Compare results.

Sol/ The dc conditions remain the same:

$$r_e = 15.76\ \Omega \text{ and } \beta r_e = 1.576\text{ k}\Omega$$

Midband Gain $A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel R_L}{r_e} \cong -90 \text{ as before}$

The input impedance is given by

$$\begin{aligned} Z_i = R_i &= R_1 \parallel R_2 \parallel \beta r_e \\ &= 40\text{ k}\Omega \parallel 10\text{ k}\Omega \parallel 1.576\text{ k}\Omega \\ &\cong 1.32\text{ k}\Omega \end{aligned}$$

and from Fig. 9.35,

$$V_b = \frac{R_i V_s}{R_i + R_s}$$

or $\frac{V_b}{V_s} = \frac{R_i}{R_i + R_s} = \frac{1.32\text{ k}\Omega}{1.32\text{ k}\Omega + 1\text{ k}\Omega} = 0.569$

so that $A_{v_s} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_b}{V_s} = (-90)(0.569)$
 $= -51.21$

C_s $R_i = R_1 \parallel R_2 \parallel \beta r_e = 40\text{ k}\Omega \parallel 10\text{ k}\Omega \parallel 1.576\text{ k}\Omega \cong 1.32\text{ k}\Omega$

$$\begin{aligned} f_{L_s} &= \frac{1}{2\pi(R_s + R_i)C_s} = \frac{1}{(6.28)(1\text{ k}\Omega + 1.32\text{ k}\Omega)(10\ \mu\text{F})} \\ f_{L_s} &\cong 6.86\text{ Hz vs. } 12.06\text{ Hz without } R_s \end{aligned}$$

C_c $f_{L_c} = \frac{1}{2\pi(R_C + R_L)C_C}$
 $= \frac{1}{(6.28)(4\text{ k}\Omega + 2.2\text{ k}\Omega)(1\ \mu\text{F})}$
 $\cong 25.68\text{ Hz as before}$

C_E $R'_s = R_s \parallel R_1 \parallel R_2 = 1\text{ k}\Omega \parallel 40\text{ k}\Omega \parallel 10\text{ k}\Omega \cong 0.889\text{ k}\Omega$
 $R_e = R_E \parallel \left(\frac{R'_s}{\beta} + r_e \right) = 2\text{ k}\Omega \parallel \left(\frac{0.889\text{ k}\Omega}{100} + 15.76\ \Omega \right)$
 $= 2\text{ k}\Omega \parallel (8.89\ \Omega + 15.76\ \Omega) = 2\text{ k}\Omega \parallel 24.65\ \Omega \cong 24.35\ \Omega$
 $f_{L_E} = \frac{1}{2\pi R_e C_E} = \frac{1}{(6.28)(24.35\ \Omega)(20\ \mu\text{F})} = \frac{10^6}{3058.36}$
 $\cong 327\text{ Hz vs. } 87.13\text{ Hz without } R_s.$



1.4. High Frequency response BJT Amplifier

At the high-frequency end, there are two factors that define the -3-dB cutoff point: the network capacitance (parasitic and introduced) and the frequency dependence of h_{fe} (β).

In the high-frequency region, the RC network of concern has the configuration appearing in Fig.6. At increasing frequencies, the reactance X_C will decrease in magnitude, resulting in a shorting effect across the output and a decrease in gain. The derivation leading to the corner frequency for this RC configuration follows along similar lines to that encountered for the low-frequency region. The most significant difference is in the following general form of A_v :

$$A_v = \frac{1}{1 + j(f/f_H)}$$

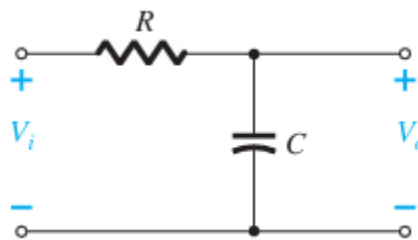


Fig.6. RC combination that will define a high-cutoff frequency.

This results in a magnitude plot such as shown in Fig. 7. that drops off at -6 dB/octave with increasing frequency. Note that f_H is in the denominator of the frequency ratio rather than the numerator as occurred for f_L .

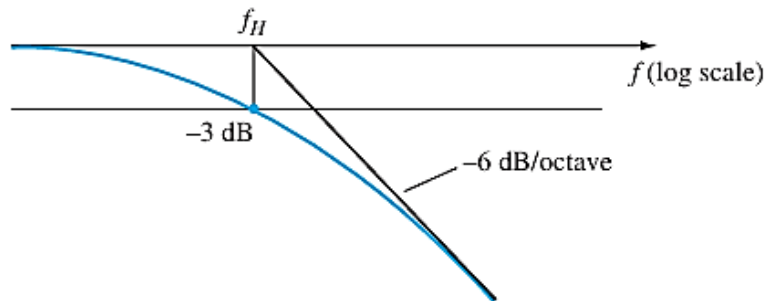


Fig.7. Asymptotic plot as defined

In Fig. 8, the various parasitic capacitances (C_{be} , C_{bc} , C_{ce}) of the transistor are included with the wiring capacitances (C_{Wi} , C_{Wo}) introduced during construction.

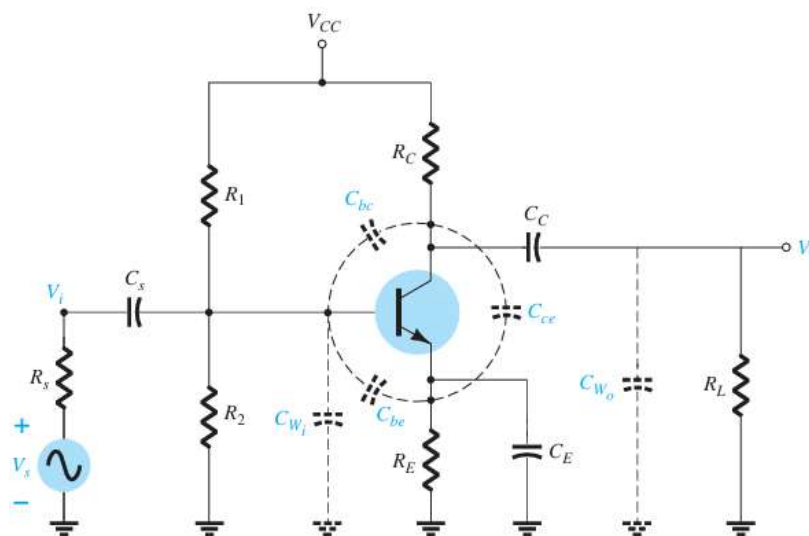


Fig.8. the capacitors that affect the high-frequency response.

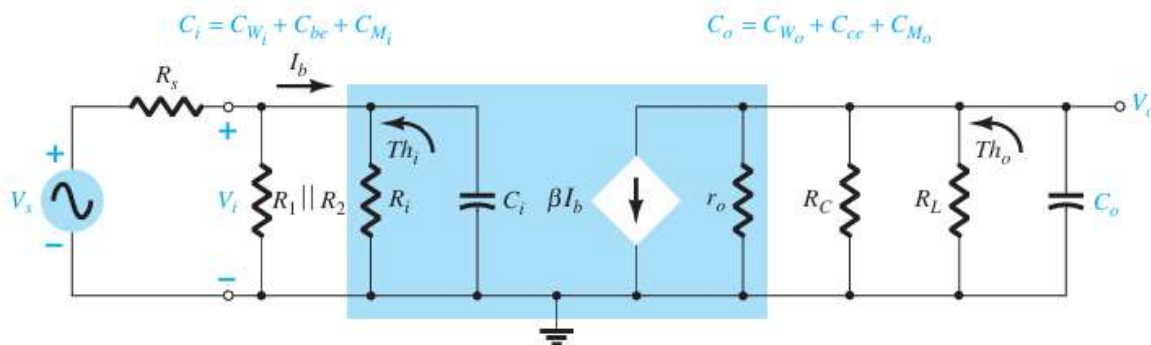


Fig.9. High-frequency ac equivalent model for the network of Fig.8



Determining the Thevenin equivalent circuit for the input and output networks of Fig.8 results in the configurations of Fig.9. For the input network, the 3-dB frequency is defined by:


$$f_{H_i} = \frac{1}{2\pi R_{Th_i} C_i}$$

with

$$R_{Th_i} = R_s \parallel R_1 \parallel R_2 \parallel \beta r_e$$

and
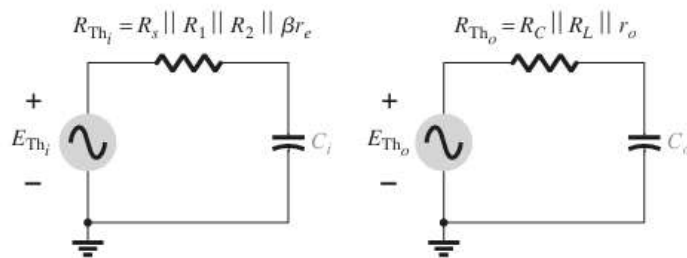
$$C_i = C_{W_i} + C_{be} + C_{M_i} = C_{W_i} + C_{be} + (1 - A_v)C_{bc}$$



At very high frequencies, the effect of C_i is to reduce the total impedance of the parallel combination of R_1 , R_2 , βr_e , and C_i in Fig.9. The result is a reduced level of voltage across C_i , a reduction in I_b , and a gain for the system. For the output network,

$$f_{H_o} = \frac{1}{2\pi R_{Th_o} C_o}$$

with

$$R_{Th_o} = R_C \parallel R_L \parallel r_o$$

and

$$C_o = C_{W_o} + C_{ce} + C_{M_o}$$

or

$$C_o = C_{W_o} + C_{ce} + (1 - 1/A_v)C_{bc}$$

For A_v large (typical):

$$1 \gg 1/A_v$$

and

$$C_o \cong C_{W_o} + C_{ce} + C_{bc}$$



The variation of h_{fe} (or β) with frequency will approach, with some degree of accuracy, the following relationship:

$$h_{fe} = \frac{h_{fe_{mid}}}{1 + j(f/f_{\beta})}$$

In terms of these parameters,

$$f_{\beta}(\text{often appearing as } f_{h_{fe}}) = \frac{1}{2\pi r_{\pi}(C_{\pi} + C_u)}$$

or, because $r_{\pi} = \beta r_e = h_{fe_{mid}} r_e$,

$$f_{\beta} = \frac{1}{h_{fe_{mid}}} \frac{1}{2\pi r_e(C_{\pi} + C_u)}$$

The basic format of Eq. above is exactly the same as Eq. above if we extract the multiplying factor $h_{fe_{mid}}$, revealing that h_{fe} will drop off from its midband value with a -6-dB/octave slope. The same figure has a plot of h_{fb} (or α) versus frequency. Note the small change in h_{fb} for the chosen frequency range, revealing that the common-base configuration displays improved high-frequency characteristics over the common-emitter configuration. Recall also the absence of the Miller effect capacitance due to the noninverting characteristics of the common-base configuration. For this very reason, common-base high-frequency parameters rather than common-emitter parameters are often specified for a transistor especially those designed specifically to operate in the high-frequency regions.

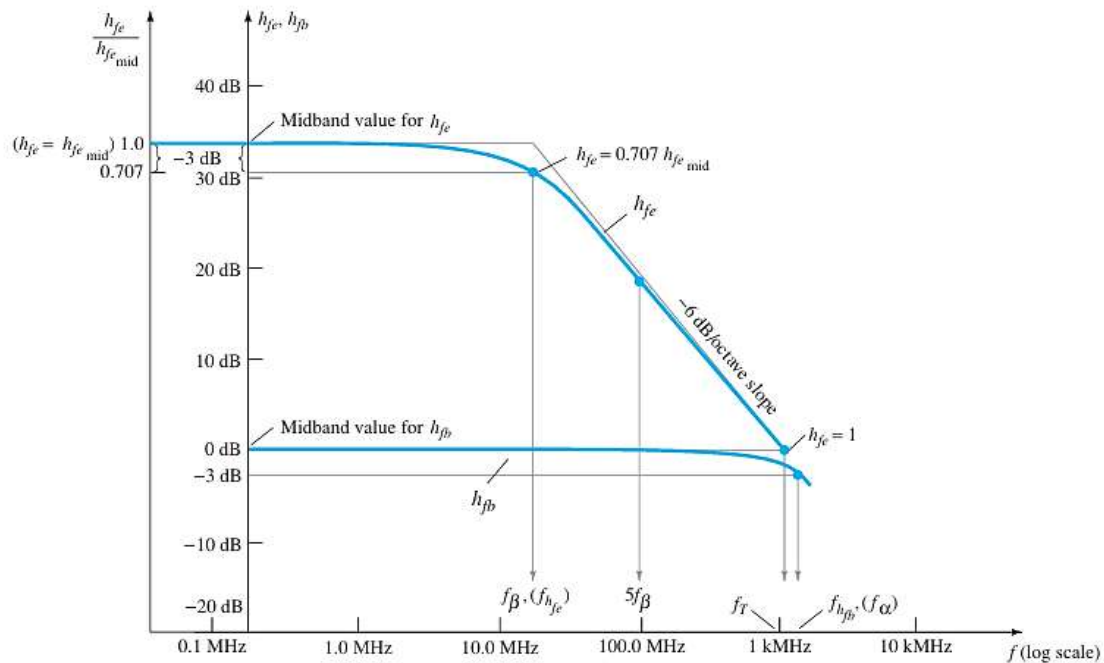


Fig.11. h_{fe} and h_{fb} versus frequency in the high-frequency region.

The following equation permits a direct conversion for determining f_{β} if f_{α} and α are specified:

$$f_{\beta} = f_{\alpha}(1 - \alpha)$$

There is a Figure of Merit applied to amplifiers called the Gain-Bandwidth Product (GBP) that is commonly used to initiate the design process of an amplifier. It provides 581 important information about the relationship between the gain of the amplifier and the expected operating frequency range. In Fig. 9.52 the frequency response of an amplifier with a gain of 100, a low cutoff frequency of 250 Hz, and an upper cutoff frequency of 1 MHz has been plotted on a linear scale rather than the typical log scale. Note that because a linear scale was chosen for the horizontal axis it is impossible to show the low cutoff frequency, and the curve appears as essentially a straight vertical line at $f = 0$ Hz. Because $f = 0$ Hz.

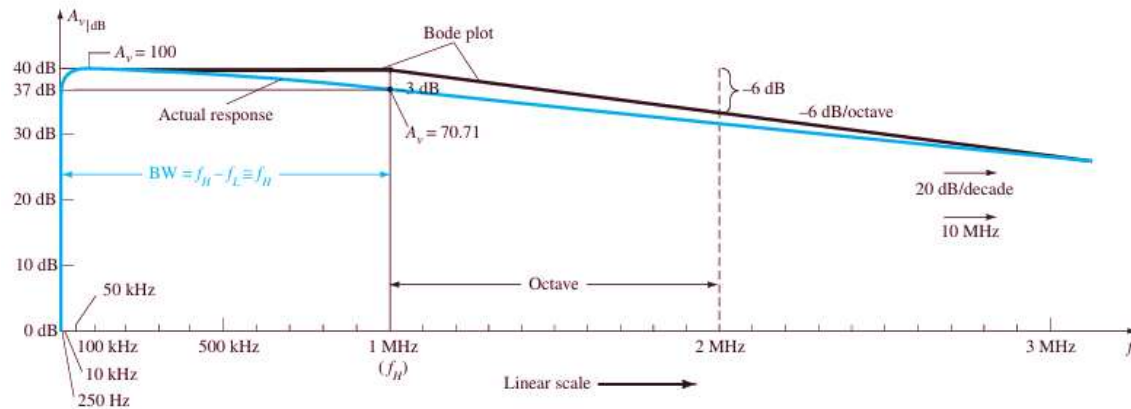


Fig.12. Plotting the dB gain of an amplifier in a linear-frequency plot.

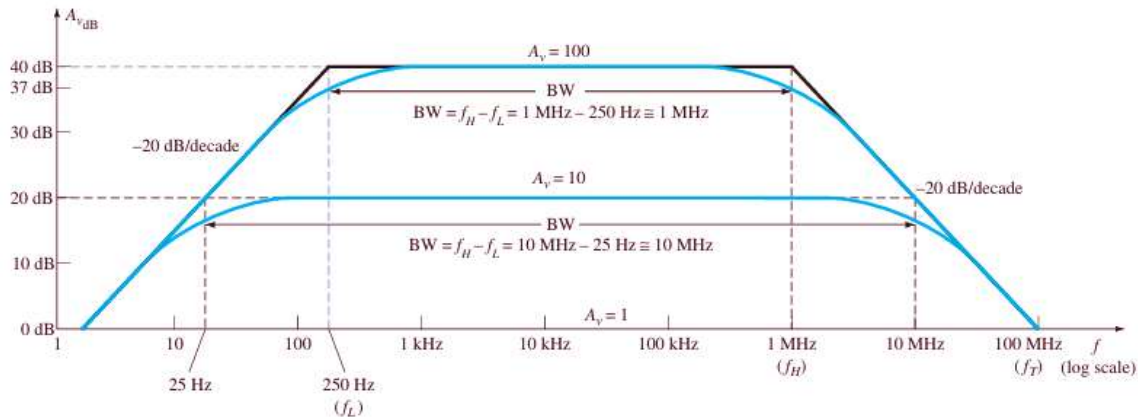


Fig.13. Finding the bandwidth at two different gain levels.

The gain-bandwidth product is

$$\text{GBP} = A_{v_{\text{mid}}} \text{BW}$$

which for this example is

$$\text{GBP} = (100)(1 \text{ MHz}) = 100 \text{ MHz}$$

At $A_v = 10$, $20 \log_{10} 10 = 20$ and the bandwidth as shown in Fig. 9.53 is approximately 10 MHz.

The resulting gain-bandwidth product is now

$$\text{GBP} = (10)(10 \text{ MHz}) = 100 \text{ MHz}$$

In fact, at any level of gain the product of the two remains a constant.

At $A_v = 1$ or $A_v|_{\text{dB}} = 0$ bandwidth is defined as f_T in Fig. 9.53.

In general,

the frequency f_T is called the unity-gain frequency and is always equal to the product of the midband gain of an amplifier and the bandwidth at any level of gain.

That is,

$$f_T = A_{v_{\text{mid}}} f_H \quad (\text{Hz})$$



The general equation for the hfe variation with frequency is defined by Eq. For the amplifier it is defined by:

$$A_v = \frac{A_{v_{mid}}}{1 + j(f/f_H)}$$

Note that in each case the frequency f_H defines the corner frequency. Substituting Eq. above for f_β in Eq below gives:

$$f_T = h_{fe_{mod}} \frac{1}{2\pi h_{fe_{mod}} r_e (C_\pi + C_u)}$$

$$f_T \cong \frac{1}{2\pi r_e (C_\pi + C_u)}$$

Example 3: Use the network of Fig.1. with the same parameters as in

Example.1, that is,

$R_s = 1 \text{ k}\Omega$, $R_1 = 40 \text{ k}\Omega$, $R_2 = 10 \text{ k}\Omega$,

$R_E = 2 \text{ k}\Omega$, $R_C = 4 \text{ k}\Omega$, $R_L = 2.2 \text{ k}\Omega$

$C_s = 10 \text{ mF}$, $C_c = 1 \text{ mF}$, $C_E = 20 \text{ mF}$

$hfe = 100$, $r_o = \infty$, $V_{CC} = 20 \text{ V}$

with the addition of $C_\pi(C_{be}) = 36 \text{ pF}$, $C_u(C_{bc}) = 4 \text{ pF}$, $C_{ce} = 1 \text{ pF}$, $C_{wi} = 6 \text{ pF}$,

$C_{wo} = 8 \text{ pF}$

- Determine f_{Hi} and f_{Ho} .
- Find f_β and f_T .
- Sketch the frequency response for the low- and high-frequency regions using the results of Example 1 and the results of parts (a) and (b).



Sol/

a. From Example 9.12:

$$\beta r_e = 1.576 \text{ k}\Omega, \quad A_{v_{mid}}(\text{amplifier—not including effects of } R_s) = -90$$

$$\text{and} \quad R_{Th} = R_s \parallel R_1 \parallel R_2 \parallel \beta r_e = 1 \text{ k}\Omega \parallel 40 \text{ k}\Omega \parallel 10 \text{ k}\Omega \parallel 1.576 \text{ k}\Omega \\ \cong 0.57 \text{ k}\Omega$$

$$\text{with} \quad C_i = C_{W_i} + C_{be} + (1 - A_v)C_{bc} \\ = 6 \text{ pF} + 36 \text{ pF} + [1 - (-90)]4 \text{ pF} \\ = 406 \text{ pF}$$

$$f_{H_i} = \frac{1}{2\pi R_{Th} C_i} = \frac{1}{2\pi (0.57 \text{ k}\Omega)(406 \text{ pF})} \\ = 687.73 \text{ kHz}$$

$$R_{Th_o} = R_C \parallel R_L = 4 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega = 1.419 \text{ k}\Omega$$

$$C_o = C_{W_o} + C_{ce} + C_{M_o} = 8 \text{ pF} + 1 \text{ pF} + \left(1 - \frac{1}{-90}\right)4 \text{ pF} \\ = 13.04 \text{ pF}$$

$$f_{H_o} = \frac{1}{2\pi R_{Th_o} C_o} = \frac{1}{2\pi (1.419 \text{ k}\Omega)(13.04 \text{ pF})} \\ = 8.6 \text{ MHz}$$

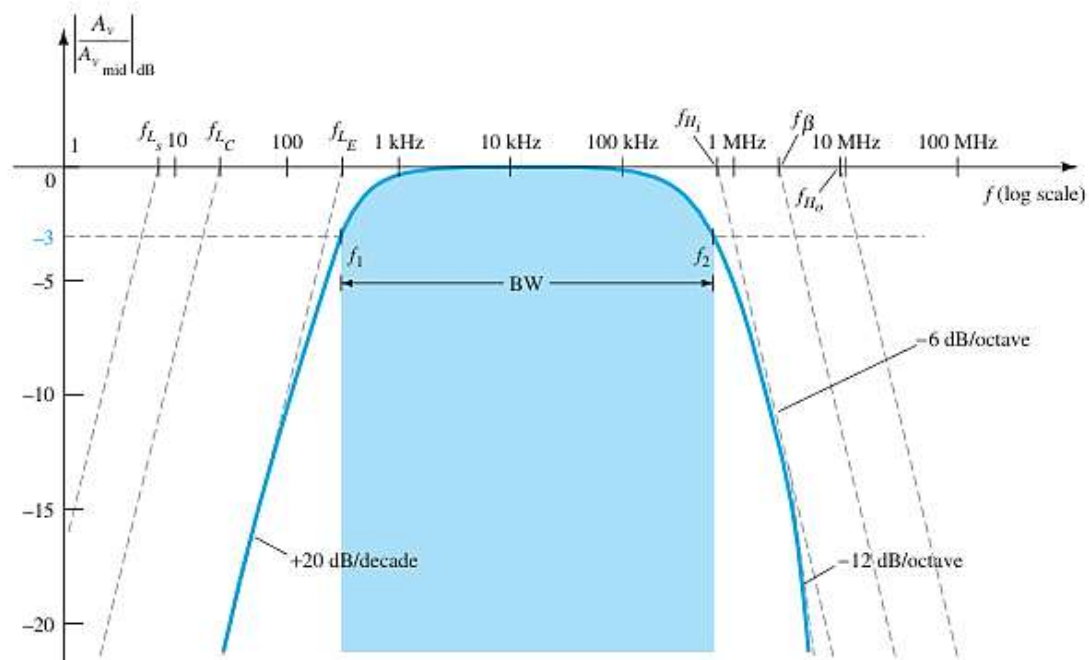


Fig.14. Full frequency response for the network



b. Applying Eq. (9.63) gives

$$\begin{aligned} f_{\beta} &= \frac{1}{2\pi h_{fe_{mid}} r_e (C_{be} + C_{bc})} \\ &= \frac{1}{2\pi(100)(15.76 \Omega)(36 \text{ pF} + 4 \text{ pF})} = \frac{1}{2\pi(100)(15.76 \Omega)(40 \text{ pF})} \\ &= \mathbf{2.52 \text{ MHz}} \\ f_T &= h_{fe_{mid}} f_{\beta} = (100)(2.52 \text{ MHz}) \\ &= \mathbf{252 \text{ MHz}} \end{aligned}$$

c. See Fig 14 The corner frequency f_{H_i} will determine the high cutoff frequency and the bandwidth of the amplifier. The upper cutoff frequency is very close to 600 kHz.

1.5. Low Frequency Response FET Amplifier

The analysis of the FET amplifier in the low-frequency region will be quite similar to that of the BJT amplifier. There are again three capacitors of primary concern as appearing in the network of Fig.15. C_G , C_c , and C_s .

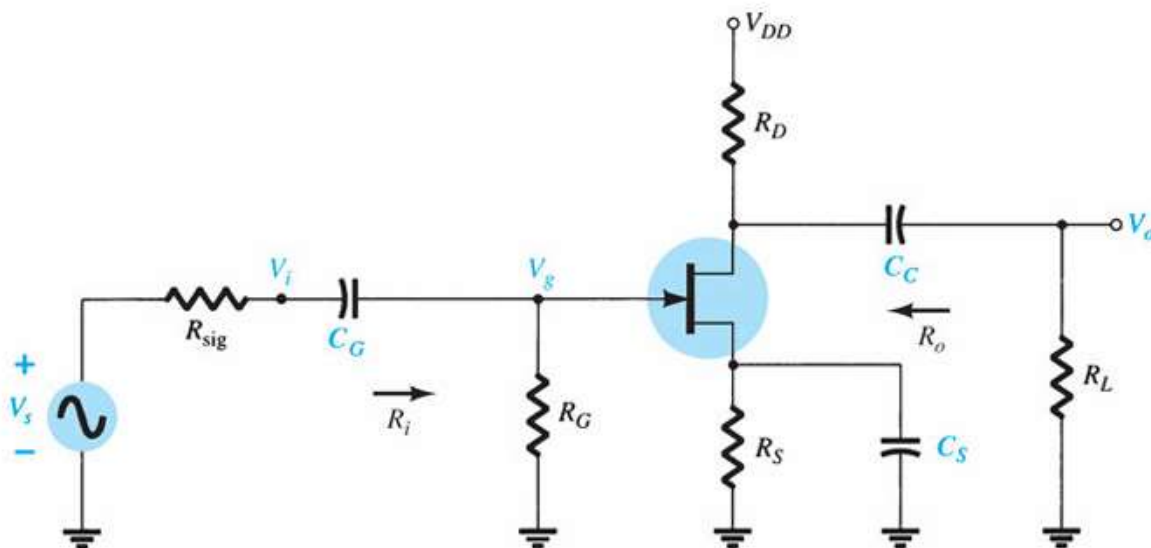


Fig.15. Capacitive elements that affect the low-frequency response of a JFET amplifier.



CG For the coupling capacitor between the source and the active device, the ac equivalent network is as shown in Fig. 16. The cutoff frequency determined by **CG** is:

$$f_{LG} = \frac{1}{2\pi(R_{sig} + R_i)C_G}$$

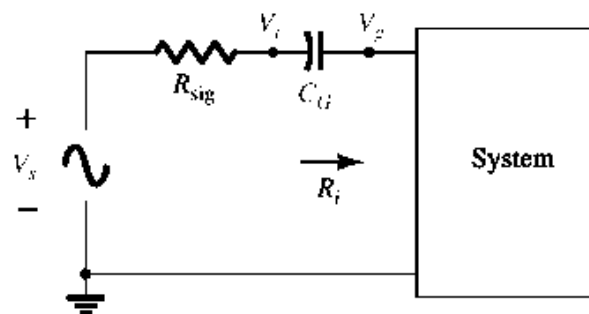


Fig.16. Determining the effect of C_G on the low-frequency response.

$$R_i = R_G$$

Typically, $R_G \gg R_{sig}$, and the lower cutoff frequency is determined primarily by R_G and C_G . The fact that R_G is so large permits a relatively low level of C_G while maintaining a low cutoff frequency level for f_{LG} .

CC For the coupling capacitor between the active device and the load the network of Fig.17.results. The resulting cutoff frequency is:

$$f_{LC} = \frac{1}{2\pi(R_o + R_L)C_C}$$

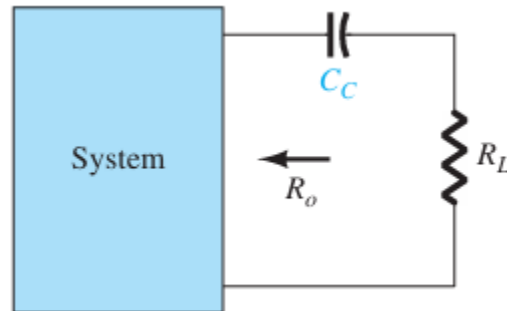


Fig.17. RL Determining the effect of Cc on the low-frequency response.

For the source capacitor C_S , the resistance level of importance. The cutoff frequency is defined by:

$$f_{Ls} = \frac{1}{2\pi R_{eq} C_S}$$

the resulting value of R_{eq} is

$$R_{eq} = \frac{R_S}{1 + R_S(1 + g_m r_d)/(r_d + R_D \parallel R_L)}$$

which for $r_d \cong \infty \Omega$ becomes

$$R_{eq} = R_S \parallel \frac{1}{g_m} \quad r_d \cong \infty \Omega$$



Example 4:

Determine the lower cutoff frequency for the network of Fig. 15 using the following parameters:

$$\begin{aligned} C_G &= 0.01 \mu\text{F}, \quad C_C = 0.5 \mu\text{F}, \quad C_S = 2 \mu\text{F} \\ R_{\text{sig}} &= 10 \text{ k}\Omega, \quad R_G = 1 \text{ M}\Omega, \quad R_D = 4.7 \text{ k}\Omega, \quad R_S = 1 \text{ k}\Omega, \quad R_L = 2.2 \text{ k}\Omega \\ I_{DSS} &= 8 \text{ mA}, \quad V_P = -4 \text{ V}, \quad r_d = \infty \Omega, \quad V_{DD} = 20 \text{ V} \end{aligned}$$

Sol

DC analysis: Plotting the transfer curve of $I_D = I_{DSS}(1 - V_{GS}/V_P)^2$ and superimposing the curve defined by $V_{GS} = -I_D R_S$ results in an intersection at $V_{GS_Q} = -2 \text{ V}$ and $I_{D_Q} = 2 \text{ mA}$. In addition,

$$g_{m0} = \frac{2I_{DSS}}{|V_P|} = \frac{2(8 \text{ mA})}{4 \text{ V}} = 4 \text{ mS}$$

$$g_m = g_{m0} \left(1 - \frac{V_{GS_Q}}{V_P} \right) = 4 \text{ mS} \left(1 - \frac{-2 \text{ V}}{-4 \text{ V}} \right) = 2 \text{ mS}$$

$$C_G \quad f_{L_G} = \frac{1}{2\pi(R_{\text{sig}} + R_i)C_G} = \frac{1}{2\pi(10 \text{ k}\Omega + 1 \text{ M}\Omega)(0.01 \mu\text{F})} \cong 15.8 \text{ Hz}$$

$$C_C \quad f_{L_C} = \frac{1}{2\pi(R_o + R_L)C_C} = \frac{1}{2\pi(4.7 \text{ k}\Omega + 2.2 \text{ k}\Omega)(0.5 \mu\text{F})} \cong 46.13 \text{ Hz}$$


$$C_S \quad R_{\text{eq}} = R_S \parallel \frac{1}{g_m} = 1 \text{ k}\Omega \parallel \frac{1}{2 \text{ mS}} = 1 \text{ k}\Omega \parallel 0.5 \text{ k}\Omega = 333.33 \Omega$$

$$\text{Eq. (9.40): } f_{L_S} = \frac{1}{2\pi R_{\text{eq}} C_S} = \frac{1}{2\pi(333.33 \Omega)(2 \mu\text{F})} = 238.73 \text{ Hz}$$



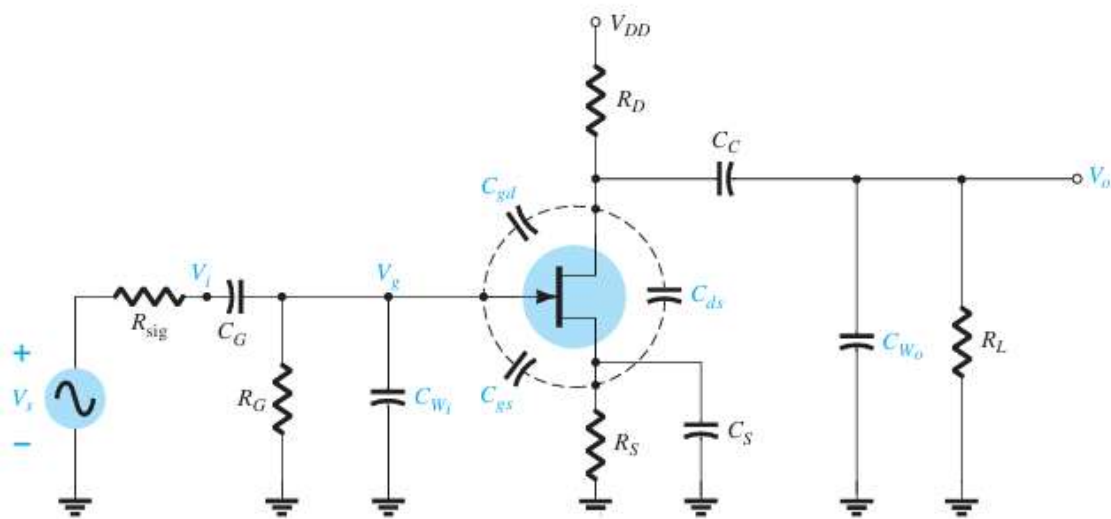1.5. High Frequency Response FET Amplifier

The analysis of the high-frequency response of the FET amplifier will proceed in a very similar manner to that encountered for the BJT amplifier. As shown in Fig. 18, there are interelectrode and wiring capacitances that will determine the high-frequency characteristics of the amplifier. The capacitors C_{gs} and C_{gd} typically vary from 1 pF to 10 pF, whereas the capacitance C_{ds} is usually quite a bit smaller, ranging from 0.1 pF to 1 pF.



Capacitive elements that affect the high-frequency response of a JFET amplifier.

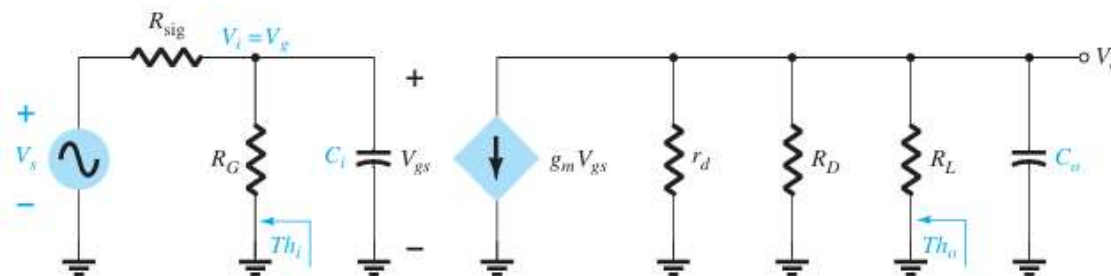


Fig.18. High-frequency ac equivalent circuit



The cutoff frequencies defined by the input and output circuits can be obtained by first finding the Thevenin equivalent circuits for each section as shown in Fig.

18. For the input circuit,

$$f_{H_i} = \frac{1}{2\pi R_{Th_i} C_i}$$

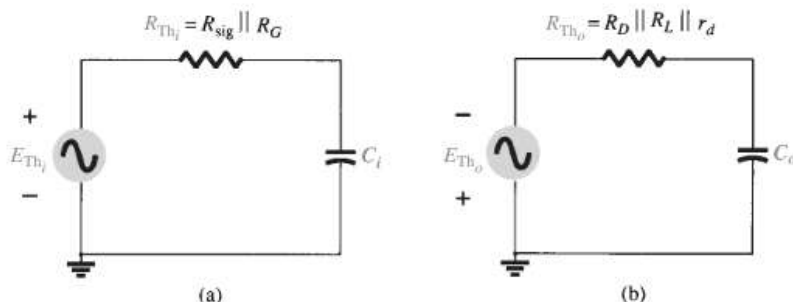


Fig.18. The Thevenin equivalent circuits for: (a) the input circuit and (b) the output circuit.

and

$$R_{Th_i} = R_{sig} || R_G$$

with

$$C_i = C_{W_i} + C_{gs} + C_{M_i}$$

and

$$C_{M_i} = (1 - A_v)C_{gd}$$

for the output circuit,

$$f_{H_o} = \frac{1}{2\pi R_{Th_o} C_o}$$

with

$$R_{Th_o} = R_D || R_L || r_d$$

and

$$C_o = C_{W_o} + C_{ds} + C_{M_o}$$

and

$$C_{M_o} = \left(1 - \frac{1}{A_v}\right)C_{gd}$$



Homework

Determine the high-cutoff frequencies for the network of Fig.18. using the same parameters as Example 4:

$$\begin{aligned}C_G &= 0.01 \mu\text{F}, & C_C &= 0.5 \mu\text{F}, & C_S &= 2 \mu\text{F} \\R_{\text{sig}} &= 10 \text{ k}\Omega, & R_G &= 1 \text{ M}\Omega, & R_D &= 4.7 \text{ k}\Omega, & R_S &= 1 \text{ k}\Omega, & R_L &= 2.2 \text{ k}\Omega \\I_{DSS} &= 8 \text{ mA}, & V_P &= -4 \text{ V}, & r_d &= \infty \Omega, & V_{DD} &= 20 \text{ V} \\&\text{with the addition of} \\C_{gd} &= 2 \text{ pF}, & C_{gs} &= 4 \text{ pF}, & C_{ds} &= 0.5 \text{ pF}, & C_{W_i} &= 5 \text{ pF}, & C_{W_o} &= 6 \text{ pF}\end{aligned}$$