



COLLEGE OF ENGINEERING AND TECHNOLOGIES
ALMUSTAQBAL UNIVERSITY

Electronics Circuits
CTE 204

Lecture 8

- OP AMP CIRCUITS -
(2024 - 2025)

Dr. Zaidoon AL-Shammari


Lecturer / Researcher

zaidoon.waleed@mustaqbal-college.edu.iq

- The op-amp can be connected in a large number of circuits to provide various operating characteristics.
- In this section, we cover a few of the most common of these circuit connections.

Inverting Amplifier

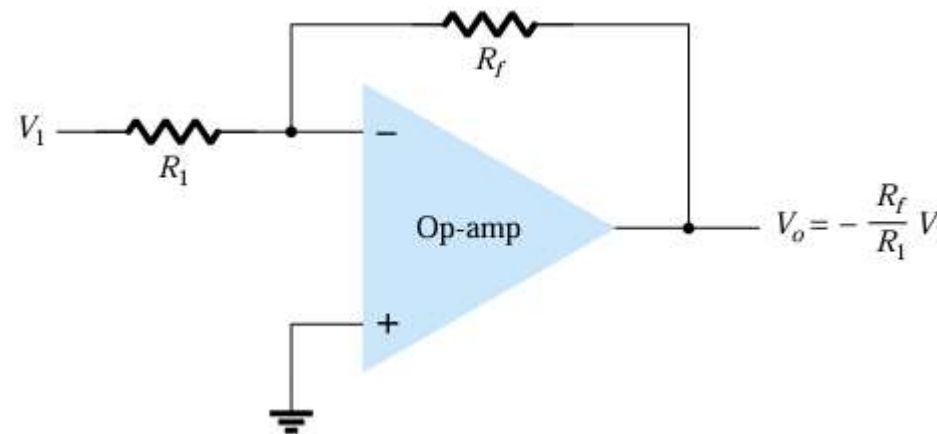- In this and the following sections, we consider some useful op amp circuits that often serve as modules for designing more complex circuits.
- The first of such op amp circuits is the inverting amplifier shown in Figure below.



Inverting Amplifier

- In this circuit, the noninverting input is grounded, v_i is connected to the inverting input through R_1 , and the feedback resistor R_f is connected between the inverting input and output.
- Our goal is to obtain the relationship between the input voltage v_i and the output voltage v_o .

Inverting Amplifier

- Applying KCL at node 1,

$$i_1 = i_2 \Rightarrow \frac{v_i - v_1}{R_1} = \frac{v_1 - v_o}{R_f}$$

- But $v_1 = v_2 = 0$ for an ideal op amp, since the noninverting terminal is grounded.
- Hence,


$$\frac{v_i}{R_1} = -\frac{v_o}{R_f}$$

$$v_o = -\frac{R_f}{R_1}v_i$$

- An inverting amplifier reverses the polarity of the input signal while amplifying it.
- Notice that the gain is the feedback resistance divided by the input resistance which means that the gain depends only on the external elements connected to the op amp.

Inverting Amplifier

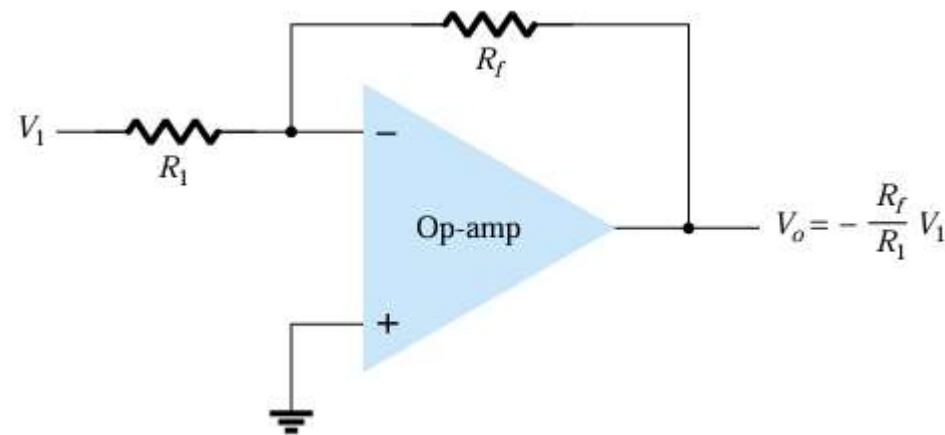Example 1 : If the circuit of Figure below has $R_1 = 100 \text{ k}$ and $R_f = 500 \text{ k}$, what output voltage results for an input of $v_1 = 2\text{v}$?




Solution

$$V_o = -\frac{R_f}{R_1} V_1 = -\frac{500 \text{ k}\Omega}{100 \text{ k}\Omega} (2 \text{ V}) = -\mathbf{10 \text{ V}}$$

Inverting Amplifier

Example 2 : Refer to the op amp in Figure below. If $v_i = 0.5$ V, calculate:

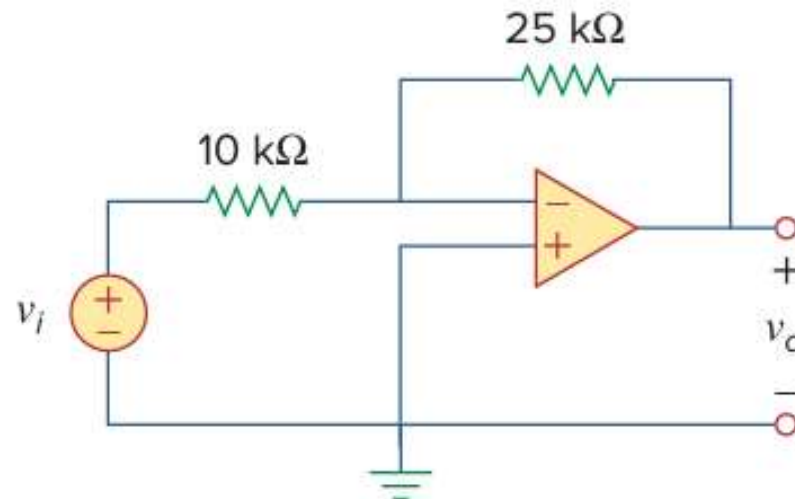- (a) The output voltage v_o .
- (b) The current in the 10-k Ω resistor.



Inverting Amplifier

Solution:

(a)

$$\frac{v_o}{v_i} = -\frac{R_f}{R_1} = -\frac{25}{10} = -2.5$$


$$v_o = -2.5v_i = -2.5(0.5) = -1.25 \text{ V}$$

(b) The current through the 10-k Ω resistor is

$$i = \frac{v_i - 0}{R_1} = \frac{0.5 - 0}{10 \times 10^3} = 50 \mu\text{A}$$

Noninverting Amplifier

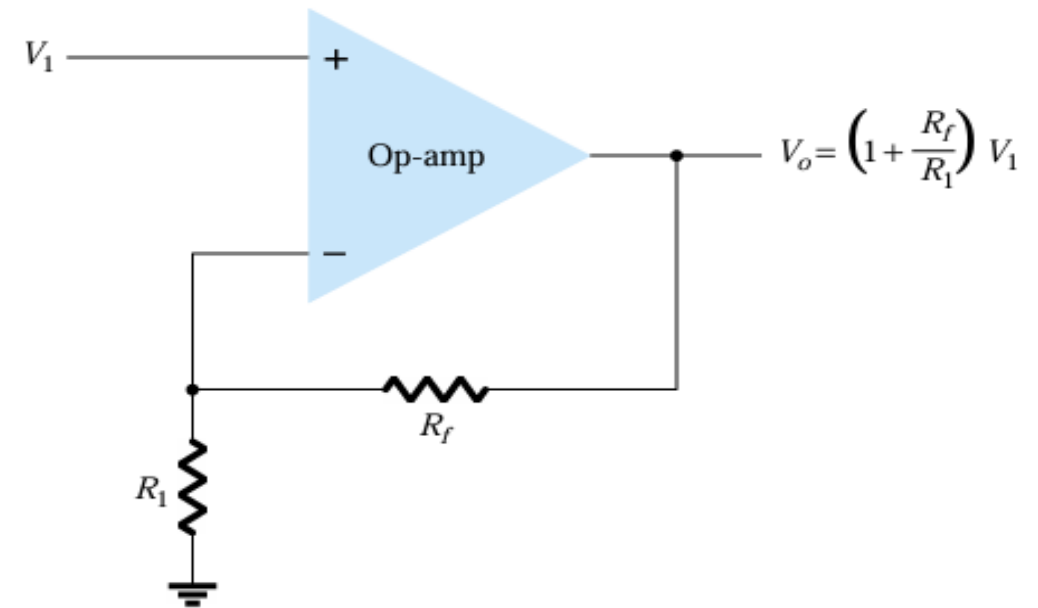- Another important application of the op amp is the noninverting amplifier shown in Figure below.
- In this case, the input voltage v_i is applied directly at the noninverting input terminal, and resistor R_1 is connected between the ground and the inverting terminal.



Noninverting Amplifier

- We are interested in the output voltage and the voltage gain.
- Application of KCL at the inverting terminal gives

$$i_1 = i_2 \Rightarrow \frac{0 - v_1}{R_1} = \frac{v_1 - v_o}{R_f}$$

Noninverting Amplifier

But $v_1 = v_2 = v_i$.

$$\frac{-v_i}{R_1} = \frac{v_i - v_o}{R_f}$$

or


$$v_o = \left(1 + \frac{R_f}{R_1}\right)v_i$$

Noninverting Amplifier

- A noninverting amplifier is an op amp circuit designed to provide a positive voltage gain.
- Again we notice that the gain depends only on the external resistors.
- Notice that if feedback resistor $R_f = 0$ (short circuit) or $R_1 = \infty$ (open circuit) or both, the gain becomes 1.

Noninverting Amplifier

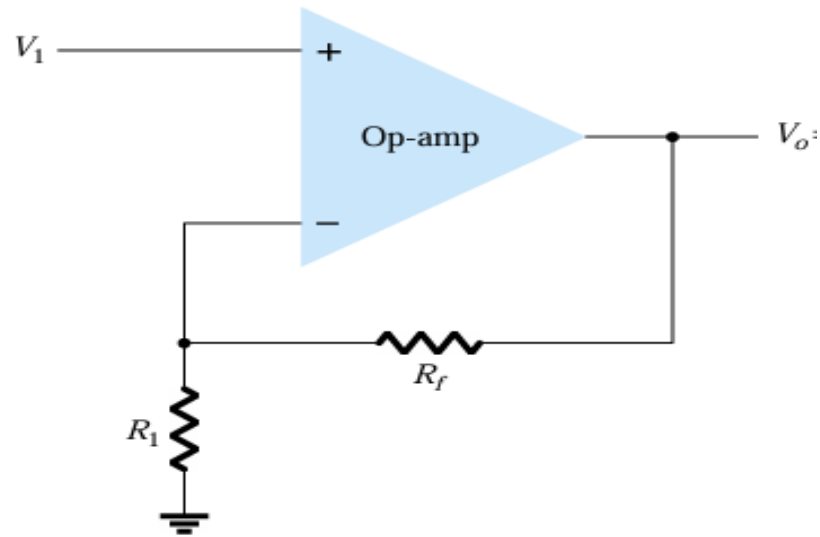Example 3 : Calculate the output voltage of a noninverting amplifier (as shown in Figure below) for values of $V_1 = 2 \text{ V}$, $R_f = 500 \text{ k}$, and $R_1 = 100 \text{ k}$.



Solution

$$V_o = \left(1 + \frac{R_f}{R_1}\right) V_1 = \left(1 + \frac{500 \text{ k}\Omega}{100 \text{ k}\Omega}\right) (2 \text{ V}) = 6(2 \text{ V}) = +12 \text{ V}$$

