



COLLEGE OF ENGINEERING AND TECHNOLOGIES
ALMUSTAQBAL UNIVERSITY

Electronics Circuits
CTE 204

Lecture 6

- Op amp Equivalent Circuit -
(2024 - 2025)


Dr. Zaidoon AL-Shammari

Lecturer / Researcher

zaidoon.waleed@mustaqbal-college.edu.iq

Equivalent Circuit

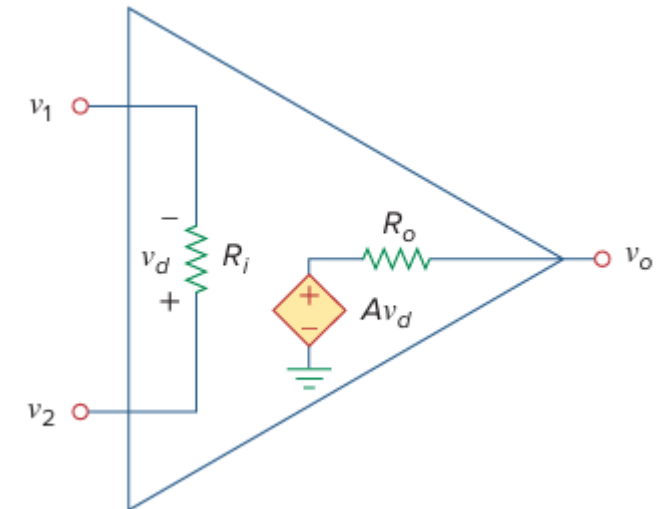
- The equivalent circuit model of an op amp is shown in Figure below.
- The output section consists of a voltage-controlled source in series with the output resistance R_o .



Equivalent Circuit

- It is evident from Figure below that the input resistance R_i is the Thevenin equivalent resistance seen at the input terminals.
- While the output resistance R_o is the Thevenin equivalent resistance seen at the output.
- The differential input voltage V_d is given by


$$V_d = V_2 - V_1$$

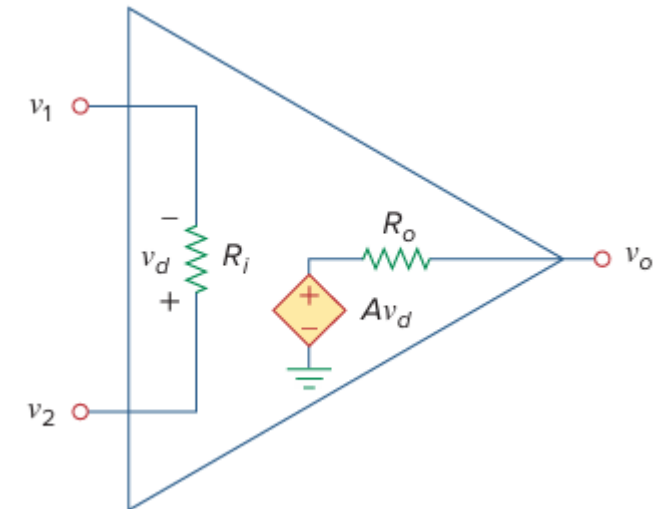

Equivalent Circuit

- Where v_1 is the voltage between the inverting terminal and ground and v_2 is the voltage between the noninverting terminal and ground.
- The op amp senses the difference between the two inputs, multiplies it by the gain A , and causes the resulting voltage to appear at the output.
- Thus, the output V_o is given by

$$v_o = Av_d = A(v_2 - v_1)$$

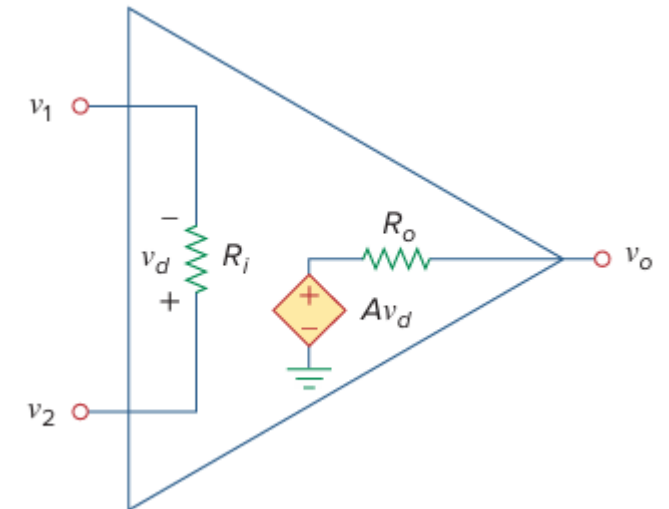

- A is called the open-loop voltage gain because it is the gain of the op amp without any external feedback from output to input.
- Table below shows typical values of voltage gain A , input resistance R_i , output resistance R_o , and supply voltage V_{CC} .


Typical ranges for op amp parameters.

| Parameter | Typical range | Ideal values |
|--------------------------|----------------------------|-----------------|
| Open-loop gain, A | 10^5 to 10^8 | ∞ |
| Input resistance, R_i | 10^5 to $10^{13} \Omega$ | $\infty \Omega$ |
| Output resistance, R_o | 10 to 100Ω | 0Ω |
| Supply voltage, V_{CC} | 5 to 24 V | |

- The concept of feedback is crucial to our understanding of op amp circuits.
- A negative feedback is achieved when the output is fed back to the inverting terminal of the op amp.
- When there is a feedback path from output to input, the ratio of the output voltage to the input voltage is called the closed-loop gain.

- As a result of the negative feedback, it can be shown that the closed-loop gain is almost insensitive to the open-loop gain A of the op amp.
- For this reason, op amps are used in circuits with feedback paths.
- A practical limitation of the op amp is that the magnitude of its output voltage cannot exceed $|V_{CC}|$.

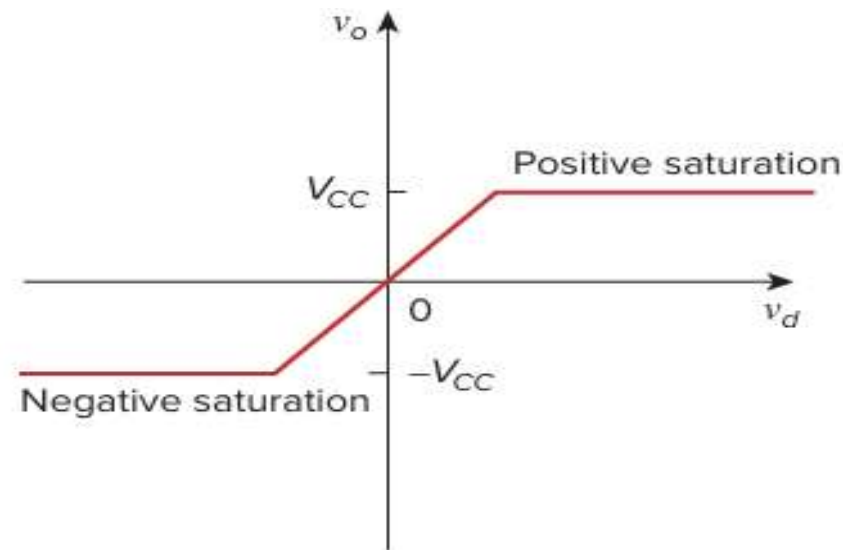- In other words, the output voltage is dependent on and is limited by the power supply voltage.
- Figure below illustrates that the op amp can operate in three modes, depending on the differential input voltage V_d :




Equivalent Circuit

1. Positive saturation, $v_o = V_{CC}$.
2. Linear region, $-V_{CC} \leq v_o = Av_d \leq V_{CC}$.
3. Negative saturation, $v_o = -V_{CC}$.

- If we attempt to increase V_d beyond the linear range, the op amp becomes saturated and yields $V_o = V_{CC}$ or $V_o = -V_{CC}$.
- Throughout this level of study, we will assume that our op amps operate in the linear mode.
- This means that the output voltage is restricted by $-V_{CC} \leq v_o \leq V_{CC}$

Common-Mode Operation

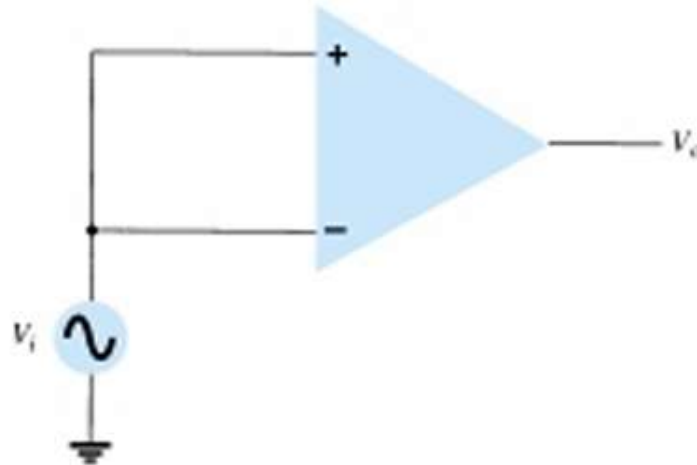
- When the same input signals are applied to both inputs, common-mode operation results, as shown in Figure below.
- Ideally, the two inputs are equally amplified, and since they result in opposite polarity signals at the output, these signals cancel, resulting in (0) V output. Practically, a small output signal will result.



- The difference output is referred to as a floating signal since neither output terminal is the ground (reference) terminal.
- Notice that the difference output is twice as large as either V_{o1} or V_{o2} since they are of opposite polarity and subtracting them results in twice their amplitude [i.e., $10\text{ V} - (-10\text{ V}) = 20\text{ V}$].

Double-Ended Output

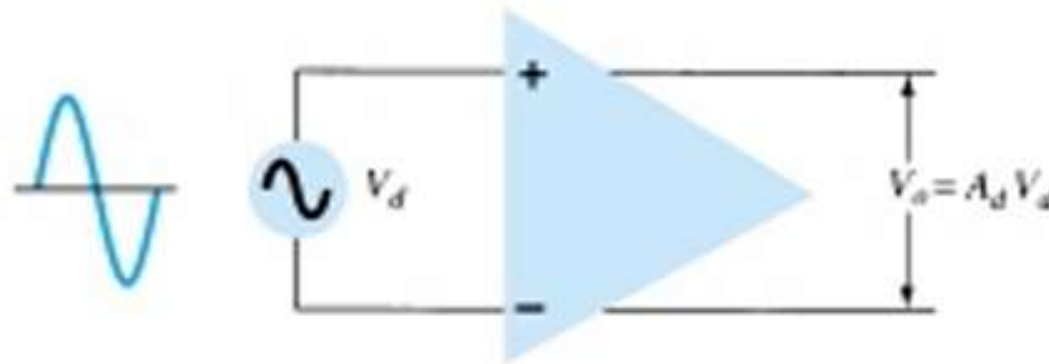- Figure below shows a differential input, differential output operation.
- The input is applied between the two input terminals and the output taken from between the two output terminals.
- This is fully differential operation.




- Having obtained A_d and A_c .
- We can now calculate a value for the common-mode rejection ratio (CMRR).
- Which is defined by the following equation:

$$\text{CMRR} = \frac{A_d}{A_c}$$

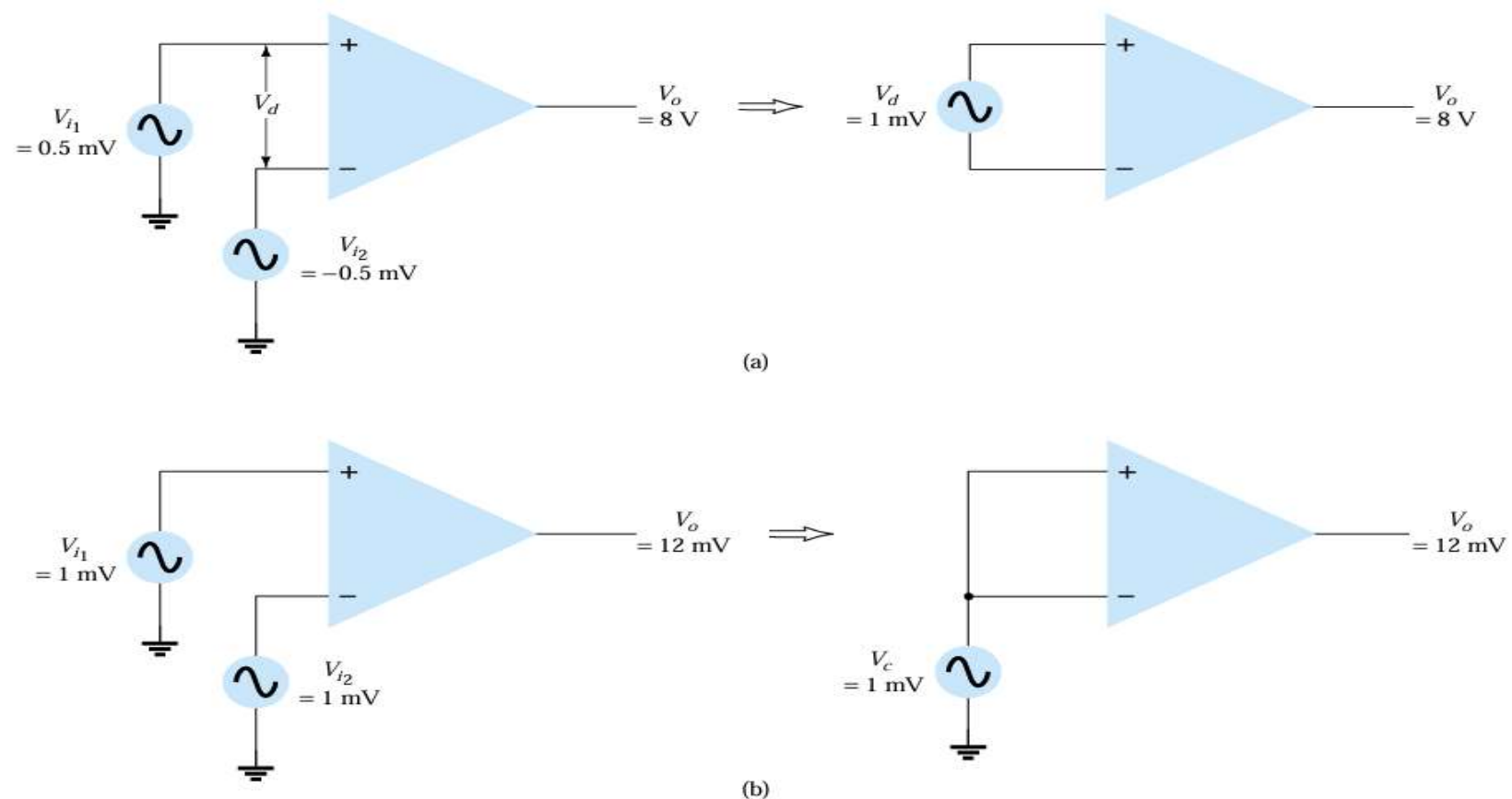Example

Calculate the CMRR for the circuit measurements shown in Figure below



From the measurement shown in Figure a, using the procedure in step 1 above, we obtain

$$A_d = \frac{V_o}{V_d} = \frac{8 \text{ V}}{1 \text{ mV}} = 8000$$

From the measurement shown in Figure b, using the procedure in step 2 above, we obtain

$$A_c = \frac{V_o}{V_c} = \frac{12 \text{ mV}}{1 \text{ mV}} = 12$$

The value of CMRR is

$$\text{CMRR} = \frac{A_d}{A_c} = \frac{8000}{12} = \mathbf{666.7}$$

