

# **Types of ADC**

## Types of A/D Converters

- Flash ADC
- Delta-Sigma ADC
- Dual Slope (integrating) ADC
- Successive Approximation ADC


### 1. Flash A/D Converter

#### **Fundamental Components**

**Resistors** use the resistors to form a ladder voltage divider, which divides the reference voltage into equal intervals.

**Comparators** Consists of a series of comparators, which comparing the input signal to a unique reference voltage.

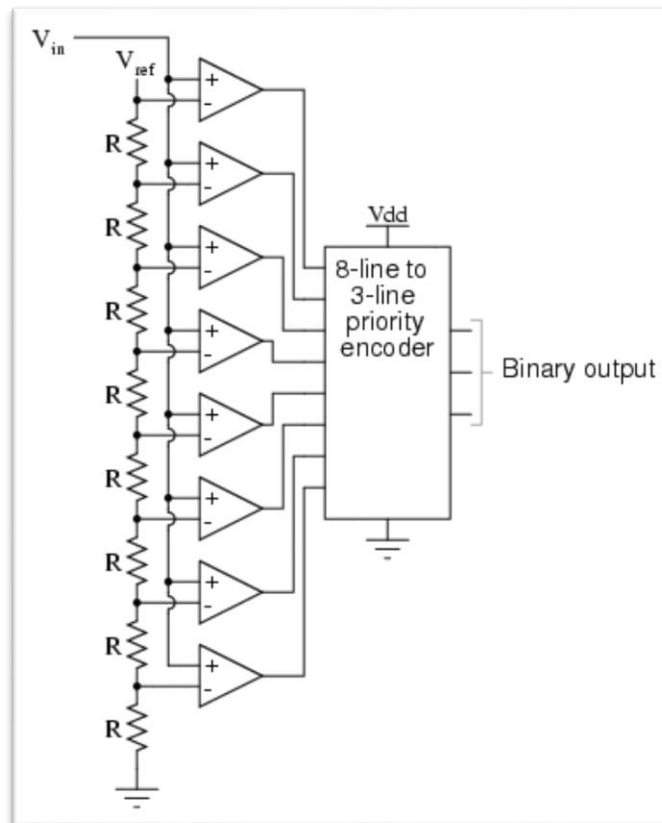**Priority encoder** the comparator outputs connect to the inputs of a priority encoder circuit, which produces a binary output.



#### **How does it work?**

- Uses the comparators to determine in which the input voltage  $V_{in}$  is exceed or not the  $V_{ref}$ .
- When the analog input voltage exceeds the reference voltage at each comparator, the comparator outputs will sequentially saturate to a high state.
- The priority encoder generates a binary number based on the highest-order active input, ignoring all other active inputs.


### Advantages and Disadvantages

- Simplest in terms of operational theory, most efficient in terms of speed (very fast).
- Lower resolution, Expensive, for each additional output bit, the number of comparators is increase.

## 2. Sigma Delta ADC
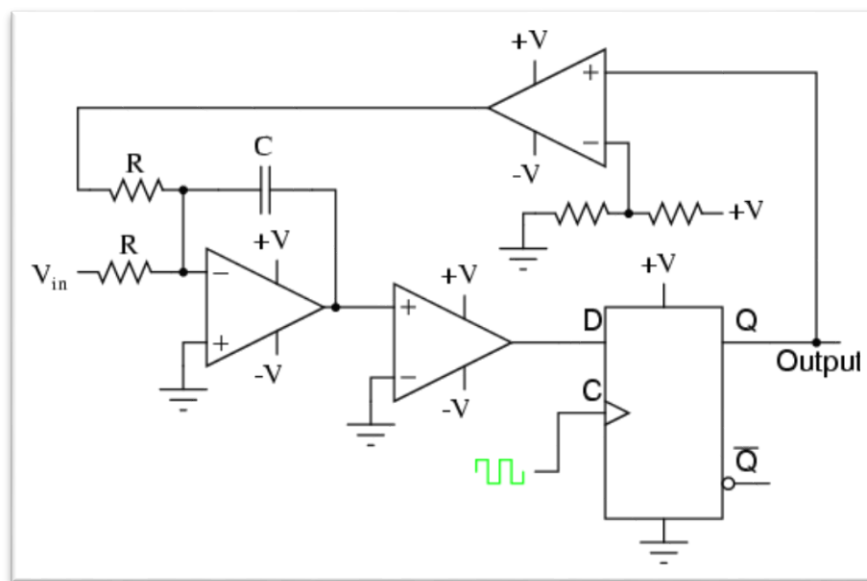
### Main Components

- Resistors
- Integrator
- Capacitor
- Comparators
- Control Logic



### How does it work?

- Input is over sampled, and goes to integrator.
- The integration is then compared to ground.
- Iterates and produces a serial bit stream.
- Output is a serial bit stream which is proportional to  $V_{in}$ .


### Advantages and Disadvantages

- High resolution.
- Slow due to oversampling.

## 3. Dual Slope Converter
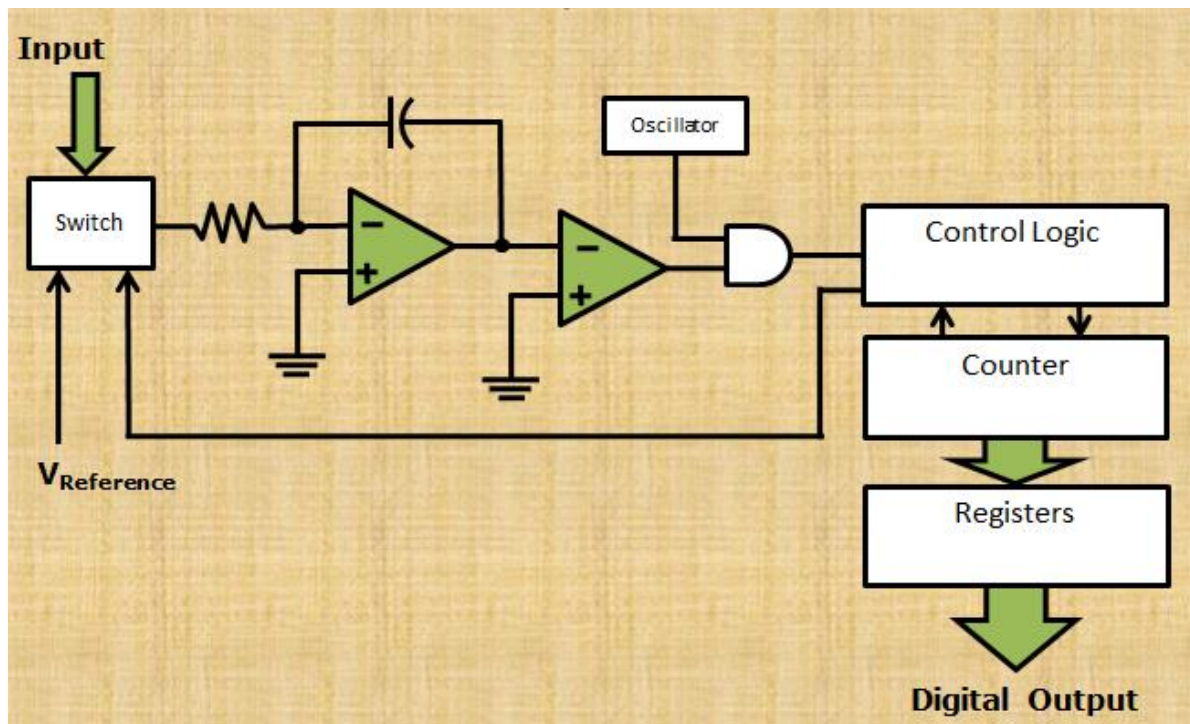
### Fundamental components

- Integrator
- Electronically Controlled Switches
- Counter
- Clock
- Control Logic
- Comparator



#### The Dual Slope ADC functions in this manner:


- When an analog value is applied, the capacitor begins to charge in a linear manner and the oscillator passes to the counter.
- The counter continues to count until it reaches a predetermined value. Once this value is reached the count stops and the counter is reset. The control logic switches the input to the first comparator to a reference voltage, providing a discharge path for the capacitor.
- As the capacitor discharges the counter counts.
- When the capacitor voltage reaches the reference voltage the count stops and the value is stored in the register.

#### Advantages and Disadvantages

- High Accuracy.
- Slow, Cost.
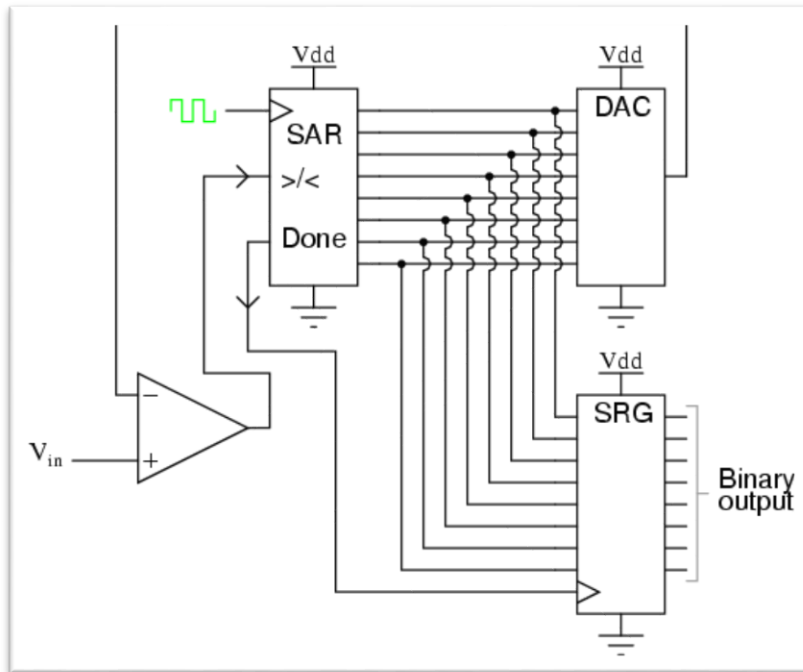
#### 4. Successive Approximation ADC

- Much faster than the Dual Slope.
- A comparator and a DAC are used in the process.
- A Successive Approximation Register (SAR) is added to the circuit
- Instead of counting up in binary sequence, this register counts by trying all values of bits starting with the MSB and finishing at the LSB.
- The register monitors the comparators output to see if the binary count is greater or less than the analog signal input and adjusts the bits accordingly.



### Advantages and Disadvantages

- Capable of high speed and reliable, medium accuracy compared to other ADC types, Good tradeoff between speed and cost.
- Higher resolution successive approximation ADC's will be slower.

### Example

10 bit ADC,  $V_{in} = 0.6$  volts (from analog device),  $V_{ref} = 1$  volts, Find the digital value of  $V_{in}$ ?

**Solu:**

#### ● MSB (bit 9)

- Divided  $V_{ref}$  by 2
- Compare  $V_{ref}/2$  with  $V_{in}$
- If  $V_{in}$  is greater than  $V_{ref}/2$ , turn MSB on (1)
- If  $V_{in}$  is less than  $V_{ref}/2$ , turn MSB off (0)
- $V_{in} = 0.6V$  and  $V = 0.5$
- Since  $V_{in} > V$ , MSB = 1 (on)

1									
---	--	--	--	--	--	--	--	--	--

#### ● Next Calculate MSB-1 (bit 8)

- Compare  $V_{in} = 0.6$  V to  $V = V_{ref}/2 + V_{ref}/4 = 0.5 + 0.25 = 0.75V$
- Since  $0.6 < 0.75$ , MSB is turned off

#### ● Calculate MSB-2 (bit 7)

- Go back to the last voltage that caused it to be turned on (Bit 9) and add it to  $V_{ref}/8$ , and compare with  $V_{in}$
- Compare  $V_{in}$  with  $(0.5 + V_{ref}/8) = 0.625$
- Since  $0.6 < 0.625$ , MSB is turned off

1	0	0							
---	---	---	--	--	--	--	--	--	--

- Calculate the state of MSB-3 (bit 6)
  - Go to the last bit that caused it to be turned on (In this case MSB-1) and add it to  $V_{ref}/16$ , and compare it to  $V_{in}$
  - Compare  $V_{in}$  to  $V = 0.5 + V_{ref}/16 = 0.5625$
  - Since  $0.6 > 0.5625$ , MSB-3=1 (turned on)


MSB	MSB-1	MSB-2	MSB-3	...					
1	0	0	1						

- This process continues for all the remaining bits.

•Digital Results:

MSB	MSB-1	MSB-2	MSB-3	...					LSB
1	0	0	1	1	0	0	1	1	0

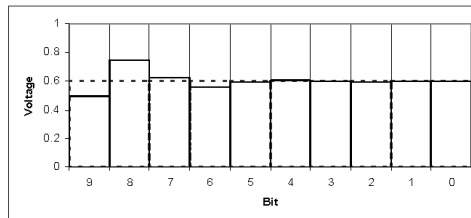•Results:  $\frac{1}{2} + \frac{1}{16} + \frac{1}{32} + \frac{1}{256} + \frac{1}{512} = .599609375 \text{ V}$



## ADC Specifications:

- Conversion time
- Resolution
- Accuracy
- Linearity
- Missing code

**ADC Errors** due to Noise and Aliasing.

## How to choose the ADC according to the resolution?

Two ways for find the resolution needed in ADC, first way is to find the **dynamic range** of input signal and to choose the number of bits based on this.

$N \geq \ln(V_{max}/V_{noise})$  --- dynamic range (stage) (sensor)

Another way to choose the number of bits is based on the **resolution required** in input signal.

$N \geq \ln(S_{max}/S_{noise})$  --- required resolutions (stage before ADC) (transducer)

## Example

A transducer is to be used to find the temperature over a range of 0 to 100 C. we are required to read and display the temperature to a resolution of  $\pm 1$  C. the transducer produces a voltage from 0 to 3v over this temperature range with  $\pm 3$ mv noise. Specify the number of bits in ADC: a) Based on dynamic range. b) Based on required resolutions.

- **Conversion time** is the time required to complete a conversion of the input signal, in other words it's the time it takes for an analog-to-digital conversion.

$$F_{\max} = \frac{1}{2 * \text{Conversion time}}$$

**Ex:**

1. An ADC has a conversion time of 100  $\mu$ s. what is the maximum frequency that can be converted?
2. A 1 KHz sinusoidal signal to be digitized using 8-bit ADC. Find the conversion time that can be used?

- **Resolution** is the number of bits used for conversion (8 bits, 12 bits, ...)

$$\text{resolution} = \frac{\text{full Scale Signal}}{2^n}$$

**Ex:**

An 8-bits ADC is used to digitize a five volt (5v) full scale signal. What is the resolution?

- **Quantization error** is defined as the difference between the actual analog input and the digital representation of that value.

$$\text{Maximum Quantization (q}_{\max}) = \frac{A}{2^{n+1}}$$

$$\text{Average Quantization (q}_{\text{av}}) = \frac{A}{2^{n+2}}$$

Where A is the amplitude and n is the number of bits.

**Ex:**

An analog signal of amplitude 12v is sampled with an 8bit ADC; calculate the maximum and average quantization error?