

**PC Interfacing**

**Fourth Level**


**Lecture 5**

**USB to RS232, USB to  
Parallel Design**

## USB to RS232 circuit design:

The USB to Serial RS232 adapter is very useful in many situations we need to connect a device with RS232 to a computer without RS232 port. Using FT232BM chip manufactured by Future Technology Devices International FTDI we can make a very simple USB to Serial RS232 adapter using few external components. This USB to RS232 adapter based on the FT232BM driver can support many operating systems (windows, mac, Linux).
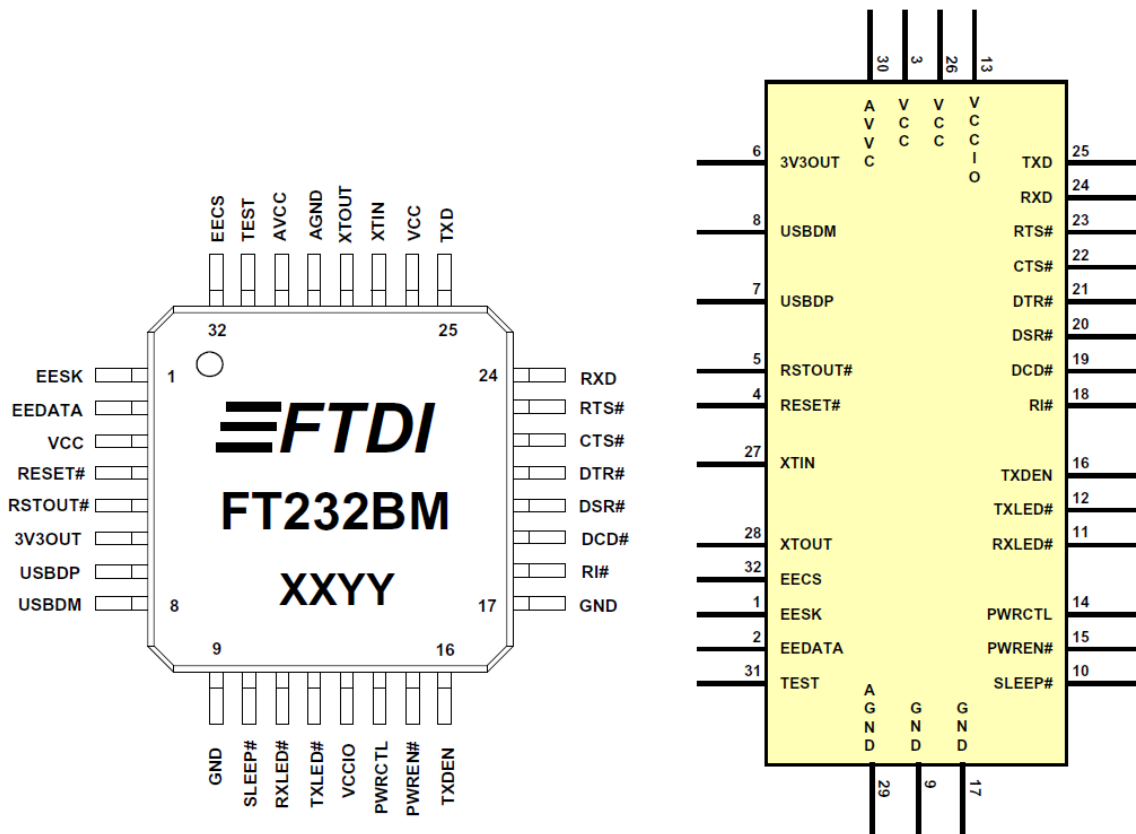
## What is FT232BM? And what is used for?



The FT232BM is a USB to serial UART interface with the following advanced features:


- Consist of 32-pin.
- Compatible with USB 1.1 and USB 2.0
- Single chip USB to asynchronous serial data transfer interface.
- Full Handshaking & Modem Interface Signals.
- UART interface support for 7 or 8 data bits.
- Data transfer rates from 300 baud to 3 M baud at TTL levels.
- 384 byte receive buffer and 128 byte transmit buffer.


## Typical Applications

- USB to RS232 Converters.
- Cellular and Cordless Phone USB data transfer cables and interfaces.
- Interfacing MCU / FPGA based designs to USB.
- USB Smart Card Readers.
- USB Instrumentation.
- USB Industrial Control.
- USB MP3 Player Interface.
- USB FLASH Card Reader and Writers.
- USB Digital Camera Interface.
- USB Hardware Modems.
- USB Wireless Modems.

The FT8U232AM requires a small number of external components to produce a device that converts USB to TTL level RS232 signals. The FT8U232AM and supporting components is also available as a complete module - called a USBMOD1 - in a 32 pin IC, making the whole project very easy to build.

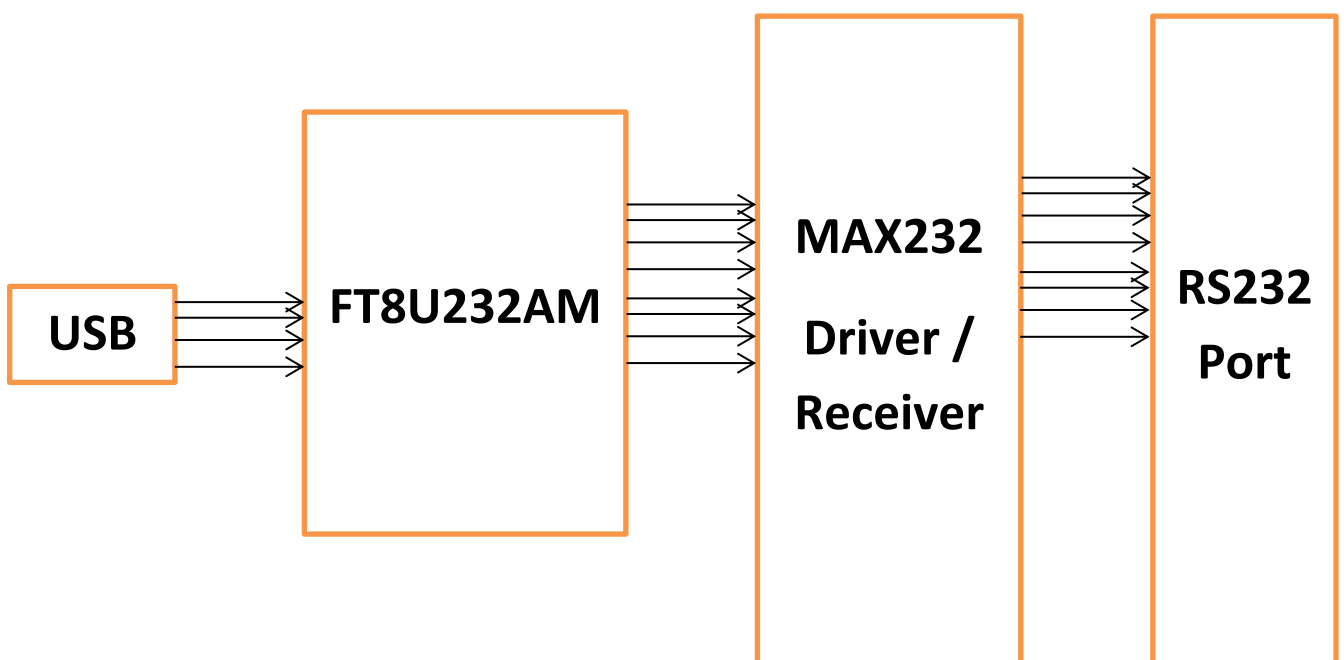
As you can see in the schematic below the circuit is very simple and the voltage needed for the circuit is obtained from the USB port.



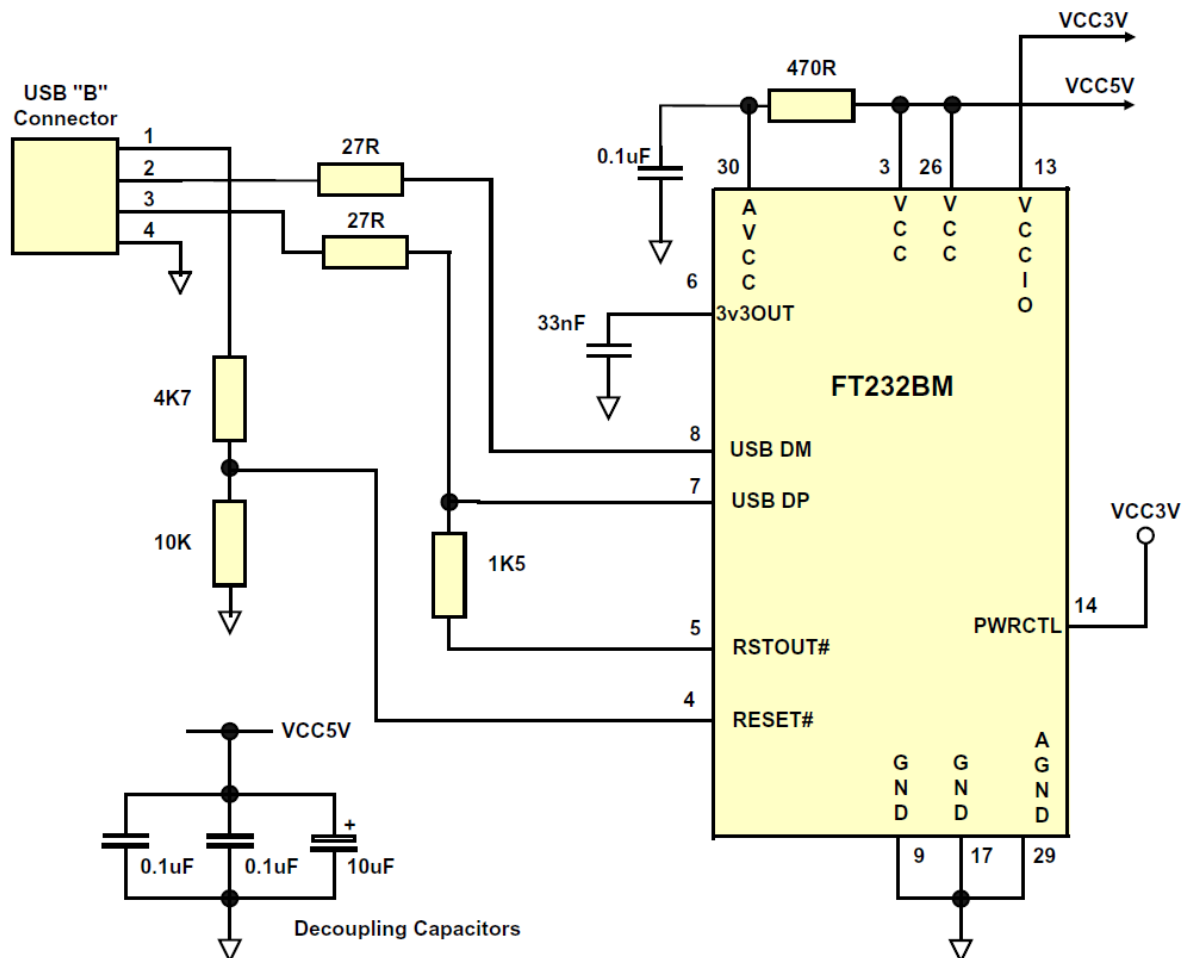

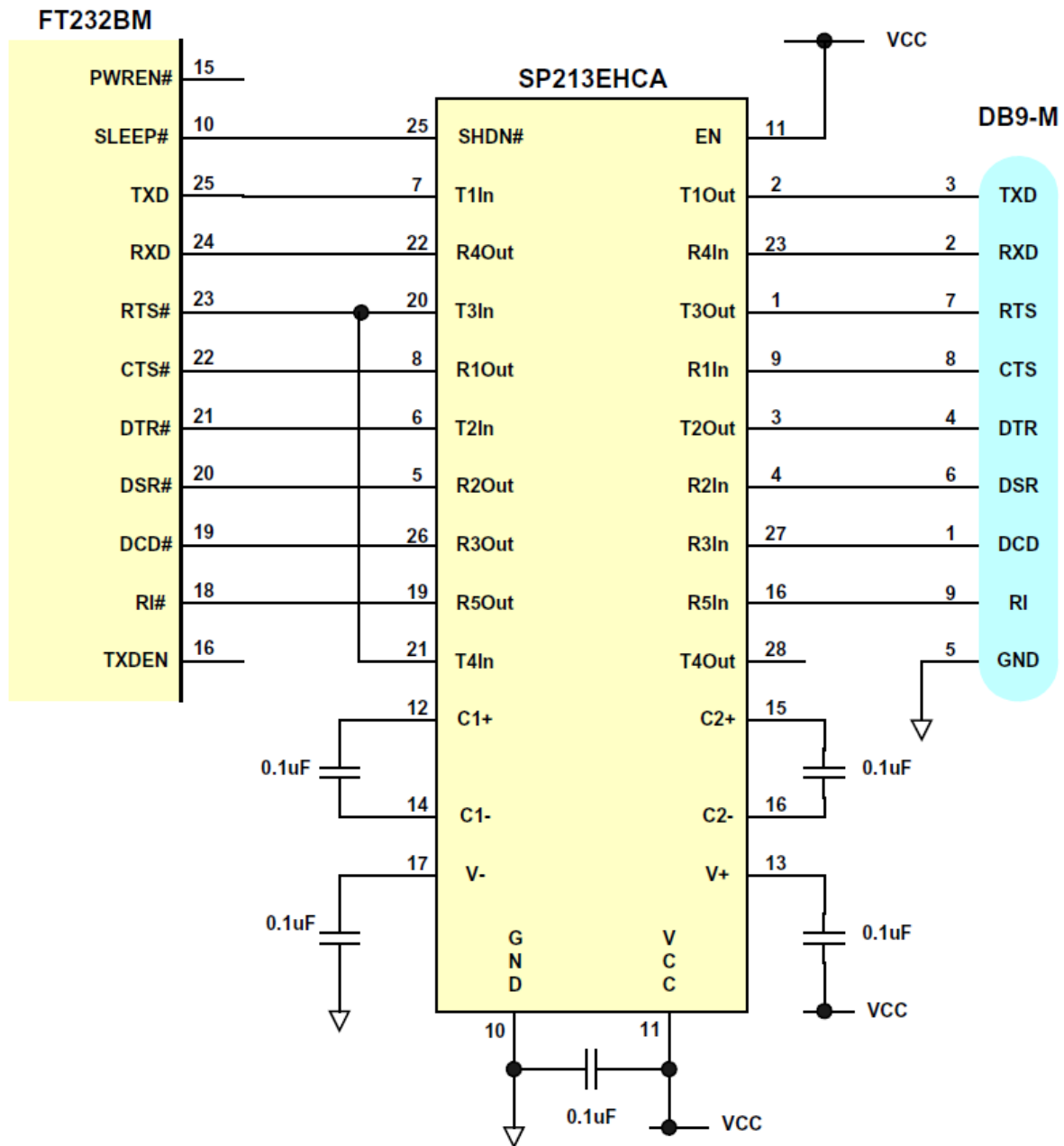
## The second part:

The schematic below explain the connections between FT232BM and RS232 through MAX232.



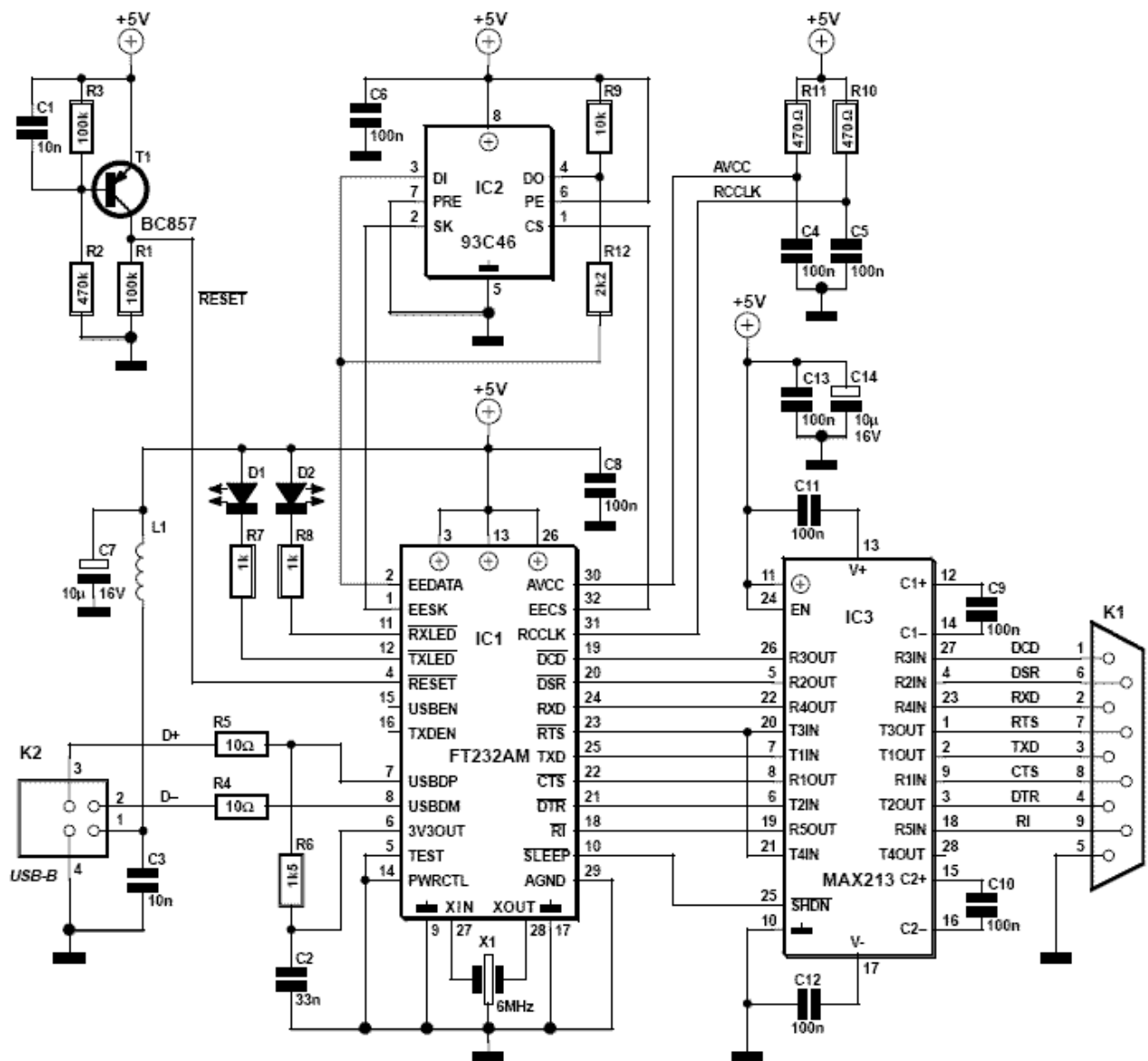The full design with its connections is present in the next page.



The photo of finished Adapter:




## USB to Parallel circuit design:

There are several ways to convert the USB to Parallel:
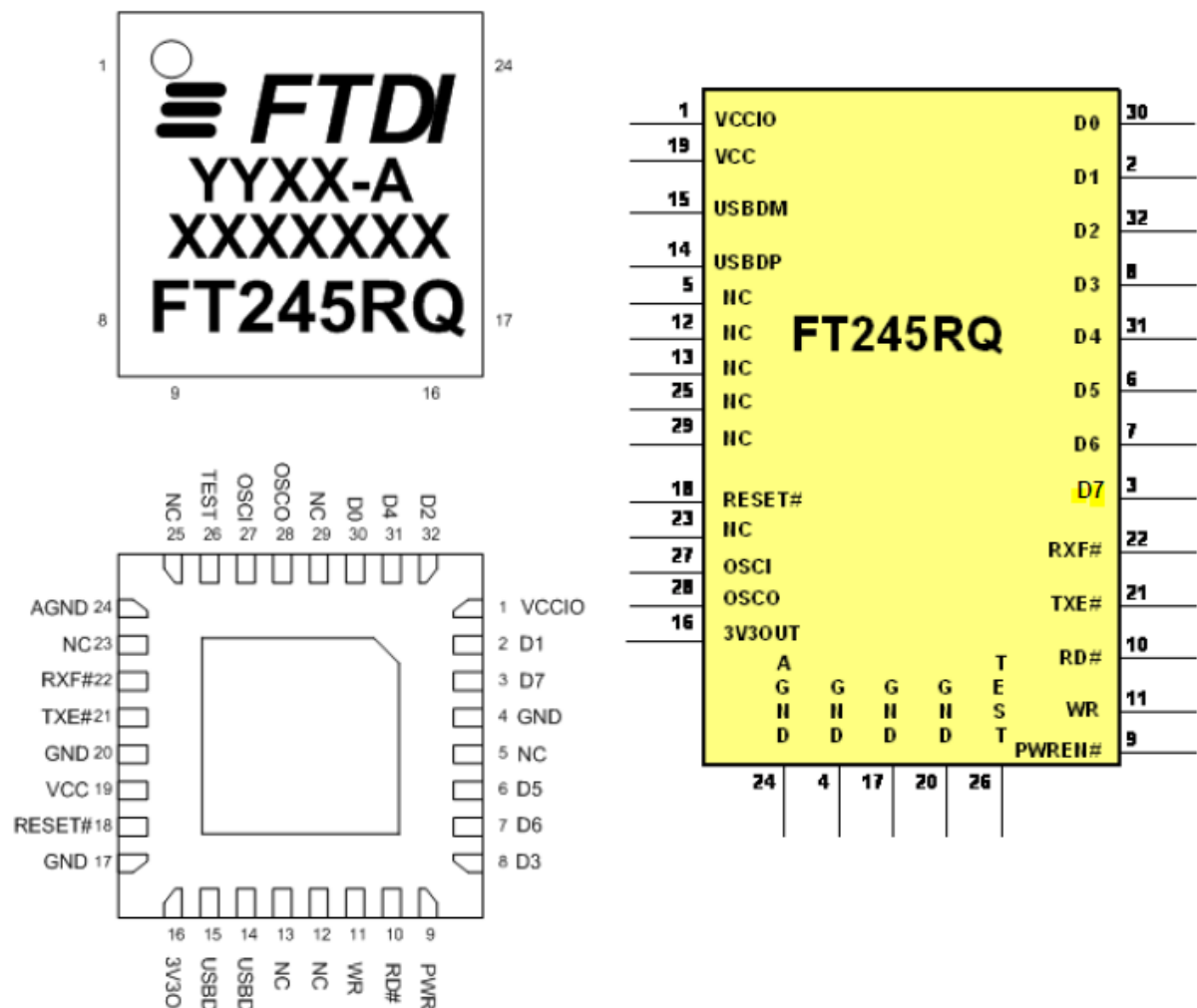
### 1. Using FT245RQ:

The USB to Parallel adapter is very useful in many situations we need to connect a device with Parallel to a computer without Parallel port. Using FT245RQ chip manufactured by Future Technology Devices International FTDI we can make a very simple USB to Parallel adapter using few external components. This USB to Parallel adapter based on the FT245RQ driver can support many operating systems (windows, mac, Linux).



The FT245R is a USB to parallel FIFO interface with the following advanced features:


- Consist of 32-pin.
- Compatible with USB 1.1 and USB 2.0
- Single chip USB to parallel FIFO bidirectional data transfer interface.

- USB protocol handled on the chip. No USB specific firmware programming required.
- Data transfer rates up to 1Mbyte / second.
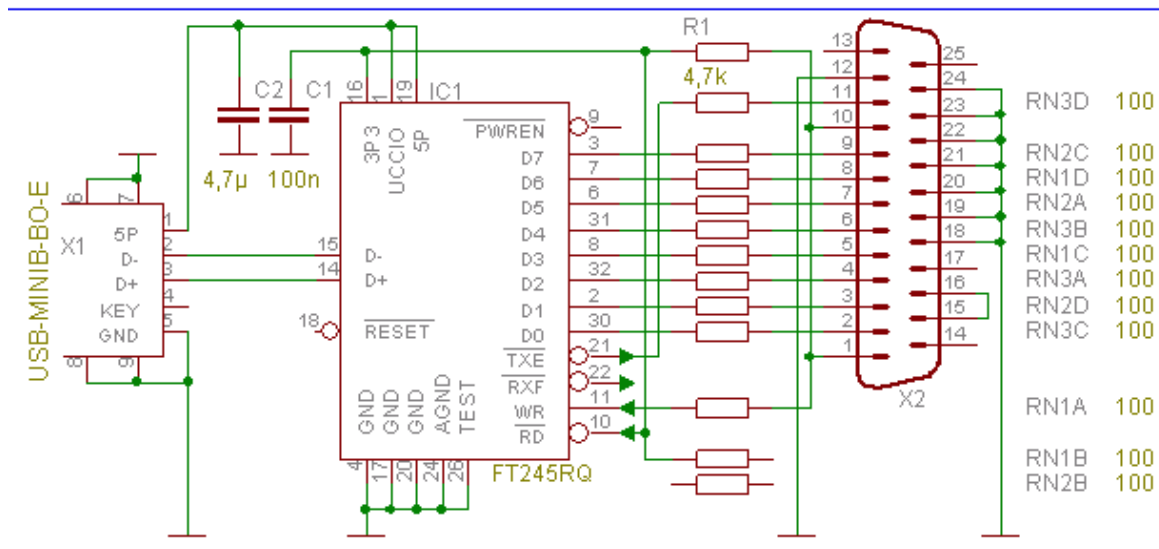
## Typical Applications


Exactly same as FT232BM.

As you can see in the schematic below the circuit is very simple and the voltage needed for the circuit is obtained from the USB port.


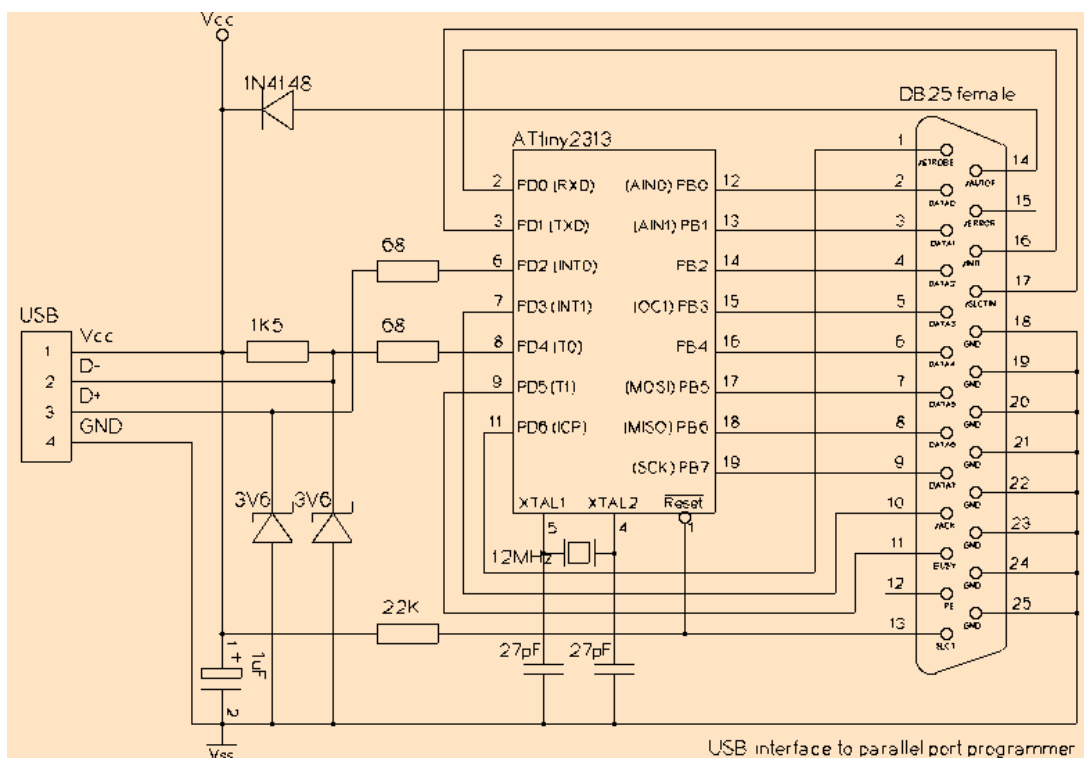
## 2. Using Attiny2313:


The ATtiny2313 is a low-power 8-bit microcontroller.




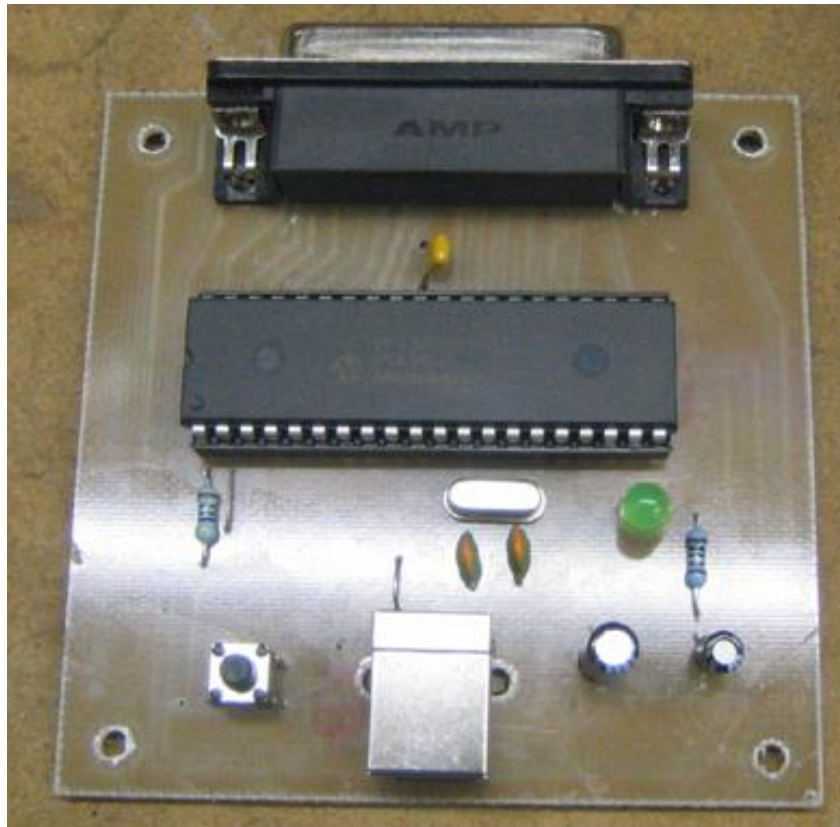
### 3. Using PIC:

Also we can convert the USB to parallel by using PIC microcontroller.



The most commonly used is the first way because it doesn't need any program to convert the data from USB to Parallel, unlike the second and third way.

**The photo of finished Adapter:**

