



Interfacing I/O Devices

❖ I/O devices are the communications channels between the MP and the outside world.

❖ Data transfer

Parallel I/O mode (group of bits transferred simultaneously via group of lines)


Serial I/O mode (one bit is transferred via single line at a time)

❖ Interfacing techniques

Peripheral- mapped I/O

Memory – mapped I/O

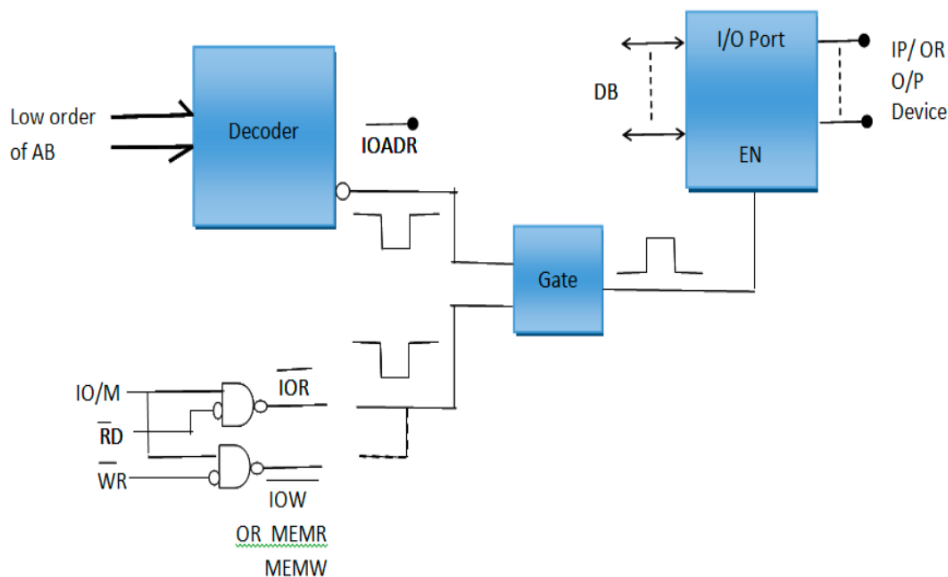❖ Typical block diagram representing the interfacing between MP and I/O device.





Explain:

1. Decoder:

- The low-order address bus (AB) is given as input to the decoder.
- It generates a specific I/O address (IOADR) for the required I/O device.

2. Gate Control:

- The decoder's output is combined with the control signals to enable data transfer.
- It ensures that only the addressed I/O port is activated.

3. I/O Port:

- It serves as an interface between the microprocessor and the input/output device.
- It connects to an external input (IP) or output (OP) device.

4. Control Logic (AND Gates):

- IO/\bar{M} , $R\bar{D}$, and $W\bar{R}$ signals determine whether the operation is a read or write.
- **IOR (I/O Read):** Generated when $IO/\bar{M} = 1$ and $R\bar{D} = 0$, indicating a read operation from an input device.
- **IOW (I/O Write):** Generated when $IO/\bar{M} = 1$ and $W\bar{R} = 0$, indicating a write operation to an output device.

5. Data Bus (DB):

- Transfers data between the microprocessor and the I/O port.

How It Works:

1. I/O Read Operation:

- The microprocessor places the I/O address on the address bus.
- The decoder selects the corresponding I/O port.
- The control logic confirms IOR to enable data transfer from the input device to the microprocessor.

2. I/O Write Operation:

- The microprocessor places the I/O address on the address bus.
- The decoder selects the corresponding I/O port.
- The control logic confirms IOW, allowing data transfer from the microprocessor to the output device.



Peripheral- mapped	Memory- mapped
<ul style="list-style-type: none">I/O device is identified by 8 bit ($A_7 \rightarrow A_0$) only <p>i.e. 8085 MP can address 256 I/P 8256 O/P device.</p>	<ul style="list-style-type: none">I/O device is identified by 16 bit ($A_{15} \leftarrow A_0$) <p>8085 MP considers each device as a memory location.</p>
<ul style="list-style-type: none">IOR & IOW are used to control the data transfer.	MEMR & MEMW are used to control the data transfer.
<ul style="list-style-type: none">IN & OUT instruction are used for programming.	<ul style="list-style-type: none">ALL memory related instructions for data transfer can be used e.g. MOV A, M, STA, LDA etc.


BUS timing during the execution of IN & OUT instruction:

Ex. OUT FF Stored in M.L 2050 H, the content of Acc. Equals to (BBH)	<ul style="list-style-type: none">2 byte instruction with opcode (D3)
	<ul style="list-style-type: none">During the execution of this instruction the content of register (A) is transferred to the O/P device through O/P port which is addressed by (FF)
	<ul style="list-style-type: none">Need O/P code fetch & memory read machine cycles for fetching part and I/O write machine cycle for execution part.




A. Interfacing O/P devices:

1. Lighting Emitting Diode (LED)

 

If $V_A > V_B \implies$ LED is in forward biasing \implies LED emits light \equiv logic (1)

Ex: Analyze the cct. Shown below:

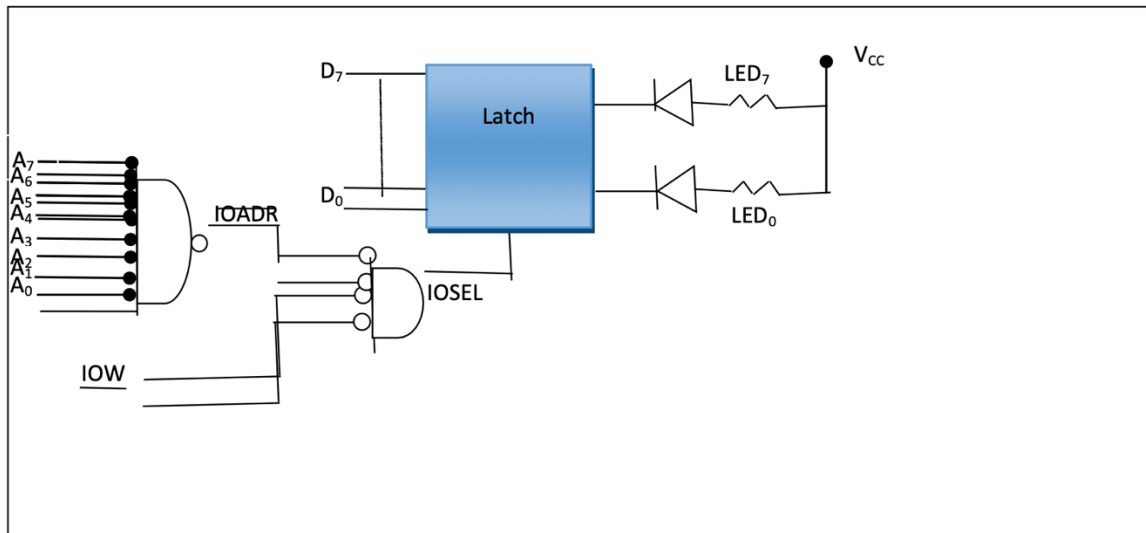

Explanation of Components:

1. Address Decoding (IOADR Generation):

- The low-order address bits (A0 to A7) are provided as inputs to the AND gate.
- This AND gate acts as a decoder, generating the IOADR (I/O Address Recognition Signal) when the specified address matches.
- This ensures that only the intended I/O device is selected.

2. Control Signal Generation (IOSEL - I/O Select):

- The IOW (I/O Write) signal is combined with IOADR using another AND gate to generate IOSEL.
- IOSEL acts as an enabling signal that activates the latch, allowing data transfer.

3. Latch (Output Storage) for LED Control:

- The latch stores the data (D0 to D7) received from the microprocessor.
- The stored data remains available even after the microprocessor moves on to other tasks.
- This is crucial for output devices like LEDs, as they need to stay ON/OFF without continuous microprocessor intervention.

4. LED Connection:

- Each bit (D0 to D7) in the latch corresponds to an LED.



- If a data bit is **high (1)**, the LED turns **ON**; if it is **low (0)**, the LED turns **OFF**.
- Current-limiting resistors are used to protect the LEDs.

5. Power Supply (Vcc):

- The LEDs are connected to **Vcc** and are controlled by the **latch outputs through transistors or drivers**.


How It Works:

1. The **microprocessor sends an address** on the address bus.
2. The **decoder recognizes the address** and generates **IOADR**.
3. The microprocessor issues an **I/O Write (IOW) signal**.
4. The **AND gate combines IOADR and IOW** to generate **IOSEL**, enabling the latch.
5. The **latch captures the data from the data bus (D0 to D7)** and **holds it**.
6. The stored data **controls the LEDs**:


- A bit **1 (HIGH)** → **LED ON**.
- A bit **0 (LOW)** → **LED OFF**.

2. Segment Display:

Each segment is a LED

 

 
There are two types of 7segment display as below:-





<p style="text-align: center;">D₀</p> <div style="text-align: center;"> </div> <p style="text-align: center;">D₃</p> <p>Ex. No. 3</p> <p style="text-align: center;">DB= 4FH</p>	<p>Ex. No. 3</p> <p style="text-align: center;">DB= BOH</p>
--	---

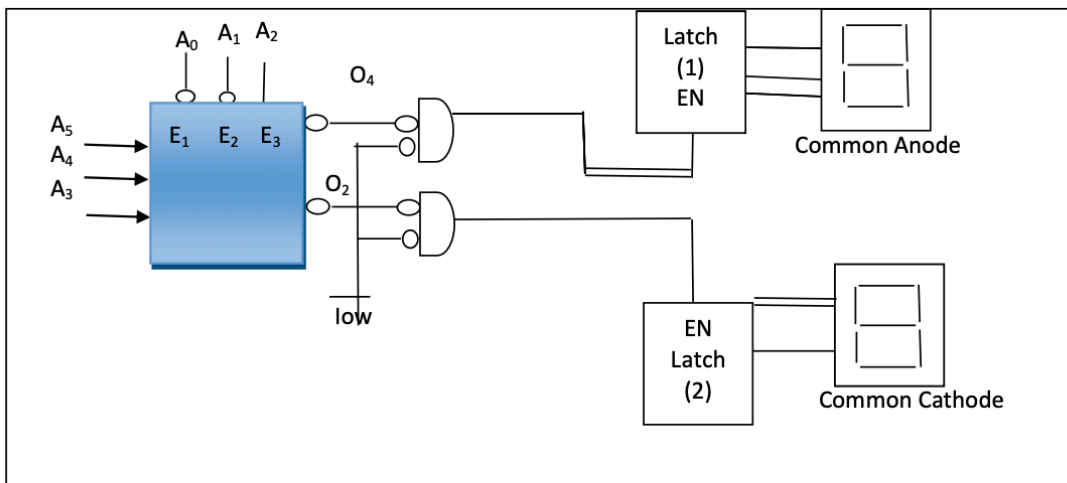Ex. What is the range of addresses, interfacing technique & type of decoding for each port in the following cct. What will be display if (Acc) = 06H



Sol: Both O/P port are interfaced through peripheral techniques both ports are identified by lines $A_7 \leftarrow A_0$.

Latch. (2)

Latch (2) can be address one of the following:

14H, 54H, 94H, D4H (linear decoding)

A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
X	X	0	1	0	1	0	0



Latch (1)

Latch (1) can be addressed by:


24H, 64H, A4H, E4H (linear decoding)

To transfer (Acc) through latch (1)

A ₇	A ₆	A ₅	A ₄	A ₃	A ₂	A ₁	A ₀
X	X	1	0	0	1	0	0

MVI A,06

OUT 24 H, OUT A4H, OUT E4H, OUT 64H

 

E will be displayed

- To transfer (Acc) through latch (2), MVI A 06

OUT 14, OUT 54, OUT 94, OUT D4



No. (1) will be displayed



The interfacing of Input Devices

- The basic concepts are similar to interfacing of output devices.
- The address lines are decoded to generate a signal that is active when the particular port is being accessed.
- An *IORD* signal is generated by combining the *IO/M* and the *RD* signals from the microprocessor.
- A tri-state buffer is used to connect the input device to the data bus.
- The control (Enable) for these buffers is connected to the result of combining the address signal and the signal *IORD*.

