




Al-Mustaqbal University
Department of Medical Instrumentation Techniques Engineering
Class: Third
Subject: Medical Communication Systems
Lecturer: Prof. Adnan Ali
Lecture:3

Mode Unit 3

Regulated Power Supplies (Part 2)

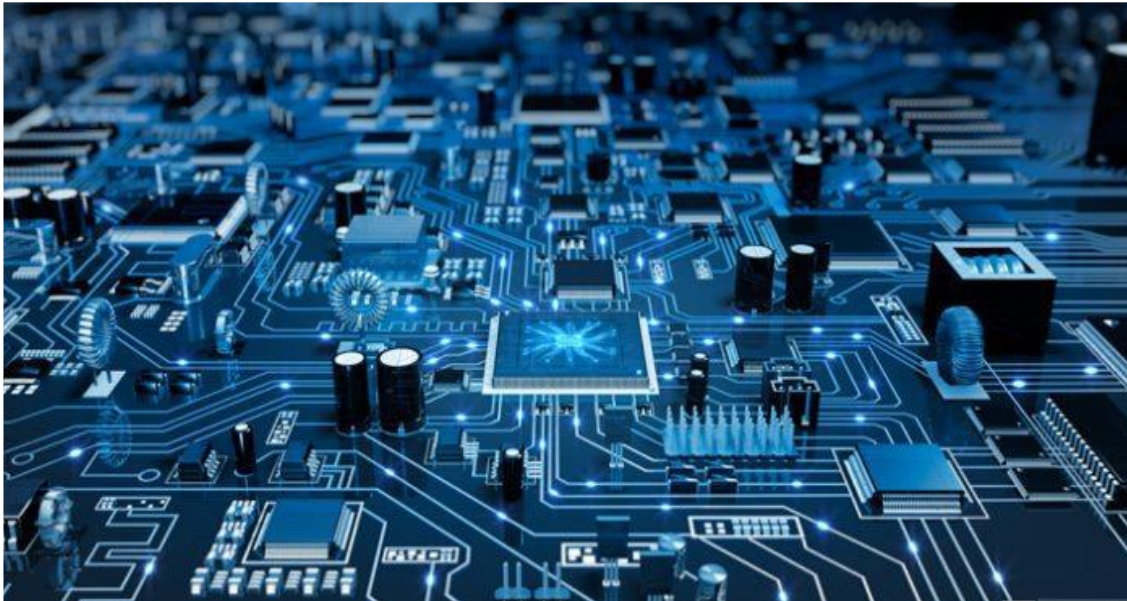For
Students of Third Stage
Department of Medical Instrumentation Techniques Engineering



By

Adnan Ali
Professor
Dep. Medical Instrumentation
Techniques Engineering



1. Overview

a. Target population:

For students of third class of Department of Medical Instrumentation Techniques Engineering, Electrical Engineering Technical College, Middle Technical University, Baghdad, Iraq.

b. Rationale:

A regulated power supply converts unregulated AC (Alternating Current) to a constant DC (Direct Current). A regulated power supply is used to ensure that the output remains constant even if the input changes.

c. Objectives:

The student will be able after finishing lecture on:

- Identify the main components of regulated power supply.

2. Introduction:


A **regulated power supply** converts unregulated AC (Alternating Current) to a constant DC (Direct Current). A regulated power supply is used to ensure that the output remains constant even if the input changes.

A regulated DC power supply is also known as a linear power supply, it is an embedded circuit and consists of various blocks.

The regulated power supply will accept an AC input and give a constant DC output. The figure below shows the block diagram of a typical regulated DC power supply.

The basic building blocks of a regulated DC power supply are as follows:

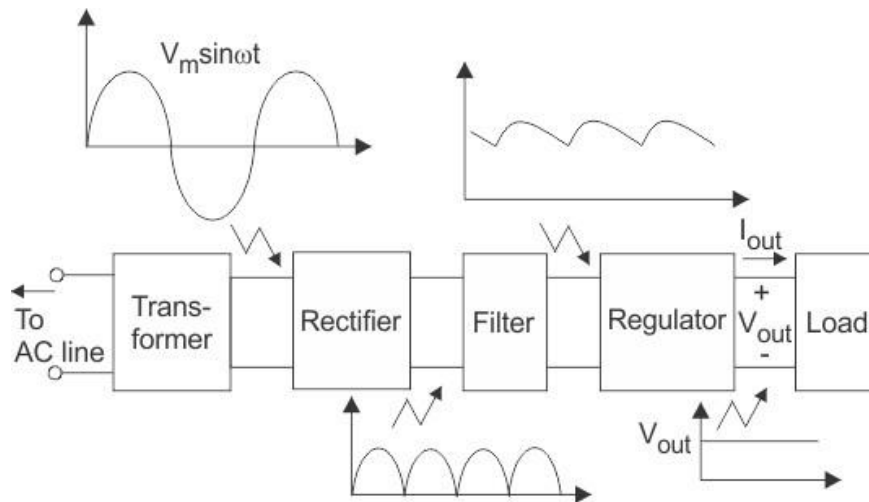
1. A step-down transformer
2. A rectifier
3. A DC filter
4. A regulator



Components of typical linear power supply

DC Filtration (Capacitor Filter)

The rectified voltage from the rectifier is a pulsating DC voltage having very high ripple content. But this is not we want, we want a pure ripple free DC waveform. Hence a filter is used. Different types of filters are used such as [capacitor](#) filter, LC filter, Choke input filter, π type filter. The figure below shows a capacitor filter connected along the output of the **half-wave rectifier** and the resultant output waveform.

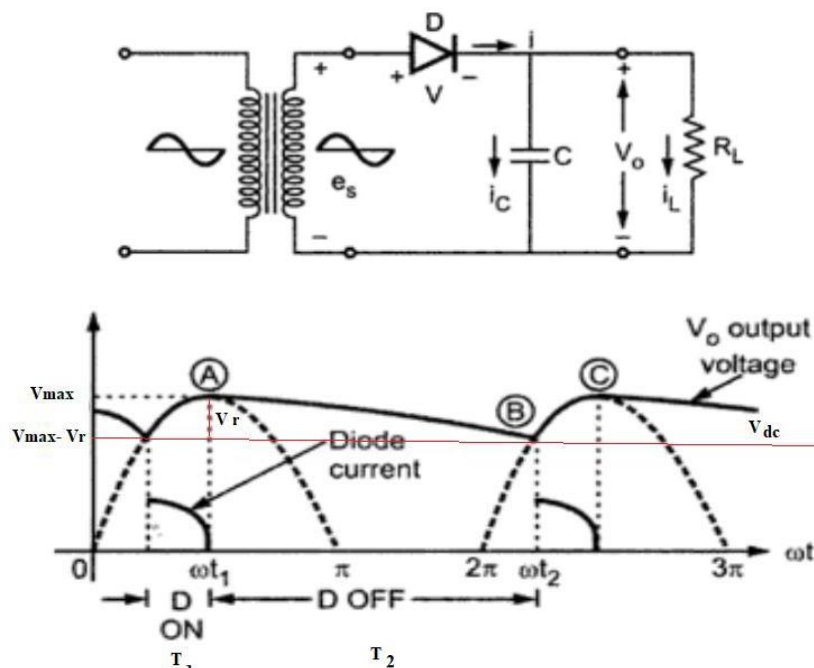



During the time interval T_1 the diode is conducting and the capacitor C is getting charged.

While in the time interval T_2 , the diode is reverse biased and the capacitor discharges through the load resistance R_L .

$$T = T_1 + T_2, \quad T_2 \gg T_1,$$

From Figure above $T_2 \approx 0.8 T$

At T_2 (discharging of C), the charge lost $Q = C V_{r(p.p)}$

The current through C is

$$i = \frac{dQ}{dt}$$

$$\int dQ = \int i dt$$

$$= \frac{V_{dc}}{1.25 R_L C F}$$

$$Q = \int_0^{T_2} i dt = I_{dc} T_2$$

$$C V_r = I_{dc} T_2$$

$$V_r = \frac{I_{dc} T_2}{C} = \frac{I_{dc}}{1.25 C F}$$

$$V_{dc} = V_{max} \frac{V_{max} - V_{r(p)}}{1 + \frac{1}{2.5 R_L C F}}$$


$$V_{r(p)} = \frac{V_{r(p.p)}}{2}$$

$$V_{dc} = V_{max} - \frac{1.25 R_L C F}{2} = V_{max} - \frac{V_{dc}}{2.5 R_L C F}$$

$$V_{rms} = \frac{V_{r(p.p)}}{2\sqrt{3}}$$

Al-Mustaqbal University
Department of Medical Instrumentation Techniques Engineering
Class: Third
Subject: Medical Communication Systems
Lecturer: Prof. Adnan Ali
Lecture:3


Triangular waveform – DC component

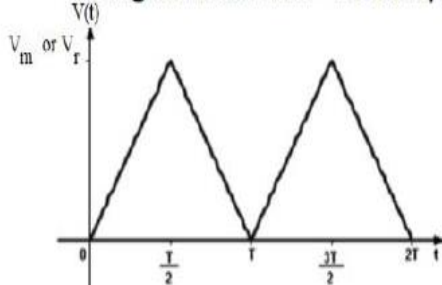

$$V_{DC} = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{T} \left(\frac{V_m T}{2} \right)$$

$$V_{DC} = \frac{V_m}{2}$$

Triangular waveform – RMS value

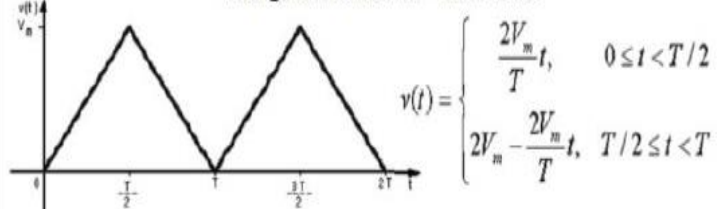


$$\begin{aligned} V_{rms}^2 &= \frac{1}{T} \int_0^T v^2(t) dt = \frac{1}{T} \left(\int_0^{T/2} \left(\frac{2V_m}{T}t \right)^2 dt + \int_{T/2}^T \left(2V_m - \frac{2V_m}{T}t \right)^2 dt \right) \\ &= \frac{1}{T} \left(\frac{4V_m^2}{T^2} \int_0^{T/2} t^2 dt + 4V_m^2 \int_{T/2}^T \left(1 - \frac{t}{T} \right)^2 dt \right) = \frac{4V_m^2}{T^3} \int_0^{T/2} t^2 dt + \frac{4V_m^2}{T} \int_{T/2}^T \left(1 - \frac{t}{T} + \frac{t^2}{T^2} \right) dt \\ &= \frac{4V_m^2}{T^3} \left[\frac{t^3}{3} \right]_0^{T/2} + \frac{4V_m^2}{T} \left[t - \frac{t^2}{2} + \frac{t^3}{3T} \right]_{T/2}^T \\ &= \frac{4V_m^2}{T^3} \frac{T^3}{24} + \frac{4V_m^2}{T} \left[\frac{T}{2} - \frac{3T^2}{4T} + \frac{7T^3}{24T^2} \right] \\ &= \frac{V_m^2}{6} + 4V_m^2 \left[\frac{1}{2} - \frac{3}{4} + \frac{7}{24} \right] = \frac{V_m^2}{3} \end{aligned}$$


$$V_{rms} = \frac{V_m}{\sqrt{3}}$$

Triangular waveform – AC component
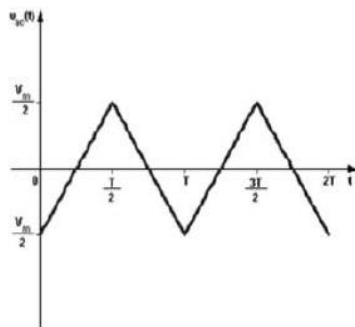
$$v_{ac}(t) = v(t) - V_{DC} = v(t) - V_m / 2$$



AC Triangular Waveform – RMS value

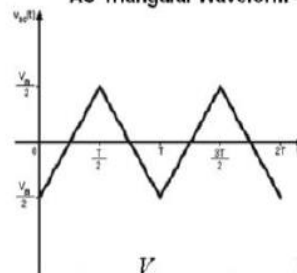

$$V_{rms} = \frac{V_m}{\sqrt{3}} \quad V_{DC} = \frac{V_m}{2}$$

$$\begin{aligned} (V_{ac})_{rms}^2 &= V_{rms}^2 - V_{DC}^2 \\ &= \frac{V_m^2}{3} - \frac{V_m^2}{4} \\ &= \frac{V_m^2}{12} \end{aligned}$$

$$(V_{ac})_{rms} = \frac{V_m}{2\sqrt{3}}$$

$$\text{Ripple factor } (r) = \frac{V_{rms}}{V_{dc}} = \frac{\frac{V_r(p.p)}{2\sqrt{3}}}{\frac{V_{dc}}{2\sqrt{3}}} = \frac{\frac{1.25 R_L C F}{2\sqrt{3}}}{\frac{V_{dc}}{2\sqrt{3}}} = \frac{1}{2.5\sqrt{3} R_L C F}$$



Ex1: For the half-wave rectifier circuit below, determine $V_{r(p.p)}$, V_{dc} and ripple factor (r)

Ans:

$$v_{s\text{ms}} = \frac{V_{s\text{max}}}{\sqrt{2}}$$

$$V_{s\text{max}} = 24 \times \sqrt{2} = 33.94 \text{ V}$$


$$V_{dc} = \frac{V_{\text{max}}}{1 + \frac{1}{2.5 R_l C F}} = \frac{33.94}{1 + \frac{1}{2.5 \times 220 \times 100 \times 10^{-6} \times 50}} = 24.96 \text{ V}$$

The Answer with MULTISIM



$$V_r = \frac{V_{dc}}{1.25 R_l C F} = \frac{24.96}{1.25 \times 50 \times 220 \times 100 \times 10^{-6}} = 18.1$$

$$r = \frac{1}{2.5\sqrt{3} R_l C F} = \frac{1}{2.5\sqrt{3} \times 220 \times 100 \times 10^{-6} \times 50} = 0.21$$

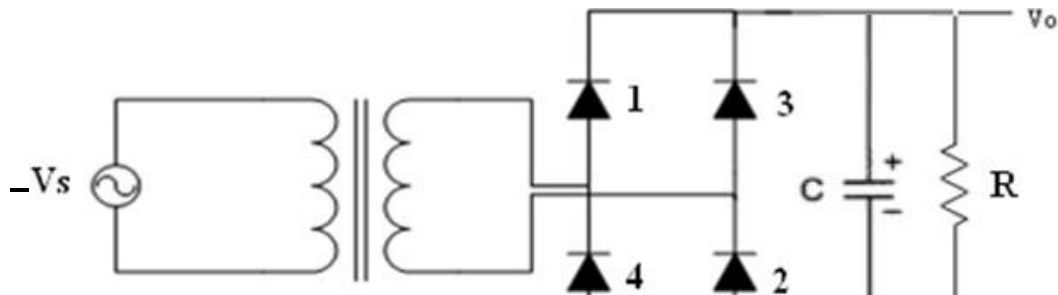Ex2 (H.W): For the half-wave rectifier circuit above, change C to $200 \mu\text{F}$ and load resistor R to 500Ω and determine V_{dc} , $V_{r(p.p)}$, $V_{r(p)}$ and ripple factor (r) .



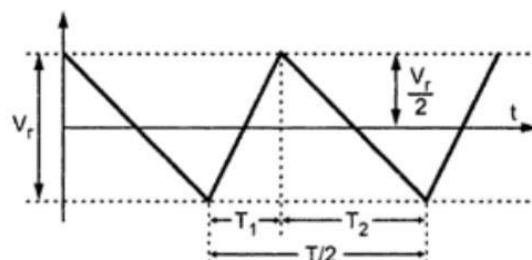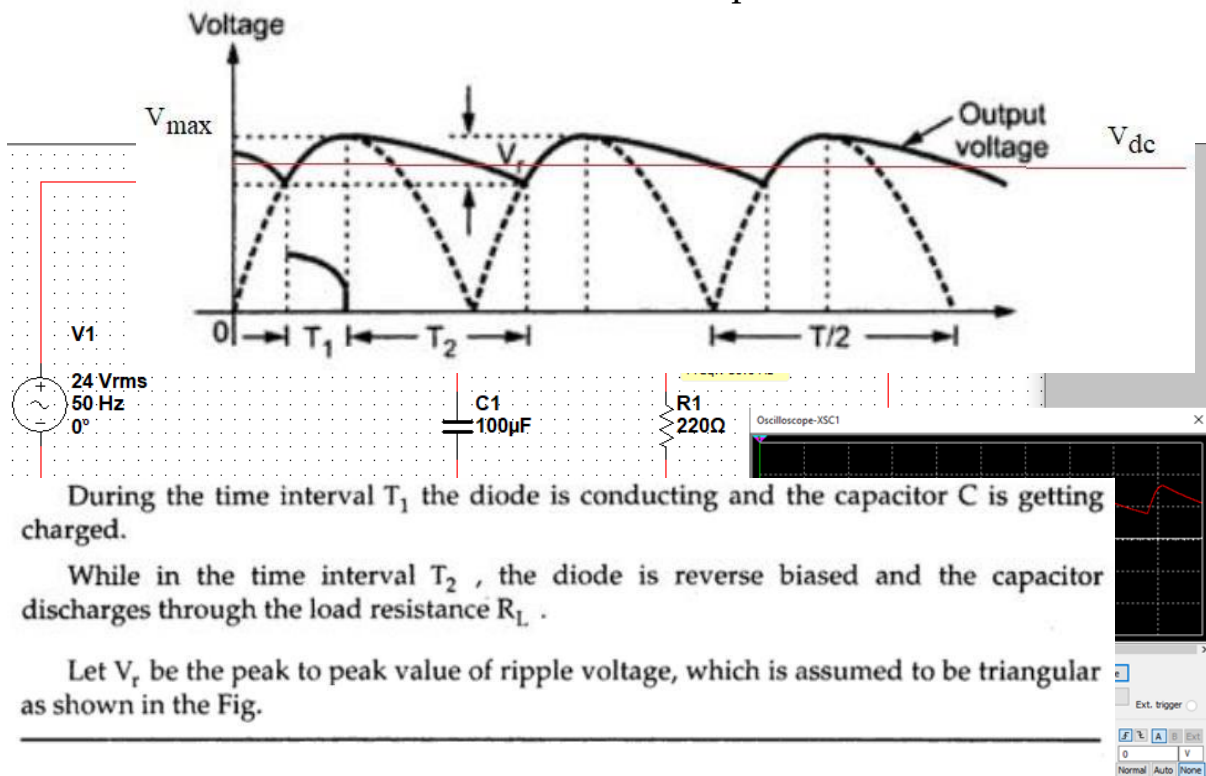The figure below shows a capacitor filter connected along the output of the **full-wave rectifier** and the resultant output waveform.



It can be shown mathematically that the r.m.s. value of such a triangular waveform is

$$V_{rms} = \frac{V_r}{\sqrt{3}}$$



Al-Mustaqbal University
Department of Medical Instrumentation Techniques Engineering
Class: Third
Subject: Medical Communication Systems
Lecturer: Prof. Adnan Ali
Lecture:3

$$T/2 = T_1 + T_2, \quad T_2 \gg T_1,$$

From the output waveform of the full wave rectifier $T_2 \approx T/2 =$

At T_2 (discharging of C), the charge lost $Q = C V_{r(p.p)}$

The current through C is

$$i = \frac{dQ}{dt}$$

$$\int dQ = \int i dt$$

$$= \frac{V_{dc}}{2 R_l C F}$$

$$Q = \int_0^{T_2} i dt = I_{dc} T_2$$

$$C V_r = I_{dc} T_2$$

$$V_r = \frac{I_{dc} T_2}{C} = \frac{I_{dc} T}{2C}$$

$$\frac{V_{dc}}{V_{dc}} = \frac{V_{max}}{V_{max}} - \frac{1}{4 R_l C F}$$

$$V_{dc} = V_{max} - \frac{V_{dc}}{2 R_l C F} / 2$$

$$\therefore V_{rms} = \frac{V_{r(p.p)}}{2\sqrt{3}}$$


$$\text{Ripple factor (r)} = \frac{V_{rms}}{V_{dc}} = \frac{\frac{V_{r(p.p)}}{2\sqrt{3}}}{V_{dc}} = \frac{\frac{V_{dc}}{2 R_l C F}}{V_{dc}} = \frac{1}{4\sqrt{3} R_l C F}$$



Al-Mustaqbal University
Department of Medical Instrumentation Techniques Engineering
Class: Third
Subject: Medical Communication Systems
Lecturer: Prof. Adnan Ali
Lecture:3



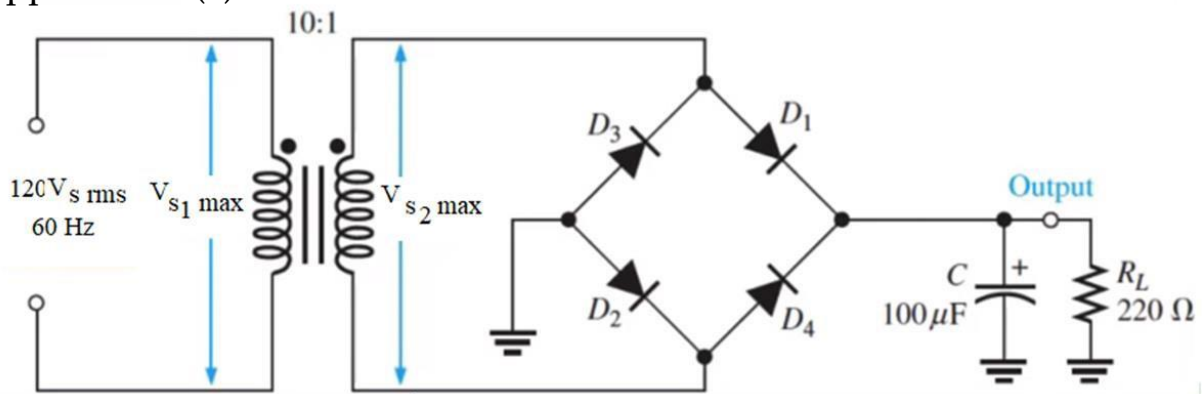Ex3: For the full-wave rectifier circuit below, determine $V_{r(p.p)}$, V_{dc} and ripple factor (r)



Ans:

$$V_{s1 \max} = 120 \times \sqrt{2} = 169.71 \text{ V}$$

$$\therefore \frac{V_{s1 \max}}{V_{s2 \max}} = \frac{n_1}{n_2}$$

$$\frac{169.71}{V_{s2 \max}} = \frac{10}{1}$$

$$V_{s2 \max} = 16.97 \text{ V}$$


$$V_{dc} = \frac{V_{\max}}{1 + \frac{1}{4 R_L C F}} = \frac{V_{s2 \max}}{1 + \frac{1}{4 R_L C F}} = \frac{16.97}{1 + \frac{1}{4 \times 220 \times 100 \times 10^{-6} \times 60}} = 14.2 \text{ V}$$

$$V_r = \frac{V_{dc}}{2 R_L C F} = \frac{V_{dc}}{2 R_L C F} = \frac{14.2}{2 \times 220 \times 100 \times 10^{-6} \times 60} = 5.3$$

$$r = \frac{1}{4\sqrt{3} R_L C F} = \frac{1}{4\sqrt{3} \times 220 \times 100 \times 60} = 0.109$$

Al-Mustaqbal University
Department of Medical Instrumentation Techniques Engineering
Class: Third
Subject: Medical Communication Systems
Lecturer: Prof. Adnan Ali
Lecture:3

The Answer with MULTISIM

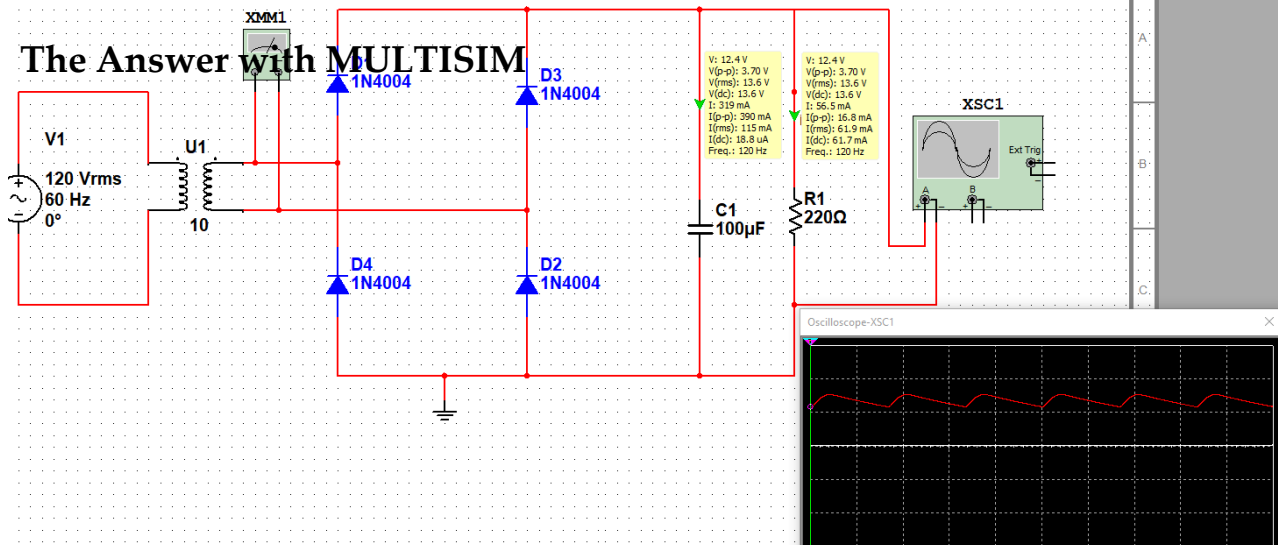

Ex. 4 : A $100\ \mu\text{F}$ capacitor, when used as filtering element, has 12 V, d.c. across it with a terminal load resistance of $2\ \text{k}\Omega$. If the rectifier is full-wave and supply frequency is 50 Hz, what is the percentage of ripple in the output ? Draw the neat circuit diagram.

Sol. : The circuit diagram is shown in the Fig.

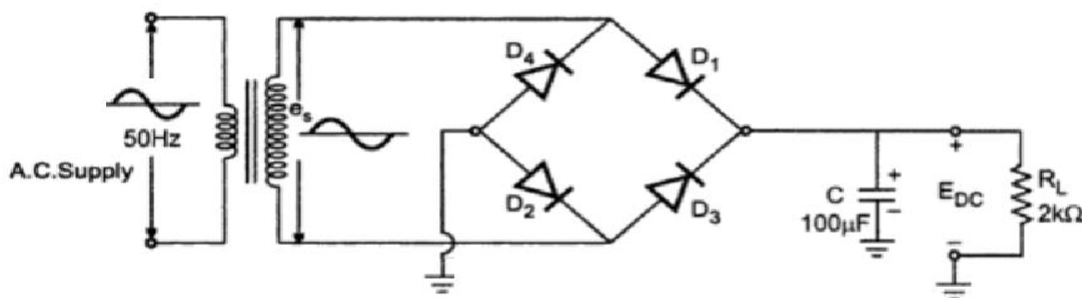


Fig. 3.28

Given : $R_L = 2\ \text{k}\Omega$, $C = 100\ \mu\text{F}$, $E_{DC} = 12\ \text{V}$, Supply frequency = 50 Hz

$$\text{Ripple factor} = \frac{1}{4\sqrt{3} f C R_L} = \frac{1}{4\sqrt{3} [50] [100 \times 10^{-6}] [2 \times 10^3]}$$

$$= \frac{1}{4\sqrt{3} (50) (2 \times 10^{-1})} = 0.01443$$


\therefore % of ripple in the output = $0.01443 \times 100 = 1.443\%$

Ex5 (H.W): For the full-wave rectifier circuit below,

1) For only resistive load, Calculate

V_{Lmean} , I_{Lmean} , $v_{o.r.m.s}$, $i_{o.r.m.s}$, and ripple factor (RF).

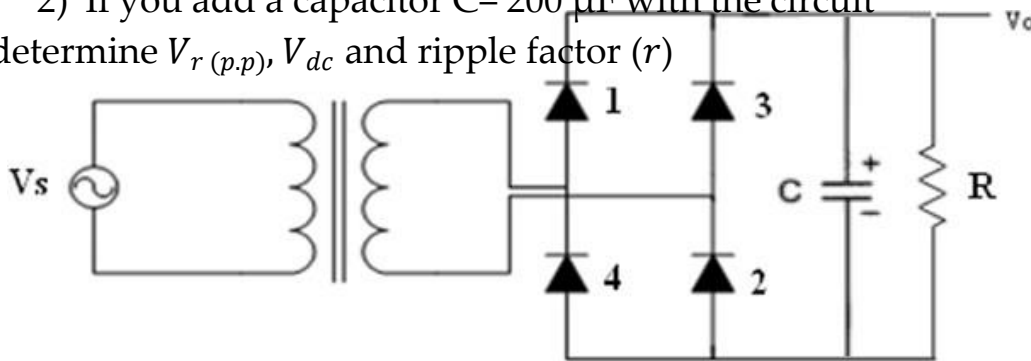2) If you add a capacitor $C = 200 \mu F$ with the circuit determine $V_{r(p.p)}$, V_{dc} and ripple factor (r)



Ex6 (H.W): A full-wave bridge rectifier supplies a load with 50 V dc, 100mA using 100 μF of filtering capacitor. Assume ideal diodes and $V_s = V_{smax} \sin 314 t$, determine $V_{r(p.p)}$, V_{smax} and $V_{s rms}$.