



Module Title: Fundamental of Electrical Engineering (AC)

Module Code: UOMU024021

Week (3)

3. EFFECTIVE (rms) VALUES

The effective value (or the rms value) of an alternating waveform is given by the steady (dc) current which when flowing through a given circuit, for a given time produces the same heat produced by the alternating current when flowing the same circuit for the same time.

Effective value of the sinusoidal is:

$$I_{\text{eff}} = 0.707I_m$$

$$E_{\text{eff}} = 0.707E_m$$


The effective value of any quantity plotted as a function of time can be found by using the following equation:

$$I_{\text{eff}} = \sqrt{\frac{\int_0^T i^2(t) dt}{T}}$$

$$I_{\text{eff}} = \sqrt{\frac{\text{area } (i^2(t))}{T}}$$



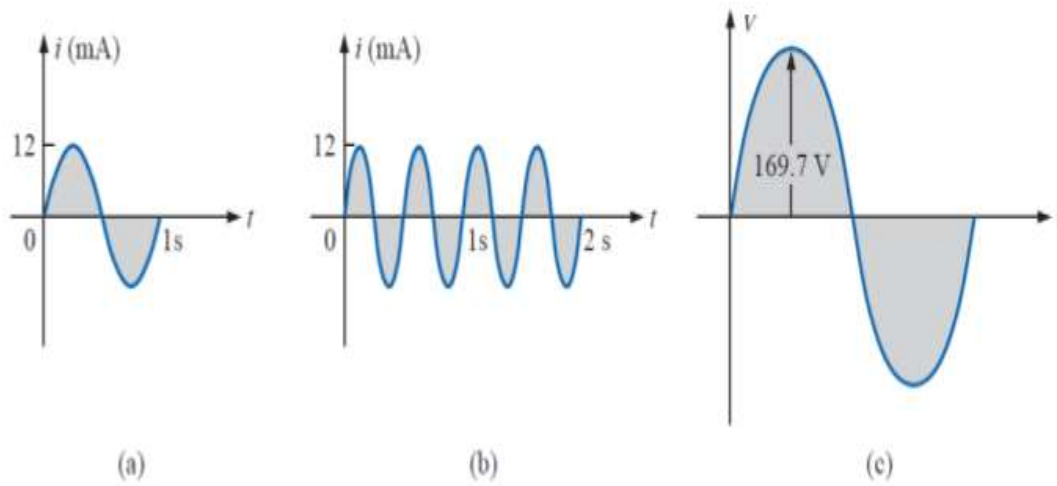EXAMPLE: Find the **rms** values of the sinusoidal waveform




Solution:

For part (a), $I_{rms} = 0.707(12 * 10^{-3} \text{ A}) = \mathbf{8.484 \text{ mA}}$. For part (b), again $I_{rms} = \mathbf{8.484 \text{ mA}}$. Note that frequency did not change the effective value

in (b) above compared to (a). For part (c), $V_{rms} = 0.707(169.73 \text{ V}) \cong \mathbf{120 \text{ V}}$.



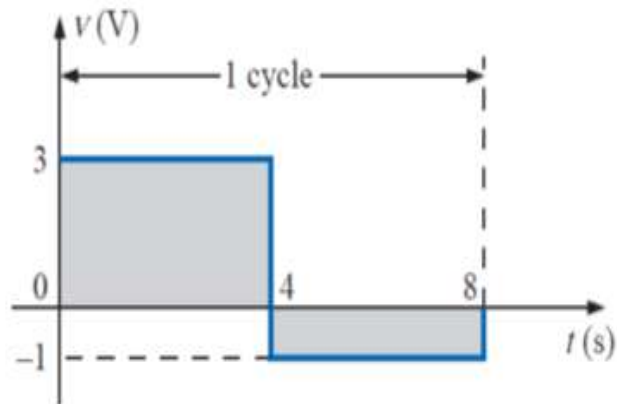EXAMPLE: Find the effective or rms value of the waveform




Solution:

$$V_{\text{rms}} = \sqrt{\frac{(9)(4) + (1)(4)}{8}} = \sqrt{\frac{40}{8}} = 2.236 \text{ V}$$



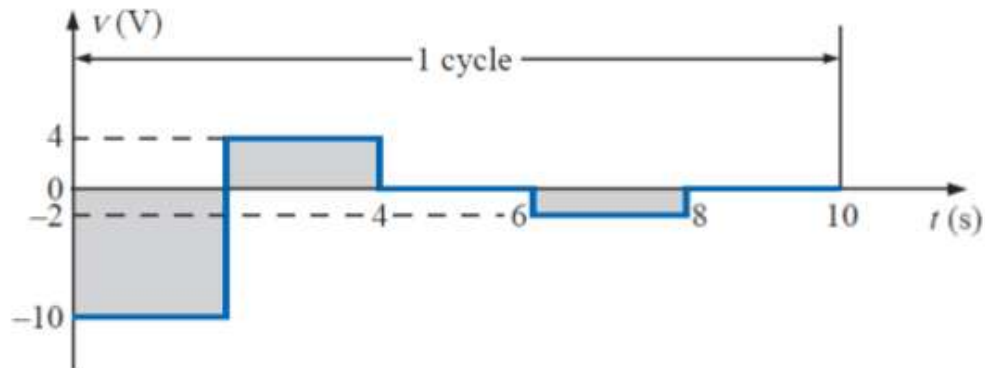
EXAMPLE: Calculate the rms value of the voltage



Solution:

$$V_{\text{rms}} = \sqrt{\frac{(100)(2) + (16)(2) + (4)(2)}{10}} = \sqrt{\frac{240}{10}} \\ = 4.899 \text{ V}$$

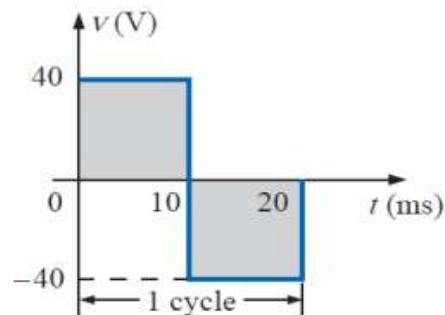EXAMPLE: Determine the average and rms values of the square wave.





Solution:

$$V_{\text{rms}} = \sqrt{\frac{(1600)(10 \times 10^{-3}) + (1600)(10 \times 10^{-3})}{20 \times 10^{-3}}}$$

$$= \sqrt{\frac{32,000 \times 10^{-3}}{20 \times 10^{-3}}} = \sqrt{1600}$$


$$V_{\text{rms}} = 40 \text{ V}$$

4. RESPONSE OF BASIC R, L, AND C ELEMENTS TO A SINUSOIDAL VOLTAGE OR CURRENT

R, L, and C circuit elements each have quite different electrical properties. Resistance, for example, opposes current, while inductance opposes changes in current, and capacitance opposes changes in voltage.

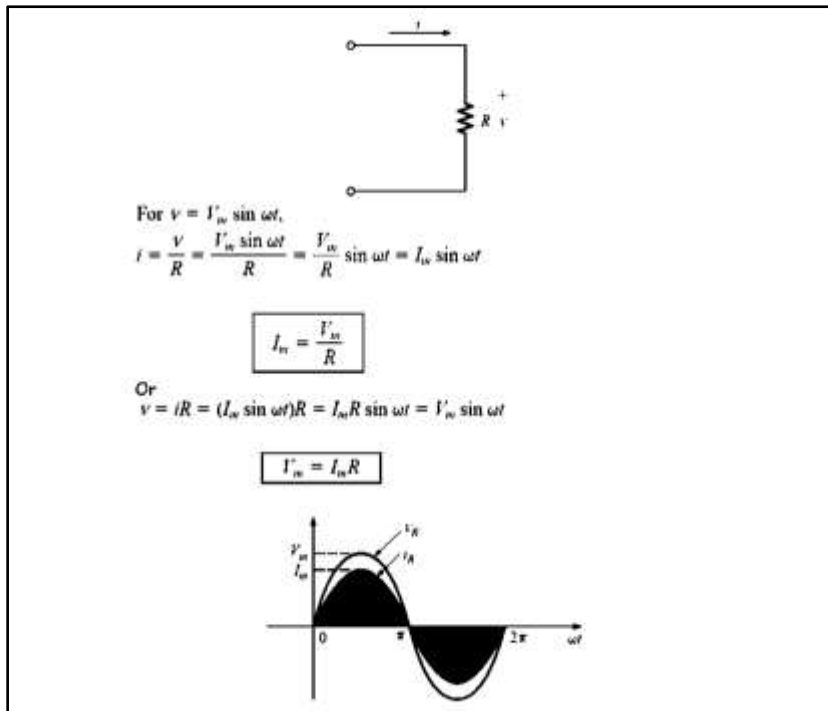1) Resistor

For a purely resistive element, the voltage across and the current through the element are in phase, with their peak values related by Ohm's law.






$$X_L = \frac{V_m}{I_m} \quad (\text{ohms}, \Omega)$$

$$X_L = \omega L = 2\pi fL = 2\pi Lf$$

2) Inductor

For an inductor, v_L leads i_L by 90° , or i_L lags v_L by 90° .

$$v_L = L \frac{di_L}{dt}$$

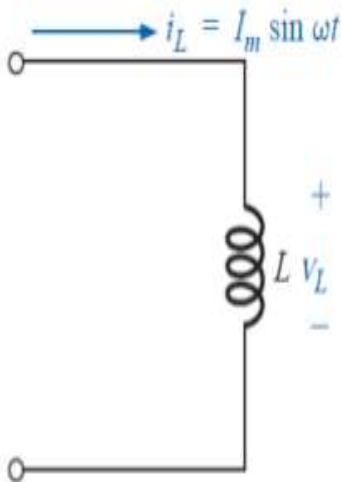



$$\frac{di_L}{dt} = \frac{d}{dt}(I_m \sin \omega t) = \omega I_m \cos \omega t$$


$$v_L = L \frac{di_L}{dt} = L(\omega I_m \cos \omega t) = \omega L I_m \cos \omega t$$

$$v_L = V_m \sin(\omega t + 90^\circ)$$

$$V_m = \omega L I_m$$

$$i_L = I_m \sin(\omega t \pm \theta)$$
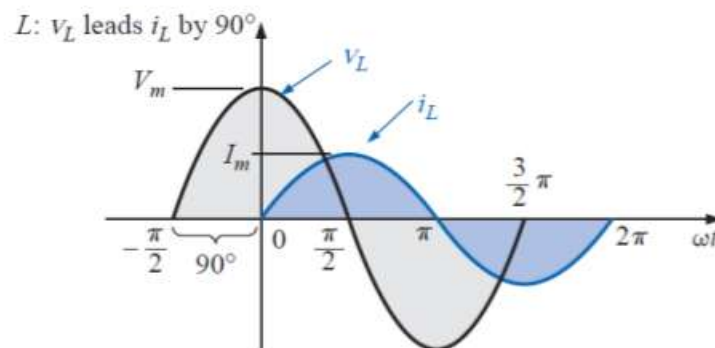
$$v_L = \omega L I_m \sin(\omega t \pm \theta + 90^\circ)$$



The quantity ωL , called the **reactance** (from the word *reaction*) of an inductor, is symbolically represented by X_L and is measured in ohms; that is,

$$X_L = \omega L \quad (\text{ohms}, \Omega)$$

$$X_L = \frac{V_m}{I_m} \quad (\text{ohms}, \Omega)$$


$$X_L = \omega L = 2\pi fL = 2\pi Lf$$



3) Capacitor

For a particular capacitance, the greater the rate of change of voltage across the capacitor, the greater the capacitive current.

$$i_C = C \frac{dv_C}{dt}$$

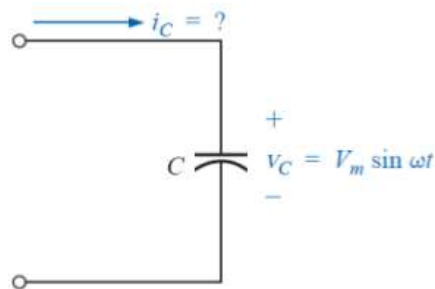

$$\frac{dv_C}{dt} = \frac{d}{dt}(V_m \sin \omega t) = \omega V_m \cos \omega t$$

$$i_C = C \frac{dv_C}{dt} = C(\omega V_m \cos \omega t) = \omega C V_m \cos \omega t$$

$$i_C = I_m \sin(\omega t + 90^\circ)$$

$$I_m = \omega C V_m$$

For a capacitor, i_C leads v_C by 90° , or v_C lags i_C by 90° .

$$v_C = V_m \sin(\omega t \pm \theta)$$

$$i_C = \omega C V_m \sin(\omega t \pm \theta + 90^\circ)$$


The quantity $1/\omega C$, called the **reactance** of a capacitor, is symbolically represented by X_C and is measured in ohms; that is,



$$X_C = \frac{1}{\omega C} \quad (\text{ohms}, \Omega)$$

$$X_C = \frac{V_m}{I_m} \quad (\text{ohms}, \Omega)$$

$$X_C = \frac{1}{2\pi fC}$$

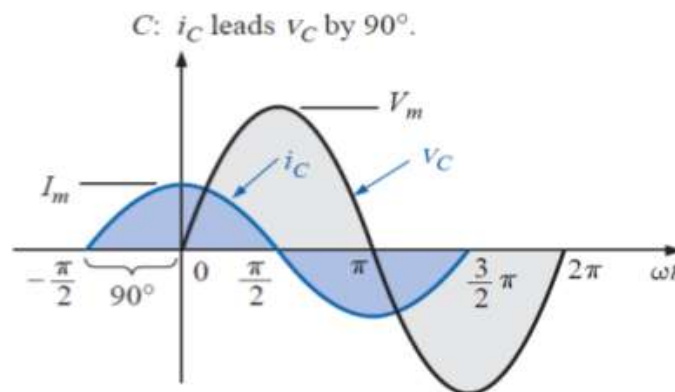

EXAMPLE 7: The voltage across a resistor is indicated. Find the sinusoidal expression for the current if the resistor is 10 Ohms . Sketch the curves for v and i .




Solutions:

a)

$$I_m = \frac{V_m}{R} = \frac{100 \text{ V}}{10 \Omega} = 10 \text{ A}$$

(v and i are in phase)

$$i = 10 \sin 377t$$

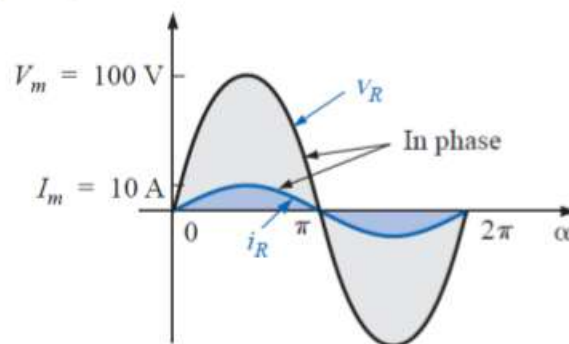


b)

$$I_m = \frac{V_m}{R} = \frac{25 \text{ V}}{10 \Omega} = 2.5 \text{ A}$$

(v and i are in phase)

$$i = 2.5 \sin(377t + 60^\circ)$$

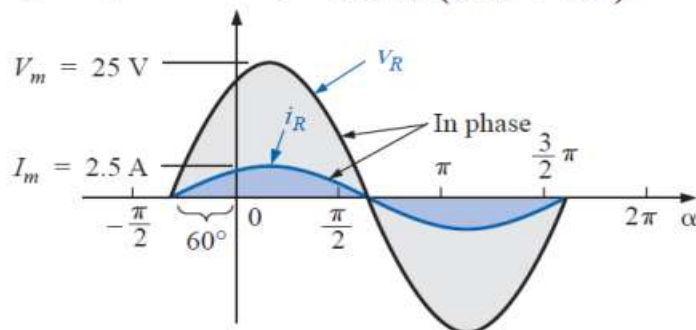



EXAMPLE: The current through a 0.1-H coil is provided. Find the sinusoidal expression for the voltage across the coil. Sketch the v and i curves.

a) $i = 10 \sin 377t$

b) $i = 7 \sin(377t - 70^\circ)$

Solutions:


a)

$$X_L = \omega L = (377 \text{ rad/s})(0.1 \text{ H}) = 37.7 \Omega$$

$$V_m = I_m X_L = (10 \text{ A})(37.7 \Omega) = 377 \text{ V}$$

v leads i by 90°

$$v = 377 \sin(377t + 90^\circ)$$

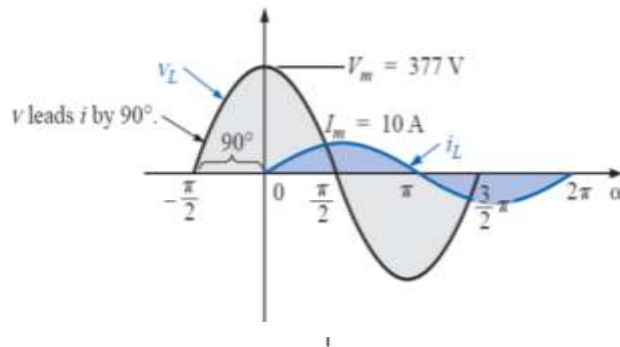


b)

$$V_m = I_m X_L = (7 \text{ A})(37.7 \Omega) = 263.9 \text{ V}$$

v leads i by 90°

$$v = 263.9 \sin(377t - 70^\circ + 90^\circ)$$

$$v = 263.9 \sin(377t + 20^\circ)$$

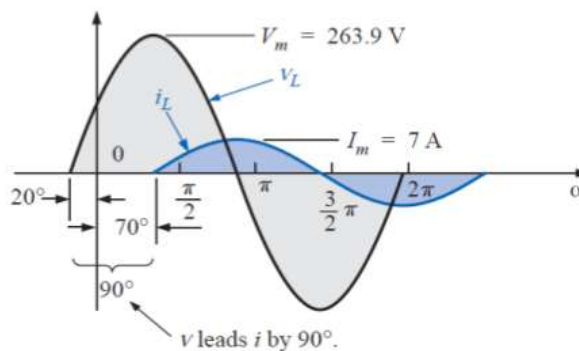




EXAMPLE: The voltage across a $1\text{-}\mu\text{F}$ capacitor is provided below. What is the sinusoidal expression for the current? Sketch the v and i curves.
 $v = 30 \sin 400t$

Solutions:

$$X_C = \frac{1}{\omega C} = \frac{1}{(400 \text{ rad/s})(1 \times 10^{-6} \text{ F})} = \frac{10^6 \Omega}{400} = 2500 \Omega$$

$$I_m = \frac{V_m}{X_C} = \frac{30 \text{ V}}{2500 \Omega} = 0.0120 \text{ A} = 12 \text{ mA}$$

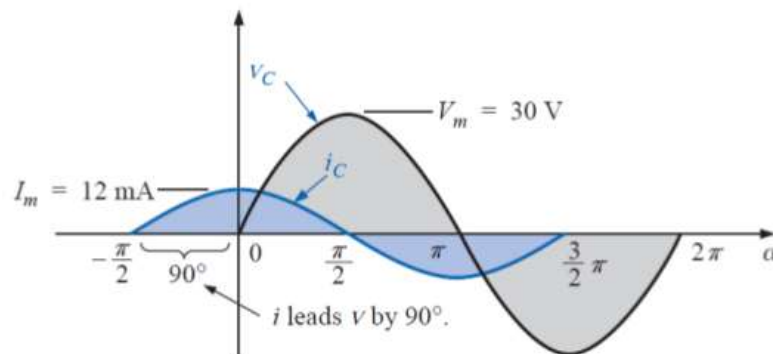i leads v by 90° $i = 12 \times 10^{-3} \sin(400t + 90^\circ)$





EXAMPLE: At what frequency will the reactance of a 200-mH inductor match the resistance level of a 5-k Ω resistor?

Solutions:

$$\begin{aligned} 5000 \, \Omega &= X_L = 2\pi fL = 2\pi Lf \\ &= 2\pi(200 \times 10^{-3} \text{ H})f = 1.257f \end{aligned}$$

$$f = \frac{5000 \text{ Hz}}{1.257} \cong 3.98 \text{ kHz}$$