



## Experiment No. 6

### SR Flip Flop

#### 1. Introduction

Flip-flops are fundamental sequential circuit elements used for storing binary states. The **SR (Set-Reset) flip-flop** can be designed using either **NAND** or **NOR** gates, each with distinct input conditions and behavior. The **NAND-based SR flip-flop** operates with active-low inputs, while the **NOR-based design** uses active-high inputs. Understanding these implementations helps in analyzing their characteristics.

#### 1.1 Objective

To design and analyze an **SR flip-flop** using **NAND and NOR gates**, demonstrating their role in implementing bistable circuits. This experiment aims to compare both designs' behavior and examine their truth tables.

#### 1.2 Work Environment

The CircuitMaker software is used to design and simulate logical circuits.


#### 1.3 Theory

Flip-flops are essential components in digital circuits, used to store and control binary data. The **SR (Set-Reset) flip-flop** is one of the fundamental bistable circuits, having two inputs—**Set (S) and Reset (R)**—and two stable output states. It can be designed using either **NAND** or **NOR** gates, each affecting its operation differently.




### 1.3.1 SR Flip-Flop Using NOR Gates

Mode of operation	Input		Output	
	S	R	Q	$\bar{Q}$
Hold	0	0	No change	
Set	0	1	1	0
Reset	1	0	0	1
Prohibited	1	1	1	1

 

### 1.3.2 SR Flip-Flop Using NAND Gates

Mode of operation	Input		Output	
	S	R	Q	$\bar{Q}$
Prohibited	0	0	1	1
Set	0	1	1	0
Reset	1	0	0	1
Hold	1	1	No change	

 

### 1.3.3 Characteristics and Applications

The SR flip-flop is the basis for more complex flip-flops (D, JK, and T) and is widely used in latches, registers, and memory circuits. The key differences between NAND and NOR implementations lie in their **input logic levels and the handling of invalid states**. Understanding these variations helps in designing stable and efficient sequential logic circuits



## 1.3 Experiment

### Designing SR Flip-Flop Using NOR Gates

1. **Open CircuitMaker** and create a new schematic.
2. **Add Components:**
  - Two **NOR gates**.
  - Two **logic switches** (for inputs S and R).
  - Two **LEDs** (for outputs Q and  $\bar{Q}$ ).
  - **Power source (Logic switch)**.
3. **Connect the Circuit:**
  - Connect the output of the first NOR gate to one input of the second NOR gate.
  - Connect the output of the second NOR gate to one input of the first NOR gate.
  - Connect **S** to the other input of the first NOR gate.
  - Connect **R** to the other input of the second NOR gate.
  - Connect **LEDs** to Q and  $\bar{Q}$  to observe output changes.
4. **Run Simulation** and observe the circuit behavior for different **S and R** combinations.

### Designing SR Flip-Flop Using NAND Gates

**Open CircuitMaker** and start a new schematic.

1. **Add Components:**
  - Two **NAND gates**.
  - Two **logic switches** (for inputs S and R).
  - Two **LEDs** (for outputs Q and  $\bar{Q}$ ).
  - **Power source (Logic switch)**.



## 2. Connect the Circuit:

- Connect the output of the first NAND gate to one input of the second NAND gate.
- Connect the output of the second NAND gate to one input of the first NAND gate.
- Connect  $\bar{S}$  (inverted S) to one input of the first NAND gate.
- Connect  $\bar{R}$  (inverted R) to one input of the second NAND gate.
- Connect LEDs to **Q** and  $\bar{Q}$  to visualize state changes.

## 3. Run Simulation and test different input conditions.

### Discussion:

- Why is the JK flip-flop preferred over the SR flip-flop?
- Compare the truth tables of an SR flip-flop implemented using NAND and NOR gates.
- Draw the circuit diagram of an SR flip-flop with a clock. What is the difference in the truth table between a clocked SR flip-flop and an SR flip-flop without a clock (using NAND gates)?
- State one function of a flip-flop.