



Module Title: Fundamental of Electrical Engineering (AC)


Module Code: UOMU024021

Week 5

5. SERIES CONFIGURATION IN AC CIRCUITS

The overall properties of series ac circuits are the same as those for dc circuits. For instance, the total impedance of a system is the sum of the individual impedances:

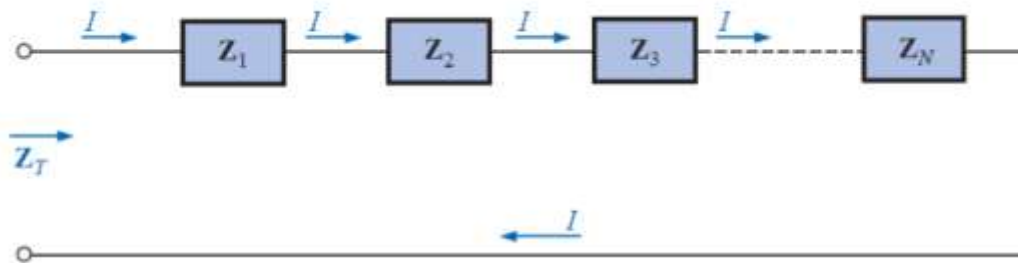Example: Draw the impedance diagram for the circuit shown below, and find the total impedance.



$$Z_T = Z_1 + Z_2 + Z_3 + \dots + Z_N$$

5.1 Series and Parallel Waveforms AC Circuits Resistive Elements

Resistive Elements:

$$I_m = \frac{V_m}{R}$$
$$V_m = I_m R$$

In phaser form,

$$v = V_m \sin \omega t = V \angle 0$$


Where $V = 0.707 V_m$

Applying Ohm's law and using phaser algebra, we have

$$I = \frac{V \angle 0}{R \angle 0}$$

So that in the time domain,
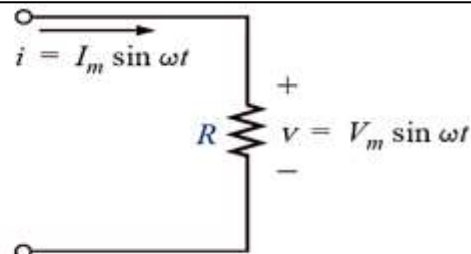
$$i = \sqrt{2} \frac{V}{R} \sin \omega t$$





Example: 1


Using complex algebra, find the current i for the circuit shown below. Sketch the waveforms of v and i .

Solution

$$v = 100 \sin \omega t = 70.7 \angle 0$$

$$I = \frac{V \angle 0}{Z_R \angle 0} = \frac{70.7 \angle 0}{5 \angle 0} = 14.14 \angle 0 \text{ A}$$
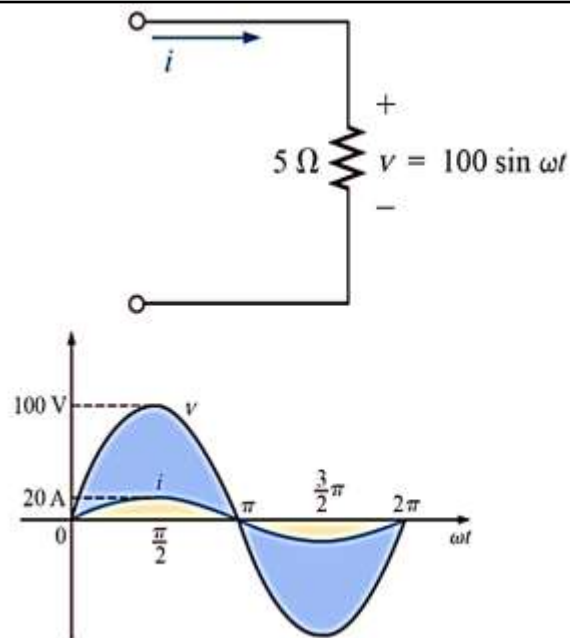
$$i = \sqrt{2} \times 14.14 \sin \omega t = 20 \sin \omega t \text{ A}$$



Inductive Reactance

The voltage leads the current by 90° and that the reactance of the coil X_L is determined by ωL .


$$v = V_m \sin \omega t = V \angle 0$$

By Ohm's law,

$$\mathbf{I} = \frac{V \angle 0}{X_L \angle 90} = \frac{V}{X_L} \angle -90$$

so that in the time domain,
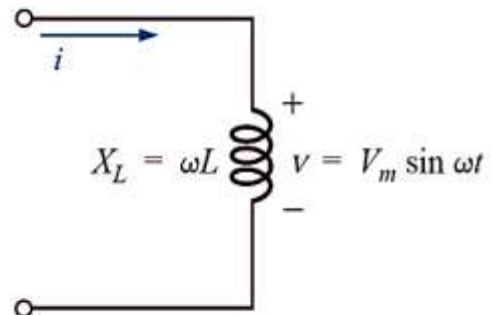
$$i = \sqrt{2} \frac{V}{X_L} \sin(\omega t - 90)$$



$$Z_L = X_L \angle 90$$



Example:

Using complex algebra, find the current i for the circuit shown below. Sketch the v and i curves.

Solution:


$$v = 24 \sin \omega t$$

In polar form

$$\mathbf{V} = 16.968 \angle 0$$

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}_L} = \frac{V \angle 0}{X_L \angle 90} = \frac{16.968 \angle 0}{3 \angle 90} = 5.656 \text{ A} \angle -90$$
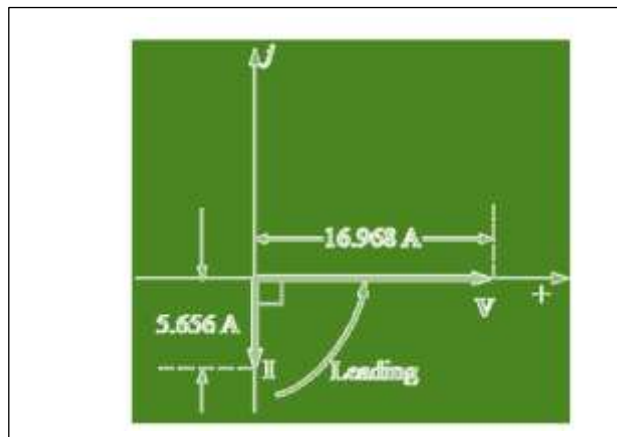
$$i = \sqrt{2}(5.656) \sin(\omega t - 90) = 8 \sin(\omega t - 90)$$



Capacitive Reactance

The current leads the voltage by 90° and that the reactance of the capacitor X_C is determined by $\frac{1}{\omega C}$.

$$v = V_m \sin \omega t$$

In polar form

$$\mathbf{V} = V \angle 0$$

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}_C} = \frac{V \angle 0}{X_C \angle -90} = \frac{V}{X_C} \angle 90$$

$$i = \sqrt{2} \frac{V}{X_C} \sin(\omega t + 90)$$

$$\mathbf{Z}_C = X_C \angle -90$$



Example:

Using complex algebra, find the current i for the circuit shown below. Sketch the v and i curves.

solution:

$$v = 15 \sin \omega t$$

In polar form


$$\mathbf{V} = 10.605 \angle 0$$

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}_C} = \frac{V \angle 0}{X_C \angle -90} = \frac{10.605 \angle 0}{2 \angle -90} = 5.303 \text{ A} \angle 90$$

$$i = \sqrt{2} \frac{V}{X_C} \sin(\omega t + 90) = 7.5 \sin(\omega t + 90)$$


(1) R-L Circuits:

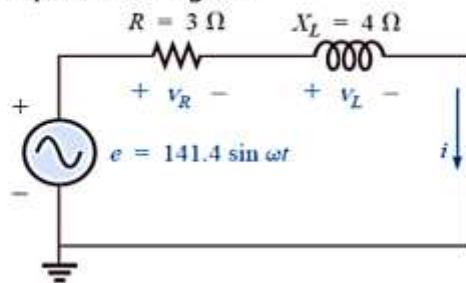EXAMPLE: Determine the input impedance to the series network and find i , V_R , V_L . Draw the impedance diagram.



Solutions:
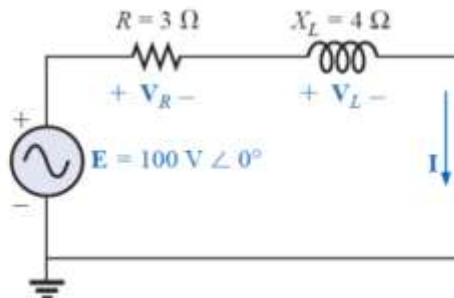
$$e = 141.4 \sin \omega t \Rightarrow \mathbf{E} = 100 \text{ V} \angle 0^\circ$$



$$\mathbf{Z}_T = \mathbf{Z}_1 + \mathbf{Z}_2 = 3 \Omega \angle 0^\circ + 4 \Omega \angle 90^\circ = 3 \Omega + j4 \Omega$$


$$\mathbf{Z}_T = 5 \Omega \angle 53.13^\circ$$



$$I = \frac{E}{Z_T} = \frac{100 \text{ V } \angle 0^\circ}{5 \Omega \angle 53.13^\circ} = 20 \text{ A } \angle -53.13^\circ$$


$$V_R = IZ_R = (20 \text{ A } \angle -53.13^\circ)(3 \Omega \angle 0^\circ) = 60 \text{ V } \angle -53.13^\circ$$
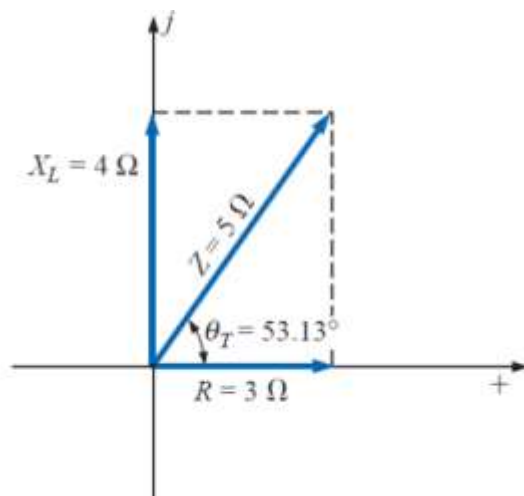
$$V_L = IZ_L = (20 \text{ A } \angle -53.13^\circ)(4 \Omega \angle 90^\circ) = 80 \text{ V } \angle 36.87^\circ$$



(2) R-C Circuits

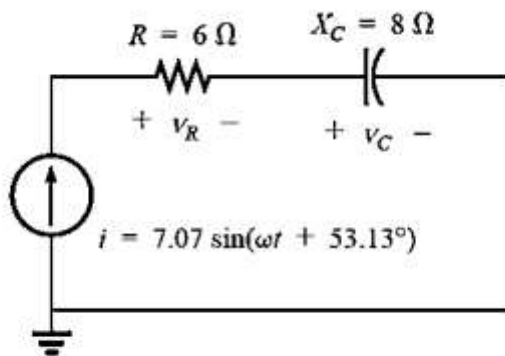
EXAMPLE: Determine the input impedance to the series network and find E , V_R , V_C . Draw the impedance diagram.





Solutions:
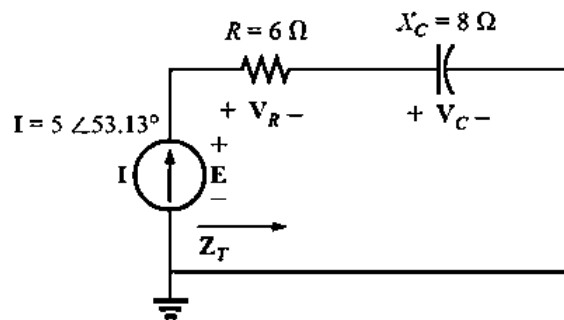
$$i = 7.07 \sin(\omega t + 53.13^\circ) \Rightarrow \mathbf{I} = 5 \text{ A } \angle 53.13^\circ$$





$$\mathbf{Z}_T = \mathbf{Z}_1 + \mathbf{Z}_2 = 6 \Omega \angle 0^\circ + 8 \Omega \angle -90^\circ = 6 \Omega - j8 \Omega$$

$$\mathbf{Z}_T = 10 \Omega \angle -53.13^\circ$$

$$\mathbf{E} = \mathbf{I}\mathbf{Z}_T = (5 \text{ A } \angle 53.13^\circ)(10 \Omega \angle -53.13^\circ) = 50 \text{ V } \angle 0^\circ$$

$$\begin{aligned} \mathbf{V}_R &= \mathbf{I}\mathbf{Z}_R = (I \angle \theta)(R \angle 0^\circ) = (5 \text{ A } \angle 53.13^\circ)(6 \Omega \angle 0^\circ) \\ &= 30 \text{ V } \angle 53.13^\circ \end{aligned}$$
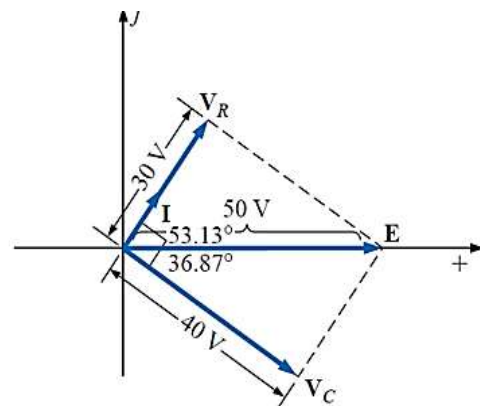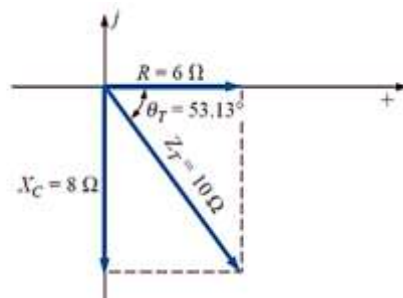
$$\begin{aligned} \mathbf{V}_C &= \mathbf{I}\mathbf{Z}_C = (I \angle \theta)(X_C \angle -90^\circ) = (5 \text{ A } \angle 53.13^\circ)(8 \Omega \angle -90^\circ) \\ &= 40 \text{ V } \angle -36.87^\circ \end{aligned}$$






(3) R-L-C Circuits

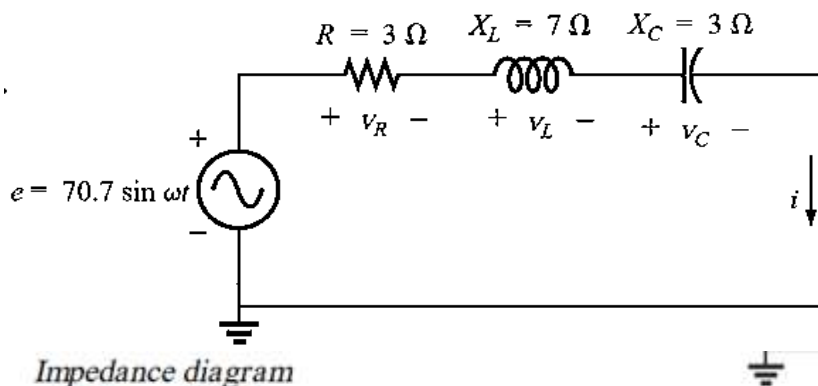Example :

$$Z_T = Z_R + Z_L + Z_C = R + jX_L - jX_C$$

$$Z_T = 3 + j7 - j3 = 3 + j4 = 5 \angle 53.13^\circ$$





Impedance diagram

$$I = \frac{E}{Z_T} = \frac{50 \angle 0^\circ}{5 \angle 53.13^\circ} = 10 \angle -53.13^\circ \text{ A}$$

$$V_R = IZ_R = 3 \times 10 \angle -53.13^\circ = 30 \angle -53.13^\circ \text{ V}$$


$$V_L = IZ_L = 7 \angle 90^\circ \times 10 \angle -53.13^\circ = 70 \angle 36.87^\circ \text{ V}$$
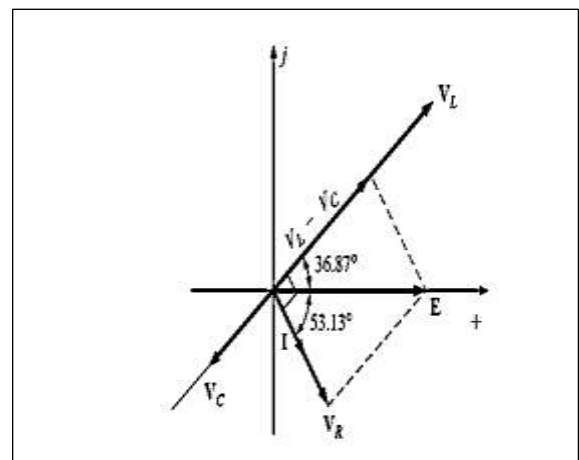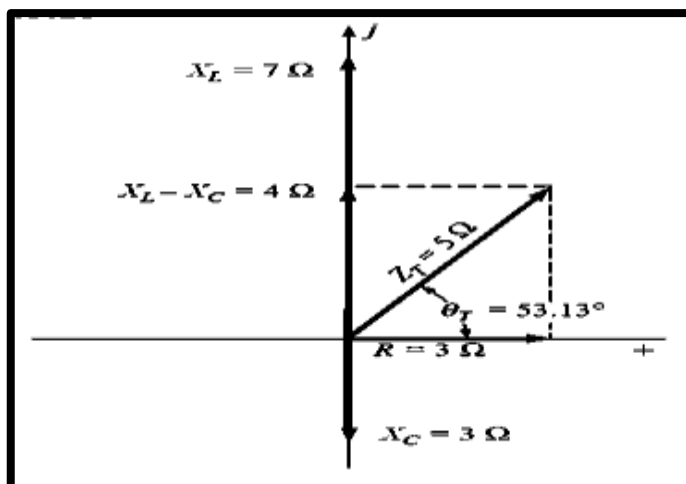
$$V_C = IZ_C = 3 \angle -90^\circ \times 10 \angle -53.13^\circ = 30 \angle -143.13^\circ \text{ V}$$





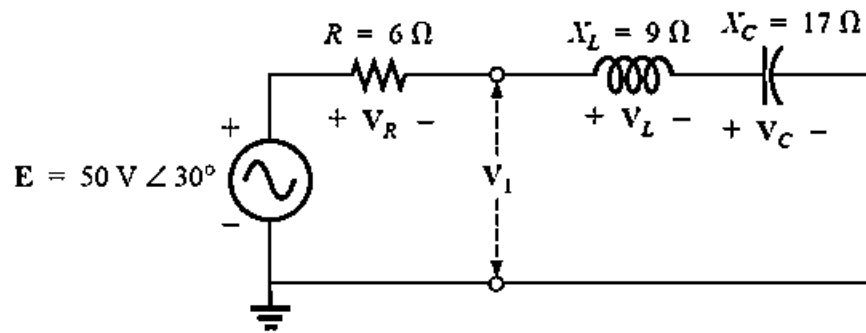EXAMPLE: Using the voltage divider rule, find the unknown voltages V_R , V_L , V_C , and V_1 for the circuit.



Solutions:

$$\begin{aligned} V_R &= \frac{Z_R E}{Z_R + Z_L + Z_C} = \frac{(6 \Omega \angle 0^\circ)(50 \text{ V} \angle 30^\circ)}{6 \Omega \angle 0^\circ + 9 \Omega \angle 90^\circ + 17 \Omega \angle -90^\circ} \\ &= \frac{300 \angle 30^\circ}{6 + j9 - j17} = \frac{300 \angle 30^\circ}{6 - j8} \\ &= \frac{300 \angle 30^\circ}{10 \angle -53.13^\circ} = 30 \text{ V} \angle 83.13^\circ \end{aligned}$$

$$\begin{aligned} V_L &= \frac{Z_L E}{Z_T} = \frac{(9 \Omega \angle 90^\circ)(50 \text{ V} \angle 30^\circ)}{10 \Omega \angle -53.13^\circ} = \frac{450 \text{ V} \angle 120^\circ}{10 \angle -53.13^\circ} \\ &= 45 \text{ V} \angle 173.13^\circ \end{aligned}$$

$$\begin{aligned} V_C &= \frac{Z_C E}{Z_T} = \frac{(17 \Omega \angle -90^\circ)(50 \text{ V} \angle 30^\circ)}{10 \Omega \angle -53.13^\circ} = \frac{850 \text{ V} \angle -60^\circ}{10 \angle -53^\circ} \\ &= 85 \text{ V} \angle -6.87^\circ \end{aligned}$$

$$\begin{aligned} V_1 &= \frac{(Z_L + Z_C)E}{Z_T} = \frac{(9 \Omega \angle 90^\circ + 17 \Omega \angle -90^\circ)(50 \text{ V} \angle 30^\circ)}{10 \Omega \angle -53.13^\circ} \\ &= \frac{(8 \angle -90^\circ)(50 \angle 30^\circ)}{10 \angle -53.13^\circ} \\ &= \frac{400 \angle -60^\circ}{10 \angle -53.13^\circ} = 40 \text{ V} \angle -6.87^\circ \end{aligned}$$