



## **AC TO AC CONVERTER**

- 1. AC-to ac converters transfer power from one ac system to another with waveforms of different amplitude, frequency, or phase.*
- 2. These converters are designed for one-quadrant to four quadrant operation..*
- 3. Typical applications are listed below :*

- Variable speed drives for appliances and tools
- Four-quadrant PWM drives for traction
- Steel mill roll drives
- Industrial heating
- On-load transformer tap changing

### **1. Direct conversion**

- *The ac input waveforms are directly converted into the desired output waveforms.*
- *Converters that do not involve change of frequency are call the **ac controllers**.*
- *The converters with the change of frequency are called **cycloconverters**.*

### **2. Indirect conversion**

- *Indirect ac-ac conversion involves an intermediate dc stage, called the **dc-link** or **dc bus** and the converters are called the **dc-link converters**.*

### **1. AC voltage controllers**

#### **(1) Single-phase controller**

- (a) unidirectional or half-wave control
- (b) bidirectional or full-wave control

#### **(2) Three-phase controller**

- (a) unidirectional or half-wave control
- (b) bidirectional or full-wave control

## 2. Cycloconverters


### (1) Single-phase cyclocontroller

### (2) Three-phase cyclocontroller



*For power transfer, two types of control are normally used :*

(1) On-off control

(2) Phase-angle control

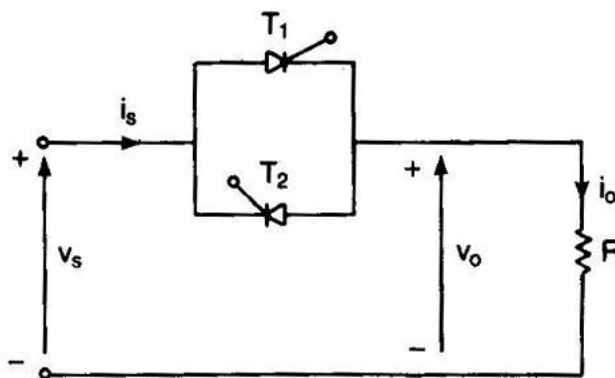

**On-off control**

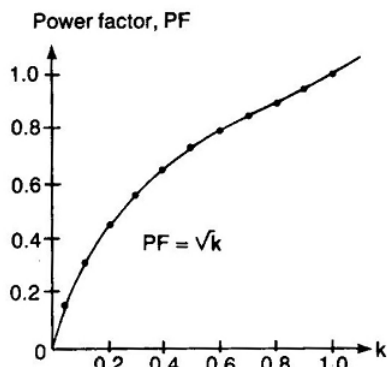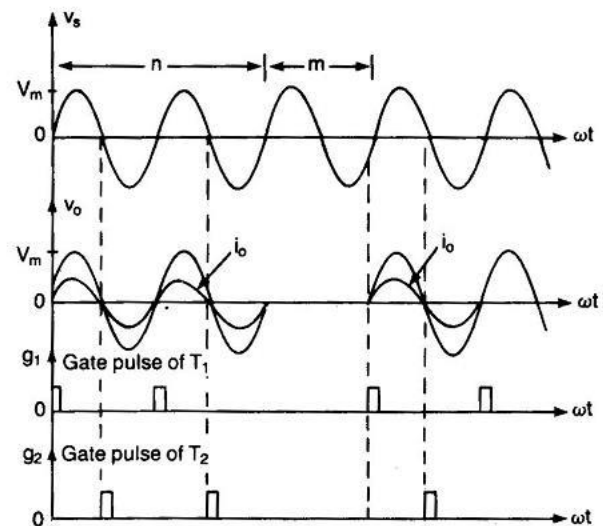

*For a sinusoidal input voltage,*

$$v_s = V_m \sin \omega t$$

$$= \sqrt{2} V_s \sin \omega t$$

*If the input voltage is connected to load for n cycles and is disconnected for m cycles, the rms output (or load) voltage can be found from*

$$V_o = \left[ \frac{n}{2\pi(n+m)} \int_0^{2\pi} 2V_s^2 \sin^2 \omega t d(\omega t) \right]^{1/2}$$

$$= V_s \sqrt{\frac{n}{m+n}} = V_s \sqrt{k}$$

$k = n/(m+n)$  : duty cycle


$V_s$  : rms phase voltage

### EXAMPLE 1:-

An ac voltage controller in figure has a resistive load of  $R=10\Omega$  and the *rms* input voltage is  $V_s=120\text{V}$ , 60Hz.

The thyristors switch is on for  $n=25$  cycles and is off for  $m=75$  cycles. Determine,

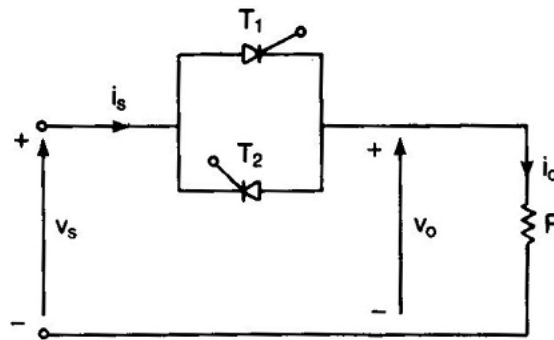- The *rms* output voltage  $V_o$
- The input power factor  $PF$
- The average and *rms* current of thyristors



$$R = 10\Omega, V_s = 120\text{ V}, V_m = \sqrt{2} \times 120 = 169.7\text{ V}, k = \frac{n}{n+m} = 0.25$$

$$(a) V_o = \left[ \frac{n}{2\pi(n+m)} \int_0^{2\pi} 2V_s^2 \sin^2 \omega t d(\omega t) \right]^{1/2}$$

$$= V_s \sqrt{k} = V_s \sqrt{\frac{n}{m+n}} = 120 \sqrt{\frac{25}{100}} = 60\text{ V}$$

$$(b) I_o = V_o / R = 60 / 10 = 6.0\text{ A}$$

$$\text{the load power, } P_o = I_o^2 R = 6^2 \times 10 = 360\text{ W}$$

Since the input current is the same as the load current,  
the input volt – amperes is

$$VA = V_s I_s = V_s I_o = 120 \times 6 = 720\text{ W}$$



Thus, input power factor,

$$PF = \frac{P_o}{VA} = \sqrt{\frac{n}{m+n}} = \sqrt{k} = \sqrt{0.25} = \frac{360}{720} = 0.5 \text{ (lagging)}$$

(c) The peak thyristor current is  $I_m = V_m / R = 169.7 / 10 = 16.97 \text{ A}$

The average current of thyristors is

$$\begin{aligned} I_A &= \frac{n}{2\pi(m+n)} \int_0^\pi I_m \sin \omega t \, d(\omega t) = \frac{I_m n}{\pi(m+n)} = \frac{k I_m}{\pi} \\ &= \frac{16.97}{\pi} \times 0.25 = 1.33 \text{ A} \end{aligned}$$

The rms current of thyristors is

$$\begin{aligned} I_R &= \left[ \frac{n}{2\pi(m+n)} \int_0^\pi I_m^2 \sin^2 \omega t \, d(\omega t) \right]^{1/2} \\ &= \frac{I_m}{2} \sqrt{\frac{n}{m+n}} = \frac{I_m \sqrt{k}}{2} \\ &= \frac{16.97}{2} \times \sqrt{0.25} = 4.24 \text{ A} \end{aligned}$$



**Example 2:- A single-phase voltage controller has input voltage of 230 V, 50 Hz and a load of  $R=15\ \Omega$ . For 6 cycles on and 4 cycles off, determine**

**(a) rms output voltage.**

**(b) input pf .**

**(c) average and rms thyristor currents.**



**Ans:-**

**a)  $V_o=178.157\ V$**

**b)  $P_f= 0.7746$**

**c)  $I_a= 4.1407\ A$  ,  $I_{rms}=8.397\ A$**

## Unidirectional Controller

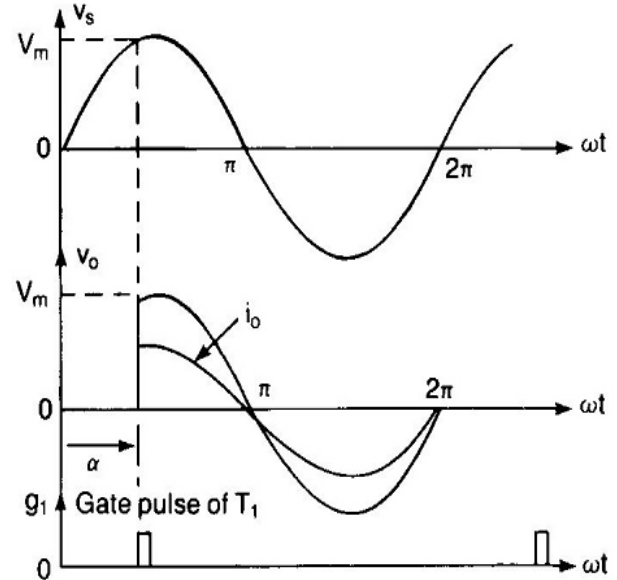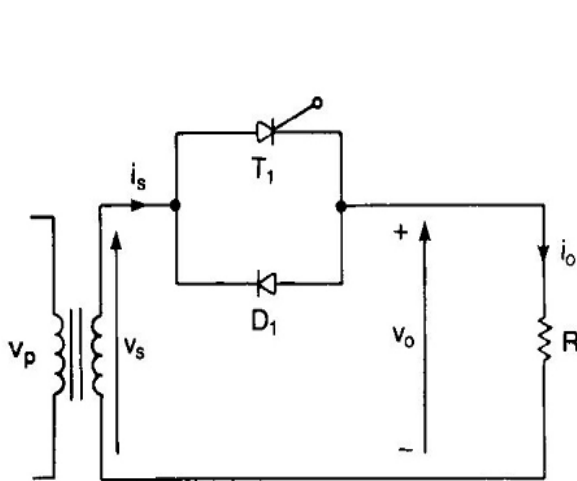

## Single-phase angle control

if input voltage,  $v_s = V_m \sin \omega t = \sqrt{2} V_s \sin \omega t$

delay angle of thyristor  $T_1$ ,  $\omega t = \alpha$

the rms output voltage,

$$\begin{aligned}
 V_o &= \left\{ \frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} 2V_s^2 \sin^2 \omega t \, d(\omega t) + \int_{\pi}^{2\pi} 2V_s^2 \sin^2 \omega t \, d(\omega t) \right] \right\}^{1/2} \\
 &= \left\{ \frac{2V_s^2}{4\pi} \left[ \int_{\alpha}^{\pi} (1 - \cos 2\omega t) \, d(\omega t) + \int_{\pi}^{2\pi} (1 - \cos 2\omega t) \, d(\omega t) \right] \right\}^{1/2} \\
 &= V_s \left[ \frac{1}{2\pi} \left( 2\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}
 \end{aligned}$$

*the average value of output voltage,*

$$V_{dc} = \frac{1}{2\pi} \left[ \int_{\alpha}^{\pi} \sqrt{2} V_s \sin \omega t \, d(\omega t) + \int_{\pi}^{2\pi} \sqrt{2} V_s \sin \omega t \, d(\omega t) \right]$$

$$= \frac{\sqrt{2} V_s}{2\pi} (\cos \alpha - 1)$$


$$\text{If, } \alpha = 0 \rightarrow \pi : V_o = V_s \rightarrow \frac{V_s}{\sqrt{2}}, \quad V_{dc} = 0 \rightarrow \frac{-\sqrt{2} V_s}{\pi}$$

### EXAMPLE 2:-

**A single-phase ac voltage controller in figure has a resistive load of  $R=10\Omega$  and the input voltage is  $V_s=120\text{V}$ , 60Hz.**

**The delay angle of thyristor  $T_1$  is  $\alpha=\pi/2$ . Determine,**

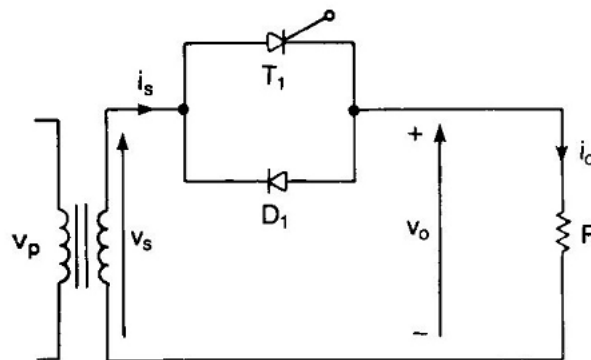- (a) The *rms* value of output voltage  $V_o$**
- (b) The input power factor  $PF$**
- (c) The average input current**



$$R = 10\Omega, \quad V_s = 120\text{ V}, \quad V_m = \sqrt{2} \times 120 = 169.7\text{ V}, \quad \alpha = \frac{\pi}{2}$$

*(a) the rms value of output voltage,*

$$V_o = V_s \left[ \frac{1}{2\pi} \left( 2\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2} = 120 \sqrt{\frac{3}{4}} = 103.92\text{ V}$$





(b) the rms load current,

$$I_o = \frac{V_o}{R} = \frac{103.92}{10} = 10.392 \text{ A}$$

the load power,  $P_o = I_o^2 R = 10.392^2 \times 10 = 1079.94 \text{ W}$

$$VA = V_s I_s = V_s I_o = 120 \times 10.392 = 1247.04 \text{ VA}$$

the input power factor,

$$PF = \frac{P_o}{VA} = \frac{V_o}{V_s} = \left[ \frac{1}{2\pi} \left( 2\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2} = \sqrt{\frac{3}{4}} = \frac{1079.94}{1247.04} \\ = 0.866 \text{ (lagging)}$$

(c) the average output voltage,

$$V_{dc} = \frac{\sqrt{2} V_s}{2\pi} (\cos \alpha - 1) = -120 \times \frac{\sqrt{2}}{2\pi} = -27 \text{ V}$$

the average input current

$$I_D = \frac{V_{dc}}{R} = -\frac{27}{10} = -2.7 \text{ A}$$