



## Lecture Three

### Methods of analysis

#### 3.1 Introduction

Having understood the fundamental laws of circuit theory (Ohm's law and Kirchhoff's laws), we are now prepared to apply these laws to develop two powerful techniques for circuit analysis: nodal analysis, which is based on a systematic application of Kirchhoff's current law (KCL), and mesh analysis, which is based on a systematic application of Kirchhoff's voltage law (KVL). With the two techniques to be developed, we can analyze almost any circuit by obtaining a set of simultaneous equations that are then solved to get the required current or voltage values.

#### 3.2 Nodal analysis

Nodal analysis provides a general procedure for analyzing circuits using node voltages as the circuit variables. Choosing node voltages instead of element voltages as circuit variables is convenient and reduces the number of equations one must solve simultaneously. To simplify matters, we shall assume in this section that circuits do not contain voltage sources. Circuits that contain voltage sources will be analyzed in the next section.

##### Steps to Determine Node Voltages:



1. Select a node as the reference node. Assign voltages  $v_1, v_2, \dots, v_{n-1}$  to the remaining **n-1** nodes. The voltages are referenced with respect to the reference node.
2. Apply **KCL** to each of the **n-1** nonreference nodes. Use Ohm's law to express the branch currents in terms of node voltages.
3. Solve the resulting simultaneous equations to obtain the unknown node voltages.



Once a reference node is selected, voltages are assigned to nonreference nodes relative to it. For example, in Fig. 3.2(a), node 0 is the reference ( $v = 0$ ), while nodes 1 and 2 have voltages  $v_1$  and  $v_2$ . These voltages represent the potential rise from the reference node. Next, we apply Kirchhoff's Current Law (KCL) to each nonreference node. To simplify visualization, Fig. 3.2(b) introduces currents  $i_1$ ,  $i_2$ , and  $i_3$  through resistors  $R_1$ ,  $R_2$ , and  $R_3$ , respectively. Applying KCL at node 1 gives:

**At node 1:**  $I_1 = I_2 + i_1 + i_2$  (3.1)

**At node 2:**  $I_2 + i_2 = i_3$  (3.2)

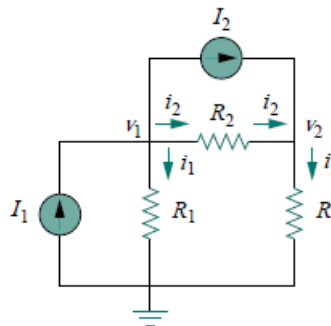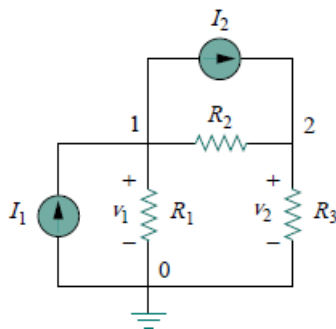

We now apply Ohm's law to express the unknown currents  $i_1$ ,  $i_2$ , and  $i_3$  in terms of node voltages.

Current flows from a **higher** potential to a **lower** potential in a resistor

We can express this principle as  $i = \frac{v_{higher} - v_{lower}}{R}$  (3.3)

With this in mind, we obtained:  $i_1 = \frac{v_1 - 0}{R_1}$ , or  $i_1 = G_1 v_1$

$$i_2 = \frac{v_1 - v_2}{R_2}, \text{ or } i_2 = G_2 (v_1 - v_2) \quad (3.4)$$

$$i_3 = \frac{v_2 - 0}{R_3}, \text{ or } i_3 = G_3 v_2$$



Substituting Eq. (3.4) in Eqs. (3.1) and (3.2) results, respectively, in

$$I_1 = I_2 + \frac{v_1}{R_1} + \frac{v_1 - v_2}{R_2} \quad (3.5)$$

$$I_2 + \frac{v_1 - v_2}{R_2} = \frac{v_2}{R_3} \quad (3.6)$$

In terms of the conductance. Eqs. (3.5) and (3.6) become

The conductance  $G$  of a resistor is the reciprocal of its resistance

$$G = \frac{1}{R}$$

$$I_1 = I_2 + G_1 v_1 + G_2 (v_1 - v_2) \quad (3.7)$$

$$I_1 - I_2 = G_1 v_1 + G_2 v_1 - G_2 v_2$$

$$I_1 - I_2 = (G_1 + G_2) v_1 - G_2 v_2$$

$$I_2 + G_2 (v_1 - v_2) = G_3 v_2 \quad (3.8)$$

$$I_2 = G_3 v_2 - G_2 (v_1 - v_2)$$

$$I_2 = G_3 v_2 - G_2 v_1 + G_2 v_2$$

$$I_2 = -G_2 v_1 + G_2 v_2 + G_3 v_2$$

$$I_2 = -G_2 v_1 + (G_2 + G_3) v_2$$


To obtain the node voltages  $v_1$  and  $v_2$  using any standard method, such as the **elimination method or Cramer's rule**.

To use Cramer's rule, one must cast the simultaneous equations in matrix form. For example, Eqs. (3.7) and (3.8) can be cast in matrix form as

$$\begin{bmatrix} G_1 + G_2 & -G_2 \\ -G_2 & G_2 + G_3 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} I_1 - I_2 \\ I_2 \end{bmatrix}$$



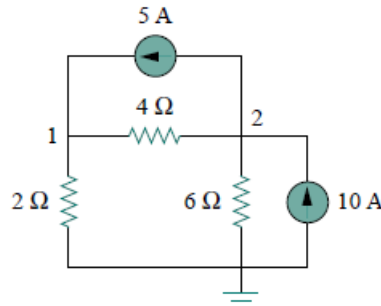**Example (1):** Calculate the node voltages in the circuit shown in the figure below



**Solution**

Assign nodes 1 and 2 to determine voltages  $v_1$  and  $v_2$ .

Selected the current to apply KCL

At node 1, applying KCL and Ohm's law gives

$$i_1 = i_2 + i_3 \Rightarrow 5 = \frac{v_1 - v_2}{4} + \frac{v_1 - 0}{2}$$

Multiplying each term in the last equation by 4, we obtain

$$20 = v_1 - v_2 + 2v_1 \Rightarrow 3v_1 - v_2 = 20 \quad \text{eq (1)}$$

At node 2, we do the same thing and get

$$i_2 + i_4 = i_1 + i_5 \Rightarrow \frac{v_1 - v_2}{4} + 10 = 5 + \frac{v_2 - 0}{6}$$


Multiplying each term by 12 results in

$$3v_1 - 3v_2 + 120 = 60 + 2v_2 \Rightarrow -3v_1 + 5v_2 = 60 \quad \text{eq (2)}$$

**Method 1** Using the elimination technique, from eq(1&2)

$$-3v_1 + 5(3v_1 - 20) = 60 \Rightarrow -3v_1 + 15v_1 - 100 = 60 \Rightarrow 12v_1 = 160$$

$$\Rightarrow v_1 = 13.33V$$

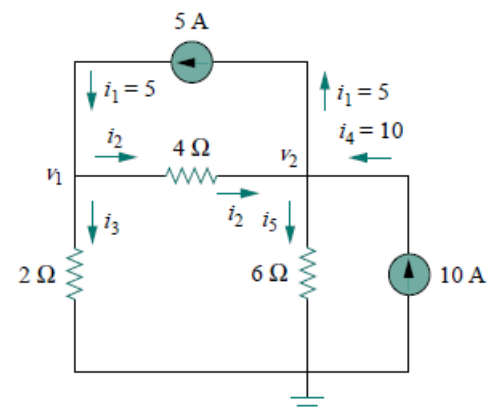



$$v_2 = 3v_1 - 20 \Rightarrow v_2 = 3(13.33) - 20 = 20V$$

**Method 2** To use Cramer's rule, we need to put Eqs. (1) and (2) in matrix form as

$$\begin{bmatrix} 3 & -1 \\ -3 & 5 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} 20 \\ 60 \end{bmatrix}$$

The Cramer's rule:  $v_1 = \frac{\Delta_1}{\Delta}$ ,  $v_2 = \frac{\Delta_2}{\Delta}$

The determinant of the matrix is:

$$\Delta = \begin{vmatrix} 3 & -1 \\ -3 & 5 \end{vmatrix} = 15 - 3 = 12$$

We now obtain  $v_1$  and  $v_2$  as

$$v_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 20 & -1 \\ 60 & 5 \end{vmatrix}}{\Delta} = \frac{100 + 60}{12} = 13.333V$$

$$v_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 3 & 20 \\ -3 & 60 \end{vmatrix}}{\Delta} = \frac{180 + 60}{12} = 20V$$

*giving us the same result as the elimination method.*

If we need the currents, we can easily calculate them from the values of the nodal voltages.

$$i_1 = 5 \text{ A}, \quad i_2 = \frac{v_1 - v_2}{4} = \frac{13.33 - 20}{4} = -1.6667 \text{ A},$$


$$i_3 = \frac{v_1}{2} = 6.666A \quad i_4 = 10 \text{ A},$$

$$i_5 = \frac{v_2}{6} = 3.333 \text{ A}$$

The fact that  $i_2$  is negative shows that the current flows in the direction opposite to the one assumed




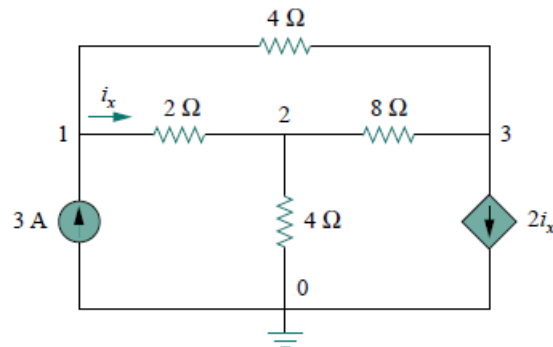**Example (2):** Determine the voltages at the nodes in the figure below



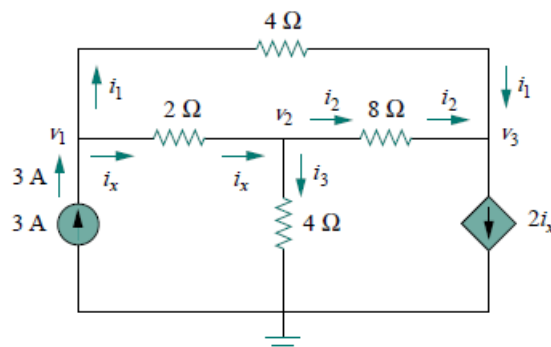**Solution**

The circuit in this example has three nonreference nodes, unlike the previous example which has two nonreference nodes. We assign voltages to the three nodes as shown in the figure below and label the currents



At node 1,  $3 = i_1 + i_x \Rightarrow 3 = \frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{2}$

Multiplying by 4 and rearranging terms, we get

$$3v_1 - 2v_2 - v_3 = 12 \quad \text{eq(1)}$$

At node 2,

$$i_x = i_2 + i_3 \Rightarrow \frac{v_1 - v_2}{2} = \frac{v_2 - v_3}{8} + \frac{v_2 - 0}{4}$$

Multiplying by 8 and rearranging terms, we get

$$-4v_1 + 7v_2 - v_3 = 0 \quad \text{eq(2)}$$



At node 3,

$$i_1 + i_2 = 2i_x \Rightarrow \frac{v_1 - v_3}{4} + \frac{v_2 - v_3}{8} = \frac{2(v_1 - v_2)}{2}$$

Multiplying by 8, rearranging terms, and dividing by 3, we get

$$2v_1 - 3v_2 + v_3 = 0 \quad \text{eq(3)}$$

We have three simultaneous equations to solve to get the node voltages  $v_1$ ,  $v_2$ , and  $v_3$ . We shall solve the equations in two ways

**METHOD 1** Using the elimination technique, we add Eqs. (1 & 3)

$$5v_1 - 5v_2 = 12$$

$$v_1 - v_2 = \frac{12}{5} \quad \text{eq(4)}$$

Adding Eqs. (2) and (3) gives

$$-2v_1 + 4v_2 = 0 \Rightarrow v_1 = 2v_2 \quad \text{eq(5)}$$

Substituting Eq. (5) into Eq. (4) yields

$$2v_2 - v_2 = 2.4 \Rightarrow v_2 = 2.4 \text{ V}, \quad v_1 = 2v_2 = 4.8 \text{ V}$$

From Eq. (3), we get

$$v_3 = 3v_2 - 2v_1 = 3v_2 - 4v_2 = -v_2 = -2.4 \text{ V}$$

Thus,

$$v_1 = 4.8 \text{ V}, \quad v_2 = 2.4 \text{ V}, \quad v_3 = -2.4 \text{ V}$$



**METHOD 2** To use Cramer's rule, we put Eqs. (1) to (3) in matrix form.

$$\begin{bmatrix} 3 & -2 & -1 \\ -4 & 7 & -1 \\ 2 & -3 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

From this, we obtain

$$v_1 = \frac{\Delta_1}{\Delta}, \quad v_2 = \frac{\Delta_2}{\Delta}, \quad v_3 = \frac{\Delta_3}{\Delta}$$

where  $\Delta_1$ ,  $\Delta_2$ , and  $\Delta_3$  are the determinants to be calculated as follows

$$\Delta = \begin{vmatrix} 3 & -2 & -1 \\ -4 & 7 & -1 \\ 2 & -3 & 1 \end{vmatrix} = \begin{vmatrix} 3 & -2 & -1 \\ -4 & 7 & -1 \\ 2 & -3 & 1 \end{vmatrix}$$

$$= 21 - 12 + 4 + 14 - 9 - 8 = 10$$

Similarly, we obtain

$$\Delta_1 = \begin{vmatrix} 12 & -2 & -1 \\ 0 & 7 & -1 \\ 0 & -3 & 1 \end{vmatrix} = \begin{vmatrix} 12 & -2 & -1 \\ 0 & 7 & -1 \\ 0 & -3 & 1 \end{vmatrix}$$

$$= 84 + 0 + 0 - 0 - 36 - 0 = 48$$

$$\Delta_2 = \begin{vmatrix} 3 & 12 & -1 \\ -4 & 0 & -1 \\ 2 & 0 & 1 \end{vmatrix} = \begin{vmatrix} 3 & 12 & -1 \\ -4 & 0 & -1 \\ 2 & 0 & 1 \end{vmatrix}$$

$$= 0 + 0 - 24 - 0 - 0 + 48 = 24$$





$$\Delta_3 = \begin{vmatrix} 3 & -2 & 12 \\ -4 & 7 & 0 \\ 2 & -3 & 0 \\ 3 & -2 & 12 \\ -4 & 7 & 0 \end{vmatrix} = 0 + 144 + 0 - 168 - 0 - 0 = -24$$

Thus, we find

$$v_1 = \frac{\Delta_1}{\Delta} = \frac{48}{10} = 4.8 \text{ V}, \quad v_2 = \frac{\Delta_2}{\Delta} = \frac{24}{10} = 2.4 \text{ V}$$

$$v_3 = \frac{\Delta_3}{\Delta} = \frac{-24}{10} = -2.4 \text{ V}$$

## PRACTICE PROBLEM

Find the voltages at the three nonreference nodes in the circuit of the figure

**Answer:**  $v_1 = 80 \text{ V}$ ,  $v_2 = -64 \text{ V}$ ,  $v_3 = 156 \text{ V}$ .

