



Sixth Week :

AC Circuits – R-L Series

Course Name: Electrical Circuits

Stage: One

Academic Year: 2024–2025

Assis.Lecturer. Zahraa Hazim Obaid

Saif Ali Abbas


What is an R-L Series Circuit?

An R-L series circuit is an alternating current (AC) circuit that consists of two fundamental components connected in series: a resistor (R) and an inductor (L). A common example of an R-L series circuit is the winding of an electric motor.

Basic Concept

An R-L series circuit is an AC circuit composed of a resistor and an inductor connected in series.

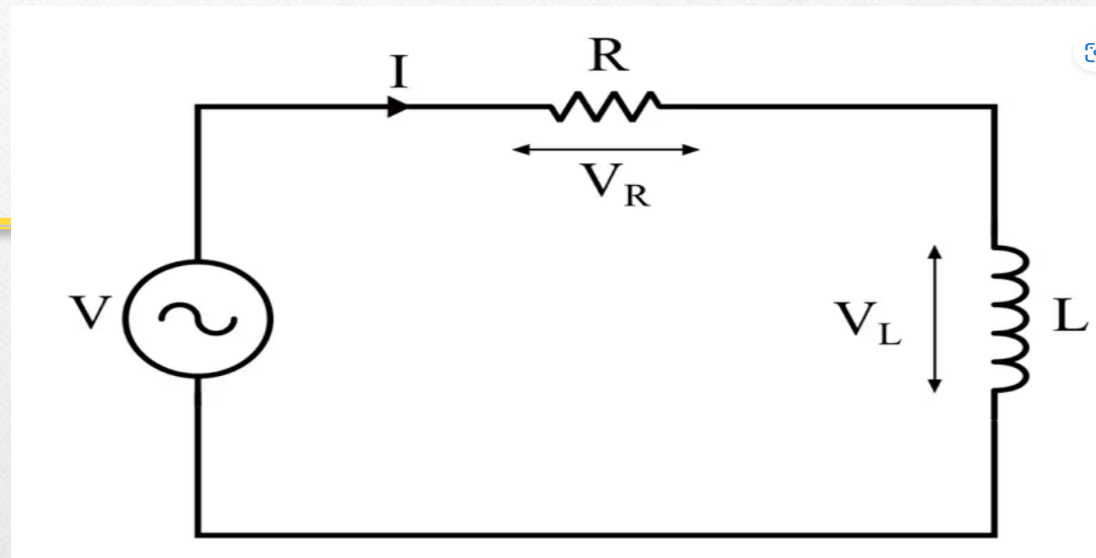A typical R-L circuit is illustrated in the following diagram.



Voltage Equation in an R-L Series Circuit

The voltage across the circuit can be expressed using the algebraic sum of the voltage drops across each component.
Here


$$V = V_R + V_L$$

- V is the RMS (Root Mean Square) value of the supply voltage.
- V_R is the RMS voltage drop across the resistor R .
- V_L is the RMS voltage across the inductor L .

The voltage drop across the resistor is given by:

$$V_R = i \times R$$

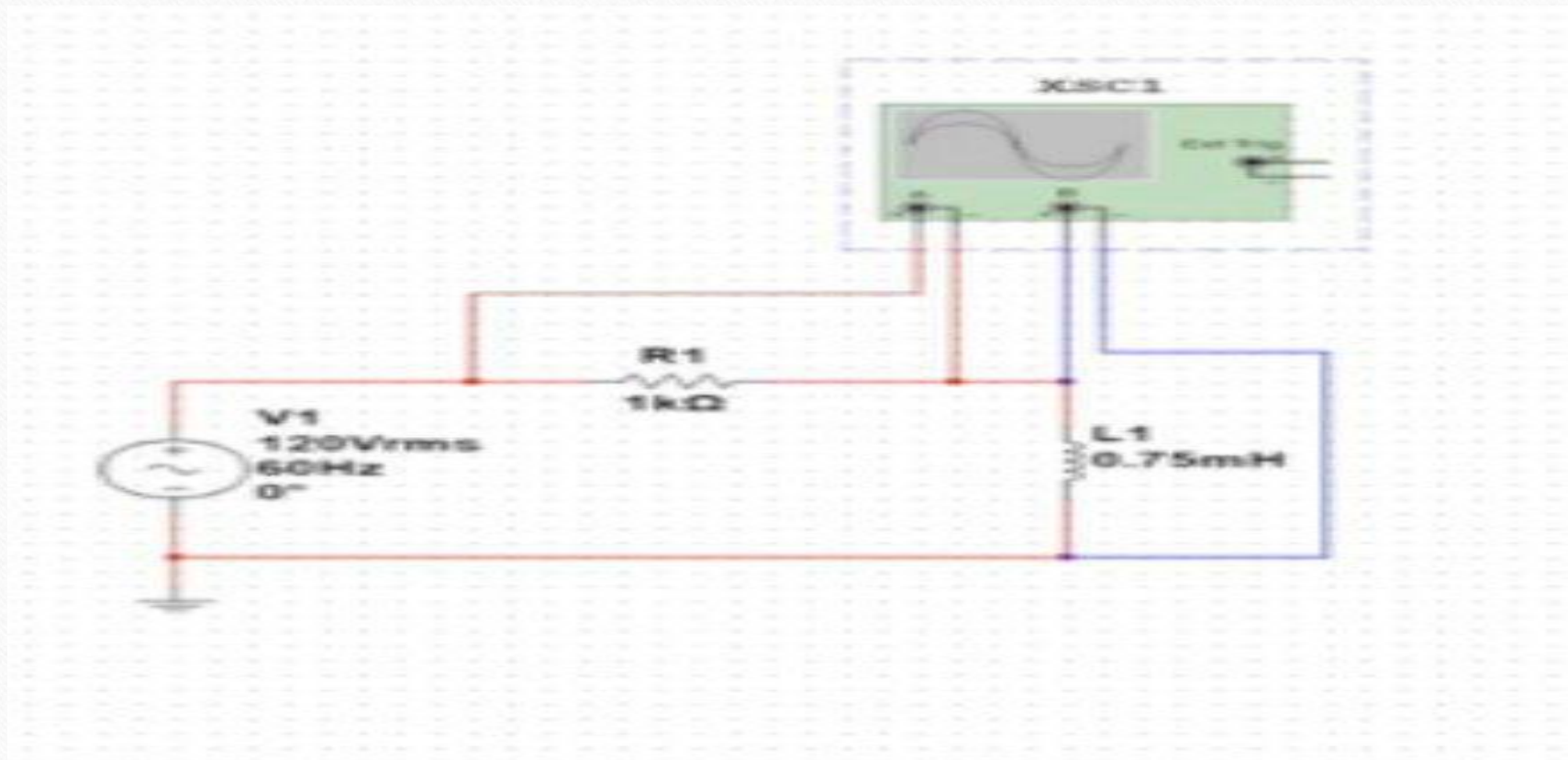The diagram shows a circuit consisting of a resistor and an inductor connected in series.



Thank you