

HomeWork 2

- 1- The voltage across a 5Ω resistor is as indicated. Find the sinusoidal expression for the current. In addition, sketch the I & v sinusoidal waveforms on the same axis.
- a. $150 \sin 200t$ b. $30 \sin (377t + 20^\circ)$
c. $40 \cos(\omega t + 10^\circ)$ d. $-80 \sin(\omega t + 40^\circ)$
- 2- A circuit dissipates 100 W (average power) at 150 V (effective input voltage) and 2 A (effective input current). What is the power factor ? Repeat if the power is 0 W ; 300 W.
- 3- Determine the inductive reactance (in ohms) of a 2 H coil
for
- a. dc
- and for the following frequencies:
- b. 10 Hz c. 60 Hz
d. 2000 Hz e. 100,000 Hz

- 4- For the system in Fig. below , find the sinusoidal expression for the unknown voltage V_a if :

$$e_{in} = 60 \sin(377t + 20^\circ)$$

$$V_b = 20 \sin(377t - 20^\circ)$$

