



Three-Phase Circuits

Unbalanced Three-Phase Systems

An unbalanced system is caused by two possible situations:

- (1) the source voltages are not equal in magnitude and/or differ in phase by angles that are unequal.
- (2) load impedances are unequal. Thus,

An **unbalanced** system is due to unbalanced voltage sources or an unbalanced load

To simplify analysis, we will assume **balanced source** voltages, but an **unbalanced load**.

Unbalanced three-phase systems are solved by direct application of mesh and nodal analysis. Fig.1 shows an example of an unbalanced three-phase system that consists of balanced source voltages (not shown in the figure) and an unbalanced Y-connected load (shown in the figure). Since the load is unbalanced, Z_A , Z_B and Z_C are not equal.

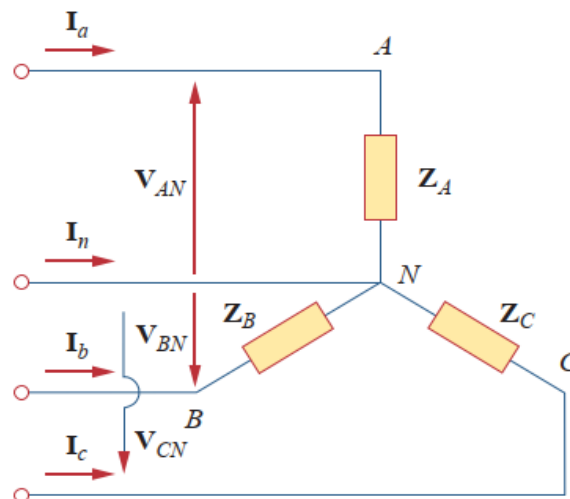


Fig.1 Unbalanced three-phase Y-connected load.



The line
determined by

currents are
Ohm's law as

$$\mathbf{I}_a = \frac{\mathbf{V}_{AN}}{\mathbf{Z}_A}, \quad \mathbf{I}_b = \frac{\mathbf{V}_{BN}}{\mathbf{Z}_B}, \quad \mathbf{I}_c = \frac{\mathbf{V}_{CN}}{\mathbf{Z}_C} \quad (1)$$

This set of unbalanced line currents produces current in the neutral line, which is not zero as in a balanced system. Applying KCL at node N gives the neutral line current as

$$\mathbf{I}_n = -(\mathbf{I}_a + \mathbf{I}_b + \mathbf{I}_c) \quad (2)$$

In a three-wire system where the neutral line is absent, we can still find the line currents $\mathbf{I}_a$, $\mathbf{I}_b$ and $\mathbf{I}_c$ using mesh analysis. At node N, KCL must be satisfied so that $\mathbf{I}_a + \mathbf{I}_b + \mathbf{I}_c = 0$ in this case. The same could be done for an unbalanced Δ -Y, Y- Δ or Δ - Δ three-wire system.

Example 1:

The unbalanced Y-load of Fig.2 has balanced voltages of 100 V and the *acb* sequence. Calculate the line currents and the neutral current. Take $\mathbf{Z}_A = 15 \, \Omega$, $\mathbf{Z}_B = 10 + j5 \, \Omega$ and $\mathbf{Z}_C = 6 - j8 \, \Omega$

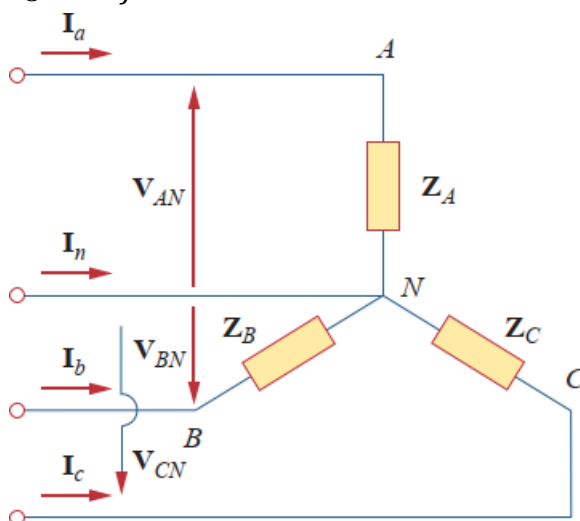


Fig.2



Solution:

The line currents are

$$\mathbf{I}_a = \frac{100 \angle 0^\circ}{15} = 6.67 \angle 0^\circ \text{ A}$$

$$\mathbf{I}_b = \frac{100 \angle 120^\circ}{10 + j5} = \frac{100 \angle 120^\circ}{11.18 \angle 26.56^\circ} = 8.94 \angle 93.44^\circ \text{ A}$$

$$\mathbf{I}_c = \frac{100 \angle -120^\circ}{6 - j8} = \frac{100 \angle -120^\circ}{10 \angle -53.13^\circ} = 10 \angle -66.87^\circ \text{ A}$$

the current in the neutral line is

$$\begin{aligned} \mathbf{I}_n &= -(\mathbf{I}_a + \mathbf{I}_b + \mathbf{I}_c) = -(6.67 - 0.54 + j8.92 + 3.93 - j9.2) \\ &= -10.06 + j0.28 = 10.06 \angle 178.4^\circ \text{ A} \end{aligned}$$