

جامعة المستقبل  
نحو جامعة مستدامة



**Al-Mustaqbal University - College of engineering**  
**Department of computer engineering**

**Second stage**

## **Lecture Week 12**

# **“Digital-to-Analog Converter (DAC)”**

**By DR. Mohammed Kadhim Rahma**

**2025**

# Learning Objectives

After this Lecture you will be able to:

- Determine the resolution and accuracy of a digitized analog signal.
- Explain how digital-to-analog converts operate
- Compare and contrast the characteristics several commonly used digital-to-analog converts operate

## Introduction

- \* Real signals (e.g., a voltage measured with a thermocouple or a speech signal recorded with a microphone) are analog quantities, varying continuously with time.
- \* Digital format offers several advantages: digital signal processing, storage, use of computers, robust transmission, etc.
- \* An ADC (Analog-to-Digital Converter) is used to convert an analog signal to the digital format.
- \* The reverse conversion (from digital to analog) is also required. For example, music stored in a DVD in digital format must be converted to an analog voltage for playing out on a speaker.
- \* A DAC (Digital-to-Analog Converter) is used to convert a digital signal to the analog format.

# Analog Signal Conversion

## Two Problems

Input

Analog-to-digital conversion (ADC):  
continuous signals converted to discrete values after sampling

Output

Digital-to-analog conversion (DAC)  
Discrete values converted to continuous signals

Number of bits in digital signal determines the resolution of the digital signals. Resolution also

# Resolution and Accuracy of Digitized Signals


**Resolution** - smallest number that can be measured

**Accuracy** - is the number measured correct
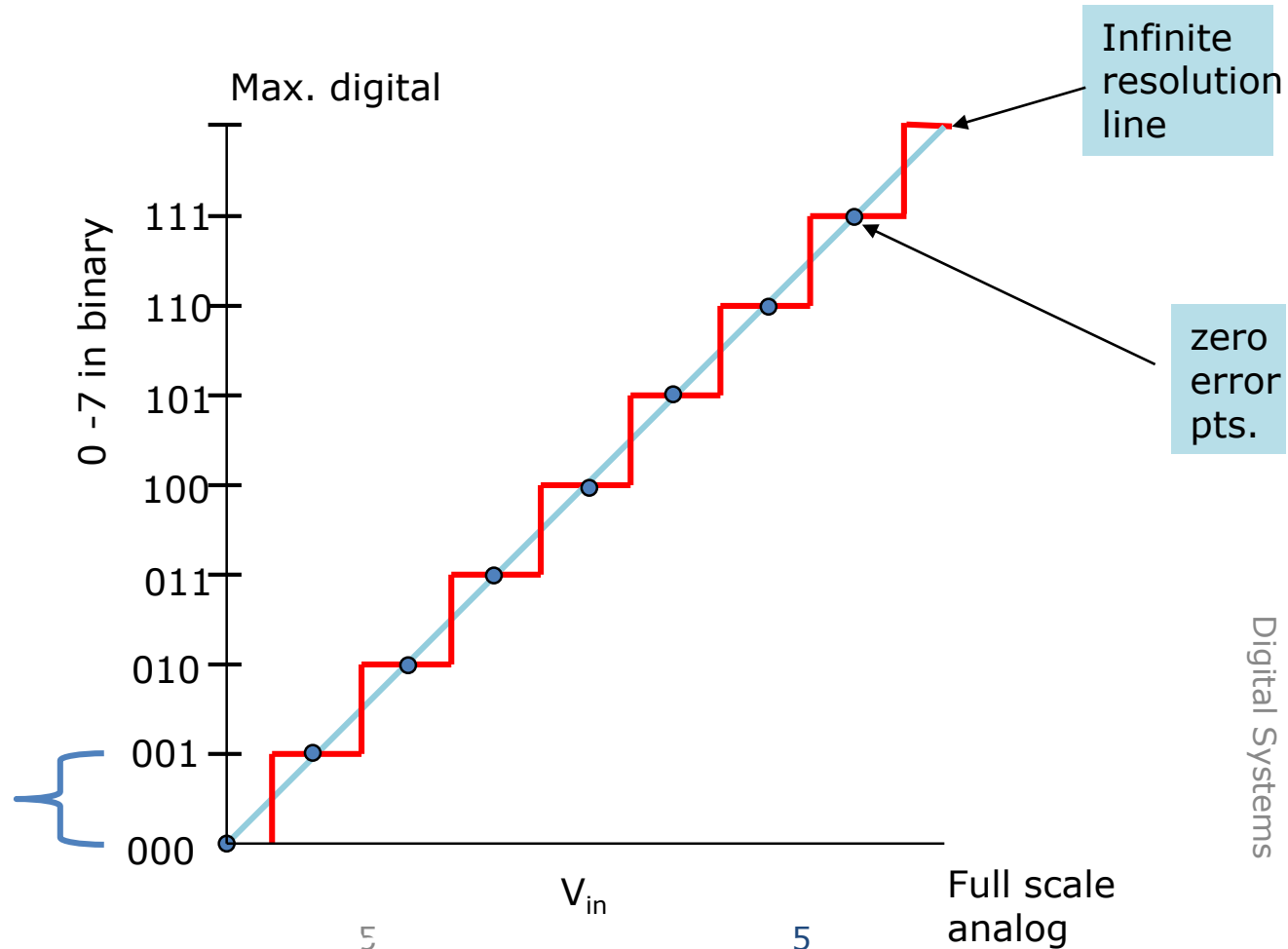
## ADC Resolution

The output is a discretized version of the continuous input.

Error determined by the step size of the digital representation



# Resolution Formulas

Resolution, in terms of full scale voltage of ADC, is equal to value of Least Significant Bit (LSB)

$$V_{LSB} = \frac{V_{fs}}{2^n}$$

Where

$V_{fs}$  = full scale voltage

$n$  = number of bits

$V_{LSB}$  = voltage value of LSB

Finite bit digital conversion introduces quantization errors that range from  $\pm V_{LSB} / 2$


Maximum  
quantization error is

$$Q.E. = \frac{V_{LSB}}{2}$$

Where Q.E. = quantization error

$V_{LSB}$  = voltage value of LSB

# Digital Resolution and Error in ADC

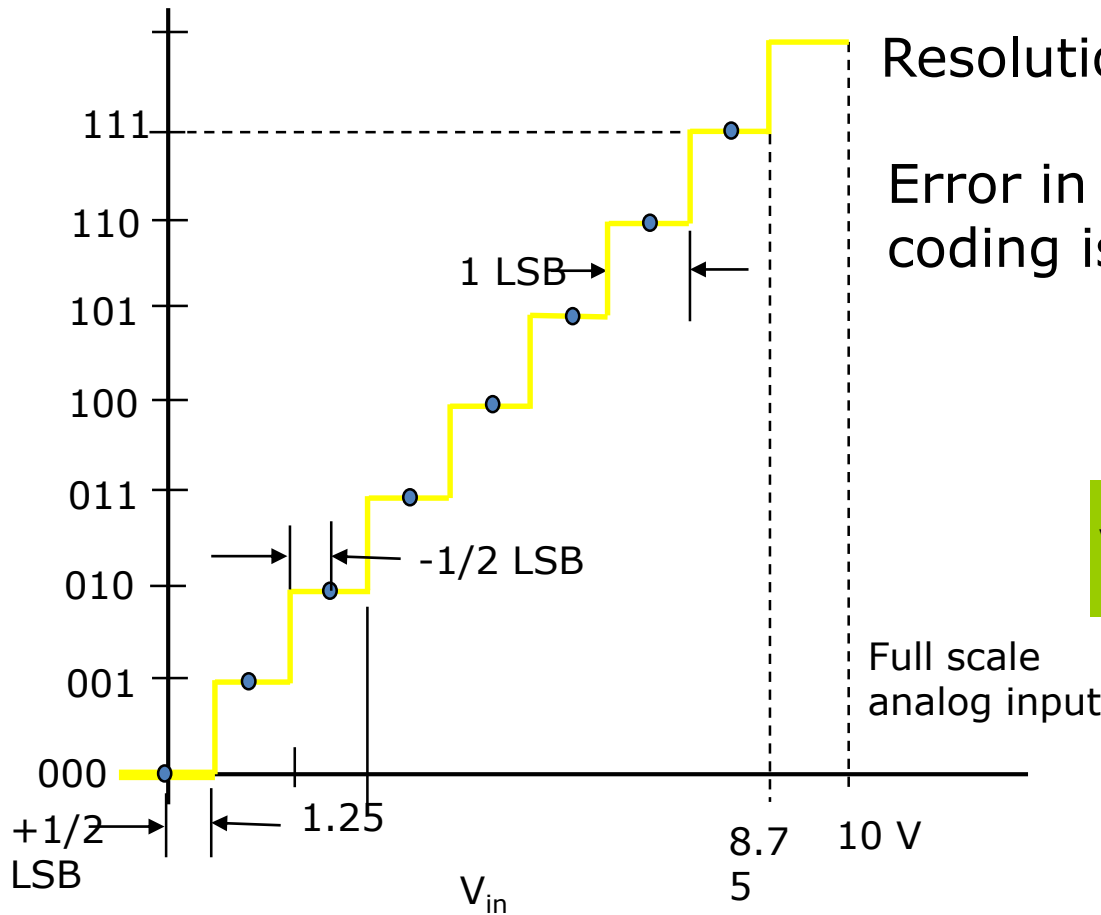

Resolution 3-bit system

Error in natural binary coding is  $\pm 1/2$  LSB

$$V_{\text{LSB}} = \frac{V_{\text{fs}}}{2^n}$$

$$V_{\text{LSB}} = \frac{10\text{V}}{2^3} = \frac{10}{8} = 1.25$$

Full scale analog input

All voltage values between 8.75-10 V map to the 111 code  
Number of counts reduced by 1

# Resolution Formulas

**Percent Resolution-** Based on the number of transitions ( $2^n - 1$ )

$$\% \text{ resolution} = \frac{1}{2^n - 1} \cdot 100\%$$

Where  $n$  = number of bits in digital representation

**Example 1:** An 8-bit digital system is used to convert an analog signal to digital signal for a data acquisition system. The voltage range for the conversion is 0-10 V. Find the resolution of the system and the value of the least significant bit

$n=8$  so signal converted to 256 different levels.

$V_{fs} = 10 \text{ Vdc}$

$$V_{\text{LSB}} = \frac{V_{fs}}{2^n}$$

$$V_{\text{LSB}} = \frac{V_{fs}}{2^n} = \frac{10 \text{ V}}{2^8} = \frac{10}{256} = 0.0390625 \text{ V}$$

$$\% \text{ resolution} = \frac{1}{2^n - 1} \cdot 100\%$$

$$\% \text{ resolution} = \frac{1}{2^8 - 1} \cdot 100\%$$

$$\% \text{ resolution} = 0.392\%$$



**Example 2:** The 8-bit converter of the previous example is replaced with a 12 bit system. Compute the resolution and the value of the least significant bit.


Signal converted to 4096 different levels  $n = 12$

$$V_{\text{LSB}} = \frac{V_{\text{fs}}}{2^n} \quad n = 12 \text{ bits } V_{\text{fs}} = 10 \text{ Vd} \quad V_{\text{LSB}} = \frac{V_{\text{fs}}}{2^n} = \frac{10 \text{ V}}{2^{12}} = \frac{10}{4096} = 0.002441 \text{ V}$$

$$\% \text{resolution} = \frac{1}{2^{12} - 1} \cdot 100\%$$


$$\% \text{resolution} = 0.0244\%$$

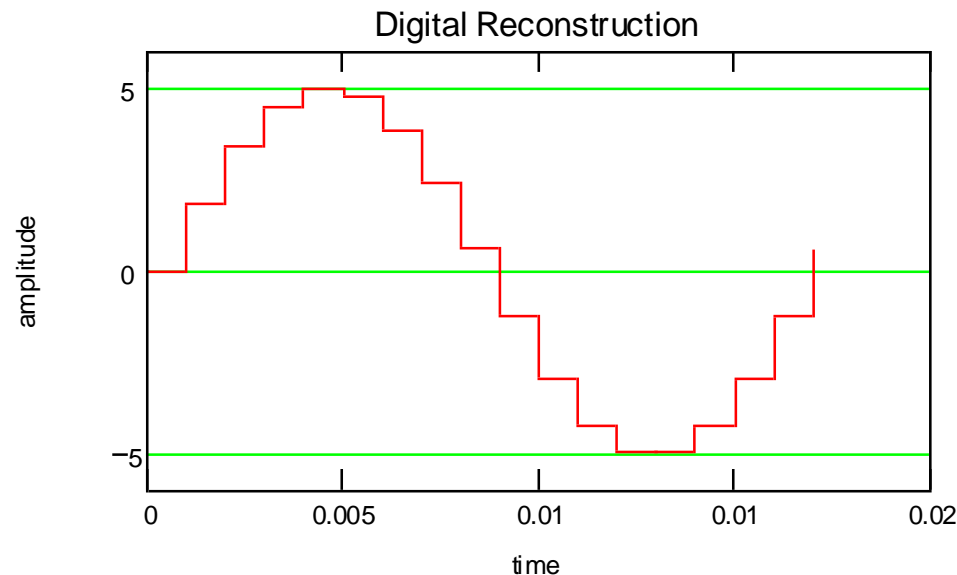Difference between analog value and digital reconstruction is quantizing error




# Digital-to-Analog Conversion
 
## Digital-to-Analog Converter (DAC) Transfer Function



# Type of Digital-to-analog converters

## Binary-Weighted Resistor DAC

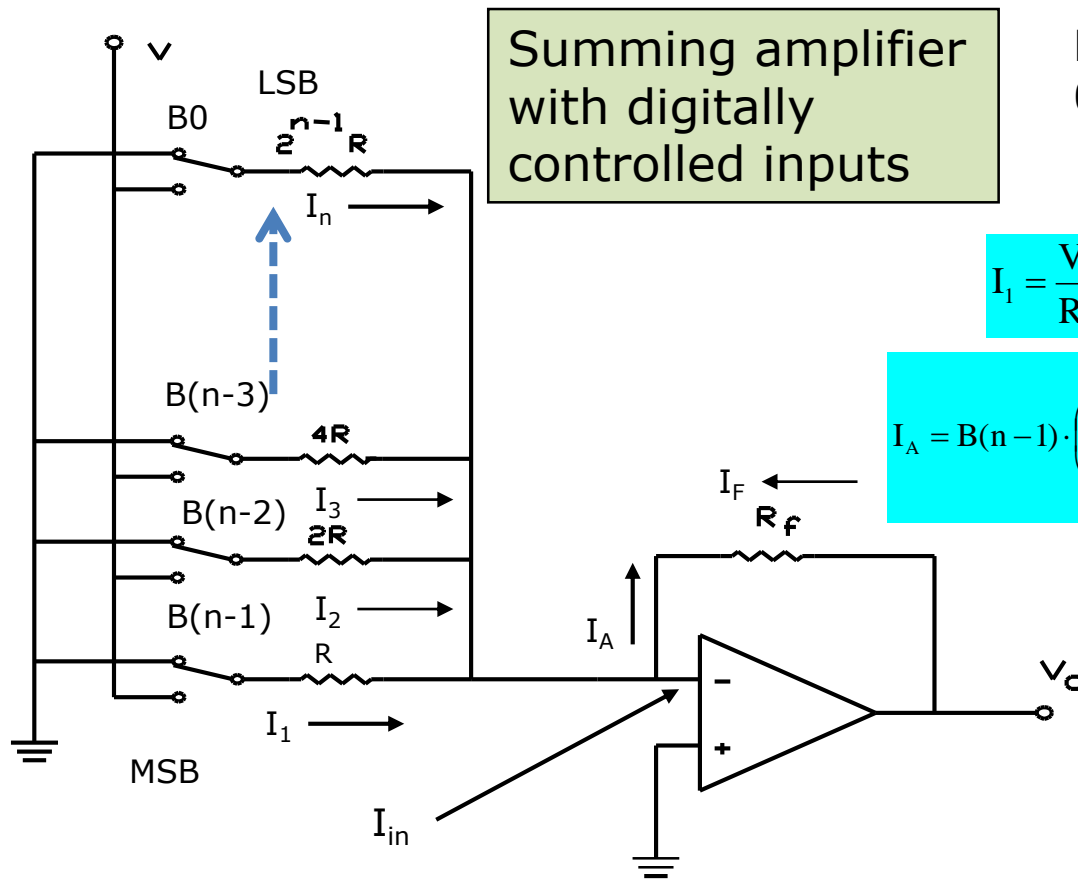

Rules of Ideal OP AMPs  $I_{in} = 0$ ,  $Z_{in} = \text{infinity}$

$$I_A = I_1 + I_2 + I_3 + \dots + I_n$$

$$I_1 = \frac{V}{R}, I_2 = \frac{V}{2R}, I_3 = \frac{V}{4R}, \dots, I_n = \frac{V}{(2^{n-1})R}$$

$$I_A = B(n-1) \cdot \left(\frac{V}{R}\right) + B(n-2) \cdot \left(\frac{V}{2R}\right) + B(n-3) \cdot \left(\frac{V}{4R}\right) + \dots + B0 \cdot \left(\frac{V}{(2^{n-1})R}\right)$$

Formula for output V

$$V_0 = -I_F \cdot R_F$$


$$V_0 = -R_F \sum_{i=1}^n \frac{B(n-i) \cdot V}{2^{i-1} R}$$

11

B0, B(n-3), B(n-2), ....B(n-1) take on values of 1 or 0 depending of the digital output controlling switch

## Binary Weighted DAC Example

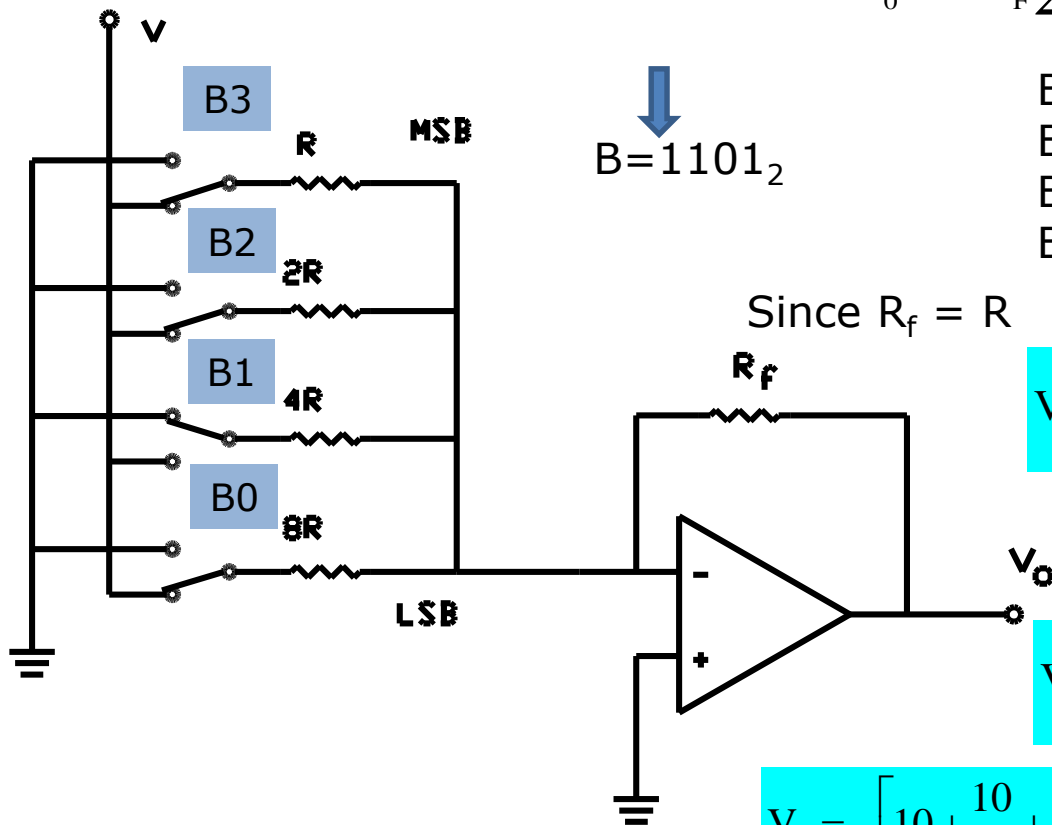**Example:** For the binary-weighted resistor DAC below find the output when the input word is  $1101_2$   $V = 10 \text{ Vdc}$ ,  $R_f = R$



$$V_o = -R_F \sum_{i=1}^n \frac{B(n-i) \cdot V}{2^{i-1} R} \quad n=4$$

$$B(4-1)=B3=1 \quad \text{MSB}$$

$$B(4-2)=B2=1$$

$$B(4-3)=B1=0$$

$$B(4-4)=B0=1 \quad \text{LSB}$$

Since  $R_f = R$

$$V_o = -R \cdot \left[ \frac{B3 \cdot V}{2^{1-1} R} + \frac{B2 \cdot V}{2^{2-1} R} + \frac{B1 \cdot V}{2^{3-1} R} + \frac{B0 \cdot V}{2^{4-1} R} \right]$$


$$V_o = -\frac{R}{R} \cdot \left[ \frac{1 \cdot V}{2^0} + \frac{1 \cdot V}{2^1} + \frac{0 \cdot V}{2^2} + \frac{1 \cdot V}{2^3} \right]$$

$$V_o = -1 \cdot \left[ \frac{1 \cdot 10}{2^0} + \frac{1 \cdot 10}{2^1} + \frac{0 \cdot 10}{2^2} + \frac{1 \cdot 10}{2^3} \right]$$

$$V_o = -\left[ 10 + \frac{10}{2} + 0 + \frac{10}{8} \right] = -[10 + 5 + 1.25] = -16.25$$
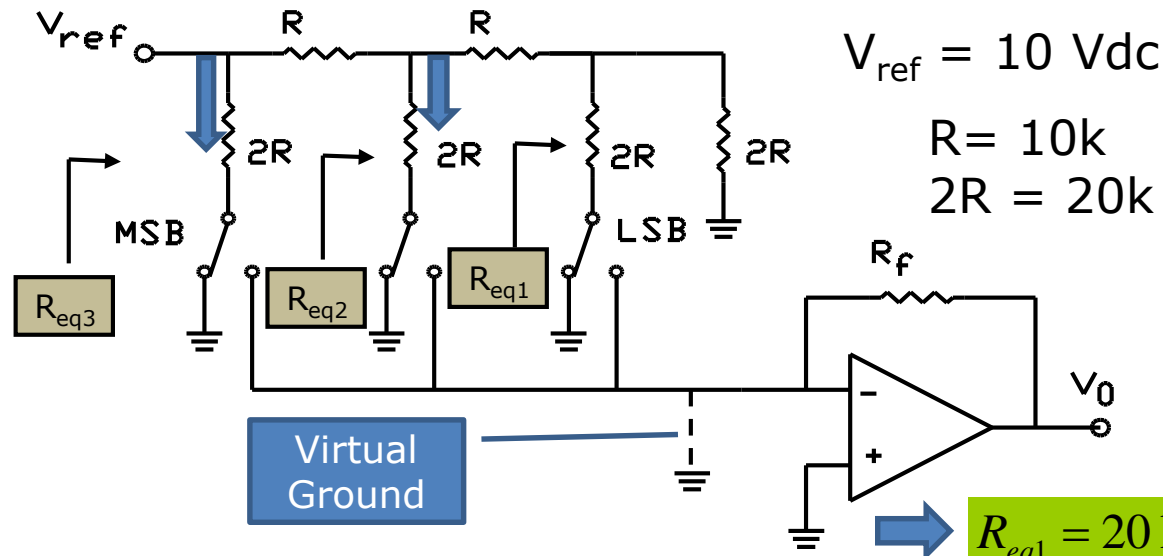
# R-2R Binary Ladder DAC

R-2R Ladder produces binary weighted current values from only 2 resistance values.



Find  $R_{eq3}$  by assuming all switches are closed to ground

## Circuit Analysis

Currents through each  $2R$  value resistor directed to OP AMP or ground by digital switch

$$R_{eq1} = 20 \text{ k}\Omega \parallel 20 \text{ k}\Omega + 10 \text{ k}\Omega = 20 \text{ k}\Omega$$


$$R_{eq2} = R_{eq1} \parallel 20 \text{ k}\Omega + 10 \text{ k}\Omega = 20 \text{ k}\Omega$$

$$R_{eq3} = R_{eq2} \parallel 20 \text{ k}\Omega = 10 \text{ k}\Omega$$

$$R_{eq3} = 10 \text{ k}\Omega$$

Network equivalent resistance is  $R_{eq3}$

## R-2R Ladder Analysis (Continued)

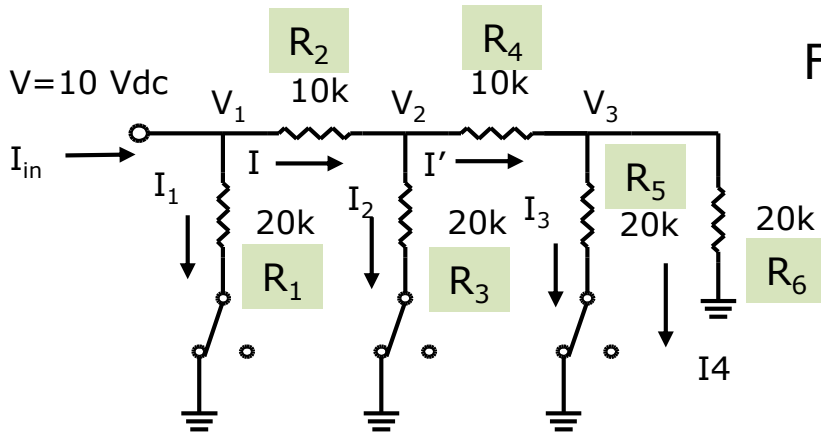

Find  $I_{in}$  from  $R_{eq3}$  and  $V$

$$I_{in} = \frac{V}{R_{eq3}} = \frac{10\text{ V}}{10\text{ k}\Omega} = 1.0\text{ mA}$$

$$I_1 = \frac{V_1}{R_1} = \frac{10\text{ V}}{20\text{ k}\Omega} = 0.5\text{ mA} \quad I = I_{in} - I_1 = 1\text{ mA} - 0.5\text{ mA} = 0.5\text{ mA}$$

$$V_2 = V_1 - I \cdot R_2 \Rightarrow V_2 = 10 - 0.5\text{ mA} \cdot 10\text{ k}\Omega = 10 - 5 = 5\text{ V}$$

$$I_2 = \frac{V_2}{R_3} = \frac{5\text{ V}}{20\text{ k}\Omega} = 0.25\text{ mA} \quad I' = I_1 - I_2 = 0.5\text{ mA} - 0.25\text{ mA} = 0.25\text{ mA}$$

$$V_3 = V_2 - I' \cdot R_4 \Rightarrow V_3 = 5 - 0.25\text{ mA} \cdot 10\text{ k}\Omega = 5 - 2.5 = 2.5\text{ V}$$

$$I_3 = \frac{V_3}{R_5} = \frac{2.5\text{ V}}{20\text{ k}\Omega} = 0.125\text{ mA} \quad I_4 = \frac{V_3}{R_6} = \frac{2.5\text{ V}}{20\text{ k}\Omega} = 0.125\text{ mA}$$

### Current Values

$$I_1 = 0.5\text{ mA} \quad \text{MSB}$$

$$I_2 = 0.25\text{ mA}$$


$$I_3 = 0.125\text{ mA} \quad \text{LSB}$$

Current values directed to OP AMP summing junction or ground. At summing junction:

$$V_o = -R_f \cdot I_T$$
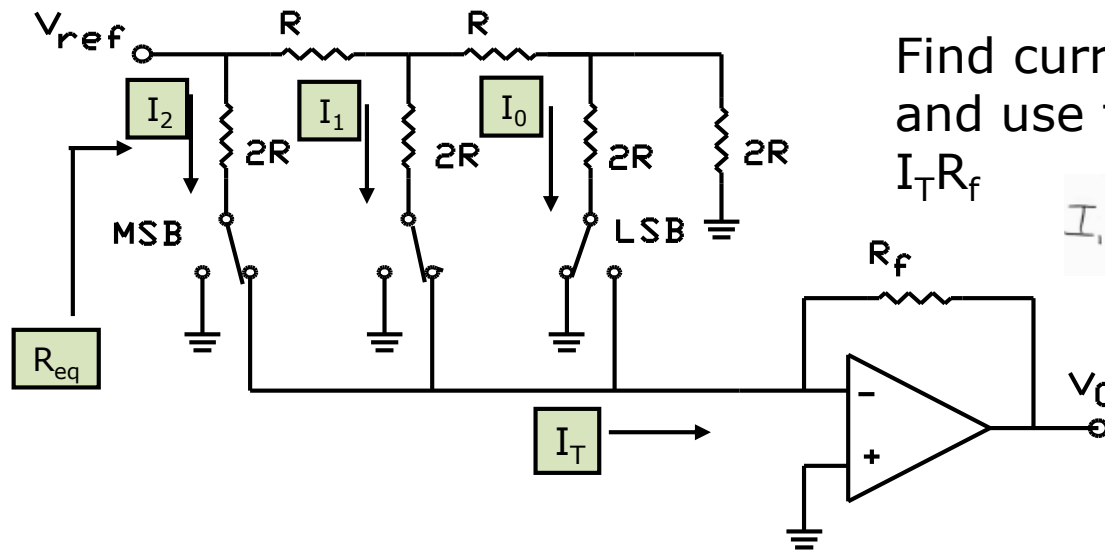
## R-2R Example

Find the output voltage for the R-2R DAC shown below. The digital input is  $110_2$ .  $R=15k$ ,  $2R=30k$  and  $R_f=15k$ ,  $V_{ref}=5$  Vdc



Find currents  $I_0$ ,  $I_1$ ,  $I_2$   
and use formula  $V_0 = -I_T R_f$

$$I_{in} = \frac{V_{ref}}{R} = \frac{5V}{15k\Omega} = 0.333 \text{ mA}$$

$$I_2 = \frac{V_{ref}}{2R} = \frac{5}{30k\Omega} = 0.1667 \text{ mA}$$

All other currents reduced by factor of 2.

$$I_1 = \frac{I_2}{2} \Rightarrow I_1 = \frac{0.1667 \text{ mA}}{2} = 0.0833 \text{ mA} = 83.33 \mu\text{A}$$


$$I_0 = \frac{I_1}{2} = \frac{0.0833 \text{ mA}}{2} = 0.04166 \text{ mA} = 41.66 \mu\text{A}$$

$$I_T = I_2 + I_1 = 0.1667 \text{ mA} + 0.0833 \text{ mA} = 0.25003 \text{ mA}$$

$$V_0 = -I_T R_f = -(0.25003 \text{ mA})(15k\Omega) = -3.75045 \text{ V}$$
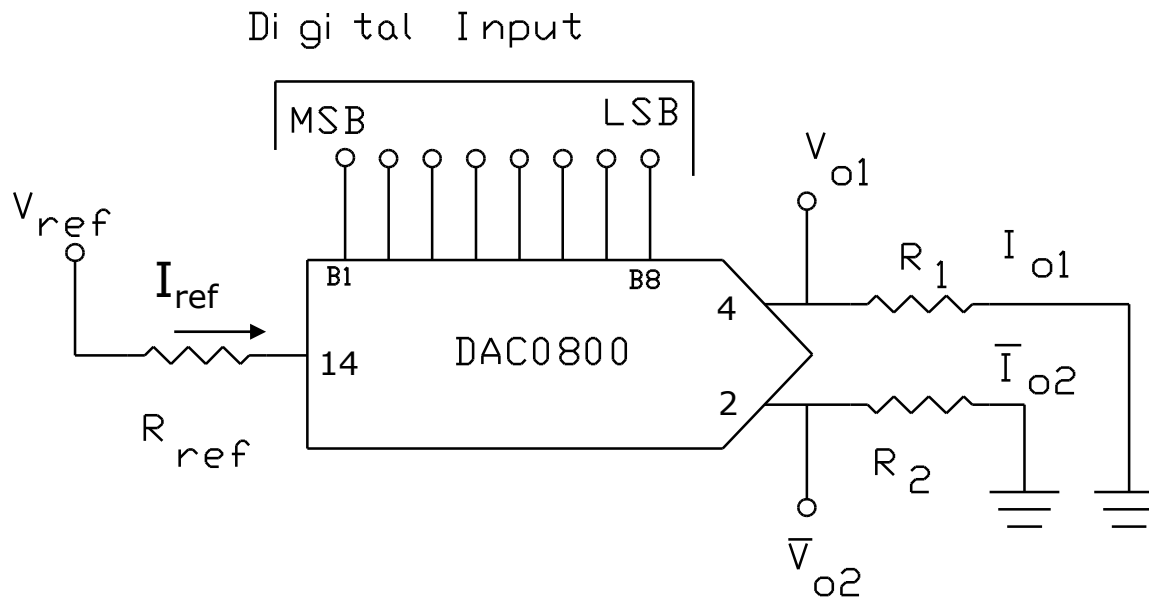
# Commercial DACs: DAC0800 Family

Devices used in practical designs use integrated R-2R networks and transistor switching. They have TTL compatible inputs.



## Design Equations

$$I_{\text{ref}} = \frac{V_{\text{ref}}}{R_{\text{ref}}}$$

$$I_0 = I_{\text{ref}} \left( \frac{D}{256} \right)$$

D = decimal equivalent of binary input


8-bit binary code converted to 256 levels of  $I_0$ . Full scale value set by reference current. 1 bit change produces change of  $1/256$  in  $I_0$

$$I_{\text{fs}} = \frac{V_{\text{ref}}}{R_{\text{ref}}} \left( \frac{255}{256} \right) \quad \text{Full scale output}$$


 
## DAC0800 Example

Use OP AMP to convert current to voltage. The reference voltage is +10 V dc and the reference resistance is 5k $\Omega$ . The value of  $R_f = 2.5\text{k}\Omega$



$$I_{\text{ref}} = \frac{V_{\text{ref}}}{R_{\text{ref}}} = \frac{10 \text{ V}}{5 \text{ k}\Omega} = 2.0 \text{ mA}$$

a.) convert binary to decimal

$$1101_2 = 2^3(1) + 2^2(1) + 2^1(0) + 2^0(1)$$

$$1101_2 = 8 + 4 + 1 = 13$$

$$D = 13$$

Find  $I_o$

$$I_o = I_{\text{ref}} \left( \frac{D}{256} \right)$$

a.) Digital input  $00001101_2$

b.) Digital input  $10001101_2$

$$I_o = (2.0 \text{ mA}) \left[ \frac{13}{256} \right] = 0.1015625 \text{ mA} = 101.5625 \mu\text{A}$$


$I_o$  enters so negative

$$V_o = -(-I_o) \cdot R_f = -(-0.1015625 \text{ mA})(2.5 \text{ k}\Omega) = 0.253906 \text{ V}$$
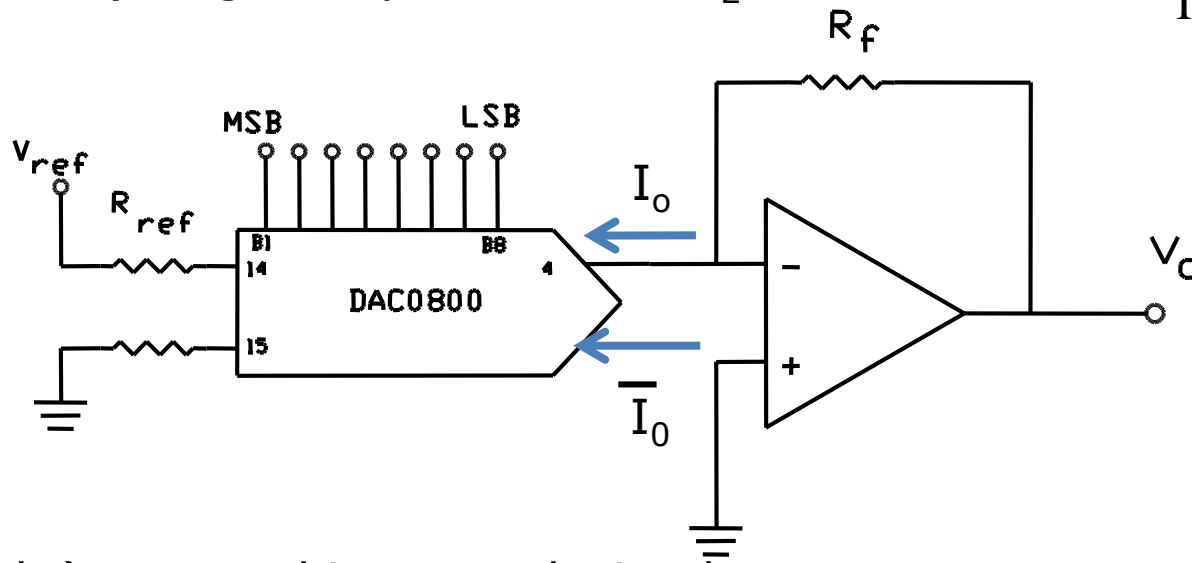
## DAC0800 Example (Continued)

b.) Digital input  $10001101_2$

$$I_{\text{ref}} = \frac{V_{\text{ref}}}{R_{\text{ref}}} = \frac{10 \text{ V}}{5 \text{ k}\Omega} = 2.0 \text{ mA}$$



b.) convert binary to decimal

$$10001101_2 = 2^7(1) + 2^6(0) + 2^5(0) + 2^4(0) + 2^3(1) + 2^2(1) + 2^1(0) + 2^0(1)$$

$$1101_2 = 128 + 8 + 4 + 1 = 141$$

$$D = 141$$


$I_0$  enters so negative

$$\bar{I}_0 = I_{\text{ref}} - I_0 = 2.0 - 1.1015625 \text{ mA} = 0.8984375 \text{ mA}$$

$$I_0 = I_{\text{ref}} \left( \frac{D}{256} \right) = (2.0) \cdot \left( \frac{141}{256} \right) = 1.1015626 \text{ mA}$$

$$V_o = -(-I_0) \cdot R_f = -(-1.1015625 \text{ mA})(2.5 \text{ k}\Omega) = 2.753906 \text{ V}$$

# DAC: home work

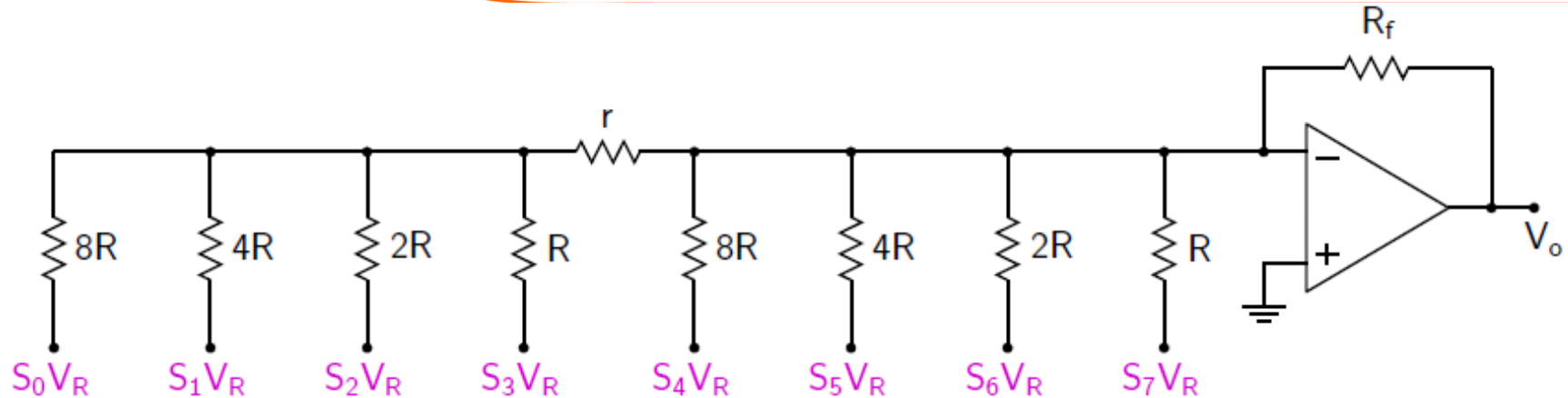


- \* Find the value of  $r$  for the circuit to work as a regular (i.e., binary to analog) DAC.
- \* Find the value of  $r$  for the circuit to work as a BCD to analog DAC

<https://docs.google.com/forms/d/e/1FAIpQLSdHTIou63HKXrUfYDB8CuxvKe8Mb0UHkR2JUqFVM02KyOPkg/viewform?usp=header>

Then Submit your answer using the QR code or the link



# Summary

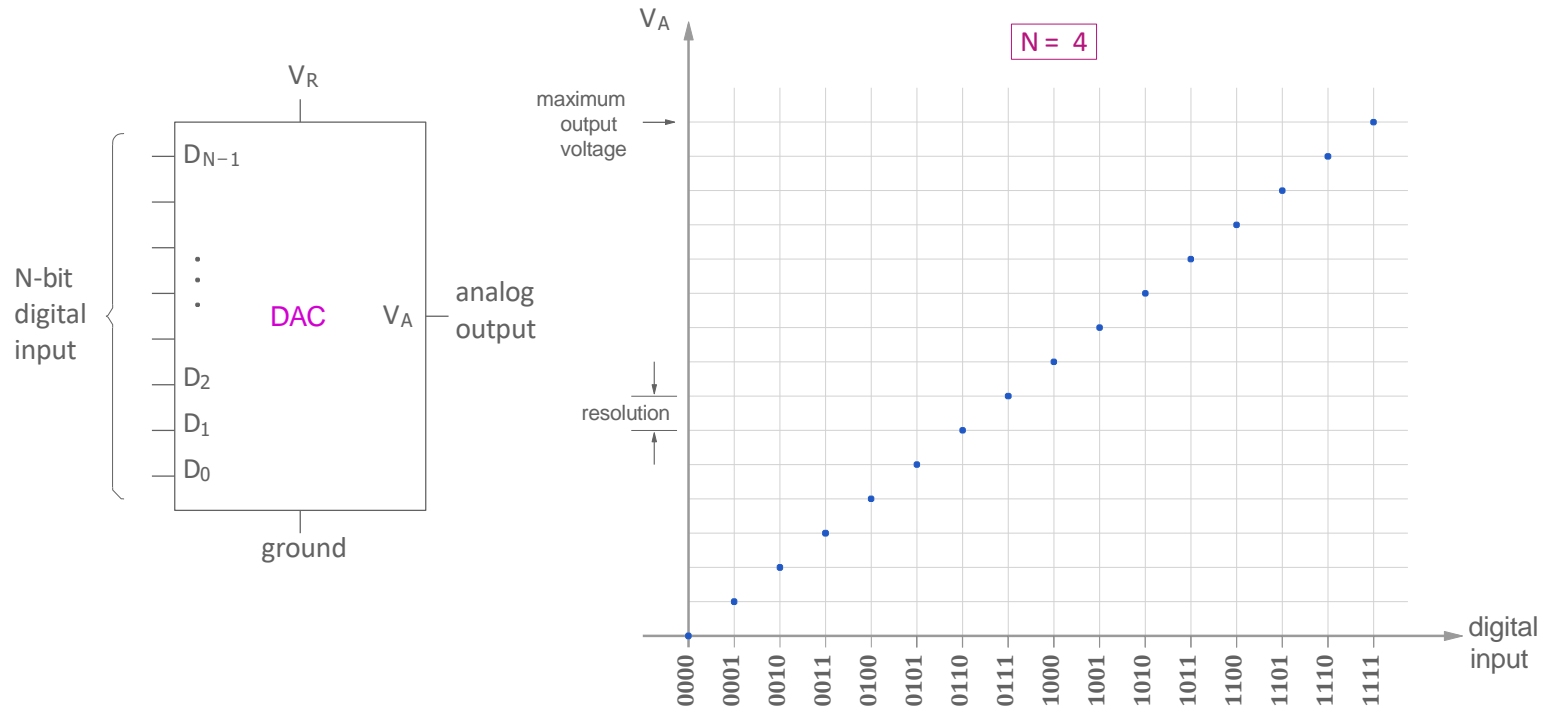


\* For a 4-bit DAC, with input  $S_3S_2S_1S_0$ , the output voltage is

$$V_A = K (S_3 \times 2^3) + (S_2 \times 2^2) + (S_1 \times 2^1) + (S_0 \times 2^0) .$$

In general, 
$$V_A = K \sum_{k=0}^{N-1} S_k 2^k .$$

\*  $K$  is proportional to the reference voltage  $V_R$ . Its value depends on how the DAC is implemented.

## DAC using binary-weighted resistors

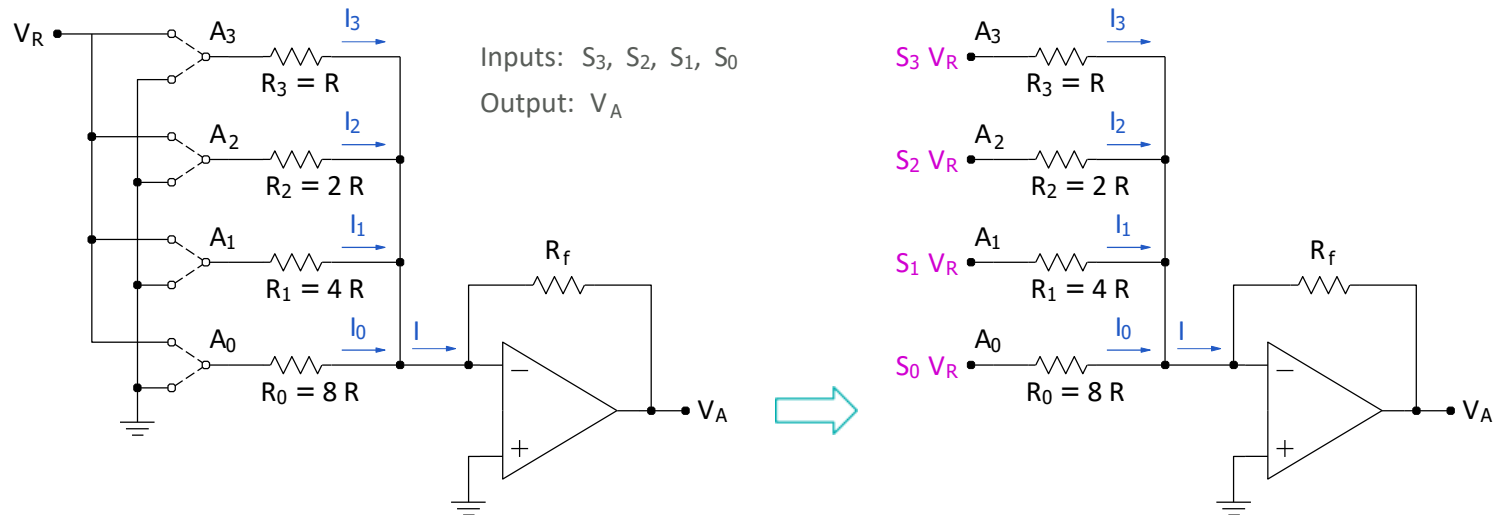


\* If the input bit  $S_k$  is 1,  $A_k$  gets connected to  $V_R$ ; else, it gets connected to ground.  $\rightarrow V(A_k) = S_k \times V_R$ .

\* Since the inverting terminal of the op-amp is at virtual ground,  $I_k = \frac{V(A_k) - 0}{R_k} = \frac{S_k V_R}{R_k}$ .

$$* I = \frac{S_0 V_R}{8R} + \frac{S_1 V_R}{4R} + \frac{S_2 V_R}{2R} + \frac{S_3 V_R}{R} = \frac{V_R}{2^{N-1} R} \sum_{k=0}^{N-1} S_k \times 2^k \quad (N=4).$$

\* The output voltage is  $V_o = -R_f I = -V_R \frac{R_f}{2^{N-1} R} \sum_{k=0}^{N-1} S_k \times 2^k$ .
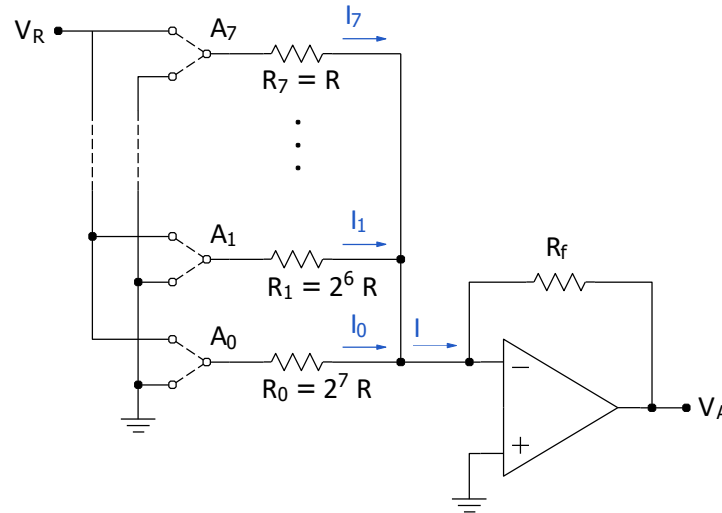
## DAC using binary-weighted resistors: Example



- \* Consider an 8-bit DAC with  $V_R = 5\text{ V}$ . What is the smallest value of  $R$  which will limit the current drawn from the supply ( $V_R$ ) to  $10\text{ mA}$ ?


Maximum current is drawn from  $V_R$  when the input is 1111 1111.

→ All nodes  $A_0$  to  $A_7$  get connected to  $V_R$ .

$$\begin{aligned} \rightarrow 10\text{ mA} &= \frac{V_R}{R} + \frac{V_R}{2R} + \cdots + \frac{V_R}{2^7 R} = \frac{1}{2^7} \frac{V_R}{R} (2^0 + 2^1 + \cdots + 2^7) \\ &= \frac{1}{2^7} \frac{V_R}{R} (2^8 - 1) = \frac{255}{128} \frac{V_R}{R} \rightarrow R_{\min} = \frac{5\text{ V}}{10\text{ mA}} \times \frac{255}{128} = 996\Omega. \end{aligned}$$

(Ref.: K. Gopalan, *Introduction to Digital Microelectronic Circuits*, Tata McGraw-Hill, New Delhi, 1998)
 
## DAC using binary-weighted resistors: Example (from Gopalan)




\* If  $R_f = R$ , what is the resolution (i.e.,  $\Delta V_A$  corresponding to the input LSB changing from 0 to 1 with other input bits constant)?

$$V_A = -V_R \frac{R_f}{2^{N-1}R} (S_7 2^7 + \dots + S_1 2^1 + S_0 2^0)$$

$$\rightarrow \Delta V_A = \frac{V_R}{2^{N-1}} \frac{R_f}{R} = \frac{5V}{2^{8-1}} \times 1 = \frac{5}{128} = 0.0391V.$$
 
## DAC using binary-weighted resistors: Example (from Gopalan)



\* What is the maximum output voltage (in magnitude)?


$$V_A = -\frac{V_R}{2^{N-1}} \frac{R_f}{R} \left( S_7 2^7 + \dots + S_1 2^1 + S_0 2^0 \right).$$

Maximum  $V_A$  (in magnitude) is obtained when the input is 1111 1111.

$$|V_A|^{\max} = \frac{5}{128} \times 1 \times \left( 2^0 + 2^1 + \dots + 2^7 \right) = \frac{5}{128} \times (2^8 - 1) = 5 \times \frac{255}{128} = 9.961 \text{ V}.$$



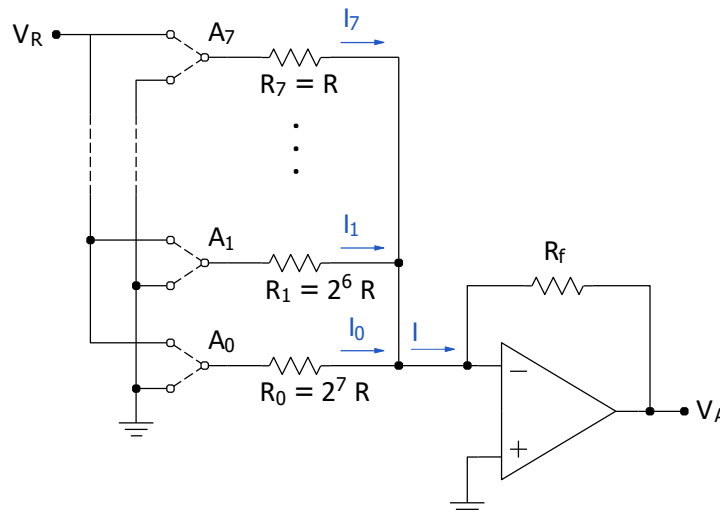
## DAC using binary-weighted resistors: Example (from Gopalan)



\* Find the output voltage corresponding to the input 1010 1101.

$$\begin{aligned}
 V_A &= -\frac{V_R}{2^{N-1}} \frac{R_f}{R} \sum_{i=0}^7 S_i 2^i \\
 &= -\frac{5}{128} \times 1 \times (2^7 + 2^5 + 2^3 + 2^2 + 2^0) = -5 \times \frac{173}{128} = -6.758 \text{ V} .
 \end{aligned}$$
 
## DAC using binary-weighted resistors: Example (from Gopalan)



\* If the resistors are specified to have a tolerance of 1%, what is the range of  $|V_A|$  corresponding to input 1111 1111?


$|V_A|$  is maximum when (a) currents  $I_0, I_1$ , etc. assume their maximum values, with  $R_k = R_k^0 \times (1 - 0.01)$  and (b)  $R_f$  is maximum,  $R_f = R_f^0 \times (1 + 0.01)$ .

(The superscript '0' denotes nominal value.)

$$\rightarrow |V_A|_{11111111}^{\max} = V_R \times \frac{255}{128} \times \frac{R_f^{\max}}{R} = 5 \times \frac{255}{128} \times \frac{1.01}{0.99} = 10.162 \text{ V.}$$


$$\text{Similarly, } |V_A|_{11111111}^{\min} = 5 \times \frac{255}{128} \times \frac{0.99}{1.01} = 9.764 \text{ V.}$$
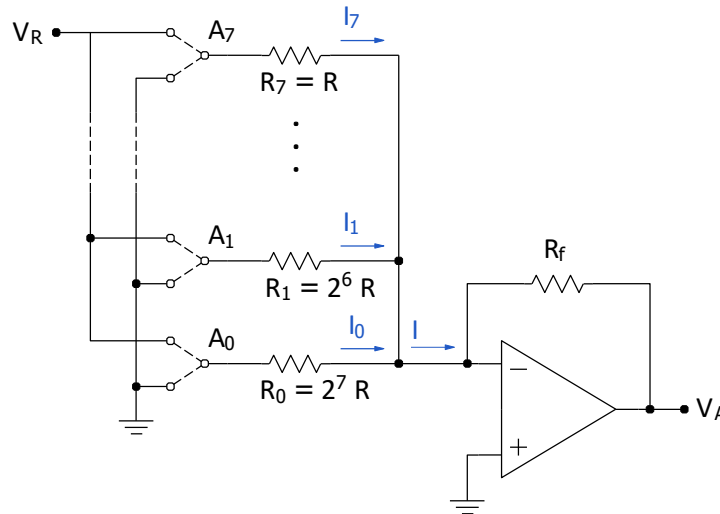
## DAC using binary-weighted resistors: Example (from Gopalan)




- \*  $\Delta V_A$  for input 1111 1111 =  $10.162 - 9.764 \approx 0.4V$  which is larger than the resolution ( $0.039V$ ) of the DAC. This situation is not acceptable.
- \* The output voltage variation can be reduced by using resistors with a smaller tolerance. However, it is difficult to fabricate an IC with widely varying resistance values (from  $R$  to  $2^{N-1}R$ ) and each with a small enough tolerance.  
→ use  $R - 2R$  ladder network instead.

# R-2R ladder network

 


Node  $A_k$  is connected to  $V_R$  if input bit  $S_k$  is 1; else, it is connected to ground.


The original network is equivalent to

 

 
## R-2R ladder network: Thevenin resistance



 
# R-2R ladder network: Thevenin resistance



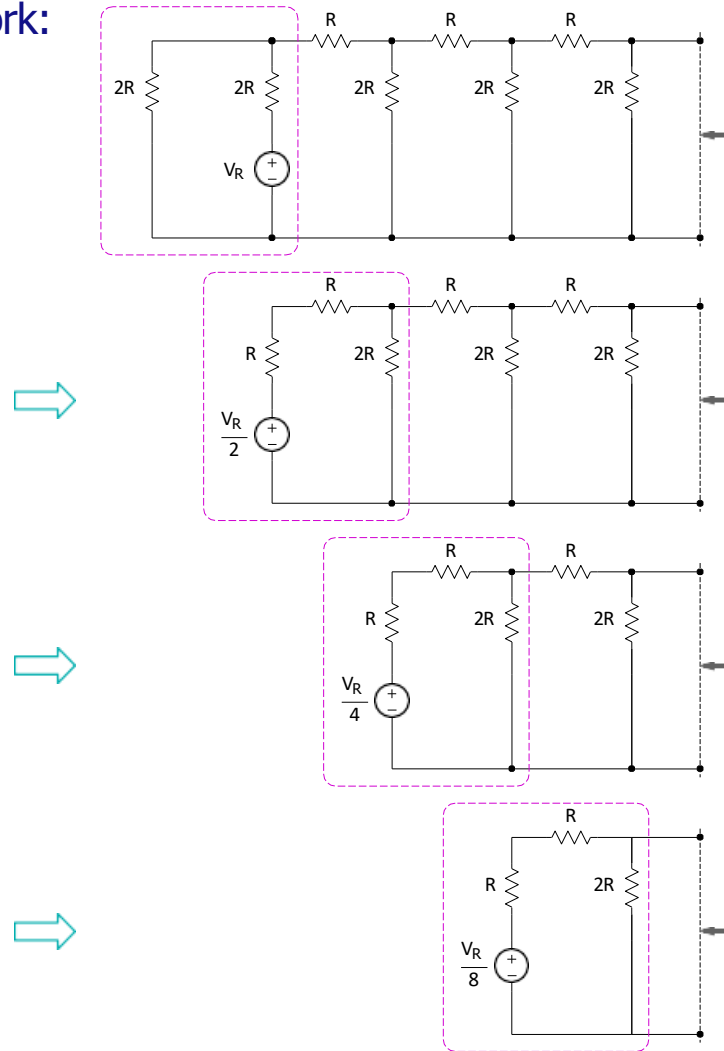R-2R ladder network:  
 $V_{Th}$  for  $S_0 = 1$






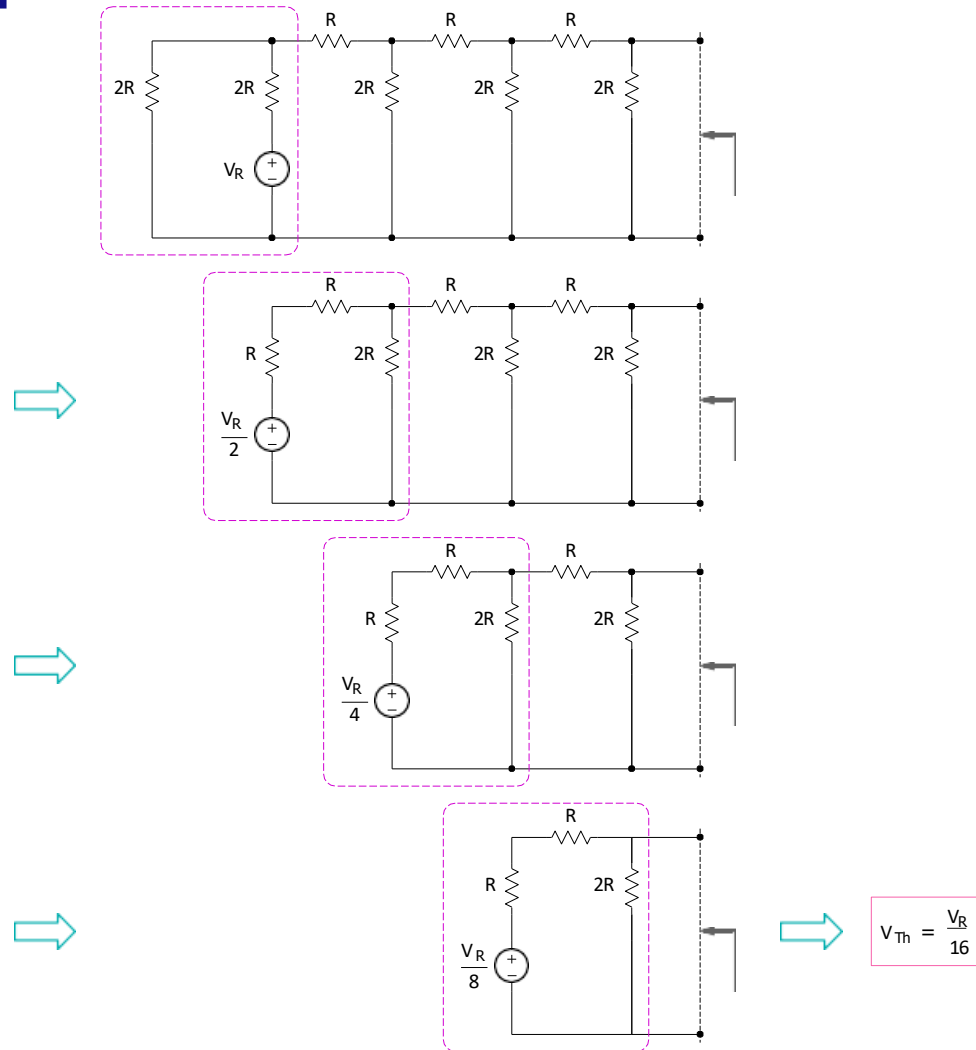
# R-2R ladder network: $V_{Th}$ for $S_0 = 1$









    R-2R ladder network:  
 $V_{Th}$  for  $S_1 = 1$





    
# R-2R ladder network: $V_{Th}$ for $S_1 = 1$





$$V_{Th} = \frac{V_R}{8}$$
   
# R-2R ladder network: $V_{Th}$ for $S_2 = 1$




$$V_{Th} = \frac{V_R}{4}$$

  R-2R ladder network:  
 $V_{Th}$  for  $S_3 = 1$



$$V_{Th} = \frac{V_R}{2}$$
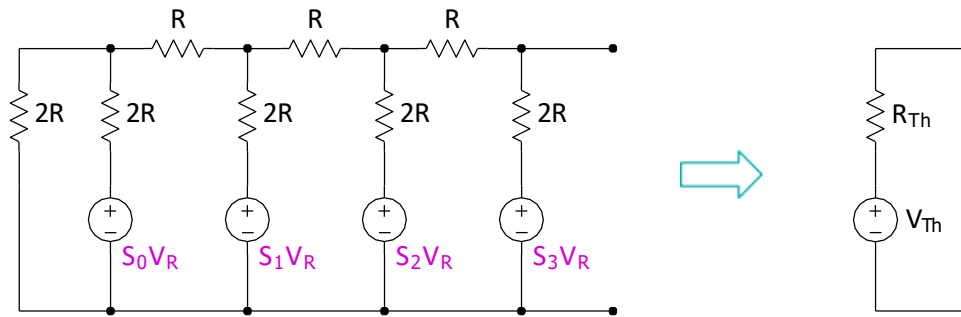
## R-2R ladder network: $R_{Th}$ and $V_{Th}$




\*  $R_{Th} = R.$

\* 
$$V_{Th} = V_{Th}^{(S0)} + V_{Th}^{(S1)} + V_{Th}^{(S2)} + V_{Th}^{(S3)}$$

$$= \frac{V_R}{16} {}^h S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3 {}^i.$$

\* We can use the R-2R ladder network and an op-amp to make up a DAC → next slide.

## DAC with R-2R ladder


 


$$* V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{16} S_0 2^0 + S_1 2^1 + S_2 2^2 + S_3 2^3$$

$$* \text{For an N-bit DAC, } V_o = -\frac{R_f}{R_{Th}} V_{Th} = -\frac{R_f}{R_{Th}} \frac{V_R}{2^N} \sum_{k=0}^{N-1} S_k 2^k$$

- \* 6- to 20-bit DACs based on the R-2R ladder network are commercially available in monolithic form (single chip).
- \* Bipolar, CMOS, or BiCMOS technology is used for these DACs.

## DAC: settling time

 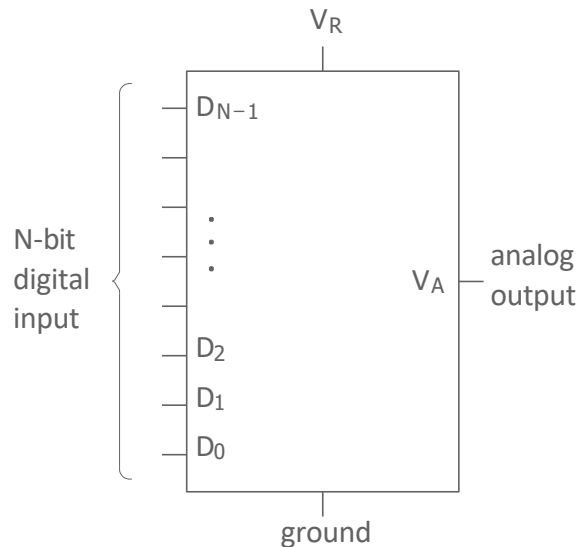

- \* When there is a change in the input binary number, the output  $V_A$  takes a finite time to settle to the new value.
- \* The finite settling time arises because of stray capacitances and switching delays of the semiconductor devices used within the DAC chip.
- \* Example: 500ns to 0.2 % of full scale.

شكراً لحسن

إصغائكم

**THANK YOU** 😊

**END LESSON 12: DIGITAL-TO-ANALOG CONVERTER (DAC)**