



## Collector-Feedback Bias

In Figure, the base resistor  $R_B$  is connected to the collector rather than to  $V_{CC}$ , as it was in the base bias arrangement discussed earlier. The collector voltage provides the bias for the base-emitter junction. The negative feedback creates an “offsetting” effect that tends to keep the Q-point stable. If  $I_C$  tries to increase, it drops more voltage across  $R_C$ , thereby causing  $V_C$  to decrease. When  $V_C$  decreases, there is a decrease in voltage across  $R_B$ , which decreases  $I_B$ . The decrease in  $I_B$  produces less  $I_C$  which, in turn, drops less voltage across  $R_C$  and thus offsets the decrease in  $V_C$ .

**Analysis of a Collector-Feedback Bias Circuit** By Ohm’s law, the base current can be expressed as

$$I_B = \frac{V_C - V_{BE}}{R_B}$$

Let’s assume that  $I_C \gg I_B$ . The collector voltage is

$$V_C \cong V_{CC} - I_C R_C$$

Also,

$$I_B = \frac{I_C}{\beta_{DC}}$$

Substituting for  $V_C$  in the equation  $I_B = (V_C - V_{BE})/R_B$ ,

$$\frac{I_C}{\beta_{DC}} = \frac{V_{CC} - I_C R_C - V_{BE}}{R_B}$$

The terms can be arranged so that

$$\frac{I_C R_B}{\beta_{DC}} + I_C R_C = V_{CC} - V_{BE}$$

Then you can solve for  $I_C$  as follows:


$$I_C \left( R_C + \frac{R_B}{\beta_{DC}} \right) = V_{CC} - V_{BE}$$
$$I_C = \frac{V_{CC} - V_{BE}}{R_C + R_B/\beta_{DC}}$$

Equation 5-13

Since the emitter is ground,  $V_{CE} = V_C$ .

$$V_{CE} = V_{CC} - I_C R_C$$

Equation 5-14

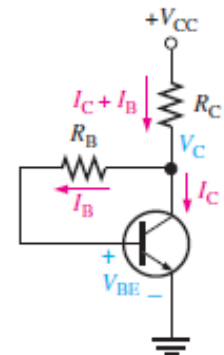


**Q-Point Stability Over Temperature** Equation 5–13 shows that the collector current is dependent to some extent on  $\beta_{DC}$  and  $V_{BE}$ . This dependency, of course, can be minimized by making  $R_C \gg R_B/\beta_{DC}$  and  $V_{CC} \gg V_{BE}$ . An important feature of collector-feedback bias is that it essentially eliminates the  $\beta_{DC}$  and  $V_{BE}$  dependency even if the stated conditions are met.

**EXAMPLE 5–10**

Calculate the Q-point values ( $I_C$  and  $V_{CE}$ ) for the circuit in Figure 5–23.

▶ **FIGURE 5–23**

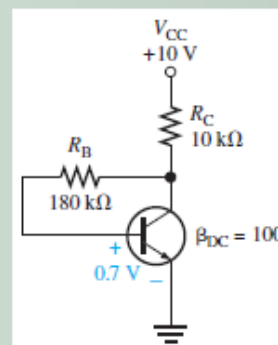

**Solution** Using Equation 5–13, the collector current is

$$I_C = \frac{V_{CC} - V_{BE}}{R_C + R_B/\beta_{DC}} = \frac{10\text{ V} - 0.7\text{ V}}{10\text{ k}\Omega + 180\text{ k}\Omega/100} = 788\ \mu\text{A}$$


Using Equation 5–14, the collector-to-emitter voltage is

$$V_{CE} = V_{CC} - I_C R_C = 10\text{ V} - (788\ \mu\text{A})(10\text{ k}\Omega) = 2.12\text{ V}$$

**Related Problem** Calculate the Q-point values in Figure 5–23 for  $\beta_{DC} = 200$  and determine the percent change in the Q-point from  $\beta_{DC} = 100$  to  $\beta_{DC} = 200$ .

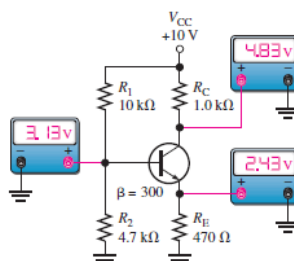**Troubleshooting a Voltage-Divider Biased Transistor**

An example of a transistor with voltage-divider bias is shown in Figure 5–24. For the specific component values shown, you should get the voltage readings approximately as indicated when the circuit is operating properly.



▶ **FIGURE 5–24**  
 A voltage-divider biased transistor with correct voltages.

For this type of bias circuit, a particular group of faults will cause the transistor collector to be at  $V_{CC}$  when measured with respect to ground. Five faults are indicated for the circuit in Figure 5–25(a). The collector voltage is equal to 10 V with respect to ground for each of the faults as indicated in the table in part (b). Also, for each of the faults, the base voltage and the emitter voltage with respect to ground are given.