



Al-Mustaqbal University / College of Engineering & Technology

Computer Techniques Department

Class three

Subject (Real time system design) / Code (UOMU0202056)

Lecturer (Dr. Hussein AbdulAmeer Abbas)

1<sup>st</sup> term – Lecture 12 & 8156-8155 PID

---

## Real Time System

### Third Level

# 8155/8156 Multipurpose Programmable Devices

Dr. Hussein AbdulAlmeer Alkhamees

[Hussein.Alkhamees@uomus.edu.iq](mailto:Hussein.Alkhamees@uomus.edu.iq)

#### Goals

Upon completing this lecture, the student should be able to:

- 1- Identify the concepts behind programmable devices
- 2- Utilize the programmable devices into the RT designs.



Al-Mustaqbal University / College of Engineering & Technology

Computer Techniques Department

Class three

Subject (Real time system design) / Code (UOMU0202056)

Lecturer (Dr. Hussein AbdulAmeer Abbas)

1<sup>st</sup> term – Lecture 12 & 8156-8155 PID

---

## Real Time System

### Third Level

# 8155/8156 Multipurpose Programmable Devices

Dr. Hussein AbdulAlmeer Alkhamees

[Hussein.Alkhamees@uomus.edu.iq](mailto:Hussein.Alkhamees@uomus.edu.iq)

#### Goals


Upon completing this lecture, the student should be able to:

- 1- Identify the concepts behind programmable devices
- 2- Utilize the programmable devices into the RT designs.


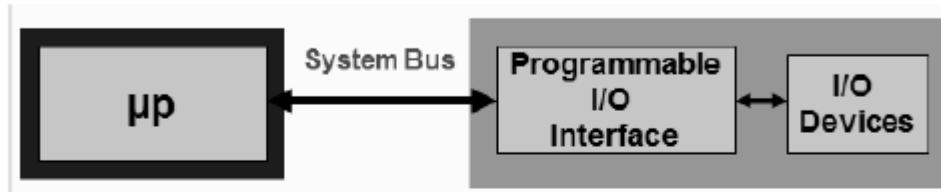
### Programmable Interface Devices

- Used to interface an I/O device to the microprocessor.
- Can be programmed/configured to perform various I/O functions by writing software instructions.



### 8155/8156 – A Multipurpose Programmable Interface


Its programmable interface device used to interface I/O device to  $\mu$ P, its multifunction device, contain RAM, I/O ports, and timer.

- Designed to be compatible with 8085.
- It includes:
  - 256 bytes of Read/Write memory.
  - Three I/O ports (programmable I/O):
    - Port A (8-bit).
    - Port B (8-bit).
    - Port C (6-bit).
  - A 14-bit timer.

PC3	Vcc
PC4	PC2
TIMER IN	PC1
RESET	PC0
PC5	PB7
TIMEROUT	PB6
IO/M	PB5
CE (CE IN 8156)	PB4
RD	PB3
WR	PB2
ALE	PB1
AD0	PB0
AD1	PA7
AD2	PA6
AD3	PA5
AD4	PA4
AD5	PA3
AD6	PA2
AD7	PA1
	PA0
	Vss



## BLOCK DIAGRAM - 8155

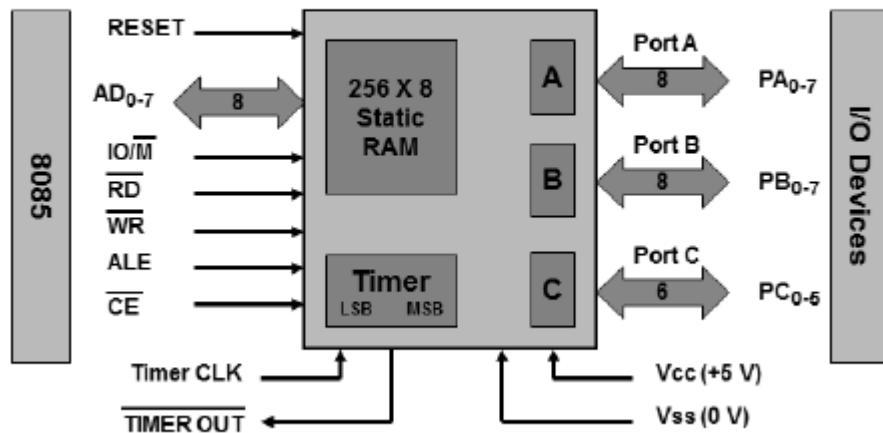


### The 8155/8156 is a device with two sections:

- The first is 256 byte static memory (RAM).
- The second is programmable I/O ports.

Functionally the two sections are used as two independent chips, the I/O section includes two 8 bit parallel I/O ports (A, B), and one 6 bit port (C), and bit timer, all ports can be simply configured as I/O ports.


- 8155 block diagram shows 5 control signals, all except CE are input signals directly generated by the processor; the (CE) is input from decoder.
  - CE: chip enable, connected to the decoder.
  - IO/M: specify whether the memory section is selected, or I/O section (including timer) is selected.
  - ALE: address latch enable.
  - RD and WR
  - RESET: connect to the RESET out of processor used to reset the chip and initializes I/O ports as input.
- In 8155 we have control register, 3 I/O ports, and 2 registers for timer, so we need 3 address lines to decode these registers.

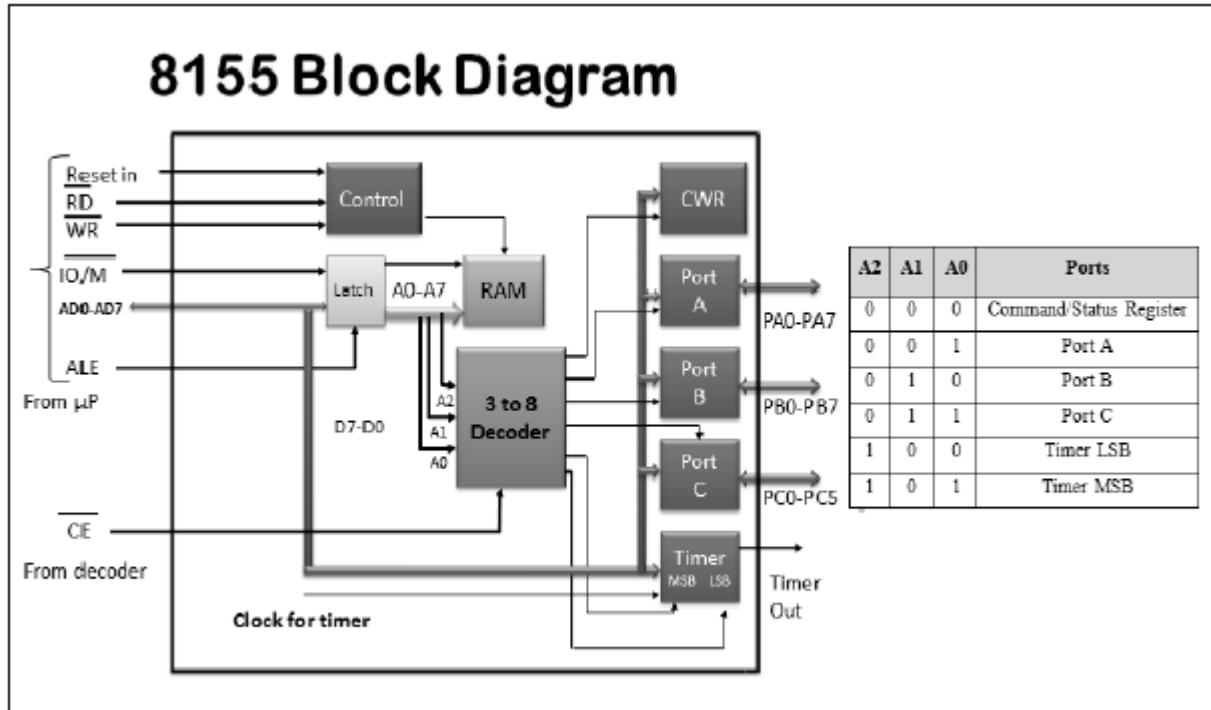


### How to Calculate Address of control register and I/O Ports of 8155?

By using 3 to 8 decoder 8205 which have 3 enables.

Why and How?

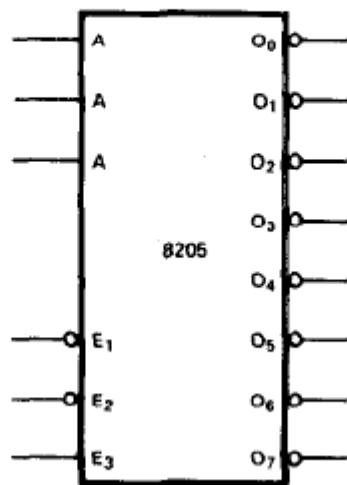

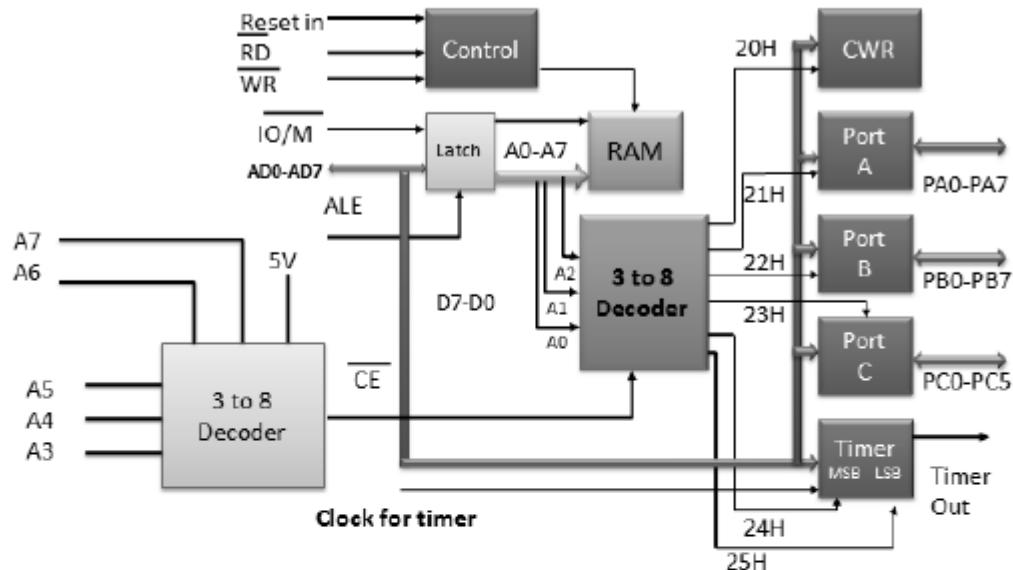

**Ex:** design (draw) and determine the address of the control/status, I/O ports and timer register of the 8155 if the output of decoder O2?

## Application design with 8155:

- Interfacing 8155 with 8085.
- Programming 8155.

**Ex: design a full system contains microprocessor and 8155 and I/O device with its connections and shows how can any output of the decoder active the interfacing proses by using 8205?**




- Timer registers of 8155.
- Instruction/Command word for 8155.
- Commands for 8155 are stored in an 8-bit Control Register inside 8155.

#### Control word for 8155:-

- A command/instruction for 8155 is also called control word.
- This control word is written to control register of 8155.
- Control word of 8155 is of 8-bits.

#### Control word (command reg) format

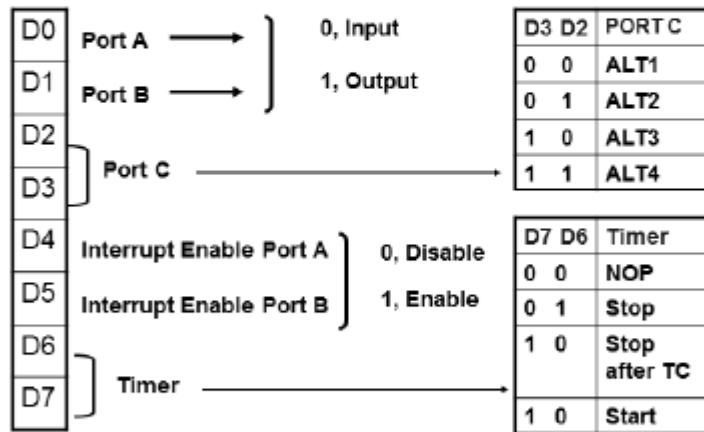


- 00: No effect
- 01: Stop if running else no effect
- 10: Stop after terminal count (TC) if running, else no effect
- 11: Start if not running.
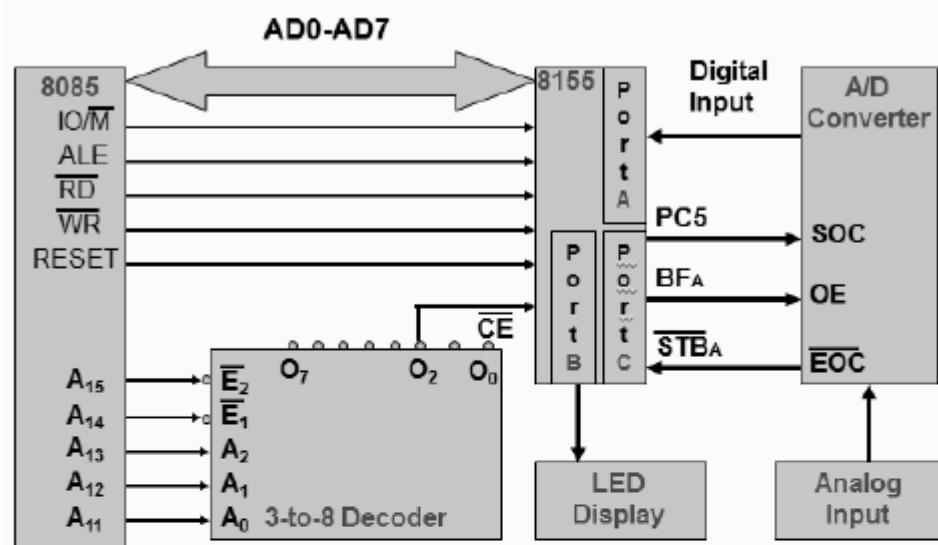
## I/O functions of Port C



**Ex:** Design an interfacing circuit to read data from an A/D converter using the 8155A in the peripheral mapped I/O.



**Chip Selection**

A7 A6 A5 A4 A3  
0 0 0 1 0

A7	A6	A5	A4	A3	Port
0	0	0	1	0	Control/Status Register
					= 10H
0	0	1			Port A
					= 11H
0	1	0			Port B
					= 12H
0	1	1			Port C
					= 13H
1	0	0			LSB Timer
					= 14H
1	0	1			MSB Timer
					= 15H