



Al-Mustaql University / College of Engineering & Technology

Computer Techniques Department

Class three

Subject (Real time system design) / Code (UOMU0202056)

Lecturer (Dr. Hussein AbdulAmeer Abbas)

1st term – Lecture 10 & Introduction to Real Time System

Real Time System


Third Level

Lecture Ten



Programmable Interface Devices

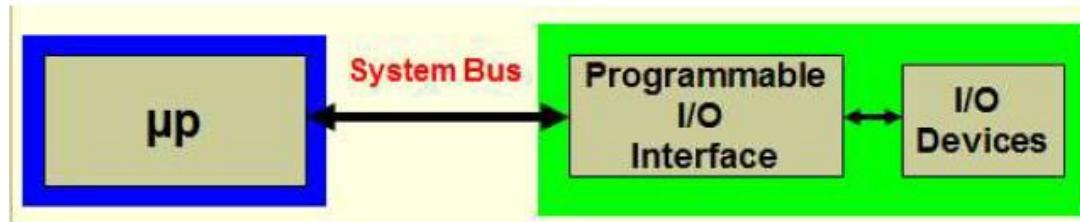
- Used to interface an I/O device to the microprocessor.
- Can be programmed/configured to perform various I/O functions by writing software instructions.



8155/8156 – A Multipurpose Programmable Interface


Its programmable interface device used to interface I/O device to μ P, its multifunction device, contain RAM, I/O ports, and timer.

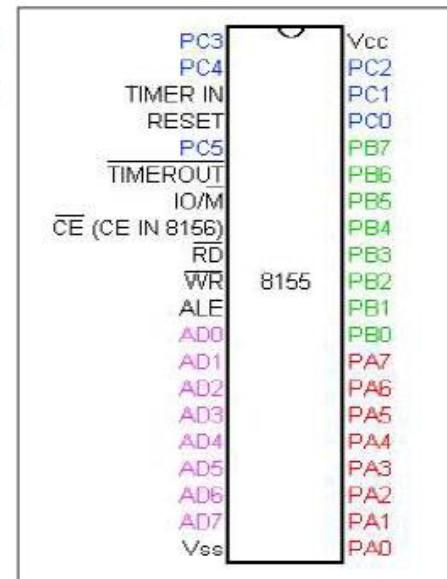- Designed to be compatible with 8085.
- It includes:
 - 256 bytes of Read/Write memory.
 - Three I/O ports (programmable I/O):
 - Port A (8-bit).
 - Port B (8-bit).
 - Port C (6-bit).
 - A 14-bit timer.





BLOCK DIAGRAM - 8155

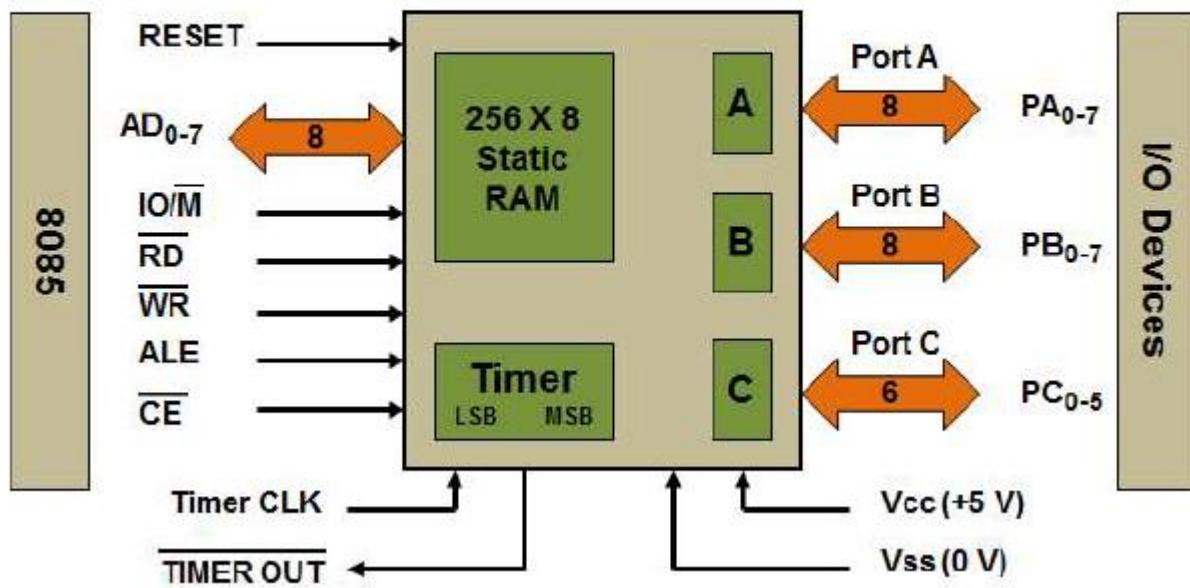



The 8155/8156 is a device with two sections:


- The first is 256 byte static memory (RAM).
- The second is programmable I/O ports.

Functionally the two sections are used as two independent chips, the I/O section includes two 8 bit parallel I/O ports (A, B), and one 6 bit port (C), and a timer, all ports can be simply configured as I/O ports.

- 8155 block diagram shows 5 control signals, all except CE are input signals directly generated by the processor; the CE is input from decoder.
 - CE: chip enable, connected to the decoder.
 - IO/M: specify whether the memory section is selected, or I/O section (including timer) is selected.
 - ALE: address latch enable.
 - RD and WR
 - RESET: connect to the RESET out of processor used to reset the chip and initializes I/O ports as input.
- In 8155 we have control register, 3 I/O ports, and 2 registers for timer, so we need 3 address lines to decode these registers.



8155 Block Diagram

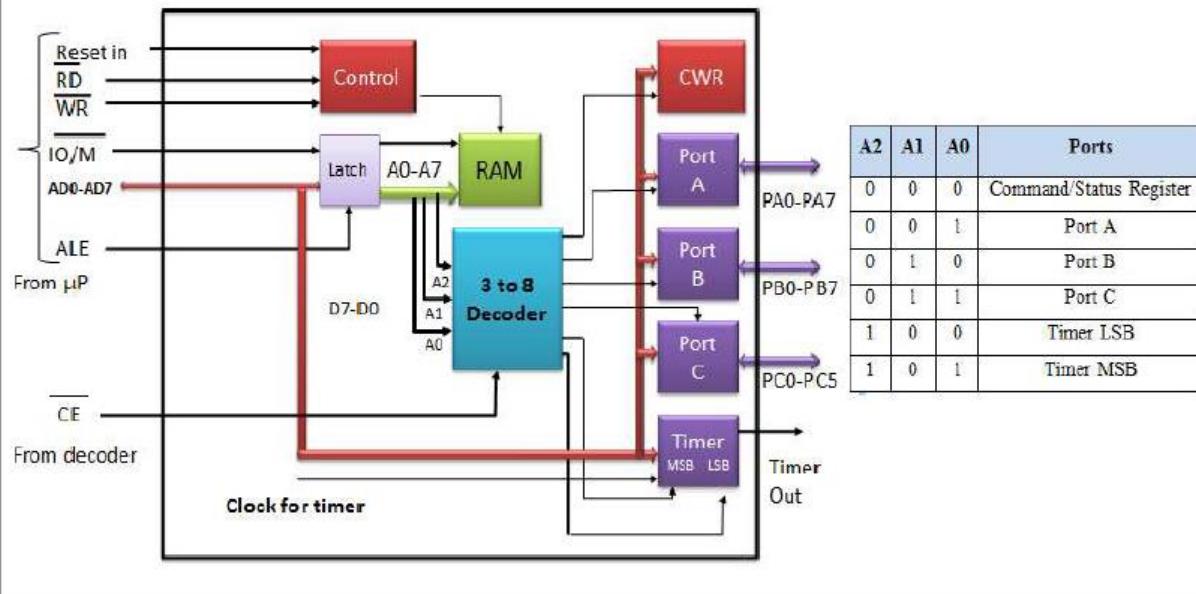




How to Calculate Address of control register and I/O Ports of 8155?


By using 3 to 8 decoder 8205 which have 3 enables.

Why and How?

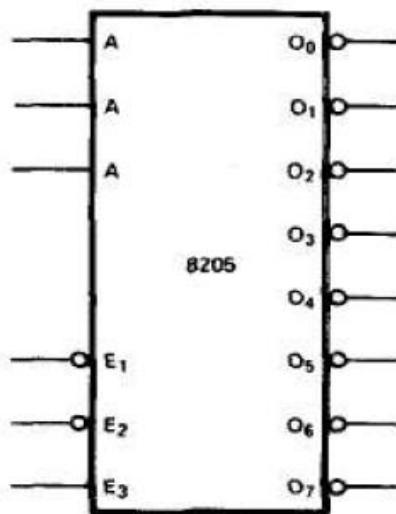

ADDRESS	ENABLE	OUTPUTS							
		0	1	2	3	4	5	6	7
A A A	E ₁ E ₂ E ₃								
L L L	L L H	L	H	H	H	H	H	H	H
H L L	L L H	H	L	H	H	H	H	H	H
L H L	L L H	H	H	L	H	H	H	H	H
H H L	L L H	H	H	H	L	H	H	H	H
L L H	L L H	H	H	H	H	L	H	H	H
H L H	L L H	H	H	H	H	H	L	H	H
L H H	L L H	H	H	H	H	H	H	L	H
H H H	L L H	H	H	H	H	H	H	H	L
X X X	L L L	H	H	H	H	H	H	H	H
X X X	H L L	H	H	H	H	H	H	H	H
X X X	L H L	H	H	H	H	H	H	H	H
X X X	H H L	H	H	H	H	H	H	H	H
X X X	H L H	H	H	H	H	H	H	H	H
X X X	H H H	H	H	H	H	H	H	H	H

Figure 1. Logic Symbol

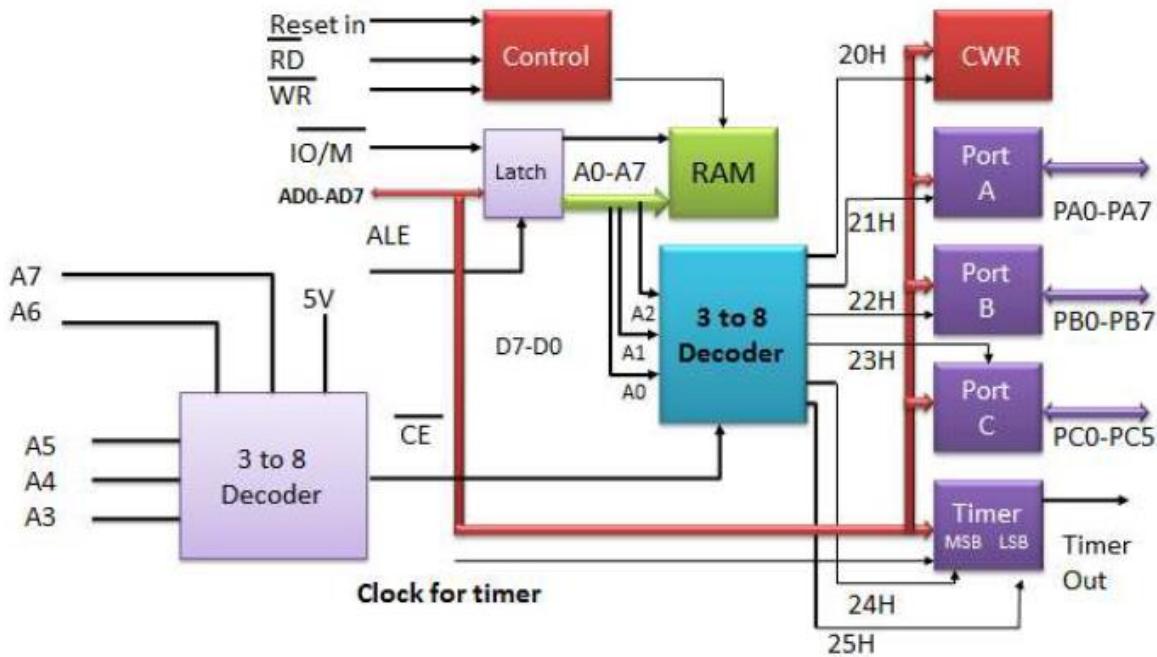

Ex: design (draw) and determine the address of the control/status, I/O ports and timer register of the 8155 if the output of decoder O2?

Application design with 8155:

- Interfacing 8155 with 8085.
- Programming 8155.

Ex: design a full system contains microprocessor and 8155 and I/O device with its connections and shows how can any output of the decoder active the interfacing proses by using 8205?



Application design with 8155:

- Interfacing 8155 with 8085.
- Programming 8155.

Ex: design a full system contains microprocessor and 8155 and I/O device with its connections and shows how can any output of the decoder active the interfacing proses by using 8205?

What type of Commands can be given to 8155?

- To configure the I/O ports as Input or Output.
- To start/stop timer.
- To use handshake mode or not.

Programming 8155:

- 8155 is a Programmable Peripheral Interface.
- 8085 can send data to 8155 using data bus.
- This data can be:-
 - For I/O devices connected to 8155.




- Timer registers of 8155.
- Instruction/Command word for 8155.
- Commands for 8155 are stored in an 8-bit Control Register inside 8155.

Control word for 8155:-

- A command/instruction for 8155 is also called control word.
- This control word is written to control register of 8155.
- Control word of 8155 is of 8-bits.

Control word (command reg) format

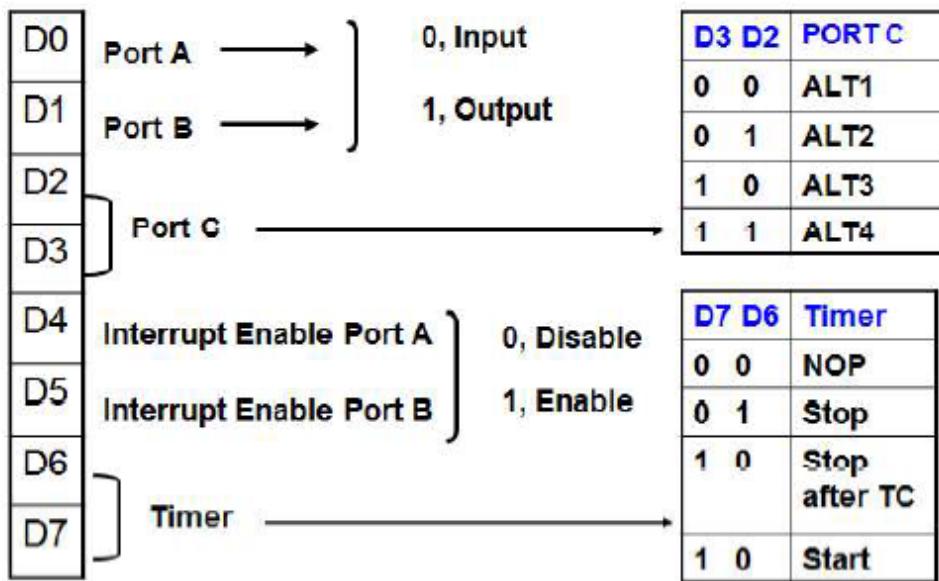


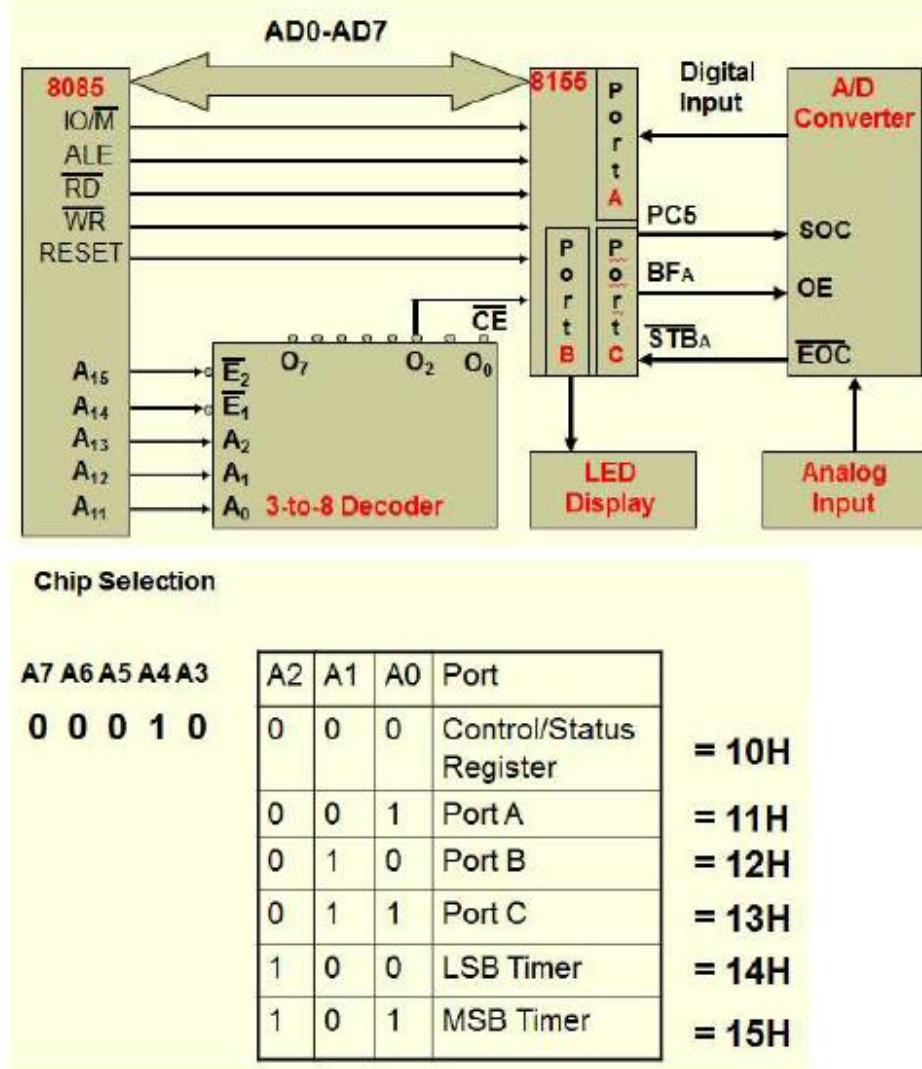- 00: No effect
- 01: Stop if running else no effect
- 10: Stop after terminal count (TC) if running, else no effect
- 11: Start if not running.

I/O functions of Port C



Ex: Design an interfacing circuit to read data from an A/D converter using the 8155A in the peripheral mapped I/O.



8155: Timers

The 8155 timer consists of two 8-bit registers, 8-bit LSB and 8-bit MSB. In these 16 bits, 14 bits are used for counter and two bit for mode selection. The counter is a 14 bit down counter. It can operate in 4 different modes of operation. We can select mode using two bits M2 and M1:

- 00 (Mode 0) Single Square Wave.




- 10 (Mode 2) Single Pulse on TC (terminal count).
- 11 (Mode 3) Pulse every TC.

Mode 0: In this mode, timer gives only one cycle of square wave, the output remains high for 1/2 count and remains low for 1/2 count (N is the count value).

Mode 1: This mode is similar to single square wave in operation but the when counter becomes zero, the count value is automatically reloaded. Thus it provides continuous square wave.

Mode 2: This mode gives a single clock pulse as an output of the end of the count the output is high normally, but it becomes low for 1 clock pulse and again it will become high and remain high.

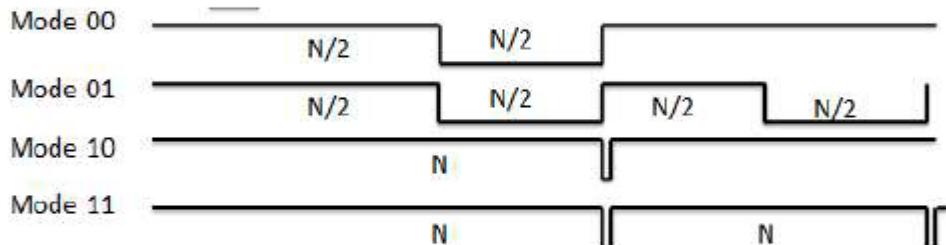
Mode 3: This mode is similar to mode 2 but when the counter becomes zero the count value is automatically reloaded. Thus it provides continuous pulses.



The 8155 I/O ports in handshake mode:

Two I/O port of 8155 (A, B) can be configured in the handshake mode, each uses three signals from port C as a control signal.

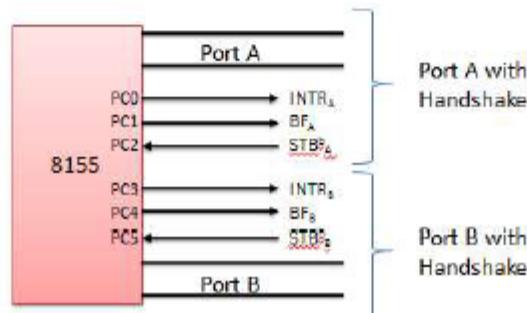When port A configured in the handshake mode, it will use the lower 3 signals of port C, PC0, PC1, PC2. When port B configured in the handshake mode, it will use the upper 3 signals of port C, PC3, PC4, PC5.





The function of these signals as follows:

- STB (strobe): this is input handshake signal from peripheral to 8155.
- BF (buffer full): this is indicating the presence of the data byte in the port.
- INTR (interrupt request): this signal used to interrupt the MPU.
- INTE (interrupt enable): used to disable or enable the interrupt capability of the 8155.

Status word:

- MPU check the status Reg of port or timer.
- Control register & Status register have same port.
- Differentiated by RD and WR signals.

Status word (Status reg) format:

D7	D6	D5	D4	D3	D2	D1	D0
X	Timer	INTEb	BFb	INTRb	INTAa	BFa	INTRa