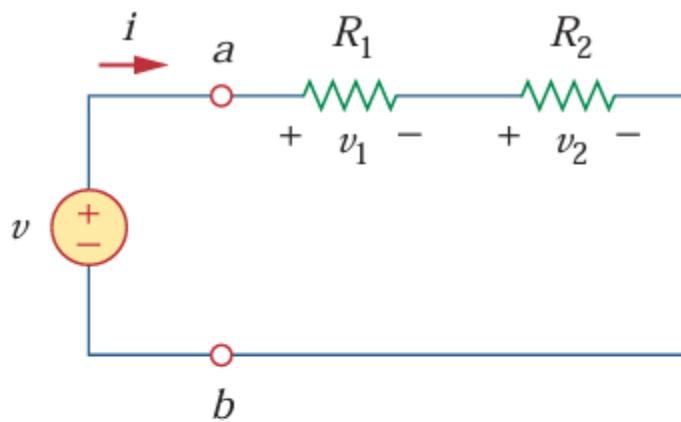


Ministry of Higher Education and Scientific Research  
Al-Mustaql University  
College of Engineering Technologies  
Medical Instrumentation Techniques Engineering Department  
Electrical Circuits  
First year



## Series Resistors and Voltage Division



**Figure 2.29**

A single-loop circuit with two resistors in series.

In the circuit shown in figure 2.29 the in the circuit is given the following equation:

$$i = \frac{v}{R_1 + R_2}$$

$$v_1 = iR_1, \quad v_2 = iR_2$$

and

$$-v + v_1 + v_2 = 0$$

$$v = v_1 + v_2 = i(R_1 + R_2)$$

$$v = iR_{\text{eq}}$$

Therefore, in series combination

$$R_{\text{eq}} = R_1 + R_2$$

The **equivalent resistance** of any number of resistors connected in series is the sum of the individual resistances.

For  $N$  resistors in series then,

$$R_{\text{eq}} = R_1 + R_2 + \cdots + R_N = \sum_{n=1}^N R_n$$

To determine the voltages across each resistor in circuit shown in figure 2.29 are as follows:

$$v_1 = \frac{R_1}{R_1 + R_2} v, \quad v_2 = \frac{R_2}{R_1 + R_2} v$$

However, for resistor  $n$  in the combination of  $N$  series resistors the voltage across  $R_n$  is

$$v_n = \frac{R_n}{R_1 + R_2 + \cdots + R_N} v$$


---



## Parallel Resistors and Current Division

Consider the circuit in Fig. 2.31, where two resistors are connected in parallel and therefore have the same voltage across them. From Ohm's law,

$$v = i_1 R_1 = i_2 R_2$$

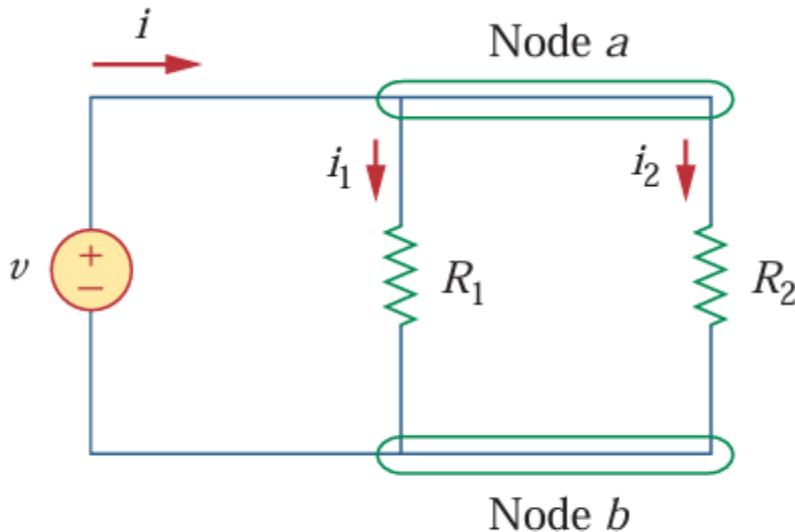

**Figure 2.31**

Two resistors in parallel.

or

$$i_1 = \frac{v}{R_1}, \quad i_2 = \frac{v}{R_2}$$

Applying KCL at node *a* gives the total current *i* as

$$i = i_1 + i_2$$

Then

$$i = \frac{v}{R_1} + \frac{v}{R_2} = v \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{v}{R_{\text{eq}}}$$

Therefore,

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

or

$$\frac{1}{R_{\text{eq}}} = \frac{R_1 + R_2}{R_1 R_2}$$

or

$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$

Thus,

The **equivalent resistance** of two parallel resistors is equal to the product of their resistances divided by their sum.

For  $N$  resistors connected in parallel, the equivalent resistance is

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_N}$$

And for equal resistors connected in parallel the equivalent resistance is:

$$R_{\text{eq}} = \frac{R}{N}$$

Or can be written by another form as:

$$G_{\text{eq}} = G_1 + G_2 + G_3 + \cdots + G_N$$

where  $G_{\text{eq}} = 1/R_{\text{eq}}$ ,  $G_1 = 1/R_1$ ,  $G_2 = 1/R_2$ ,  $G_3 = 1/R_3$ , ...,  $G_N = 1/R_N$ .

The **equivalent conductance** of resistors connected in parallel is the sum of their individual conductances.

Find  $R_{\text{eq}}$  for the circuit shown in Fig. 2.34.

### Example 2.9

**Solution:**

To get  $R_{\text{eq}}$ , we combine resistors in series and in parallel. The 6- $\Omega$  and 3- $\Omega$  resistors are in parallel, so their equivalent resistance is


$$6 \Omega \parallel 3\Omega = \frac{6 \times 3}{6 + 3} = 2 \Omega$$

(The symbol  $\parallel$  is used to indicate a parallel combination.) Also, the 1- $\Omega$  and 5- $\Omega$  resistors are in series; hence their equivalent resistance is


$$1 \Omega + 5 \Omega = 6 \Omega$$

Thus the circuit in Fig. 2.34 is reduced to that in Fig. 2.35(a). In Fig. 2.35(a), we notice that the two 2- $\Omega$  resistors are in series, so the equivalent resistance is


$$2 \Omega + 2 \Omega = 4 \Omega$$

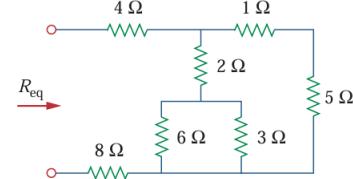

**Figure 2.34**  
For Example 2.9.

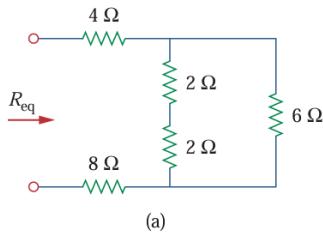

(a)

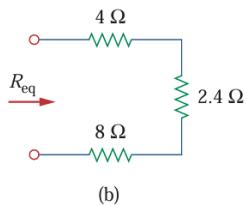

(b)

**Figure 2.35**

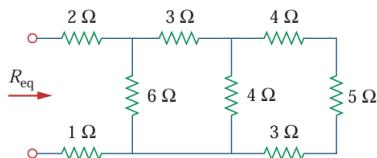
Equivalent circuits for Example 2.9.

This 4-Ω resistor is now in parallel with the 6-Ω resistor in Fig. 2.35(a); their equivalent resistance is


$$4 \Omega \parallel 6 \Omega = \frac{4 \times 6}{4 + 6} = 2.4 \Omega$$

The circuit in Fig. 2.35(a) is now replaced with that in Fig. 2.35(b). In Fig. 2.35(b), the three resistors are in series. Hence, the equivalent resistance for the circuit is

$$R_{\text{eq}} = 4 \Omega + 2.4 \Omega + 8 \Omega = 14.4 \Omega$$

**Practice Problem 2.9**By combining the resistors in Fig. 2.36, find  $R_{\text{eq}}$ .**Answer:** 6 Ω.**Figure 2.36**

For Practice Prob. 2.9.

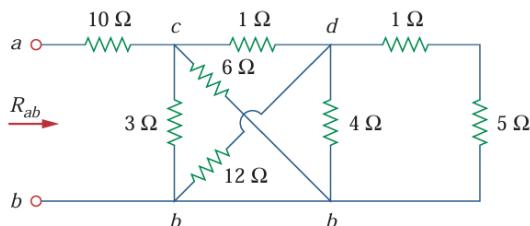**Example 2.10**Calculate the equivalent resistance  $R_{ab}$  in the circuit in Fig. 2.37.**Figure 2.37**

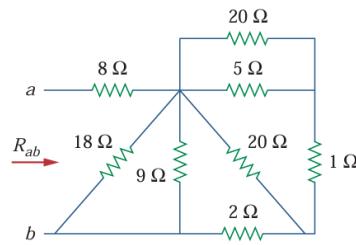
For Example 2.10.

**Example 2.12**

Find  $i_o$  and  $v_o$  in the circuit shown in Fig. 2.42(a). Calculate the power dissipated in the  $3\Omega$  resistor.

Find  $R_{ab}$  for the circuit in Fig. 2.39.

**Answer:**  $11\Omega$ .


**Practice Problem 2.10**

**Figure 2.39**

For Practice Prob. 2.10.

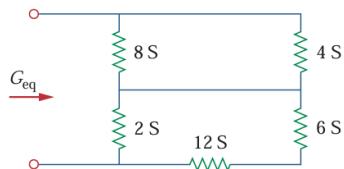**Practice Problem 2.11**

Calculate  $G_{eq}$  in the circuit of Fig. 2.41.




**Answer:**  $4\text{ S}$ .

**Figure 2.41**


For Practice Prob. 2.11.

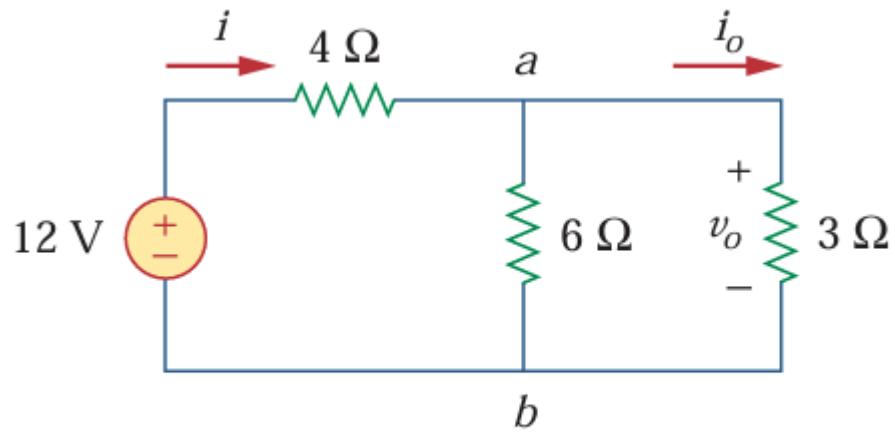**Example 2.12**

Find  $i_o$  and  $v_o$  in the circuit shown in Fig. 2.42(a). Calculate the power dissipated in the  $3\Omega$  resistor.



(a)

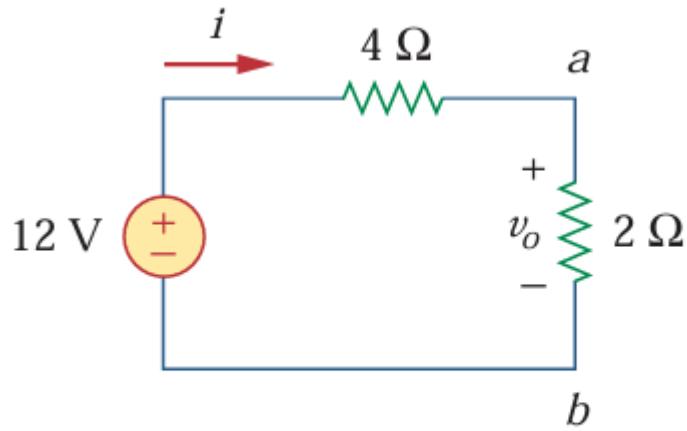

(b)

**Figure 2.42**