



COLLEGE OF ENGINEERING AND TECHNOLOGIES

ALMUSTAQBAL UNIVERSITY

Power Engineering

EET 305

Lecture 12

- Medium Transmission Lines -
(2025 - 2026)

Dr. Zaidoon AL-Shammary
Lecturer / Researcher

zaidoon.waleed@mustaqbal-college.edu.iq

- In short transmission line calculations, the effects of the line capacitance are neglected because such lines have smaller lengths and transmit power at relatively low voltages (< 20 kV).
- However, as the length and voltage of the line increase, the capacitance gradually becomes of greater importance.



- Since medium transmission lines have sufficient length (50-150 km) and usually operate at voltages greater than 20 kV, the effects of capacitance cannot be neglected.
- Therefore, in order to obtain reasonable accuracy in medium transmission line calculations, the line capacitance must be taken into consideration.
- The capacitance is uniformly distributed over the entire length of the line.

- However, in order to make the calculations simple, the line capacitance is assumed to be lumped or concentrated in the form of capacitors shunted across the line at one or more points.
- Such a treatment of localising the line capacitance gives reasonably accurate results.
- Although the above methods are used for obtaining the performance calculations of medium lines, they can also be used for short lines if their line capacitance is given in a particular problem.

- The most commonly used methods (known as localised capacitance methods) for the solution of medium transmissions lines are :
 - (i) End condenser method.
 - (ii) Nominal T method.
 - (iii) Nominal π method.

- In this method, the capacitance of the line is lumped or concentrated at the receiving or load end as shown in Figure.
- This method of localising the line capacitance at the load end overestimates the effects of capacitance.
- In Figure below, one phase of the 3-phase transmission line is shown as it is more convenient to work in phase instead of line-to-line values.

Introduction

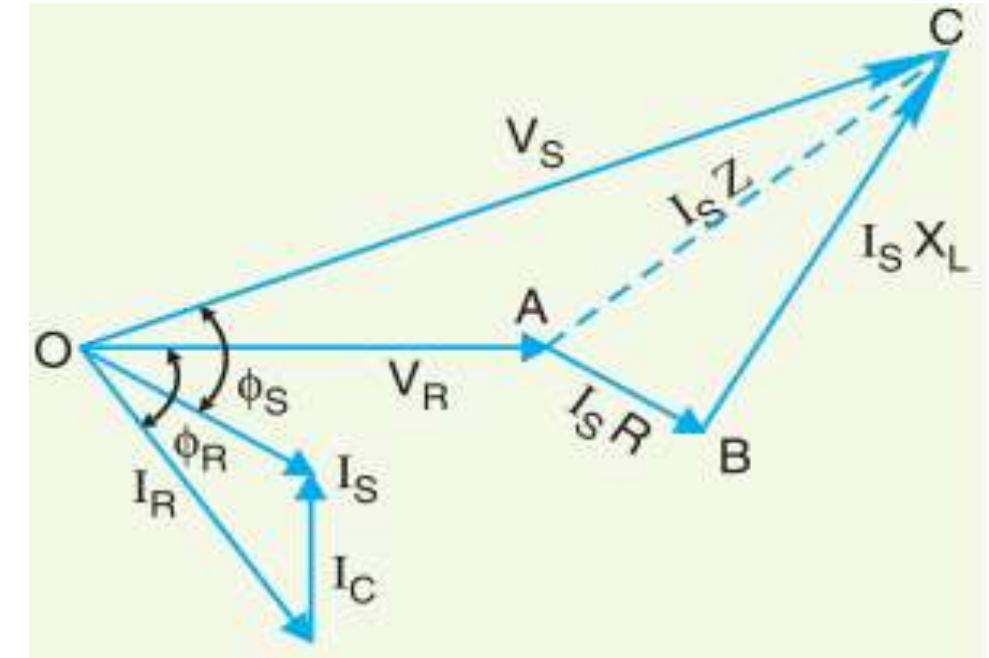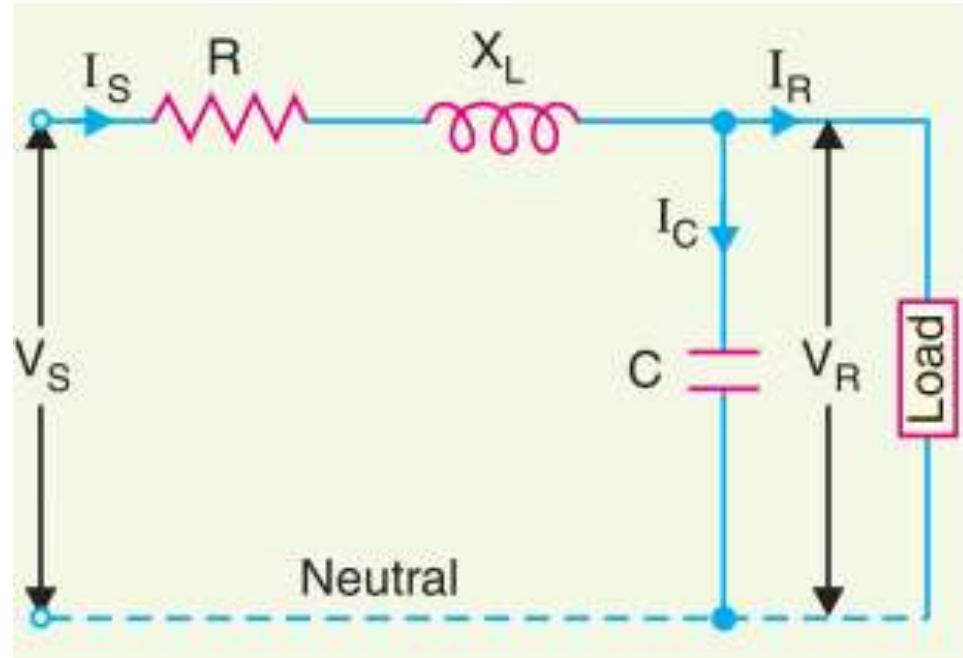



Let I_R = load current per phase

R = resistance per phase

X_L = inductive reactance per phase

C = capacitance per phase

$\cos \phi_R$ = receiving end power factor (*lagging*)

V_S = sending end voltage per phase

we have, $\vec{V}_R = V_R + j 0$

Load current, $\vec{I}_R = I_R (\cos \phi_R - j \sin \phi_R)$

Capacitive current, $\vec{I}_C = j \vec{V}_R \omega C = j 2 \pi f C \vec{V}_R$

$$\begin{aligned}\vec{I}_S &= \vec{I}_R + \vec{I}_C \\ &= I_R (\cos \phi_R - j \sin \phi_R) + j 2 \pi f C V_R \\ &= I_R \cos \phi_R + j (-I_R \sin \phi_R + 2 \pi f C V_R) \\ &= \vec{I}_S \vec{Z} = \vec{I}_S (R + j X_L)\end{aligned}$$

Voltage drop/phase

Sending end voltage, $\vec{V}_S = \vec{V}_R + \vec{I}_S \vec{Z} = \vec{V}_R + \vec{I}_S (R + j X_L)$

Thus, the magnitude of sending end voltage V_S can be calculated.

$$\% \text{ Voltage regulation} = \frac{V_S - V_R}{V_R} \times 100$$

$$\begin{aligned} \% \text{ Voltage transmission efficiency} &= \frac{\text{Power delivered / phase}}{\text{Power delivered / phase} + \text{losses / phase}} \times 100 \\ &= \frac{V_R I_R \cos \phi_R}{V_R I_R \cos \phi_R + I_S^2 R} \times 100 \end{aligned}$$

- Although end condenser method for the solution of medium lines is simple to work out calculations, yet it has the following drawbacks :
 - (i) There is a considerable error (about 10%) in calculations because the distributed capacitance has been assumed to be lumped or concentrated.
 - (ii) This method overestimates the effects of line capacitance.

Example

A (medium) single phase transmission line 100 km long has the following constants :

Resistance/km = 0.25Ω , Reactance/km = 0.8Ω , Susceptance/km = 14 Micro siemens, Receiving end line voltage = 66,000 V

Assuming that the total capacitance of the line is localised at the receiving end alone, determine

- (i) the sending end current
- (ii) the sending end voltage and
- (iii) voltage regulation.

The line is delivering 15,000 kW at 0.8 power factor lagging.

Total resistance, $R = 0.25 \times 100 = 25 \Omega$

Total reactance, $X_L = 0.8 \times 100 = 80 \Omega$

Total susceptance, $Y = 14 \times 10^{-6} \times 100 = 14 \times 10^{-4} S$

Receiving end voltage, $V_R = 66,000 V$



∴ Load current, $I_R = \frac{15,000 \times 10^3}{66,000 \times 0.8} = 284 A$

$$\cos \phi_R = 0.8; \quad \sin \phi_R = 0.6$$

$$\vec{V}_R = V_R + j 0 = 66,000 V$$

Load current, $\vec{I}_R = I_R (\cos \phi_R - j \sin \phi_R) = 284 (0.8 - j 0.6) = 227 - j 170$

Solution

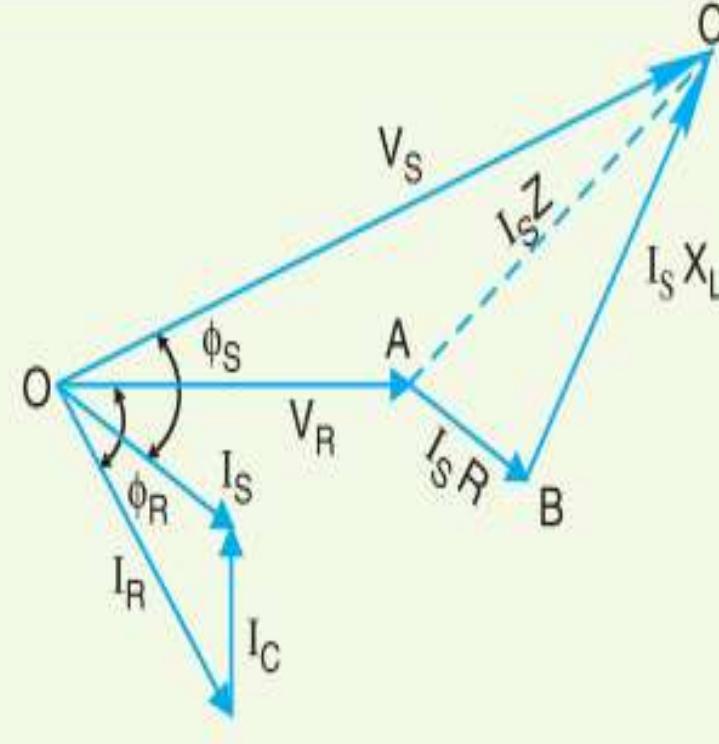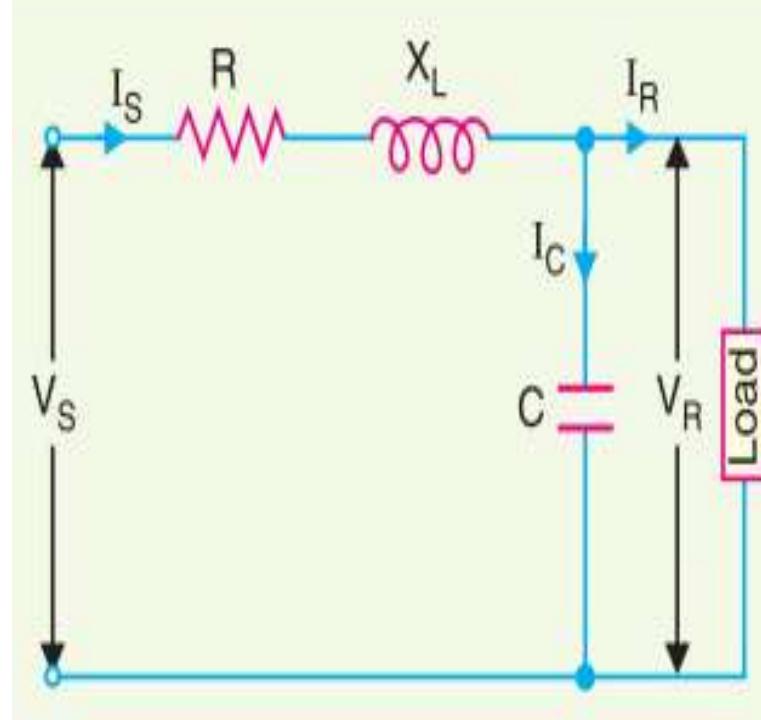

Capacitive current, $\vec{I}_C = j Y \times V_R = j 14 \times 10^{-4} \times 66000 = j 92$

(i) Sending end current, $\vec{I}_S = \vec{I}_R + \vec{I}_C = (227 - j 170) + j 92$
 $= 227 - j 78$

Magnitude of $I_S = \sqrt{(227)^2 + (78)^2} = 240 \text{ A}$

(ii) Voltage drop $= \vec{I}_S \vec{Z} = \vec{I}_S (R + j X_L) = (227 - j 78) (25 + j 80)$
 $= 5,675 + j 18,160 - j 1950 + 6240$
 $= 11,915 + j 16,210$

Sending end voltage, $\vec{V}_S = \vec{V}_R + \vec{I}_S \vec{Z} = 66,000 + 11,915 + j 16,210$
 $= 77,915 + j 16,210$

Magnitude of $V_S = \sqrt{(77915)^2 + (16210)^2} = 79583 \text{ V}$

(iii) % Voltage regulation $= \frac{V_S - V_R}{V_R} \times 100 = \frac{79,583 - 66,000}{66,000} \times 100 = 20.58\%$

