
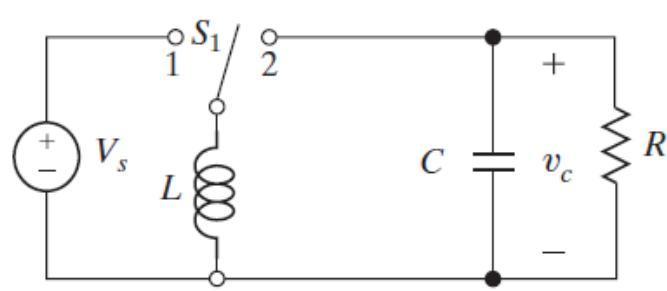

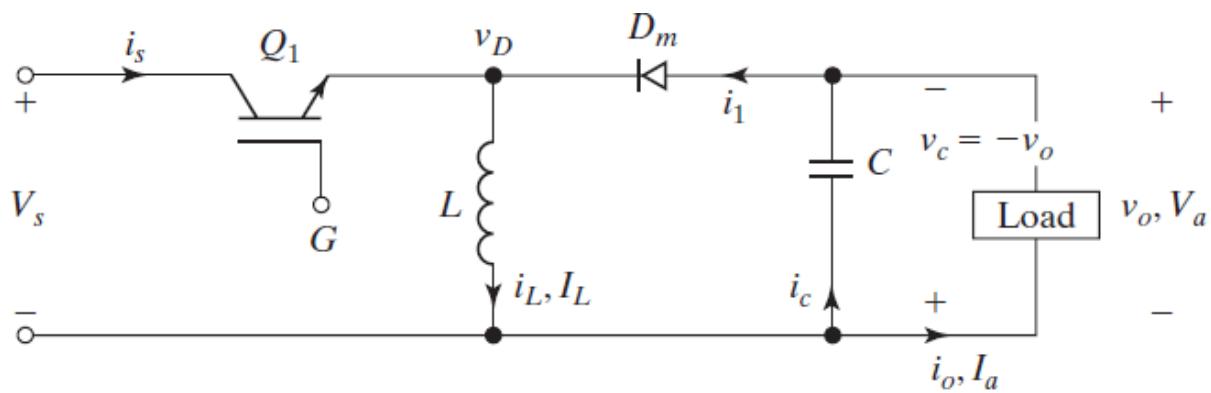
## 1. Buck-Boost Regulators

A buck-boost regulator provides an output voltage that may be less than or greater than the input voltage—hence the name “buck-boost”; the output voltage polarity is opposite to that of the input voltage. This regulator is also known as an inverting regulator. The circuit arrangement of a buck-boost regulator is shown in Figure.1 (a). Transistor Q1 acts as a controlled switch and diode Dm is an uncontrolled switch. They operate as two SPST current-bidirectional switches. The circuit in Figure.1(a) is often represented by two switches as shown in Figure.1(b).





(b) Switch representation

Figure.1: Buck-boost regulator with continuous  $i_L$



The circuit operation can be divided into two modes. During mode 1, transistor  $Q_1$  is turned on and diode  $D_m$  is reversed biased. The input current, which rises, flows through inductor  $L$  and transistor  $Q_1$ . During mode 2, transistor  $Q_1$  is switched off and the current, which was flowing through inductor  $L$ , would flow through  $L$ ,  $C$ ,  $D_m$ , and the load. The energy stored in inductor  $L$  would be transferred to the load and the inductor current would fall until transistor  $Q_1$  is switched on again in the next cycle. The equivalent circuits for the modes are shown in Figure.2.

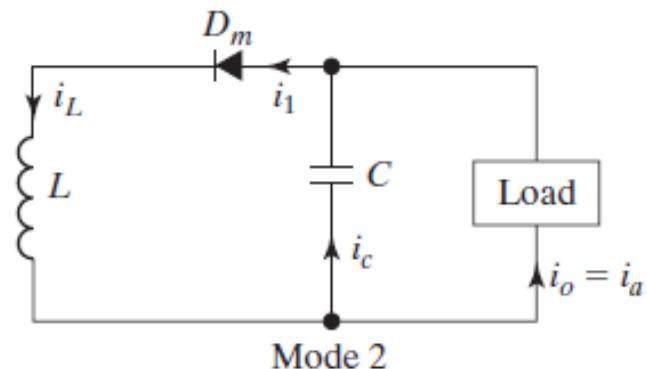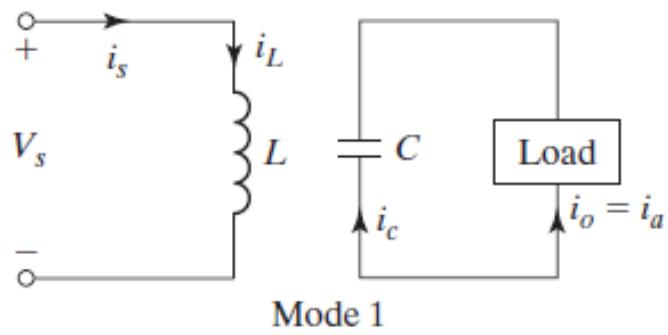

(c) Equivalent circuits

Figure.2: Two Mode

The waveforms for SteadyState voltages and currents of the buck-boost regulator are shown in Figure.3 for a continuous load current.



Assuming that the inductor current rises linearly from  $I_1$  to  $I_2$  in time  $t_1$ ,

$$V_s = L \frac{I_2 - I_1}{t_1} = L \frac{\Delta I}{t_1}$$

$$t_1 = \frac{\Delta I L}{V_s}$$


and the inductor current falls linearly from  $I_2$  to  $I_1$  in time  $t_2$ ,

$$V_a = -L \frac{\Delta I}{t_2}$$

or

$$t_2 = \frac{-\Delta I L}{V_a}$$

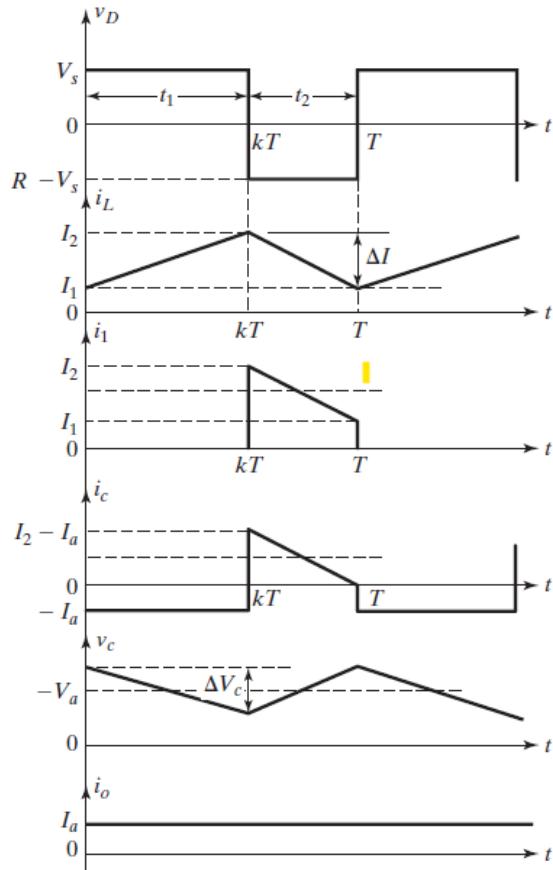where  $\Delta I = I_2 - I_1$  is the peak-to-peak ripple current of inductor L





$$\Delta I = \frac{V_s t_1}{L} = \frac{-V_a t_2}{L}$$

Substituting  $t_1 = kT$  and  $t_2 = (1 - k)T$ , the average output voltage is

$$V_a = -\frac{V_s k}{1 - k}$$

and the average input current  $I_s$  is related to the average output current  $I_a$  by

$$I_s = \frac{I_a k}{1 - k}$$

The peak-to-peak ripple current,

$$\Delta I = \frac{V_s V_a}{fL(V_a - V_s)}$$

or

$$\Delta I = \frac{V_s k}{fL}$$

The average inductor current is given by

$$I_L = I_s + I_a = \frac{kI_a}{1 - k} + I_a = \frac{I_a}{1 - k}$$

Peak-to-peak capacitor ripple voltage. When transistor Q1 is on, the filter Capacitor supplies the load current for  $t = t_1$ . The average discharging current of the capacitor is  $I_c = -I_a$  and the peak-to-peak ripple voltage of the capacitor is

$$\Delta V_c = \frac{I_a k}{fC}$$



Condition for continuous inductor current and capacitor voltage. If  $I_L$  is the average inductor current, at the critical condition for continuous conduction the inductor ripple current  $I = 2I_L$ .

which gives the critical value of the inductor  $L_c$  as

$$L_c = L = \frac{(1 - k)R}{2f} \quad (5.96)$$


If  $V_c$  is the average capacitor voltage, at the critical condition for continuous conduction the capacitor ripple voltage  $\Delta V_c = -2V_a$ . Using Eq. (5.95), we get

$$-\frac{I_a k}{C f} = -2V_a = -2I_a R$$

which gives the critical value of the capacitor  $C_c$  as

$$C_c = C = \frac{k}{2fR} \quad (5.97)$$

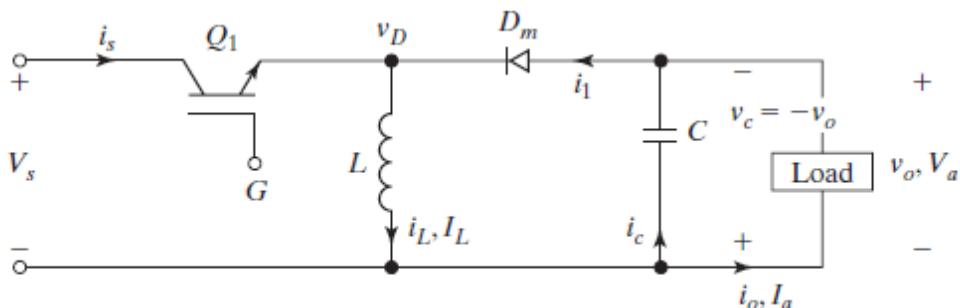**Example.1:** The buck-boost regulator in Figure has an input voltage of  $V_s = 12$  V. The duty cycle  $k = 0.25$  and the switching frequency is 25 kHz. The inductance  $L = 150 \mu\text{H}$  and filter capacitance  $C = 220 \mu\text{F}$ . The average load current  $I_a = 1.25$  A. Determine (a) the average output voltage,  $V_a$ ; (b) the peak-to-peak output voltage ripple,  $V_c$ ; (c) the peak-to-peak ripple current of inductor,  $I$ ; (d) the peak current of the transistor,  $I_p$ ; and (e) the critical values of  $L$  and  $C$ .



(a) Circuit diagram



## Solution:

$V_s = 12 \text{ V}$ ,  $k = 0.25$ ,  $I_a = 1.25 \text{ A}$ ,  $f = 25 \text{ kHz}$ ,  $L = 150 \mu\text{H}$ , and  $C = 220 \mu\text{F}$ .

a. From Eq. (5.86),  $V_a = -12 \times 0.25 / (1 - 0.25) = -4 \text{ V}$ .

b. From Eq. (5.95), the peak-to-peak output ripple voltage is

$$\Delta V_c = \frac{1.25 \times 0.25}{25,000 \times 220 \times 10^{-6}} = 56.8 \text{ mV}$$

c. From Eq. (5.92), the peak-to-peak inductor ripple is

$$\Delta I = \frac{12 \times 0.25}{25,000 \times 150 \times 10^{-6}} = 0.8 \text{ A}$$

d. From Eq. (5.89),  $I_s = 1.25 \times 0.25 / (1 - 0.25) = 0.4167 \text{ A}$ . Because  $I_s$  is the average of duration  $kT$ , the peak-to-peak current of the transistor,

$$I_p = \frac{I_s}{k} + \frac{\Delta I}{2} = \frac{0.4167}{0.25} + \frac{0.8}{2} = 2.067 \text{ A}$$

e.  $R = \frac{-V_a}{I_a} = \frac{4}{1.25} = 3.2 \Omega$

From Eq. (5.96), we get  $L_c = \frac{(1 - k)R}{2f} = \frac{(1 - 0.25) \times 3.2}{2 \times 25 \times 10^3} = 450 \mu\text{H}$ .

From Eq. (5.97), we get  $C_c = \frac{k}{2fR} = \frac{0.25}{2 \times 25 \times 10^3 \times 3.2} = 1.56 \mu\text{F}$ .