



COLLEGE OF ENGINEERING AND TECHNOLOGIES
ALMUSTAQBAL UNIVERSITY

AC Power Converter
EET 307

Lecture 11

- Bridge Inverter -
(2025 - 2026)

Dr. Zaidoon AL-Shammari

Lecturer / Researcher

zaidoon.waleed@mustaqbal-college.edu.iq

- Ideally, an inverter should give a sinusoidal voltage at its output.
- But the output of practical inverters is non-sinusoidal and contains harmonics.
- The quality of an inverter is evaluated in terms of the following performance parameters:

1. Harmonic Factor of nth Harmonic (HF_n):

A harmonic factor is a measure of the individual harmonic contribution in the output voltage of an inverter.

It is defined as:

$$HF_n = \frac{V_n}{V_1}$$

where

V_n = root mean square (RMS) value of the n th harmonic component.

V_1 = RMS value of the fundamental component of the output voltage.

2. Total Harmonic Distortion (THD):

A total harmonic distortion is a measure of closeness in shape between a waveform and its fundamental component.



It is defined as the ratio of the RMS value of the total harmonic component of the output voltage and the RMS value of the fundamental component, that is,

$$\text{THD} = \frac{\sqrt{\sum_{n=2,3,\dots}^{\infty} V_n^2}}{V_1} = \frac{\sqrt{V_{\text{rms}}^2 - V_1^2}}{V_1}$$

where V_{rms} is the RMS value of output voltage.

- Power circuit and various waveforms for single phase half-bridge configuration are shown in the figure.
- The output voltage is an alternating voltage waveform of amplitude $V_S / 2$ and frequency $1/T$ Hz.
- Frequency of inverter output AC voltage can be changed by varying the periodic time T .
- Demerits (Drawbacks) of half-bridge configuration:
 - a. It requires a three-wire DC supply.
 - b. Output voltage magnitude is $V_S/2$ only.

Half Bridge Inverter

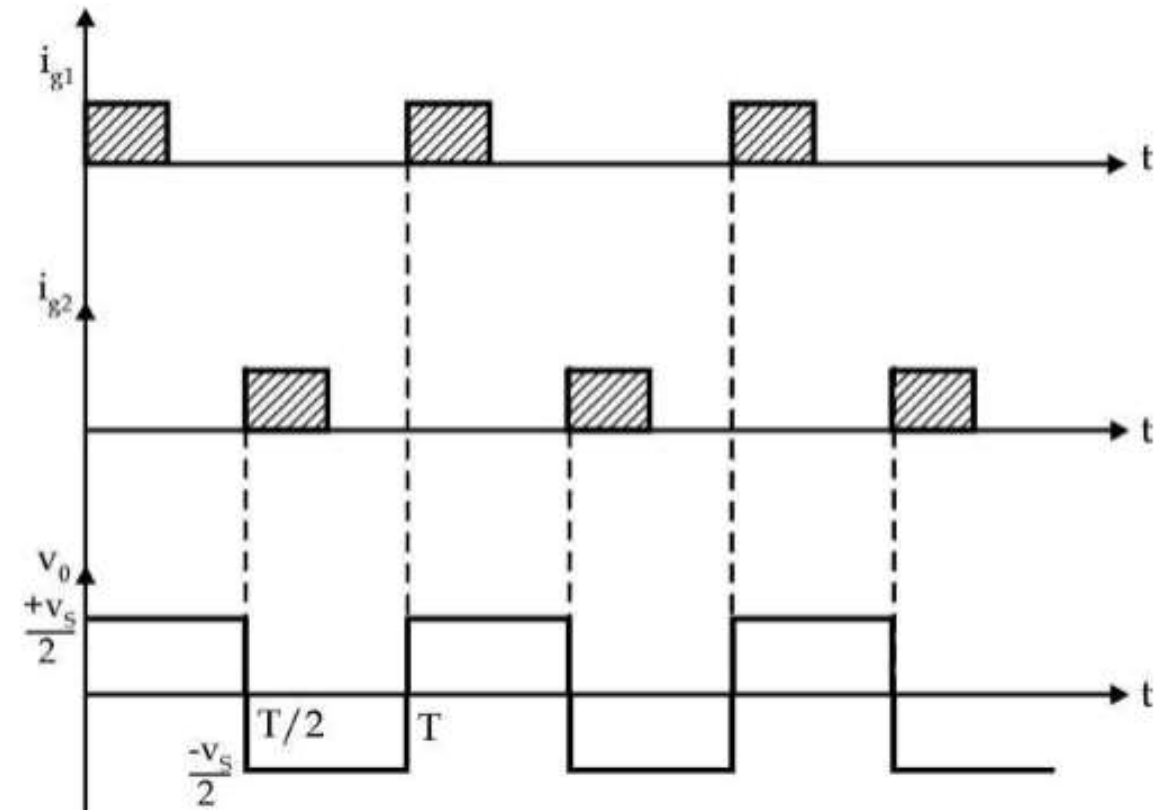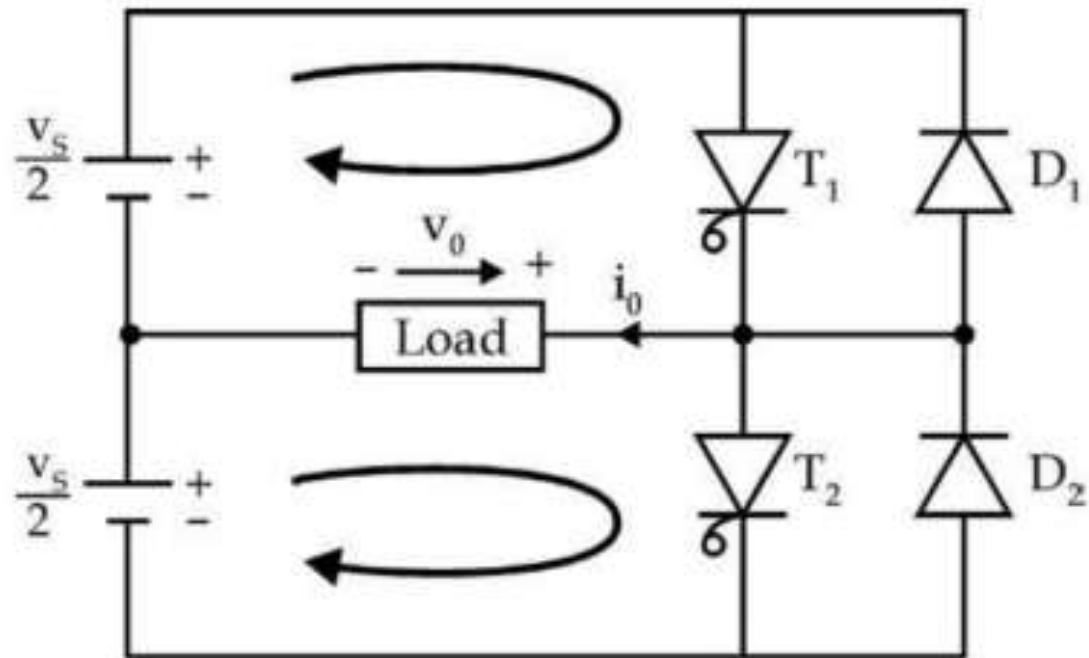

- Power circuit diagram of full-bridge configuration with various waveforms are shown in the figure.
- Frequency of the inverter output AC voltage can be changed by varying the periodic time T.
- Therefore,

$$v_0 = +V_S \text{ and } i_0 = +I_0 \quad \text{for } 0 < t < T/2$$

$$v_0 = -V_S \text{ and } i_0 = -I_0 \quad \text{for } T/2 < t < T$$

Circuit Description

- DC Source (E): Provides constant input voltage.
- Thyristors (T_1 – T_4): Controlled switches forming the full-bridge.
- Diodes (D_1 – D_4): Provide freewheeling paths for inductive current.
- Load (R–L): Series resistor and inductor.
- Output Voltage (v_L): AC voltage across R–L load.
- Load Current (i_L): Continuous current due to inductor.

Operation Principle



Positive Half Cycle:

- Trigger T_1 and T_2 .
- Current path: $T_1 \rightarrow \text{Load} \rightarrow T_2 \rightarrow \text{DC return}$.
- Diodes D_1 – D_4 allow current to continue through L during SCR turn-off.

Negative Half Cycle:



- Trigger T_3 and T_4 .
- Current path: $T_3 \rightarrow \text{Load} \rightarrow T_4 \rightarrow \text{DC return}$.
- Freewheeling diodes maintain continuous load current through L.

Full Bridge Inverter

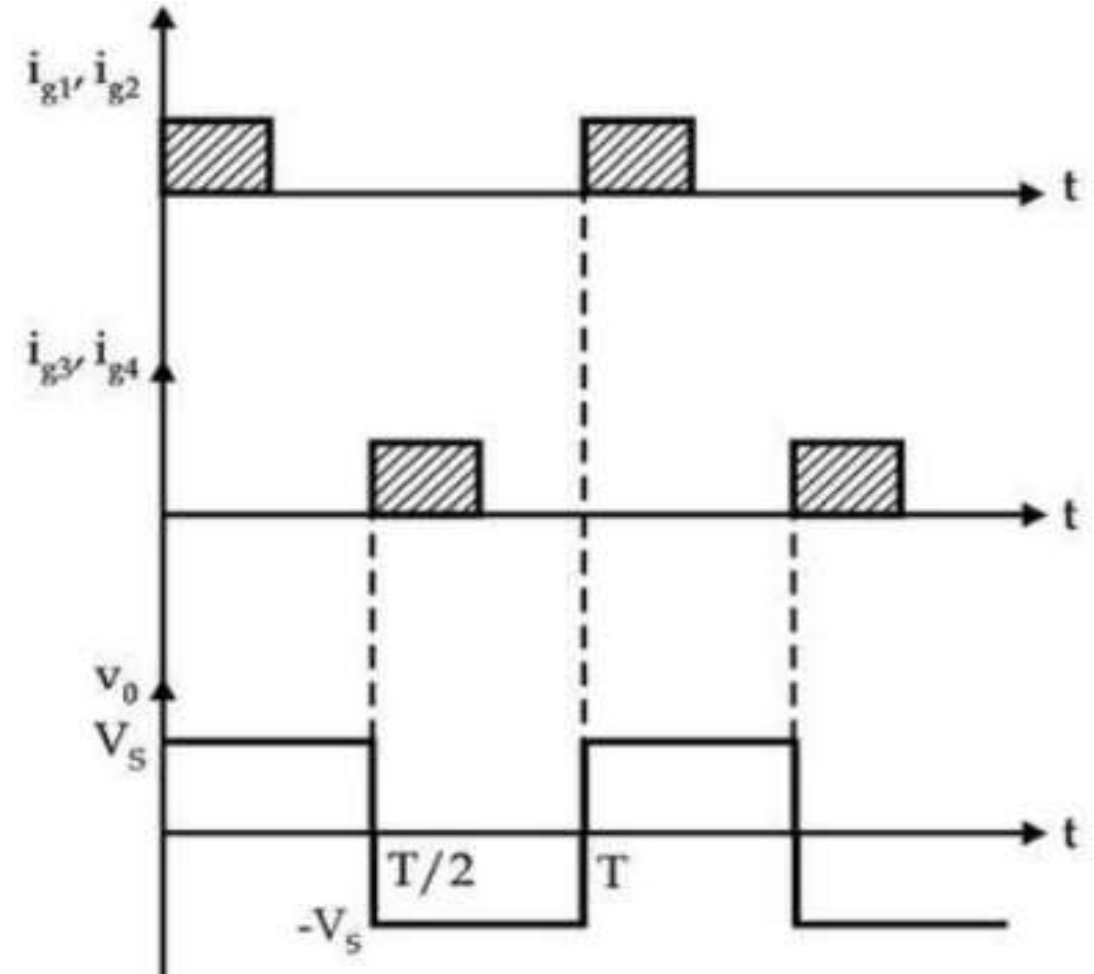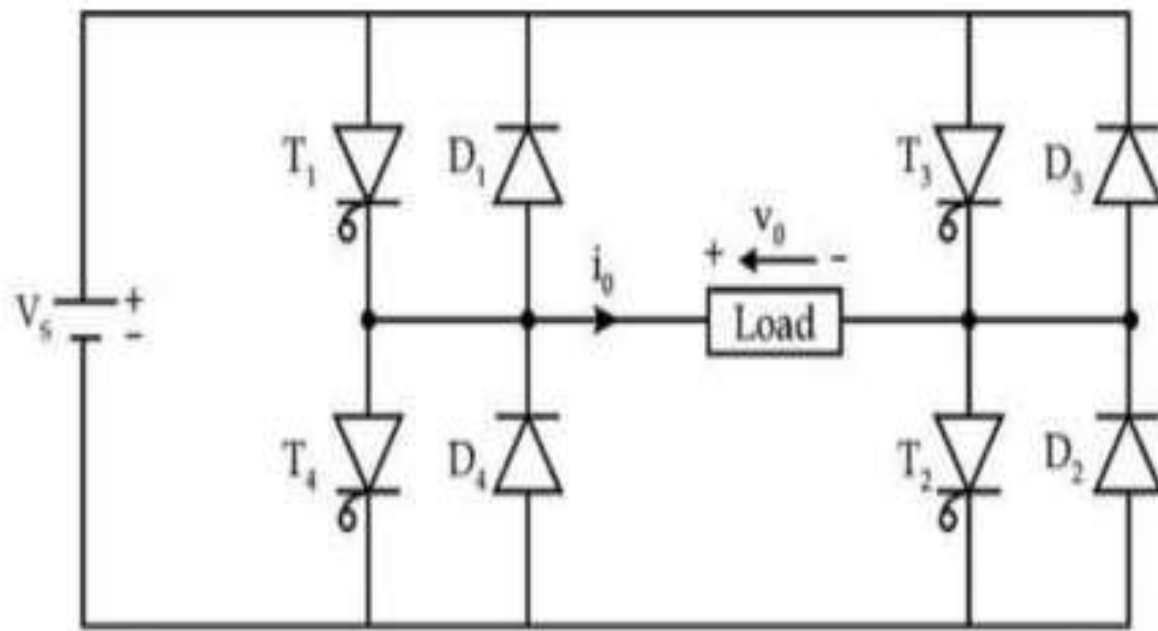



- It should be noted that in VSIs, the load voltage waveforms do not depend on the nature of load, but the load current depends on the nature of load.
- With R load:
 - For resistive load R, load current i_0 is identical with load voltage waveform v_0 and diodes D1–D4 connected in antiparallel with thyristors (called feedback diodes) are not required.

Full Bridge Inverter

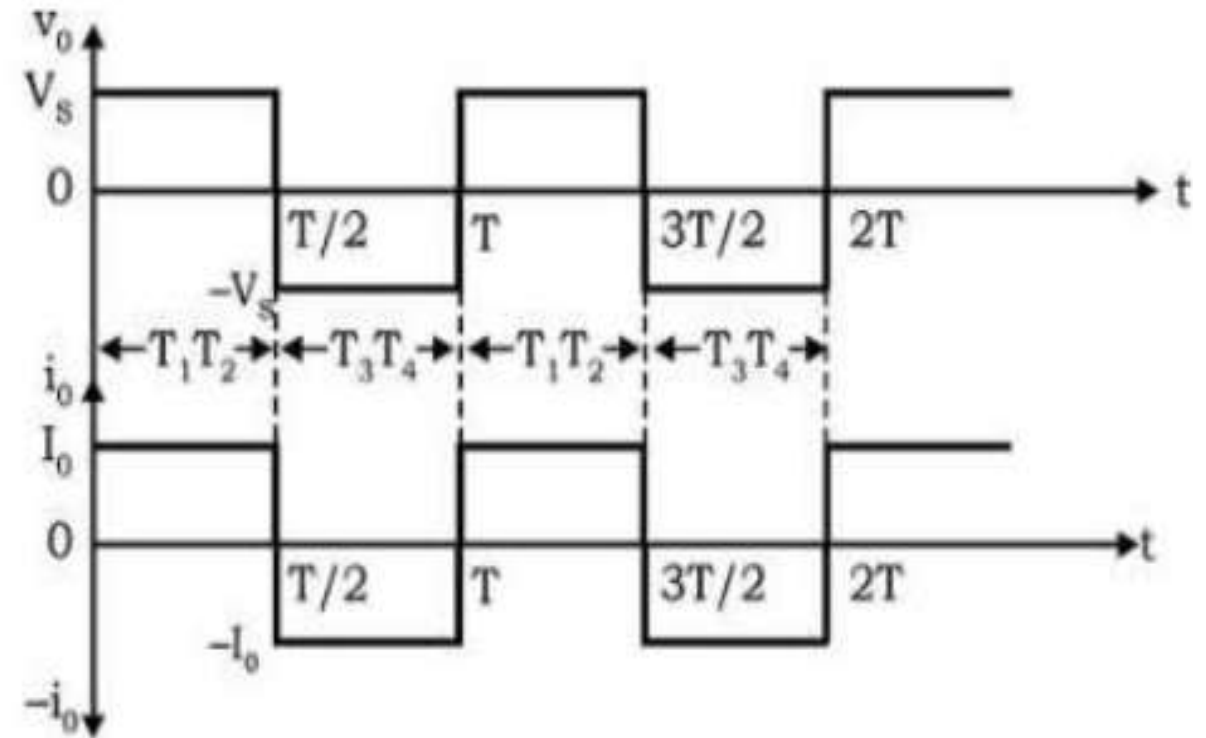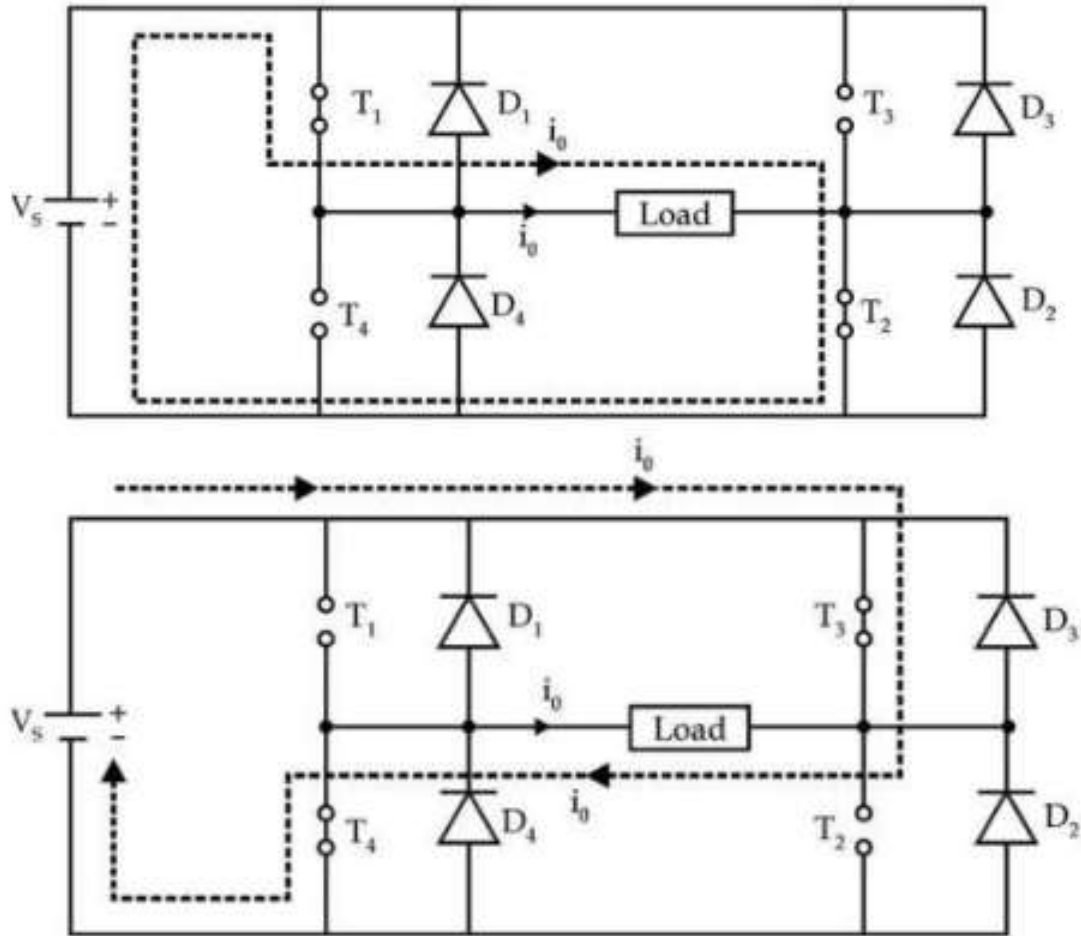

- With RL and RLC loads
 - For inductive loads, load current will not be in phase with voltage v_o , and therefore, feedback diodes D1–D4 are required to allow the current to flow when the main thyristors are turned off.
 - The load current waveforms for RL and RLC overdamped loads are shown in the Figures.
 - Before $T = 0$, thyristors T3 , T4 are conducting, and therefore load current i_0 was $-I_0$.

Full Bridge Inverter

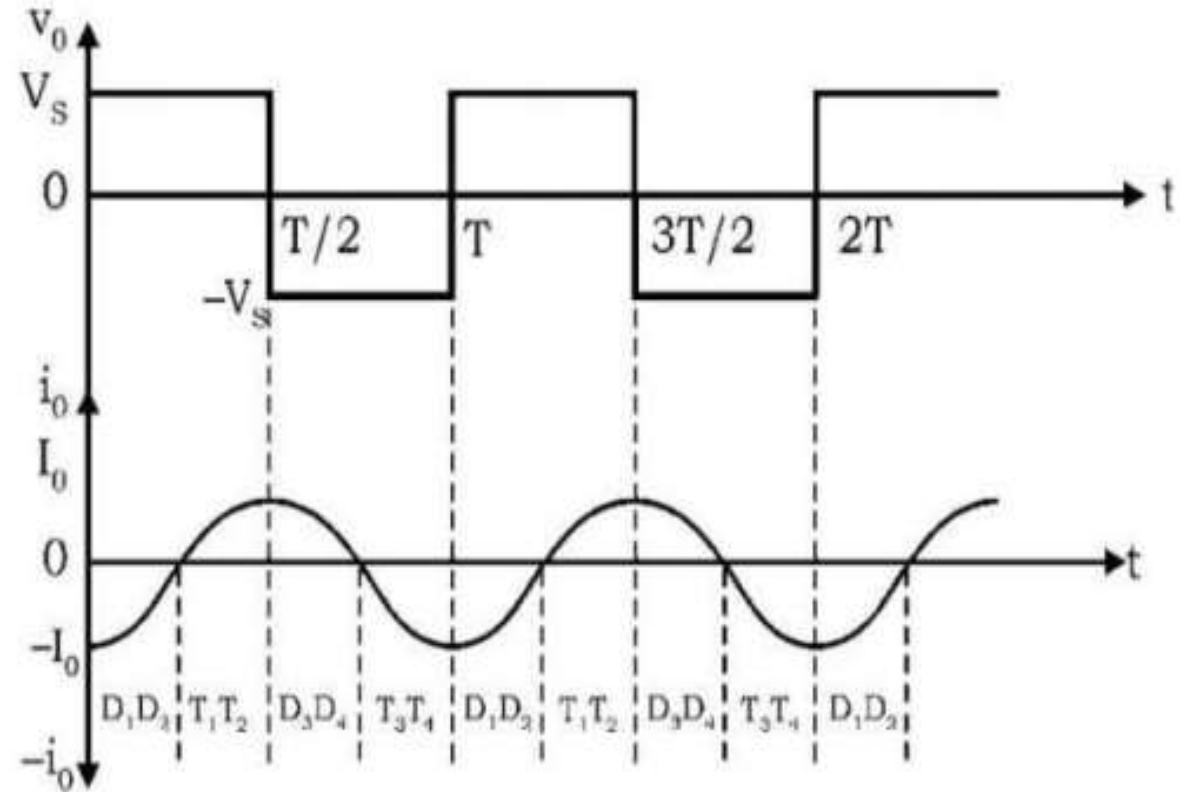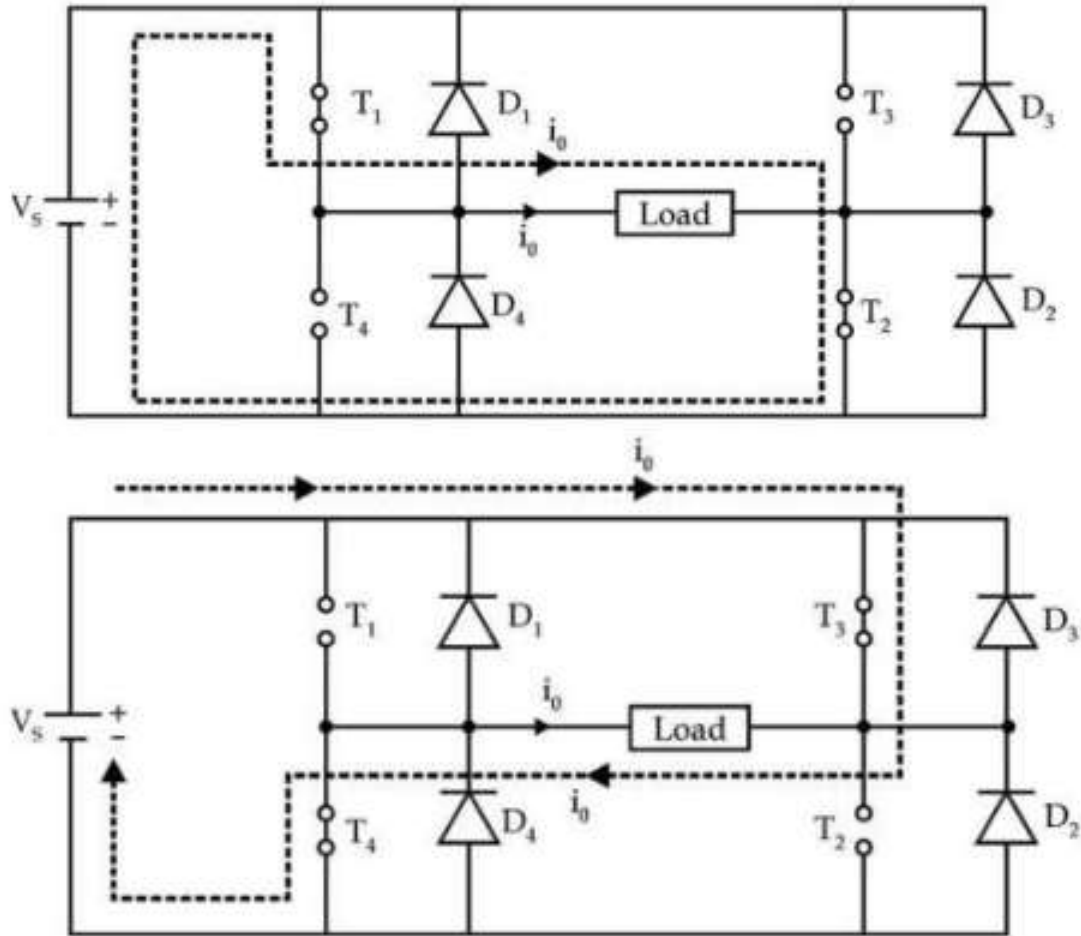

AL- MUSTAQBAL UNIVERSITY
ELECTRICAL ENGINEERING TECHNIQUES

Al-Mustaqbal
University

