



COLLEGE OF ENGINEERING AND TECHNOLOGIES
ALMUSTAQBAL UNIVERSITY

AC Power Converter

EET 307

Lecture 6

- AC Voltage Controller Circuits -
(2025 - 2026)

Dr. Zaidoon AL-Shammari

Lecturer / Researcher

zaidoon.waleed@mustaqbal-college.edu.iq

Types of Power Electronic Converters

- A power electronic system consists of one or more power electronic converters.
- A power electronic converter is made up of some power semiconductor devices controlled by integrated circuits.
- The switching characteristics of power semiconductor devices permit a power electronic converter to shape the input power of one form to output power of some other form.
- Static power converters perform these functions of power conversion very efficiently.

1. AC to DC converters (Rectifiers)

- A diode rectifier circuit converts ac input voltage into a fixed dc voltage.
- The input voltage may be single phase or three phase.
- Diode rectifiers find wide use in electric traction, battery charging, electroplating, electrochemical processing, power supplies, welding and uninterruptible power supply (UPS) systems.

2. DC to DC converters (DC Choppers)

- DC chopper converts fixed dc input voltage to a controllable dc output voltage.
- The chopper circuits require forced, or load, commutation to turn-off the thyristors.
- For lower power circuits, thyristors are replaced by power transistors.
- Choppers find wide applications in dc drives, subway cars, trolley trucks, battery-driven vehicles etc.


3. DC to AC Converters (Inverters)

- An inverter converts fixed dc voltage to a variable ac voltage.
- The output may be a variable voltage and variable frequency.
- These converters use line, load or forced commutation for turning-off the thyristors.
- Inverters find wide use in induction-motor and synchronous-motor drives, induction heating, UPS, HVDC transmission etc.

4. AC to AC Converters: AC voltage controllers

- These convert fixed ac input voltage into variable ac output voltage.
- These converter" circuits convert fixed ac voltage directly to a variable ac voltage at the same frequency.
- Output voltage is controlled by varying the firing angle delay.
- AC voltage controllers are widely used for lighting control, speed 'control of fans, pumps etc.


Types of Power Electronic Converters

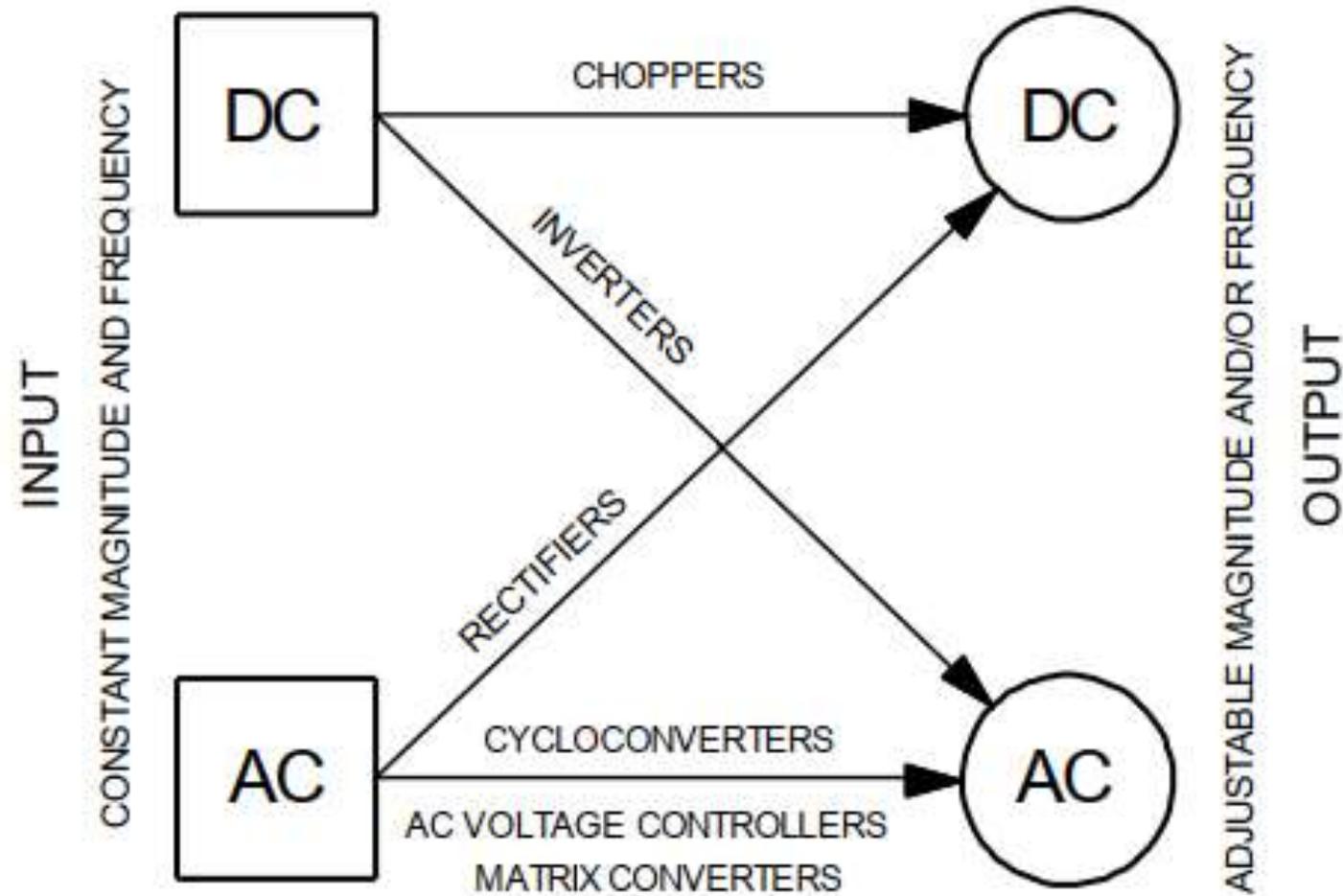

- AC voltage controllers (ac line voltage controllers) are employed to vary the RMS value of the alternating voltage applied to a load circuit by introducing Thyristors between the load and a constant voltage ac source.
- The RMS value of alternating voltage applied to a load circuit is controlled by controlling the triggering angle of the Thyristors in the ac voltage controller circuits.

- In brief, an ac voltage controller is a type of thyristor power converter which is used to convert a fixed voltage, fixed frequency ac input supply to obtain a variable voltage ac output.
- The RMS value of the ac output voltage and the ac power flow to the load is controlled by varying (adjusting) the trigger angle ' α '

AC Voltage Controllers

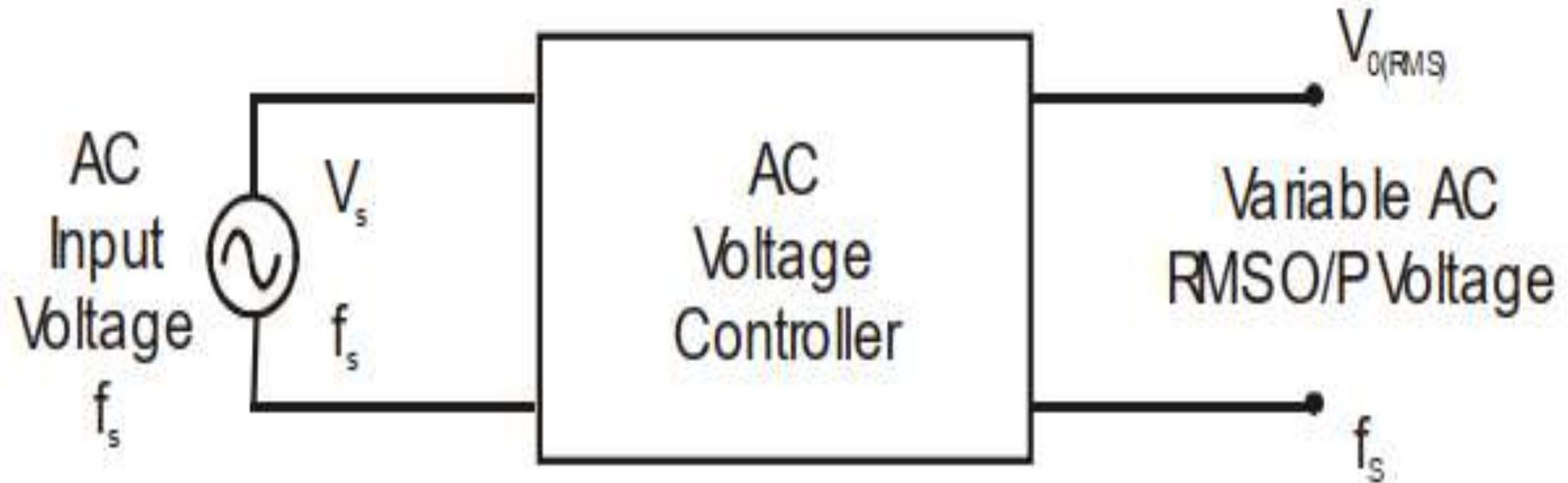

The AC voltage controllers are classified into two types based on the type of input ac supply applied to the circuit.

- Single Phase AC Controllers.
- Three Phase AC Controllers.

Type of AC Voltage Controllers

- Single phase ac controllers operate with single phase ac supply voltage of 230V RMS at 50Hz supply frequency.
- Three phase ac controllers operate with 3 phase ac supply of 400V RMS at 50Hz supply frequency.
- Each type of controller may be sub divided into
 - Uni-directional or half wave ac controller.
 - Bi-directional or full wave ac controller.

Type of AC Voltage Controllers

In brief different types of ac voltage controllers are

- Single phase half wave ac voltage controller (uni-directional controller).
- Single phase full wave ac voltage controller (bi-directional controller).
- Three phase half wave ac voltage controller (uni-directional controller).
- Three phase full wave ac voltage controller (bi-directional controller).

- Lighting / Illumination control in ac power circuits.
- Induction heating.
- Industrial heating & Domestic heating.
- Transformer tap changing (on load transformer tap changing).
- Speed control of induction motors (single phase and poly phase ac induction motor control).
- AC magnet controls.

AL- MUSTAQBAL UNIVERSITY
ELECTRICAL ENGINEERING TECHNIQUES

Al-Mustaqbal
University

