




KIRCHHOFF'S LAWS

Ohm's law by itself is not sufficient to analyze circuits. However, when coupled with Kirchhoff's two laws, we have a sufficient, powerful set of tools for analyzing a large variety of electric circuits.

Kirchhoff's current law (KCL) states that the algebraic sum of currents entering a node is zero

Mathematically, KCL implies that $\sum_{n=1}^N i_n = 0$

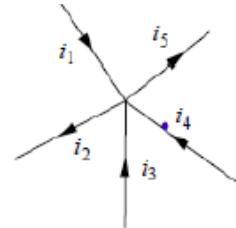
Where N is the number of branches connected to the node



and i_n is the n th current entering (or leaving) the node.

since currents i_1 , i_3 , and i_4 are entering the node, while currents i_2 and i_5 are leaving it. By rearranging the terms, we get $i_1 + i_3 + i_4 = i_2 + i_5$

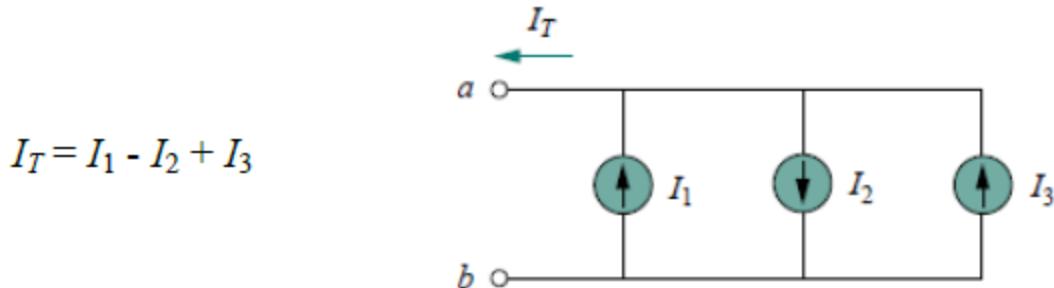The sum of the currents entering a node equals the sum of the currents leaving the node.



Kirchhoff's voltage law (KVL) states that the algebraic sum of all voltages around a closed path (or loop) is zero.

$$\sum_{m=1}^M v_m = 0$$

Where M is the number of voltages in the loop (or the number of branches in the loop) and v_m is the m th voltage.

To illustrate KVL, consider the circuit in Fig. 5.

$$-v_1 + v_2 + v_3 - v_4 + v_5 = 0$$

Rearranging terms gives

$$+ v_2 + v_3 + v_5 = v_1 + v_4$$

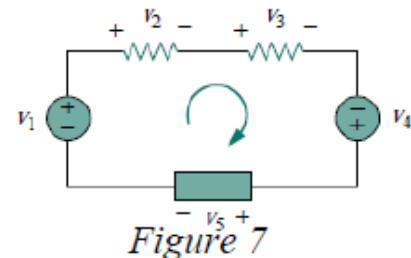


Figure 7

which may be interpreted as

Sum of voltage drops = Sum of voltage rises



Example (3): For the circuit of Fig. 8

- Find RT .
- Find I .
- Find V_1 and V_2 .
- Find the power to the 4Ω and 6Ω resistors.
- Find the power delivered by the battery, and compare it to that dissipated by the 4Ω and 6Ω resistors combined.
- Verify Kirchhoff's voltage law (clockwise direction).

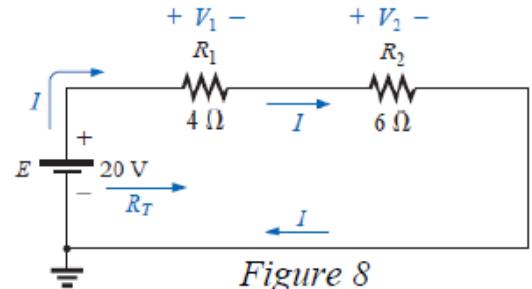


Figure 8

Solution

$$a. RT = R1 + R2 = 4 \Omega + 6 \Omega = 10 \Omega$$

$$b. I = \frac{E}{R_T} = \frac{20V}{10\Omega} = 2A$$

$$c. V_1 = IR_1 = 2A \times 4\Omega = 8V \quad V_2 = IR_2 = 2A \times 6\Omega = 12V$$

$$d. P_1 = \frac{V^2}{R_1} = \frac{8^2}{4} = 16W \quad P_2 = \frac{V^2}{R_2} = \frac{12^2}{6} = 24W$$

$$e. P_E = P_1 + P_2 = 16 + 24 = 40W$$

$$f. -E + V_1 + V_2 = 0 \quad E = V_1 + V_2 \quad 20V = 8V + 12V$$



Example (4): For the circuit of Fig. 9

- Determine V_2 using Kirchhoff's voltage law.
- Determine I .
- Find R_1 and R_3 .

Solution

a- Kirchhoff's voltage law (clockwise direction):

$$-E + V_3 + V_2 + V_1 = 0$$


$$\text{or } E = V_1 + V_2 + V_3$$

$$\text{and } V_2 = E - V_1 - V_3 = 54 \text{ V} - 18 \text{ V} - 15 \text{ V} = 21 \text{ V}$$

$$\text{b- } I = \frac{V_2}{R_2} = \frac{21}{7} = 3 \text{ A}$$

$$\text{c- } R_1 = \frac{V_1}{I} = \frac{18}{3} = 6 \Omega$$
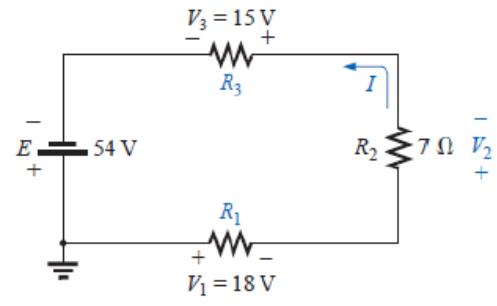
$$\text{d- } R_3 = \frac{V_3}{I} = \frac{15}{3} = 5 \Omega$$





Example (5) Find the currents and voltages in the circuit shown in the figure below


Solution

We apply Ohm's law and Kirchhoff's laws. By Ohm's law,

$$v_1 = 8i_1, \quad v_2 = 3i_2, \quad v_3 = 6i_3$$

At node a , KCL gives

$$i_1 - i_2 - i_3 = 0$$

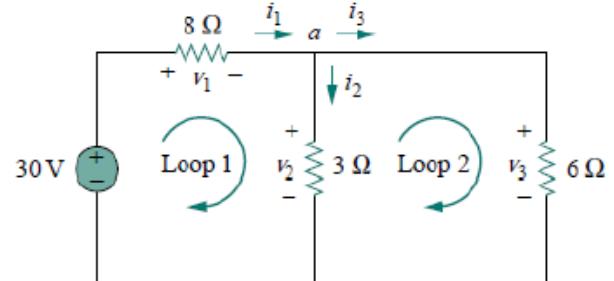

Applying KVL to loop 1

$$-30 + v_1 + v_2 = 0$$

We express this in terms of i_1 and i_2

$$-30 + 8i_1 + 3i_2 = 0$$

$$i_1 = \frac{(30 - 3i_2)}{8}$$

Applying KVL to loop 2,

$$-v_2 + v_3 = 0 \Rightarrow v_3 = v_2$$

$$6i_3 = 3i_2 \Rightarrow i_3 = \frac{3i_2}{6} = \frac{i_2}{2} \Rightarrow$$

$$i_1 - i_2 - i_3 = 0$$

$$\frac{30 - 3i_2}{8} - i_2 - \frac{i_2}{2} = 0$$



Al-Mustaql University / College of Engineering & Technology

Department of Communications technology Engineering)

Class(First)

Subject (DC Electrical Circuits Lab UOMU020701)

Lecturer (Ayat Ayad Hussein)

1st term – Lecture No.3 (KIRCHHOFF'S LAWS)



$$i_2 = 2 \text{ A}$$

$$i_1 = 3 \text{ A}, \quad i_3 = 1 \text{ A}, \quad v_1 = 24 \text{ V}, \quad v_2 = 6 \text{ V}, \quad v_3 = 6 \text{ V}$$