

Al- Mustaqbal University
College of Science
Criminal Evidence Department
First Stage



جامعة المستقبل
AL MUSTAQBAL UNIVERSITY

Lecture one: Ohm's Law

MS.c Israa hussein

B.Sc Mohammed Jamal

2025 – 2026

Aim of the Experiment

- To verify Ohm's Law experimentally.
- To find the relationship between current and voltage for a fixed resistor.

Tools and Equipment Used



- DC Power Supply (Battery or DC Source)
- Resistor
- Voltmeter
- Ammeter
- Connecting Wires
- Breadboard (optional)

Theory

Ohm's Law experiment is one of the basic experiments in physics labs. It aims to study the relationship between the electric current passing through a circuit and the voltage across its components. This experiment helps students understand how to measure voltage and current using standard lab instruments.

Ohm's law text:

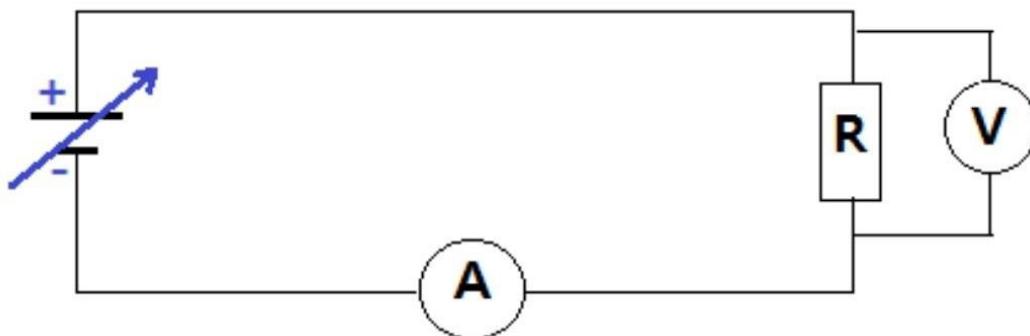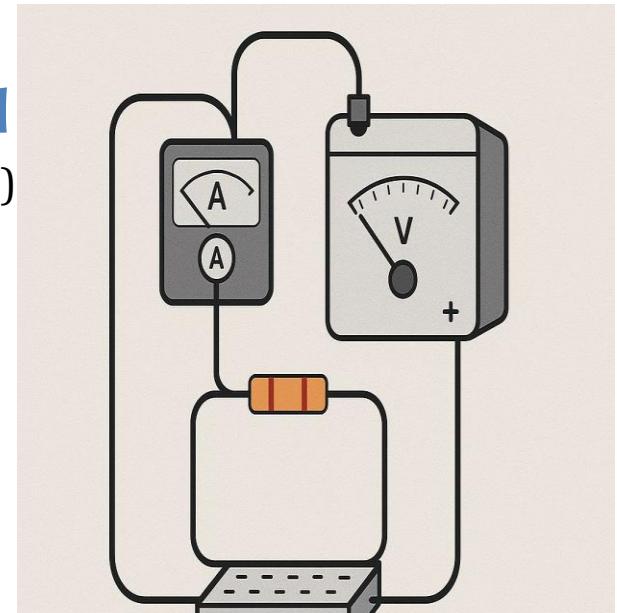"The electric current passing through a conductor is directly proportional to the voltage across it, provided the temperature remains constant."



Ohm's Law is defined by the equation:

$$V = I \times R$$

Where:

V: Voltage across the resistor (Volts) (V)

I: Electric current (Amperes) (A)

R: Resistance (Ohms) (Ω)

If the resistance is constant, the current increases linearly with the voltage.

Experimental Procedure

1. Set up the circuit: Connect the resistor to the power source using wires on a breadboard or directly.
2. Connect the ammeter: Place the ammeter in series with the resistor to measure the current.
3. Connect the voltmeter: Place the voltmeter in parallel with the resistor to measure the voltage.
4. Turn on the power supply: Start with a low voltage and record the readings of voltage and current.
5. Repeat the experiment: Gradually increase the voltage and take multiple readings of both current and voltage.
6. Create a data table: Record the corresponding values of V and I.
7. Plot the graph: Plot voltage (V) on the y-axis and current (I) on the x-axis.
8. Analyze the results: If the graph is a straight line through the origin, Ohm's Law is verified.

Mathematical Relations and Calculations

$$\begin{array}{c} V \\ | \\ I = \frac{V}{R} \end{array}$$


$$I = V \div R$$

$$\begin{array}{c} V \\ | \\ I \quad R = \frac{V}{I} \end{array}$$

$$R = V \div I$$

$$\begin{array}{c} V \\ | \\ I \times R \end{array}$$

$$V = I \times R$$

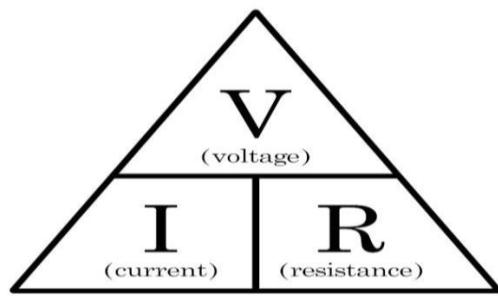


- To calculate resistance: $R = V / I$
- To calculate current: $I = V / R$
- To calculate voltage: $V = I \times R$

Voltage (V)	Current (A)	Resistance (R)
1	0.15	
2	0.36	
3	0.51	
4	0.77	
5	0.99	

- A graph is plotted between voltage and current. A straight line indicates a direct proportionality, confirming Ohm's Law.

$$R(\Omega) = \text{Slope}$$

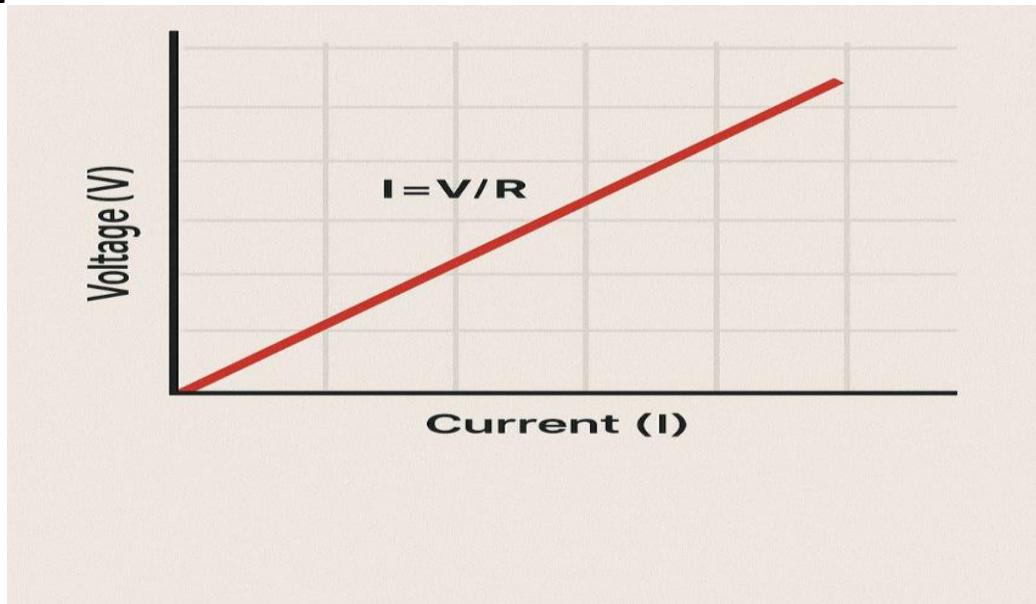

1. What does Ohm's Law describe?

- A- The relationship between power and resistance
- B- The relationship between voltage, current, and resistance
- C- The relationship between charge and time
- D- The relationship between energy and power

2. Ohm's Law is mathematically expressed as:

- A- $R = I \times V$
- B- $V = I \times R$
- C- $I = R \times V$
- D- $V = R / I$

3. The SI unit of electric current is:

- A- Volt
- B- Ohm
- C- Ampere
- D- Watt

4. Which instrument is used to measure electric current?

- A- Voltmeter
- B- Ammeter
- C- Ohmmeter
- D- Galvanometer

5. The voltmeter should be connected in the circuit:

- A- In series with the resistor
- B- In parallel with the resistor
- C- In series with the power supply
- D- Outside the circuit

6. If the resistance is constant, increasing the voltage will:

- A- Decrease the current**
- B- Keep the current constant**
- C- Increase the current linearly**
- D- Stop the current**

7. The SI unit of resistance is:

- A- Ampere**
- B- Volt**
- C- Watt**
- D- Ohm**

8. In an Ohm's Law experiment, the ammeter is connected:

- A- In parallel with the resistor**
- B- In series with the resistor**
- C- Across the power supply**
- D- Across the voltmeter**

9. A straight-line V-I graph passing through the origin indicates:

- A- Non-ohmic behavior**
- B- High resistance**
- C- Verification of Ohm's Law**
- D- Zero current**

10. Resistance can be calculated using the formula:

- A- $R = I / V$**
- B- $R = V \times I$**
- C- $R = V / I$**
- D- $R = I^2 \times V$**