



Al-Mustaqbal University  
Department of Artificial Intelligence Techniques Engineering  
Lecturer: Dr. Zahraa hashim kareem  
Subject: fundamental of electrical engineering  
1<sup>st</sup> term – Lecture: 3- Series Circuits and the Application of Ohm's Law



# الكلية التقنية الهندسية

## هندسة تقنيات الذكاء الاصطناعي



## Lecture: (3)


### Series Circuits and the Application of Ohm's Law

## Introduction

In this introduction to series resistance circuits, we will explain these three key principles you should understand:

- **Current:** The current is the same through each component in a series circuit
- **Resistance:** The total resistance of a series circuit is equal to the sum of the individual resistances.
- **Voltage:** The total voltage drop in a series circuit equals the sum of the individual voltage drops.

We'll examine these three principles using the series circuit consisting of three resistors and a single battery, as illustrated in Figure 1.

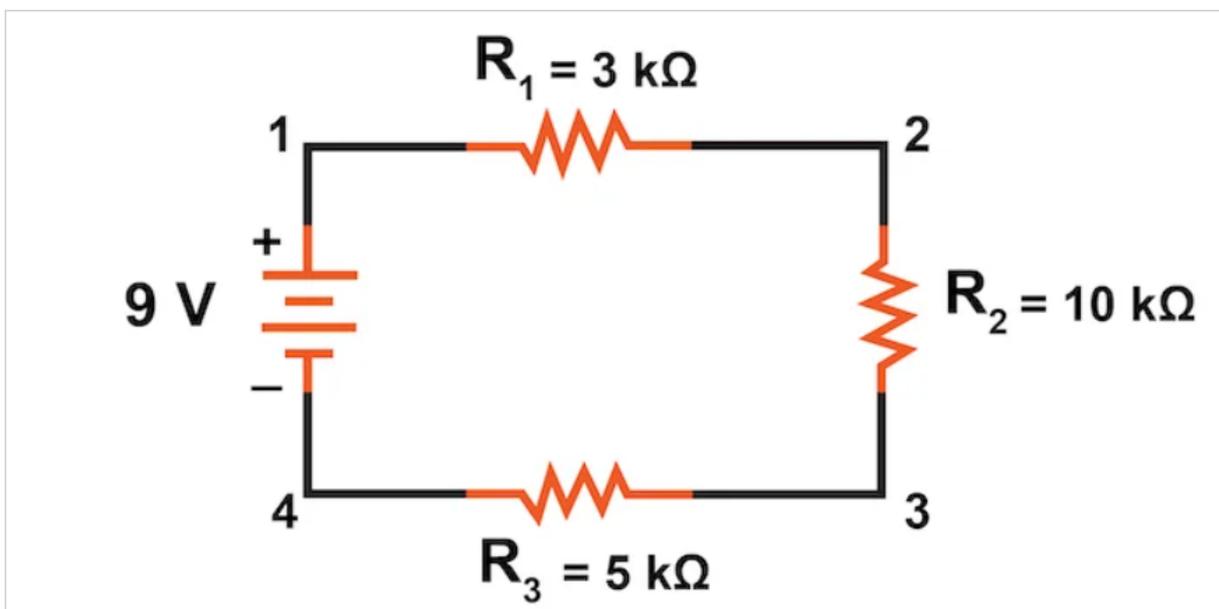

*Figure 1. Series circuit with a battery and three resistors.*

## **Current in a Series Circuit**


In a series circuit, the same amount of current flows through each component in the circuit. This is because there is only one path for the current flow. Since electric charge flows through conductors like marbles in a tube, the rate of flow (marble speed) at any point in the circuit (tube) at any specific point in time must be equal.

An important caveat to Ohm's law is that all quantities (voltage, current, resistance, and power) must relate to each other in terms of the same two points in a circuit.

Before we examine the more complex series circuit in Figure 1, let's examine this concept for a single resistor circuit.

### Using Ohm's Law in a Single Resistor Circuit

For this initial analysis, we will evaluate the current and voltage for the single resistor circuit in Figure 2.

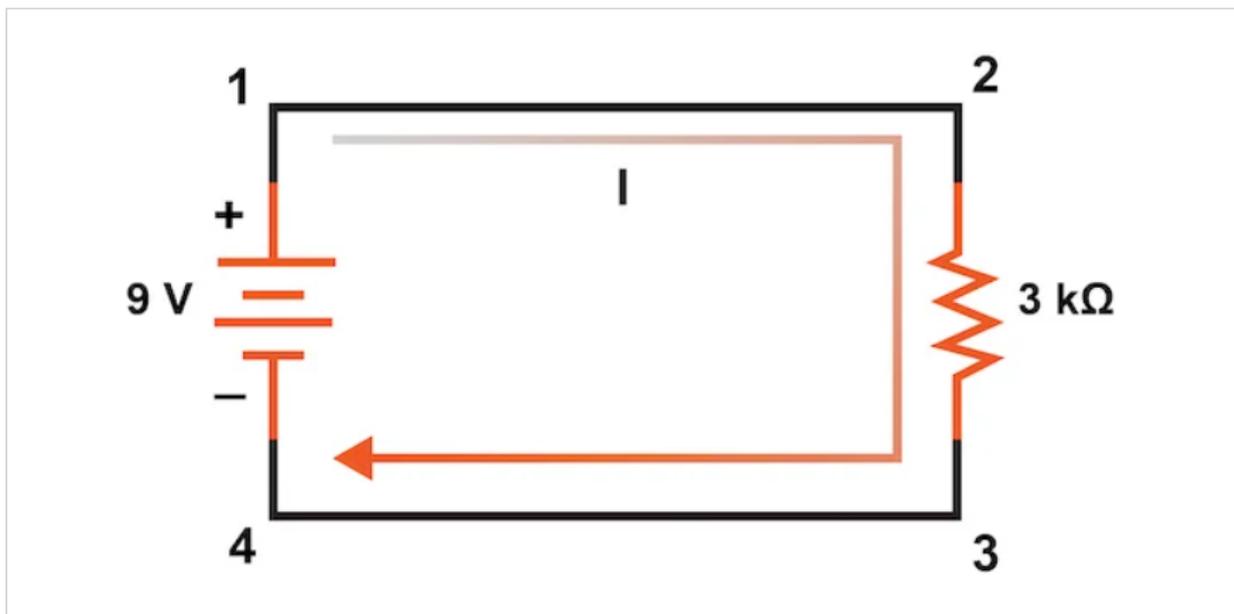

*Figure 2. Series circuit with a battery and a single resistor.*

Since points 1 and 2 are connected together with the wire of negligible resistance, as are points 3 and 4, we can say that point 1 is electrically common to point 2 and that point 3 is electrically common to point 4.

Since the circuit has 9 V of electromotive force between points 1 and 4 (directly across the battery), it must also drop 9 V between points 2 and 3 (directly across the resistor). This is because Kirchhoff's Voltage law states that the sum of all voltages in a loop must equal zero. Therefore, we can apply Ohm's Law ( $I = V/R$ ) to the current through the resistor because we know the voltage (V) across the resistor and the resistance (R) of that resistor. All terms (V, I, R) apply to the same two points in the circuit and to that resistor, so we can use Ohm's law formula with no reservation:

$$I = \frac{V}{R}$$

$$I = \frac{9 \text{ V}}{3 \text{ k}\Omega} = 3 \text{ mA}$$

### Using Ohm's Law for Series Circuits With Multiple Resistors

Returning to Figure 1's circuit, we can see that the polarity of the 9 V battery will again result in a current,  $I$ , that will flow in a clockwise direction from point 1 to 2 to 3 to 4 and back to 1. This concept is illustrated in Figure 3.

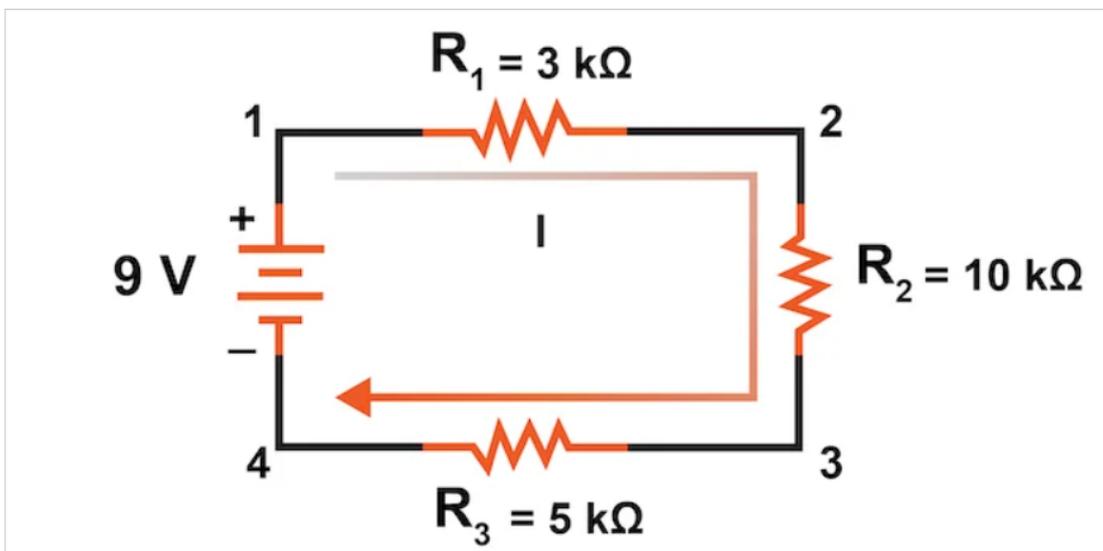


Figure 3. Current in a series circuit with a battery and three resistors.

However, we have one source of voltage and three resistances. From there, we might consider how we use Ohm's law here.

In the three-resistor example circuit of Figure 3, we have 9 V between points 1 and 4, which is the amount of electromotive force driving the current through the series combination of  $R_1$ ,  $R_2$ , and  $R_3$ . However, we cannot take the value of 9 V and divide



it by 3 k $\Omega$ , 10 k $\Omega$ , or 5 k $\Omega$  to try to find a current value because we don't know how much voltage is across any one of those resistors individually.

The voltage value of 9 V is the total quantity for the whole circuit, whereas the values of 3 k $\Omega$ , 10 k $\Omega$ , or 5 k $\Omega$  are individual quantities for individual resistors. If we were to plug a value for total voltage into an Ohm's law equation with a value for individual resistance, the result would not relate accurately to any quantity in the real circuit.

For R<sub>1</sub>, Ohm's law will relate the amount of voltage across R<sub>1</sub> with the current through R<sub>1</sub>, given R<sub>1</sub>'s resistance of 3 k $\Omega$ :

$$I_{R1} = \frac{V_{R1}}{3 \text{ k}\Omega}$$

$$E_{R1} = I_{R1} \cdot 3 \text{ k}\Omega$$

However, since we don't know the voltage across R<sub>1</sub> (only the total voltage supplied by the battery across the three-resistor series combination) and we don't know the current through R<sub>1</sub>, we can't do any calculations with either formula. The same goes for R<sub>2</sub> and R<sub>3</sub>—we can apply Ohm's law equations if and only if all terms are representative of their respective quantities between the same two points in the circuit. So what can we do? We know the voltage of the source (9 V) applied across the series combination of R<sub>1</sub>, R<sub>2</sub>, and R<sub>3</sub>, and we know the resistance of each resistor. However, since those quantities aren't in the same context, we can't use Ohm's law to determine the circuit current. If only we knew what the total resistance was for the circuit, then we could calculate the total current with our value for total voltage ( $I = V/R$ ).

### How to Calculate Total Resistance in a Series Circuit

This brings us to the second principle of series circuits: the total resistance of a series

circuit is equal to the sum of the individual resistances.

This should intuitively make sense, basically, the more resistors in series that the current must flow through, the more difficult it will be for the current to flow.


In the example problem, we had a 3 kΩ, 10 kΩ, and 5 kΩ resistors in series, giving us a total resistance of 18 kΩ:

$$R_{total} = R_1 + R_2 + R_3$$

$$R_{total} = 3 \text{ k}\Omega + 10 \text{ k}\Omega + 5 \text{ k}\Omega$$

$$R_{total} = 18 \text{ k}\Omega$$

In essence, we've calculated the total equivalent resistance of  $R_1$ ,  $R_2$ , and  $R_3$  combined. Knowing this, we can redraw the circuit (Figure 4) with a single equivalent resistor representing the series combination of  $R_1$ ,  $R_2$ , and  $R_3$ :

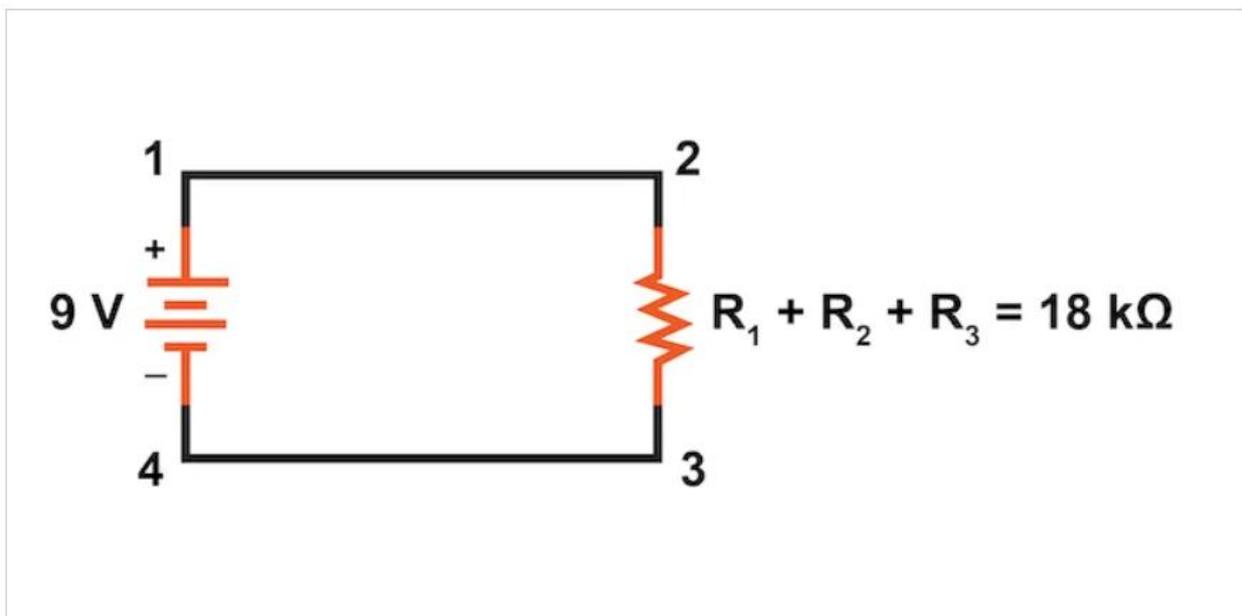

**Figure 4.** Circuit showing total equivalent resistance of series resistors.

With all those calculations completed, we now have all the necessary information to calculate the circuit current for Figure 4 since we have the voltage between points 1 and 4 (9 V) and the resistance between points 1 and 4 (18 kΩ).

$$I_{total} = \frac{V_{total}}{R_{total}}$$

$$I_{total} = \frac{9 \text{ V}}{18 \text{ k}\Omega} = 500 \mu\text{A}$$

### How to Calculate Voltage Drop in a Series Circuit

Knowing that current is equal through all components of a series circuit (and we just determined the current through the battery), we can go back to our original circuit schematic of Figure 1 and note the current through each component, shown in Figure 5 as:

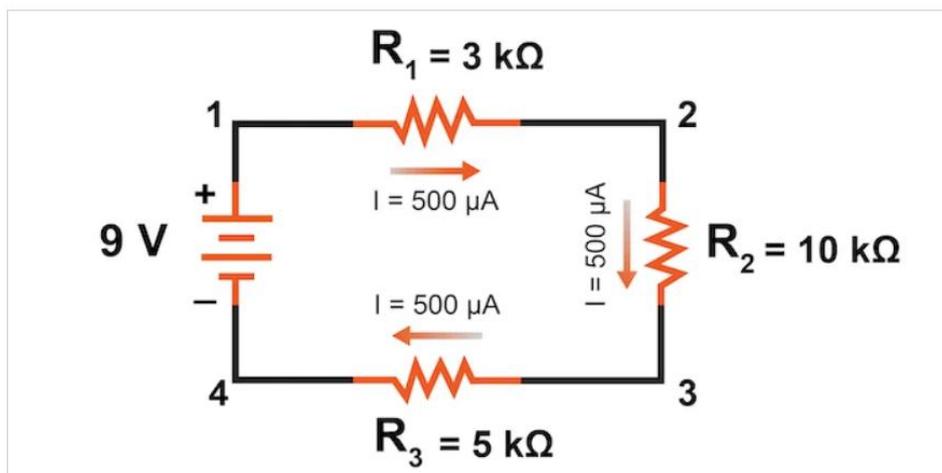


Figure 5. Calculated current for the series circuit.

Now that we know the amount of current through each resistor, we can use Ohm's law to determine the voltage drop across each one (applying Ohm's law in its proper context):



$$V_{R1} = I_{R1} \cdot R_1 = (500 \mu\text{A}) \cdot (3 \text{ k}\Omega) = 1.5 \text{ V}$$

$$V_{R2} = I_{R2} \cdot R_2 = (500 \mu\text{A}) \cdot (10 \text{ k}\Omega) = 5.0 \text{ V}$$

$$V_{R3} = I_{R3} \cdot R_3 = (500 \mu\text{A}) \cdot (5 \text{ k}\Omega) = 2.5 \text{ V}$$

Notice that sum of the voltage drops ( $1.5 + 5.0 + 2.5 = 9.0 \text{ V}$ ) is equal to the battery (supply) voltage of  $9 \text{ V}$ . This is the third principle of series circuits—the total voltage drop in a series circuit equals the sum of the individual voltage drops.

## H.W.

Three resistors ( $2\Omega$ ,  $3\Omega$ ,  $5\Omega$ ) are in series with a  $20\text{V}$  source. Calculate all voltage drops using VDR.